




ELECTRONICS TODAY INTERNATIONAL

May 1981

\$1.75* NZ \$2

CHRIST -OR NOT?

© Barrie M. Schwartz.

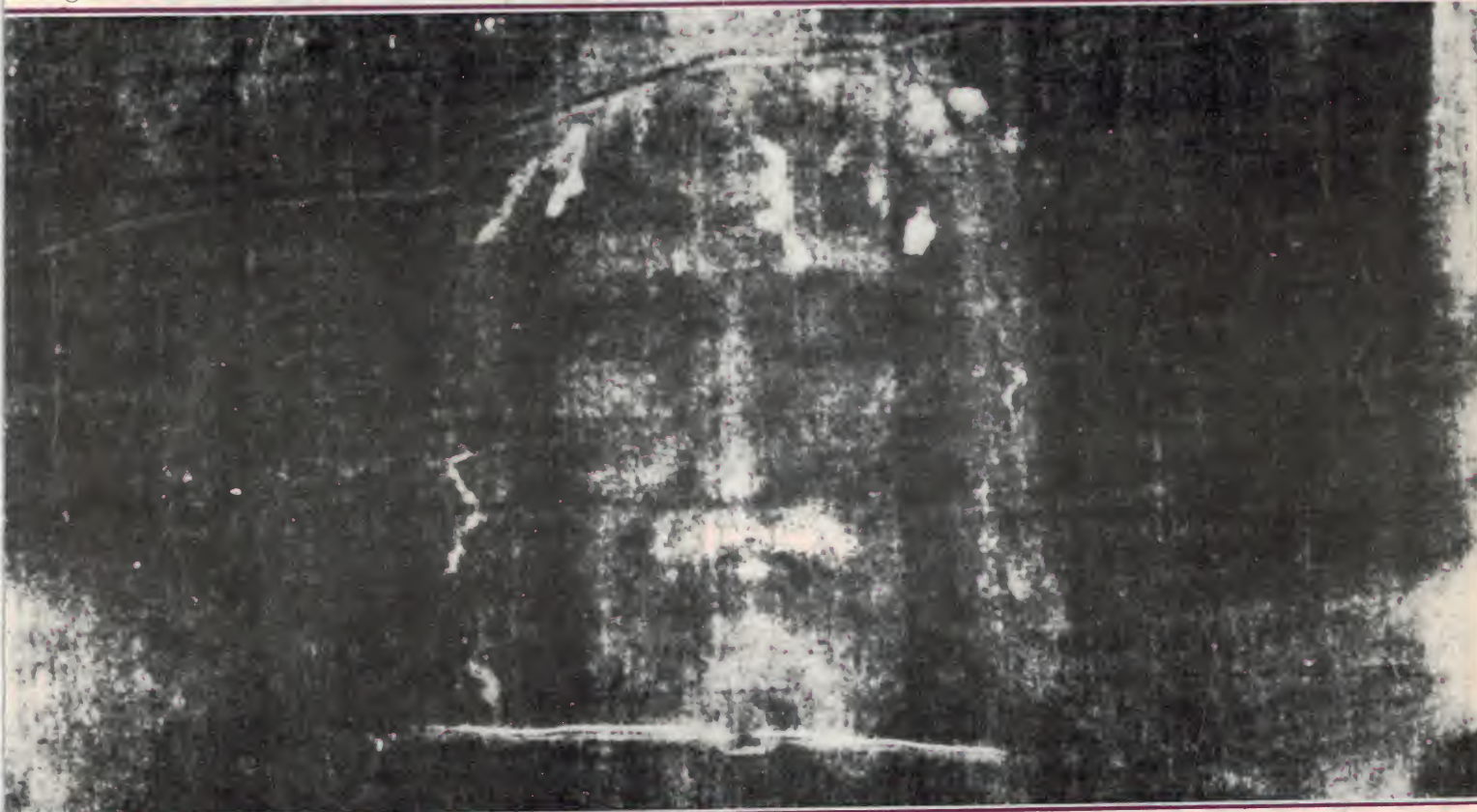


**Scientists examine
the Holy Shroud
of Turin**

AN ETI EXCLUSIVE

**UHF TV converter project
Electronic humidity meter
Videodisc-how soon?
Sony's TA-F80 hi-tech amp**

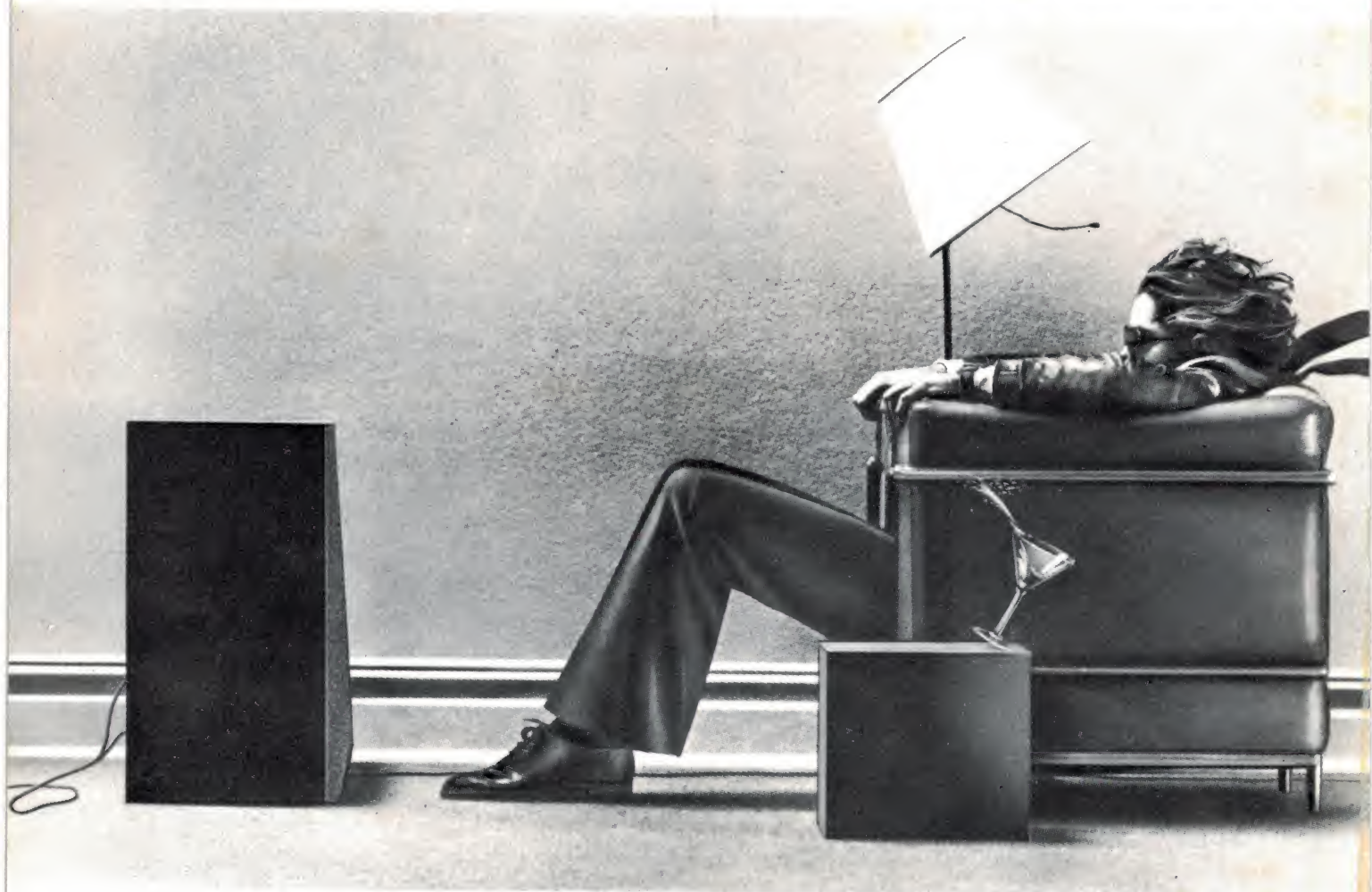AFTER 500 PLAYS OUR HIGH FIDELITY TAPE STILL DELIVERS HIGH FIDELITY.



If your old favourites don't sound as good as they used to, the problem could be your recording tape.

Some tapes show their age more than others. And when a tape ages prematurely, the music on it does too.

What can happen is, the oxide particles that are bound onto tape loosen and fall off, taking some of your music with them.

At Maxell, we've developed a binding process that helps to prevent this. When oxide particles are bound onto our tape, they stay put. And so does your music.

So even after a Maxell recording is 500 plays old, you'll swear it's not a play over five.

Distributed by
HAGEMEYER

For further information on Maxell Tapes
write to Maxell Advisory Service,
P.O. Box 307, North Ryde, N.S.W. 2113



maxell[®]
simply excellent

WT191/80



ELECTRONICS TODAY INTERNATIONAL

Registered for posting as a publication —
Category B
ISSN No. 0013-5216

QUICK INDEX

FEATURES:

- 9** Chip Shop For Canberra?
- 14** The Holy Shroud of Turin
- 25** Scientists Examine the Holy Shroud
- 34** Solar Panels — Special Offer to ETI Readers
- 143** Fantastic Offer on Steel-backed Binders

COMPUTING TODAY:

- 83** Say it Again, RAM!
- 86** Printout — news and views
- 94** A Microcomputer for Beginners
- 101** Universal Logic
- 108** Wordsquare — A Game for the TRS80
- 112** PET talk
- 115** More POKEing on the ZX80

SIGHT & SOUND:

- 117** Software — Key to Videodisc
- 118** Sight & Sound News
- 129** Videodisc — waiting in the wings
- 122** Review of Sony's TA-F80 Amplifier
- 136** Dick Smith's P-360 Auto Turntable reviewed

PROJECTS & TECHNICAL:

- 35** 735: UHF to VHF TV Converter
- 46** 256: Electronic Humidity Meter
- 53** 257: Universal Relay Driver Board
- 64** Lab Notes: Using the 555 & 7555
- 70** Ideas For Experimenters
- 77** Shoparound

BROADCASTING DILEMMA

IT IS APPARENT that television broadcasting in Australia has reached a crossroad — but it's no ordinary crossroad, it's a five-way junction! Television broadcasters, and listeners, have a number of options confronting them with regard to avenues for transmission and reception of programmes. These are: the existing 12-channel VHF system, a UHF system with over 35 channels available, direct satellite broadcasting, cable distribution or a 'mix' of these.

Cable TV is relatively remote, yet if any orderly mix of broadcasting avenues is to be looked at, it must clearly be a consideration. Satellite broadcasting, though, will be upon us later this decade, and that's not far away in planning terms. At present, UHF TV broadcasting is fulfilling an 'accessory' role. There is only one 'prime' broadcaster on UHF, the 'ethnic' station, channel 28, the others being translator services for existing VHF stations filling in where the VHF services cannot reach. The VHF system, introduced in 1956, amended in 1961, is currently in the process of being partially disassembled to make way for FM broadcasting.

The current disassembling of the old 12-channel VHF system by removal of channels 3, 4 and 5 to make way for the 88-108 MHz broadcast band has thrown the other options into high relief and this, coupled with the fact that channels 0 and 5A stations are to be phased out (see March issue, page 74 and this issue, page 81), has put enormous pressures on the existing TV broadcasting system.

The Federation of Australian Television Stations, representing the broadcasters as an 'industry', hosted a seminar in mid-March seeking ways out of their current dilemma, and we have a brief report of this on page 81. With direct satellite broadcasting fast approaching, the current broadcasters are seemingly caught between the devil — in the guise of channel reductions — and the deep blue sky! Although the satellite is supposed to provide services to those who cannot now receive them, many existing viewers could avail themselves of the opportunity. And they will.

While seeking solutions to existing problems, F.A.C.T.S. seeks to address themselves to the problems of an orderly introduction of UHF TV. But for the problems of VHF they seek solutions by proposing re-arrangements of the VHF channel allocations. It seems a short-sighted approach.

Meanwhile, the Department of Communications seems to have no really coherent attitude — let alone a policy. It came as shock news to those at the F.A.C.T.S. seminar that channel 5A was to be phased out — by direction from the Prime Minister. No time scale has been proposed, though. As I was composing this, I received a copy of a letter from the Minister of Communications, Ian Sinclair, sent to the Sydney Channel 0 Action Committee (see also March issue, page 74). Mr Sinclair says "... that while it is the Government's intention that multicultural television will eventually move to UHF only, I am not yet able to indicate when the channel 0 transmissions will cease."

At this time, the Department is also considering the Australian Table of Frequency Allocations following the WARC '79 recommendations, as well as a new Radiocommunication Act.

It is apparent that this is a critical time in the communications sphere in Australia, but especially in television broadcasting. The whole question requires some hard-nosed, dispassionate analysis in order to synthesise the appropriate solutions. And fairly soon.



Roger Harrison

Roger Harrison
Editor

advertisers

Acoustic Foundry	34
AED	98
Applied Technology	91
Archive Computer Services	55
A&R Soanar	138
Audio Engineers	135
Aust. Govt. — Air Force	128, 144
Aust. Govt. — Navy	6-7
Best Vision (Channel King)	43
Bose Australia	116
BWD Electronics	16
Calculator & Computer Discounts	139
Chadwick Audio	121
CISA	88
Commodore Australia	113
Computer Country	68
Consolidated Marketing	114
Dave Ryall Electronics	127
David Reid Electronics	42
DeForest Software	74
Dick Smith Electronics	20, 44-45, 50, 53, 61, 69, 78, 80, 82, 92, 100, 102, 104-105, 111, 139.
Dindy Marketing	124
Direct Computer Sales	141
DSA Concert Systems	124
Electrocraft	132
Electromark	132
Electronic Agencies	52
Emac Industries	124
Emona Enterprises	43
Energy Control	68
Ferguson Transformers	40
Freedman Electronics	121
Hagemeyer — JVC	147
Hagemeyer — Maxell	2
Jaycar Pty. Ltd.	17
John F. Rose	106-107
Kit Parts Australia	33
Logic Shop	74
Looky Video	97
Magnetic Media Services	68
Magnetic Video (South Pacific)	13
Marantz Australia	21
Maurice Chapman	127
McWilliams Wines	8
Mensa Computers	93
M5 Mail Order Service	67
Micro 80	99
Microtrix	110
National Panasonic	22-23
Pre-Pak Electronics	72
Radio Despatch Service	43
Radio Parts Group	132
Radofin Electronics	148
Rod Irving Electronics	51, 56-57, 84-85
Sansui Electric Co Ltd	120
Seahorse Computer	115
SI Microcomputer	110
Software Source	97
Sony	24
Standard Components (Hitachi)	141
Tandy Electronics	76
Tasman Electronics	40
TCT Micro Design	62
VSI Electronics	63, 71
Warburton Franki	75

eti

ELECTRONICS TODAY INTERNATIONAL



features



THE HOLY SHROUD OF TURIN 14

This piece of ancient linen containing the image of a crucified man believed by many to be Jesus Christ, has been the object of suspicion, curiosity and speculation ever since it appeared in Europe in the middle of the fourteenth century. Scientists, on the rare occasions they have been allowed to examine the Shroud, have been unable to state whether it is a fraud or not. We provide some background to the Shroud and its history, followed by Brian Dance's report on the first published results of the scientific investigations of 1978.

SCIENTISTS EXAMINE THE HOLY SHROUD

25

computing

COMPUTING TODAY 83

Say it again, RAM — and other stories.

ETI "READERS' DREAM" COMPUTER 94

If you'd like to make a start in the microprocessor field but don't know where or how to begin, this ETI Computer is for you!

UNIVERSAL LOGIC 101

Will we see the thousands of logic chips shrink to one small 'universal' set? If Dr Stanley Hurst of the University of Bath can translate his theories into practice a revolution in logic circuit design may well be sparked off.

WORD SQUARE — A GAME FOR THE TRS80 108

Set up this game and keep the kids quiet while you compute!

PET TALK 112

Learn how to double the plotting capacity of your PET with this routine.

MORE POKEING ON THE ZX80 115

This month we continue our series on POKEing on the ZX80 with a graphics example.

news

NEWS DIGEST 9

Chip shop for Canberra?; BHP science prize; Turning on the aurorae; ABC tests Antiope, not Telidon; etc.


PRINTOUT 86

New ZX81; Bubble cassettes; Super Text II for Apples; New address for Sorcerers; etc.

COMMUNICATIONS NEWS 81


F.A.C.T.S. seminar; 500 MHz quartz crystals; etc.

projects

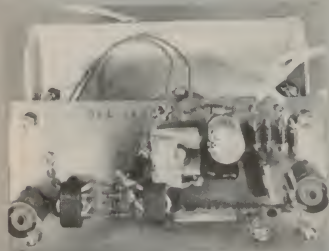

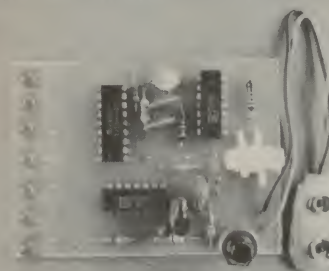735: UHF TV CONVERTER 35

This project should satisfy the deluge of people who wrote in asking us for a project to convert UHF signals for reception on a VHF TV. It's in two versions — single channel and tuneable — and is designed and constructed very simply.



256: HUMIDITY METER 46

This project will give a readout of relative humidity either on a LED dot-mode display or a conventional meter. It can be used with ETI-257 as a controller to turn on and off a water mist spray in a hothouse, for example.

257: UNIVERSAL RELAY DRIVER 53

This should turn you on — or off! A simple circuit that can be coupled to many electronic devices to operate a relay that can switch on or off an external circuit, perhaps mains operated or whatever. Features include facility to AND or OR two inputs, logic high to operate, logic low to operate and latch/unlatch inputs.

LAB NOTES 64

Gate, square, sine, modulate — with the 555 and 7555.

IDEAS FOR EXPERIMENTERS 70


Simple anemometer; Remote control with UARTS; etc.

SHOPAROUND 77

sight & sound

SIGHT AND SOUND NEWS 117

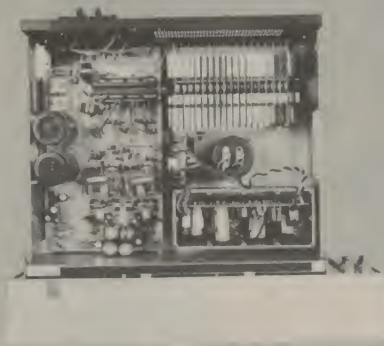Software the key to the videodisc war; Sanyo's new Beta video cassette recorders; New series TDK reel-to-reel tapes; etc.



SONY TA-F80 AMPLIFIER 122

Louis Challis didn't care much for the look of the Sony TA-F80 amp, but in every other way he has nothing but praise for it.

VIDEODISC — WAITING IN THE WINGS 129

The battle lines have been drawn, the software is being sorted out, and World War III (for the domestic videodisc market) appears to be commencing. This article reviews the three main contenders.

DICK SMITH P-360 TURNTABLE 136

Louis Challis found the P-360 turntable to be really good value for money, needing only a first-class cartridge to bring out its full potential.

general

SPECIAL OFFER
24W
SOLAR PANELS!
P. 34

ELECTRONICS BOOKS FROM ETI 58

Beginners' books, data books, circuit books, etc.

LETTERS 79

SHORT CIRCUITS 134

Simple LED VU meter

MINI-MART 142

SUPERB BINDERS FROM ETI 143

ETI SERVICES 145

DREGS 146

next month



TECHNICS' SB10 LOUDSPEAKERS

We first introduced readers to Technics' revolutionary 'Honeycomb Disc' drivers, and the SB range of speakers, back in the May '80 issue and we have been hankering for some time to review the SB10s. What surprises will Louis Challis' spectral decay analysis have in store?

ELECTROSTATIC DISCHARGE

The nemesis of electronic systems — examined in depth! Most readers are familiar with the care one usually has to take with CMOS circuitry, but there's a whole lot more behind and beyond that. Our article examines how electrostatic charges can be built up and how to protect against the damage they can wreak.

SERIES 5000 PREAMP/CONTROL UNIT

Second in our series of 'no-compromise' audio units. David Tilbrook explains the philosophy and circuit techniques behind this top-line project. Features include a moving-coil cartridge preamp along with two moving-magnet preamps, a very versatile tape monitor scheme and a unique LED level meter that simultaneously displays peak and average programme level. Construction commences with the latter unit, which can also be used as a stand-alone instrument or incorporated in other equipment.

A MICROCOMPUTER FOR BEGINNERS

As explained this month, construction starts in the June issue. Featuring simple, single-board construction, low cost and expandability, this versatile little unit can be powered from a plugpack, will plug directly into your TV set for video display (colour too!), and includes an audio output.

ADVANCED BASIC — PART 1

For those personal computing buffs who've got beyond the basic BASIC. This series follows on from Phil Cohen's popular 'Back Door Into BASIC' series. If you've worked your way through that and it's to go further — Advanced BASIC's for you!

Although these articles are in an advanced state of preparation, circumstances may affect the final content. However, we will make every attempt to include all features mentioned here.



**'YOU'LL BE WET, YOU'LL BE
AND FRIGHTENED, BUT
KNOW THAT YOU'VE GOT**

NAVY

THE PRIDE OF THE FLEET IS YOU.

'In the days when our Navy was young,
and the ship was the pride of the fleet.

You'd gaze out at her in wonder,
made an old sailor's heart skip a beat.

Well the ships have gone through
some changes,

And the roles have changed a bit too.

You'll be wet,

You'll be homesick and frightened,

But the pride of the fleet will be you.'

Our ships are equipped with
some of the finest and most
advanced technology in the world.
So it stands to reason that we're
proud of them.

It also stands to reason that we
need the men to make them work.

Men who, in the Navy, have
discovered what they do best and
have been trained to achieve it.

Men with pride in themselves
and what they can do. Whatever
the conditions.


Because pride is what it's all
about really.

In the Navy we're proud of the
Fleet. But we're prouder still of
the men who work it.


Talk to a Navy Careers Counsellor. He'll tell you about today's Navy and the kind of men that it needs. It could be a proud moment for you both. So, pick up a phone now. Or write to G.P.O. Box XYZ in your state capital.

N.S.W.: Sydney 212 1011, Parramatta 635 1511, Newcastle 2 5476,
Wollongong 28 6492. VIC.: Melbourne 613 731. QLD.: Brisbane
226 2626, Townsville 715 253. S.A.: Adelaide 212 1455. W.A.:
Perth 325 6222. TAS.: Hobart 34 7077, Launceston 31 4626.
A.C.T.: Canberra 82 2333.

Auth. Director-General Recruiting, Dept. Defence. NGE249.DPS.21



HOMESICK
YOU'LL
A TOP JOB?

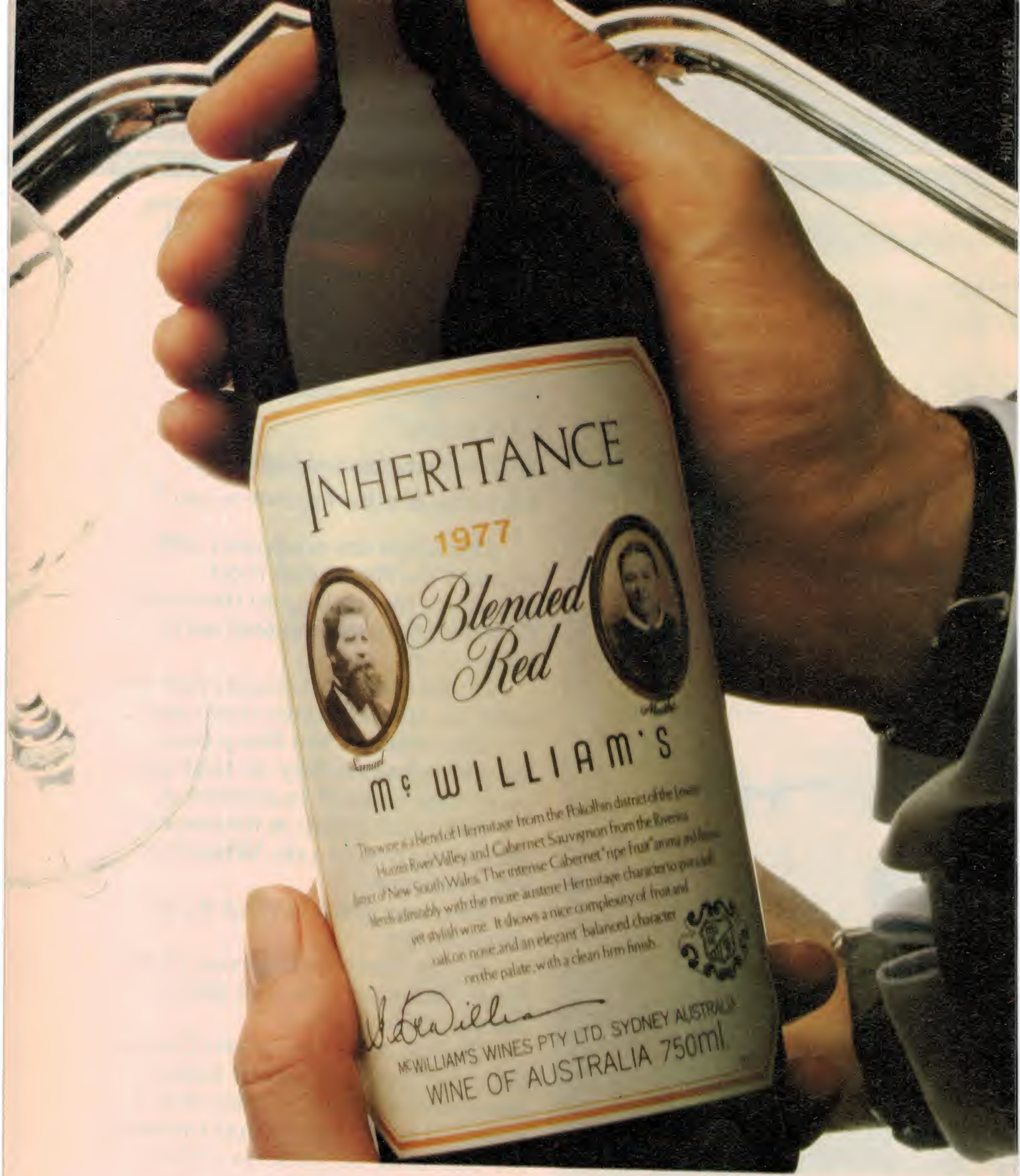

UPON RECEIVING YOUR INHERITANCE
IT'S ALWAYS WISE TO STUDY THE FINE PRINT CAREFULLY.

Chip shop for Canberra ?

The Federal Government has invited National Semiconductor to examine the feasibility of establish-

ing a silicon wafer fabrication plant in the Australian Capital Territory.

Announced in the fourth week of March by the Minister for the Capital Territory and Minister Assisting the Minister for Industry and Commerce, Mr Michael Hodgman, the news brought some criticism from South Australian and Queensland politicians.

Mr Hodgman said the Australian Government had indicated its willingness to seek an agreement with Natsemi on the basis that it would provide land and buildings (estimated to cost \$19 million), in return for which Natsemi would commit itself to the transfer of existing and future technology, 'most favoured customer' access to products, assistance with product development and the training of Australians.

Mr Hodgman said that Natsemi would employ 1200 people in operating the plant, and at least a further 800 jobs would be created by demands associated with the new industry. Construction of the plant would employ 300 people over 18 months.

"Capital cost of the project is estimated at \$100 million and would involve the construction of an 18 600 square metre complex housing a fabrication plant, a central servicing unit, and office space," the Minister said.

Natsemi expects to complete their feasibility study around the middle of the year and have a decision on whether the project will proceed at that time. However, Mr Jack Rutherford, Managing Director of Natsemi Australia, was in no doubt that he would get his board's approval. Natsemi's head office in Santa Clara, California's famed Silicon Valley, is familiar with the proposal.

Following the announcement, some observers were

wondering why Natsemi had chosen Canberra after it had apparently had counter offers from a range of other contending countries offering millions of dollars worth of concessions. It appears, however, that the answer is quite simple. Australia offers undoubted advantages in the way of a stable political climate, sound investment environment and a growth economy. But the concessions offered are not that different from those offered elsewhere. Behind the \$19.5 million offer lie a string of entitlements which have yet to be added up.

It appears that the following forms of assistance have been offered to Natsemi:

- Research and development grants.
- Export expansion grants.
- Investment allowance tax write-offs.
- The opportunity to apply to the Tax Commissioner for special depreciation write-offs to apply to the economic life (as opposed to the physical life) of the plant, and
- Training allowances for staff employed.

While local firms can get similar assistance, the difference between Natsemi and local firms is that while these forms of assistance are available to the latter, they rarely get a head-start by Government providing free land and buildings for them.

It is difficult to assess with any accuracy just what the money value of the industry incentives will be since there are as yet no publicly available figures on the likely value of output, the number of the 1500 staff who will receive specialist training, the planned investment in plant or the likely response of the Taxation Commissioner to an

application for accelerated depreciation rates.

What has been causing concern within the Public Service, however, are the equally vague indications of what Australia will receive in return.

Natsemi has yet to inform the Government exactly what kind of chips it will manufacture, and there seems to be very little pressure from the plant's enthusiasts (of whom there are plenty) for them to do so.

However, the entire utility of the scheme depends almost totally on the technology transfer benefits which its advocates say will accrue to Australian manufacturers.

One Canberra source deeply involved in the project said recently that Natsemi had given an undertaking that the plant will involve VLSI (very large scale integration) technology but has not committed itself to details such as whether bipolar or MOS modes will be employed.

Natsemi has apparently told the Government that this decision will be made later, after world market requirements are assessed.

Nor is it clear how much, if any, capital Natsemi itself will outlay, although it has been promised loan-raising assistance from the Australian Industry Development Corporation (AIDC) should it require it.

Australian firms will be required to buy the plant equipment and lease it to Natsemi and presumably the leasing fees will be tax deductible.

It has perhaps not been appreciated that the Natsemi plant will be merely an off-shore operation for the Silicon Valley major operation of the corporation. It will fabricate silicon wafers for export only and has no obligation to manufacture for the local market.

The 'encapsulation stage' of

the silicon chip production process — where the chips are separated from the wafers — will take place in low-wage, tax-free Singapore.

The aspects of the deal which excite its promoters so much are the two concessions Natsemi has offered.

One is the status of 'prime customer priority' for Australian manufacturers wanting to buy other Natsemi components (which will be able to be purchased from a central clearing house to be established by Natsemi).

The second concession will be the establishment of a technology exchange corporation (which will be operated on a 50/50 basis by Natsemi and Australia) whereby Australian manufacturers can acquire advice, for a fee, on re-design and new design of microcircuitry applications to existing products.

The Queensland Treasurer, Dr Llew Edwards, has attacked the Government's decision to site the plant in Canberra and criticised the assistance, saying it was two-faced for a Federal Government which has attacked State Government incentives to new high technology industries such as aluminium smelters to do the same thing. Such criticism is predictable, yet the proposal succeeded despite intense bureaucratic opposition, it seems.

It's not likely to gladden the hearts of Philips' Australian board, or AWA for that matter. Philips closed down their Hendon, S.A., plant around a year ago and AWA is struggling to find customers for their custom chip design facility.

It will be interesting to see what happens in a few short months when Natsemi come back with their feasibility study results.



New range of Yew multimeters

The Yew 2410 series of multimeters, just released by Parameters Pty Ltd, is intended for professional use in maintenance, test and service situations.

All feature taut-band suspension, a technique pioneered by Yew and used in many of their instruments. Other features include a common ac and dc scale with white lettering on a black background to emphasise the position of the pointer.

In all, five different models are available. Movements are diode protected with additional fuse protection against overloading. Scales are colour-coded with the selector switch to simplify readings, and a single switch is used for all range and function changing.

Cases are made in tough high-impact plastic, and a vinyl carrying case is supplied as standard.

A detailed colour brochure on the Yew 2410 series of multimeters is available from Parameters Pty Ltd — phone Sydney (02)439-3288 or Melbourne (03)90-7444.

Now it's microprocessor 'phones!

It had to come — the microprocessor telephone. But this latest electronic wonder is not just a telephone with memory, auto-dialler, etc — it's the complete bedside companion!

The Superphone 7700, just released here by Supertel Australia, features an auto-redialler, a stopwatch, a calculator, a digital clock and an alarm clock. And it's Telécom approved, according to Supertel.

The memory dialler enables you to store the 20 numbers you call most frequently — each number can be up to 14 digits long (ISD!). The number you select is displayed on the 14-digit LED display as Superphone dials it.

The auto-redialler stores the last number you dialled, whether you dialled it manually or recalled it from the memory.

All you do is pick up the receiver, press the 'redial' button and the last number called is displayed and dialled automatically.

In addition, the Superphone includes a stopwatch so you can time calls up to 99 mins 59 secs; a four-function, eight-digit calculator; a crystal-controlled digital clock and an alarm operated by the clock. Just to make sure the phone operates during power failures, standby batteries are included.

Full information can be obtained from Supertel, P.O. Box 215, Rose Bay 2029 NSW. (02)81-3007.

Turning on the aurorae

Experiments conducted by Canada's National Research Council Herzberg Institute of Astrophysics in the upper atmosphere have exceeded all expectations.

Their 'Waterhole' project involved seeding the Earth's ionosphere with water molecules at a height of about 300 km over as wide an area as possible.

The seeding was done instantly with a high explosive rocket warhead which caused a dimming of the aurora by some 50% throughout the area scanned by rocket-borne and by ground-based instruments.

This temporary intervention in the high-atmosphere processes which create the Northern Lights also produced perturbations in the particle and

magnetic flux measurements in the area.

If these first results are confirmed by similar future rocket experiments, then the National Research Council of Canada's researchers will be sure they have somehow influenced the high speed particles that induce the aurora.

They forecast that it may even be possible at some future date to dim or brighten the aurora or even turn the lights on and off again at will.

The same would apply in the Southern hemisphere.

Brian Dance



New range of panel meters features taut-band suspension

A new range of English-made SIFAM meters has recently been released by C & K Electronics.

Featuring taut-band suspension, the SIFAM meters are available as dc or ac voltmeters, millivoltmeters, ammeters, milliammeters and microammeters. Some models are available for special requirements such as dB meters or temperature indicators.

Apart from the standard pointers and scales fitted to the meters, many other types of pointers are available and scale markings (including colour printings) can be provided to suit individual requirements. Mirror scales and meters with centre or right-hand zero can

also be supplied. Customers' names or logos can be printed on dials to order. Illumination is available, if required, on most types.

VU meters and peak programme meters are generally available to the relevant specifications. A special low cost audio level indicator with VU scale is available with modified ballistics.

For further information, including a very informative catalogue, contact C & K Electronics (Aust.), P.O. Box 101, Merrylands, NSW 2160. (02)682-3144.

Science prize for students

The first BHP Science Prize, to be awarded in May 1982, is being wholeheartedly backed by both the CSIRO and the Australian Science Teachers' Association.

Areas of scientific research are biology, chemistry, geology, physics, or a combination of these, and students are eligible if they are under 19 on Jan 1 1981 and attending a registered Australian primary or secondary school or secondary college during 1981, either full or part-time.

The winner will receive \$5000 plus a gold medal; second prize is \$1000 and a silver medal, third prize \$500 and a bronze medal.

According to the CSIRO, the aim of the competition is to "encourage young scientists in the pursuit of excellence in the biological and physical sciences".

Entry forms may be obtained from members of the Australian Science Teachers' Association in each state.

Low-cost Japanese multimeters


GFS Electronic Imports of Mitcham, Victoria, recently announced they would soon have available two handheld digital multimeters manufactured by the well-established Japanese electronics instrument maker, Soar Corporation.

The ME-501 and ME-503 are both 3½-digit DMMs with liquid crystal displays. They employ LSI solid state technique and are consequently highly durable, with a battery life of up to 200 hours, according to GFS. Low battery and automatic polarity indication are provided for in their displays, all ranges are fully overload protected, and zero adjustment is automatic.

The ME-503 (photographed) reads ac and dc voltage up to 1000 V, and ac and dc current up to 10 A, as well as resistance. Input impedance on the ac and dc voltage ranges is 10 megaohms. The ME-501 is similar except for having only two ac voltage ranges, 200 V and 1000 V.

The expected selling prices are \$135 + sales tax for the ME-503 and \$99 + sales tax for the ME-501.

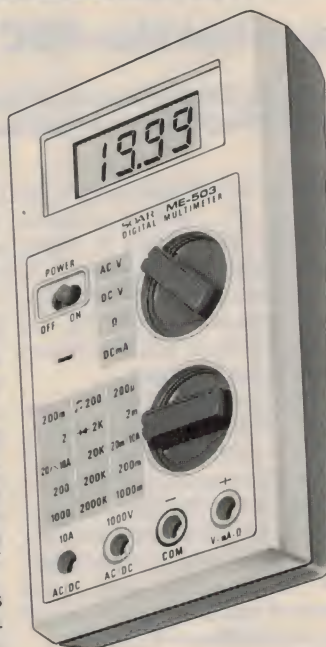For further information contact GFS Electronic Imports,



15 McKeon Rd, Mitcham Vic. 3132. (03)873-3939; telex AA38053 GFS.

Heathkit earth station?

American sources advise us to look for Heath to add a low-cost satellite earth station kit to its Heathkit line of build-it-yourself electronic products.

The Benton Harbor, Michigan, subsidiary of Zenith Radio Corp. is eyeing the market for direct satellite TV viewing at home and could be ready with a product by late this year or early 1982. Early speculation is that it will sell for less than US\$10 000.

People, products and appointments

Soanar Electronics have been appointed as sole Australian and New Zealand agents for Supertex Inc. of the USA. Supertex manufacture a wide range of N-Channel and P-Channel VMOS power FETs specially designed for applications requiring high input impedance and fast switching time, and programmable encoder/decoders for CMOS PROMs.

Mr James Donnelly has been appointed national manager, technical services, of Bell & Howell Australia Pty Ltd. He will be directly responsible to Bell & Howell Australia's general manager, operations, Mr John Londregan. A graduate of the RMIT in industrial electronics, Mr Donnelly has also taken a post-graduate course in electronics at the Gordon Institute of Technology and gained his certificate from the School of Small Business Studies. Prior to joining Bell & Howell, he was an executive of A-M International for 21 years.

David Christopher, former managing director of Tandy Electronics in Australia, has been named vice president of Tandy International Electronics, a new position. He will head retail operations in Australia, Belgium, Canada, France, Germany, Holland, Japan and the United Kingdom.

BWD Instruments, who have 25 years of experience in the electronics field behind them, are approaching the 1980s with a new, vigorous management team headed by John Opie and Ron Wheeldon as joint managing directors. BWD won the Design Award of the Australian Industrial Design Council for their 880 Powerscope, and are at present trying to enter the American and Japanese markets to consolidate their success in the southern hemisphere. Philip Cohen as newly created Corporate Development and Marketing Manager will be responsible for the marketing effort and increased production.

Tecnico Electronics have been appointed Australian distributors for Tekel handheld digital tachometers for rotational or peripheral speed measurement. Two models are available — a mechanical contact type and a non-contact infrared device.

In March this year the A & R Soanar Electronics Group opened their Queensland branch and warehouse complex in Brisbane. The Group now has branches in all mainland states of Australia, and like the other branches the new Queensland setup provides field representation, a showroom, telephone sales and warehouse facilities.

Dick Smith Electronics Pty Ltd plans to open a sales office in Auckland, New Zealand, early this year. Dick Smith visited New Zealand in 1980 to gauge prospects, and was swamped by calls and letters from the public there wanting to know when Dick Smith Electronics would open in New Zealand. Initially the NZ branch will concentrate on distributing a selected range of Dick Smith products to NZ resellers, but a retail outlet should follow shortly. Dick Smith Electronics hope to gain skills and experience in this New Zealand venture which will enable them to achieve their ultimate goal of opening in the US by 1984. Mr David Milson, a Dick Smith company executive with many years of experience in Australia, will become the resident manager of the New Zealand operation until he has trained a New Zealander to take over the position.

Dick Smith Electronics also recently opened a new store at 145 Parramatta Road, Auburn (phone 648-0558), to serve Sydney's Western Suburbs. The store will be open seven days a week and has plenty of parking available. Manager will be Ildio Teixeira, formerly manager of Dick Smith's Parramatta store.

ERRATA

A rather obvious, but potentially dangerous error occurred in the circuit on the top left of page 60 ('Power Monitor') in the March issue. It shows the mains active input connected to the earth at the output. The mains active input should instead go to the fuse. Correct your copy now. Correction slips were inserted in the majority of copies distributed.

AAAAARRGH!

Every now and then, it's the little things in life that get to you. This month (or last month, really) it was the picture on page 38 of the April issue, showing the pc board for the ETI-567 Core-Balance Relay. Just in case you hadn't noticed, look carefully and you'll see the writing on the potcore and the transformer is laterally reversed. In the trade (as they say . . .) this is known as a "flopped pic". Sometimes we'd like to do the same thing to the person responsible. Here it is (hopefully, this time . . .) the right way round.

That wasn't the only thing the wrong way round. The two red wires from T2 (L1) are shown incorrectly on the overlay, page 39, and the picture. Transpose them for correct operation. The picture at right is correct. The How It Works is correct, but the dot on the top wire of L1 on the circuit should go on the lower wire.

ERRATA, page 17, April

The caption beneath the chart at the top right of page 17 contains an error. The fourth line should read "... balanced positive-to-negative ion ratio of 1.2:1.0 . . .".



Telidon given world standard rating — but the ABC does different

The plenary assembly of the International Telegraph and Telephone Consultative Committee (CCITT) ratified in December 1980 the Canadian videotex (two-way TV)

system, Telidon, as one of the world standards, alongside competing French and British systems.

Canadian representatives displayed Telidon in Australia in February this year with a view to making their system the adopted standard in this country.

Telidon can be used at home, in business and in education, and according to its developers is a highly flexible, efficient and easy to use system that adapts easily to many uses and transmission methods, as well as having been designed to be immune to technological obsolescence. Information can be displayed in textual, graphic or photographic form.

It can provide access to the data banks of libraries, stock exchanges, newspapers, weather offices, advertising directories, government agencies — in fact to virtually any computerised information system. As an interactive computer system, Telidon can be used for services such as electronic mail, tele-shopping, telebanking and home video games.

Telidon was first demon-

strated in Australia in August 1979, but since that time has made many advances, both technologically and in distribution. As well as having been approved as an international standard, Telidon systems have been sold for use in Washington in the USA and Caracas, Venezuela; a Telidon demonstration system is fully operational in Switzerland; Telidon technology is an integral part of new cable TV networks proposed in several US cities; and major home computer firms in North America are designing equipment and software that will allow more than one million home computers in the US to take advantage of Telidon's data storage and image creation technology. Teleglobe Canada has also announced a C\$4.1 million project to establish a 100 000-page Telidon data base for the international videotex market.

Within Canada hundreds of terminals have already been installed across the country, and

dozens of companies are involved in Telidon projects. Telidon information is being transmitted by satellite, TV broadcast, telephone lines, coaxial cable and optical fibre. The cost of Telidon sets is declining as demand increases.

The Canadian developers regard Telidon as ideally suited to be the videotex standard for Australia because they say it was developed with the broadest possible range of applications in mind, is immune to technological obsolescence, and each piece of equipment can be used for many different functions.

However, despite all this heavy propaganda for the Canadian product, the ABC has decided to go its own way and start field trials of the competing French system, Antiope.

Some Australian TV channels have already been testing the British Teletext system, but since this system was designed for use with UHF TV channels it is unlikely to be the most appropriate for the ABC, which

largely uses low-numbered channels. Using the British system on Channel 2, tests have shown that the data may be easily distorted in its passage from the transmitter to the TV set, causing a high probability of errors or omissions.

With the French Antiope system, rows of alphabetical characters and other data are transmitted without the need to synchronise them with the TV line structure, as must happen with the UK Teletext. Antiope displays 40 characters on each row of the 'page' as does Teletext, but the French system allows reduction in the speed of transmission to minimise the number of errors — a vital consideration in such things as stock exchange listings, where an error in a single digit could be vital. If the ABC's field trials of Antiope are a success, it will recommend that the French system be given careful consideration by the Department of Communications for adoption by Australia.



Music, Murder, Money and Mirth

With these exciting new movie releases from Magnetic Video. Reprinted on top quality videotape. Slot in the video cassette, switch on and settle down to a night of uncensored entertainment.

Beyond the Valley of the Dolls. An all-girl rock trio and their manager meet bizarre characters, and murder in Hollywood. Stars the voluptuous Edy Williams, Dolly Reed and Cynthia Myers. **Myra Breckenridge.** The story of a young homosexual man who undergoes a trans-sexual operation. Stars Rex Reed and Raquel Welch. **Julia.** Academy Award winner, set in the turmoil of World War II and Nazi Germany. A young writer is asked to smuggle money into Berlin. Stars Jane Fonda and Vanessa Redgrave. **Breaking Away.** Comedy about an illusive high school graduate's addiction to bicycle racing. Stars Dennis Christopher, Dennis Quaid and Daniel Stern. **There's No Business Like Show Business.** Irving Berlin's classic musical comedy about a 'show biz' family. Stars Marilyn Monroe, Ethel Merman and Johnny Ray.

Plus a star spangled list of titles already in the world wide library.

Buy your Magnetic Video cassettes from these selected retailers:
VICTORIA: Intercape Video Recorder Centre, Natsound Pty. Ltd., Douglas Hi Fi, Batman Book Club, Brashs/Allans Music Stores - Melbourne. John Bruce Market Place - St. Kilda. Canberra Television Services - Camberwell, Dandy Sound, Gleeson & Tonta - Dandenong, Maxwells - All Stores, Myer - City, Suburbs and Country Stores, Pal TV & Stereo Pty. Ltd. - East Malvern, Photobin - Seaford, Reilly Bishop Pty. Ltd. - Blackburn, Video Sound - Mildura, Hollywood & Vine - South Yarra, Compucolour Pty. Ltd. - Armadale, Video Pak - Doncaster. **TASMANIA:** Centertainment, Canberra Television Services, Doug McDougall TV Rentals Pty. Ltd., Myer Ltd. - Hobart. **WILLS & Co. Pty. Ltd.,** Launceston Video Centre, Myer Ltd. - Launceston. James Loughran & Sons Pty. Ltd. - Burnie. **QUEENSLAND:** Cost Less Video Centre, Video Home Systems, Sound Centre, Chandlers - Brisbane Selected Stores - Brisbane. J. Michelmores Pty. Ltd. - Mackay, Paul Mow & Co. - Fortitude Valley, Saunders Electronics Pty. Ltd. - Longreach, Stereo World - Cairns, Vints Electrical & Sound Centre - Mt. Isa, Canberra Television Services - Milton, Home Service Centre - Charleville. **NEW SOUTH WALES:** Fletchers Photographics, Rastar/The Movie Book Shop, Bernie Silver, Sydney Hi-Fi All Stores - Sydney, David Jones, Grace Bros, Myer, Norman Ross, Woolworths Homemakers Division, Waltons - All Stores, Hi-Fi House, L & B Television Service Pty. Ltd. - Wollongong, Geoffrey Button Pty. Ltd. - Sans Souci, Canberra Television Services - Annandale, Centre Sound Music, Seleka Sound - Dubbo, Ron Chapman Hi-Fi Centre Pty. Ltd. - Newcastle West, Cuban Radio - Broken Hill, Electronic Enterprises - All Stores, Fred Cole Pty. Ltd. - Griffith, Mid States Records Pty. Ltd. - Bondi, Sonarta Entertainment Electronics - Hornsby, Trumps - North Newsagent - Bourke, Sydney Video Programmes Intl. Sales Pty. Ltd. - Northbridge, Wardell Sight & Sound - Broadmeadow, MacArthur Radio & T.V. - Bathurst, Sound Components - Tamworth, Taree Photographic - Taree. **A.C.T.:** Reel Classics, J. B. Young Pty. Ltd., Homecraft World of Music - Canberra. **SOUTH AUSTRALIA:** Focus Video, John Martin & Co. C.P.S., Video World, Myer - Rundle Mall - Adelaide, Sprys Electrical, Wisemans Electrical - Ceduna, Harding & Manning Pty. Ltd. - Whyalla, Video Centre - Salisbury. **NORTHERN TERRITORY/ALICE SPRINGS:** Pfitzners Music House, Norman Ross, Video Productions - Darwin, Murray Neck Retravision, Ascom Electronics, Weber Sales Pty. Ltd. - Alice Springs. Tennant Creek Newsagency - Tennant Creek. **WESTERN AUSTRALIA:** Videolink Pty. Limited, Boans, Musgroves, Parrys, Vox Adeon, Myer Ltd. - Perth.

 **Magnetic Video**
A Twentieth Century-Fox Company

Write to Magnetic Video (South Pacific), North Point, 100 Miller Street, North Sydney, 2060 for a free full colour, comprehensive Magnetic Video catalogue, absolutely obligation free.

Name: _____

Address: _____

Postcode: _____

MAG011

The Holy Shroud of Turin

Since its mysterious appearance in the fourteenth century, the piece of linen cloth with the strange image of a crucified man, now known as the Holy Shroud of Turin, has elicited awe, disbelief, scepticism, and scientific curiosity. Its history and its authenticity are, as one scientific punster put it, "shrouded in mystery". This article fills in some background on the Shroud, including its known and conjectured history and the conclusions — or lack of them — of scientific investigations up to the latest scientific enquiry of 1978.

Jane Clarke (B.A. Hons)
— Production Editor, ETI Group

THE HOLY SHROUD of Turin is kept, well wrapped in silk, asbestos and lead, in the Royal Chapel of Turin's Cathedral of St. John the Baptist, which has been its home since 1578. Officially the property of the House of Savoy, former rulers of Italy, the Shroud has for centuries been equally jealously guarded by the Catholic Church, who have seldom allowed it to be viewed by the general public and have consistently shown resistance to scientific examination which might prove, once and for all, whether the Shroud is at least authentically from the time of Christ or whether it could be the work of a mediaeval forger. Even on its first

appearance in the West in the fourteenth century there were doubters of its authenticity, notably Bishop Henry of Poitiers around the middle of the century, and some years later the Bishop of Troyes, Pierre d'Arcis, both of whom tried to stop the exposition of the Shroud on the grounds that it was not genuine.

This cloth that has caused so much controversy is a piece of linen a little over 14 feet long and about a yard wide — in excellent condition considering its supposed age — which bears on it an image, formed by some unknown means, of a crucified man. The man

appears to have been laid on his back on the cloth, which was then folded over his head to cover his front, since there is a complete image of both the front and back of the body.

The colour of the imprint is best described as a sepia monochrome with variations in the intensity of the colour, but there is no clear outline of the body; the impression is rather of a blurry, almost impressionistic figure, which melts away into insubstantiality as one comes closer to it.

The man of the image was about 181 cm (5ft 11in) — tall for his supposed time, but not impossibly so — with a powerful and well-proportioned

© 1978 Barrie M. Schwartz

Photographs of the frontal and dorsal images on the Shroud taken with reflected light. This is how the Shroud appears under normal viewing con-



physique. A leading ethnologist has described him as "of a physical type found in modern times among Sephardic Jews and noble Arabs", and his age has been estimated as between 30 and 45. There is a good deal of evidence that this man was a crucifixion victim, and there are also traces of what could be taken to be blood spilled due to the Crown of Thorns, the scourging, etc. that Christ is said to have undergone.

There is no definite evidence in the Gospels that Christ would leave a 'sign' like this Shroud of his resurrection; mention is made of the disciples finding 'othonia' (linen bands used to bind the body according to Jewish ritual) and a 'soudarion' (sweat cloth) in the tomb, but these cannot be specifically tied in with the Shroud, as there is no mention of any image left on them. Many people, however, have discovered in the Shroud details which correspond closely to the description in the Gospels of what Christ underwent before death, and most of these people would welcome a comprehensive scientific examination of the Shroud in order to at least discover whether this apparent miracle could in fact be man-made.

Scientific investigation

True scientific investigation of the Shroud really only started in 1898, when Secondo Pia used the new science of photography to take pictures of the Shroud — and discovered that the image was a negative one. Instead of the masklike, ghostly appearance of the Shroud, the man stood out on photographic negatives as a positive, lifelike image — especially the face. This discovery alone makes the likelihood of the

Shroud's being an artist's forgery much more remote; it would be practically impossible for any artist to reproduce tones that are the reverse of all he has learnt to depict in nature, especially without the photographic means of checking his work. Besides, who would *want* to produce artificially such a negative image?

Medical men have also shown a good deal of interest in the Shroud. They claim that the anatomical data of the image would be far beyond the capabilities of any fourteenth century artist, judging from what contemporary works show us of the prevailing knowledge of anatomy. They also deduced from experiments that a crucifixion victim would have to be nailed through the wrists, as is the man of the Shroud, since the palm of the hand would not be strong enough to bear the weight of the body. Subsequent discovery of a crucified man proved them to be right — but would a mediaeval forger have known this, considering that all contemporary portrayals of the Crucifixion show nails through the hands?

Angles of blood flow also indicate crucifixion, and markings on the forehead and in the side would correspond exactly with wounds Christ is said to have received.

In tests done before 1978, no trace of pigments has been discovered, as would be expected if the Shroud were the work of an artist. As well, it has been discovered that whatever caused the image has not penetrated right through the fibre of the linen, nor has it encrusted between the fibres. This would also seem to rule out paint, or any kind of 'wet' process of image-formation.

Analysis has been made of the weaving of the linen to try and trace its origins. Whilst the style — a three-to-one herringbone twill — is unusual in linen, it is by no means unique, and could certainly come from first-century Palestine. Whilst the linen was being examined, minute traces of cotton were also found, suggesting that the linen had been woven on equipment also used for the weaving of cotton. By analysing the species of cotton, scientists determined that it originated from the Middle Eastern area. Whilst a forger might have gone to the length of obtaining a piece of linen from this precise area, it is one more piece of evidence pointing towards the authenticity of the Shroud's provenance.

Up till 1978 scientists had been unable to identify any actual blood on the Shroud; it has been conjectured that either the age of the cloth or the fire and water damage it sustained in the sixteenth century might account for this, but since there is in any case no sign of penetration of any liquid into the cloth, it is arguable that scientists might perhaps not expect to find traces of actual blood.

The Shroud was also subjected to pollen-testing by means of removing surface particles from it on pieces of sticky tape. Dr. Max Frei of Switzerland in this way determined four predominant areas where the Shroud had been in its history: near to the Dead Sea in Palestine; in the area of the Anatolian steppe; Istanbul; and Northern Europe. The latter corresponds to our knowledge of the Shroud's history, but the other areas could offer vital clues to its earlier existence. ►

ditions. Shroud is mounted on a specially constructed stainless steel table and held in place with magnets to avoid damage to the cloth.

© 1978 Barrie M. Schwartz



We're viewing the 80's on a greater scope.

BWD have combined the expertise of highly qualified personnel with a dynamic management team to forge ahead stronger than ever before. The strength of our future is reflected in the ever increasing demand for our high quality instruments. A policy of continuous development assures a constant output of original and innovative designs for both general and specialised needs.

BWD manufacture first class instruments, widely accepted for their simple, functional designs that can out-perform far more complex competitive products.

In the fields of research, design, education and servicing, BWD provide a wide range of instruments from pure electronics to power line systems, and this range will be rapidly expanded throughout the 80's.

- 1 BWD 880 POWERSCOPE 4 independent differential channels for measurement of phase, voltage and current across non-isolated power line equipment
- 2 BWD 845 Variable persistence storage dual trace delayed sweep oscilloscope 30MHz bandwidth, 1mV/div sensitivity with 1cm/ μ Sec writing speed, auto erase and store. Mains or battery operation
- 3 BWD 820 Versatile portable oscilloscope Dual trace or differential 25MHz bandwidth 2mV/div sensitivity DC coupled X-Y-Z operation

- 4 BWD 603B 'MINI-LAB' A portable laboratory instrument combining 5 power supplies, 2 amplifiers, a wide range function generator and sweep ramp in a single unit
- 5 A range of power supplies with fully adjustable outputs up to 72 Volts 5 Amps and 18 Volts 12 Amps
- 6 BWD 804 single beam with isolated ground, 10MHz oscilloscope Internal or External trigger with auto or level select
- 7 BWD 540 portable dual trace 100MHz oscilloscope 5mV/div sensitivity with delayed trigger or sweep. Mains or battery operation



DISTRIBUTORS

Victoria BWD Instruments Pty Ltd, Melbourne
 Victoria Browntronic Pty Ltd, Melbourne
 New South Wales Amalgamated Wireless (A/sia) Ltd, Sydney
 New South Wales George Brown & Co. Pty Ltd, Sydney
 South Australia Protronics Pty Ltd, Adelaide
 Queensland LE Boughen & Co., Brisbane
 Western Australia Warburton Franki, Perth
 Tasmania D & I Agencies, Hobart
 New Zealand PH Rothschild & Co. Limited, Lower Hutt
 New Zealand W Arthur Fisher Limited, Auckland

Ph 561 2888
 Ph 419 3355
 Ph 888 8111
 Ph 519 5855
 Ph 212 3111
 Ph 36 4277
 Ph 277 7000
 Ph 23 2842
 Ph 66 3581
 Ph 59 2629

BWD INSTRUMENTS Pty. Ltd.

Miles Street, Mulgrave, Victoria, 3170. Phone (03) 561 2888

STRING SYNTHESISER KIT BACK!

(*STRING ENSEMBLE)

Due to unprecedented demand we now have new stocks of this fantastic synthesiser.

This **complete kit** includes professional Italian made 49-note keyboard, all timber cabinetry, and **all** components needed — down to the last nut and bolt. It comes complete with a comprehensive 35-page instruction and assembly manual!

Anyone considering the purchase of a string synthesiser would be **mad** not to check this out.

This is the fabulous English designed unit capable of synthesising:

- String section of orchestra (i.e. a chorus)
- Single stringed instruments
- Brass, e.g. Trumpet sounds
- Woodwind, e.g. Clarinet
- Organ
- Piano Accordion
- Even a "Mighty Wurlitzer" effect!
- Plus several combinations of above!!

\$445⁰⁰

And the price for all this wizardry? just plus \$10.00 shipped anywhere in Australia.

SHOWBAG SELLOUT

What can we say but "Thanks"

As you know, last April we advertised our goodies for enthusiasts. Well, the demand was fantastic as well as the complimentary comments about our brand new store layout. If you have not visited as yet — why not do so soon?

Remember, we are open 7 days a week and we probably have a broader range of components and kits than your present supplier!

200W (RMS) FULL RANGE P.A. BIN!!

You asked for it — a **kit version** of those heavy-duty P.A. Bins! This professionally designed pre-tuned Bass-reflex enclosure contains a **massive 18"** — yes 18" — Celestion 200 watt main driver especially cone-stiffened for higher power Bass or general PA work. Also included are 2 x 100 watt Piezo horns. System crossover is around 2KHz.

Complete kit includes all pre-cut panels, 2 horns, 18" driver, cannon connector, etc.

Build this system yourself and save a fortune on built-up prices. Remember 200 watts **RMS** capability!!

ONLY

\$495⁰⁰

complete

+ \$20.00 sent anywhere in Australia.

E. A. Graphic Analyser Kit (E. A. March '81)
Complete kit of parts including transformer, modulator, Xtals, front panel, etc.\$89.00
Colour Option\$20.00
Horwood Box to suit\$14.50

E.T.I. 477 Mosfet Amp Module (E.T.I. Jan-March '81)

Complete kit including high voltage Hitachi Mosfets, fibreglass P.C.B., **pre wound** coil, etc.\$59.00
Cast front panel\$39.50
Power Transformer\$39.50
Other components for 5000 amp available.

"Le Gong" Kit (Refer E. A. March '81)\$13.95

"P. C. Birdies" Kit (Refer E. A. May '81) only\$14.95
Contains all parts, including Jiffy Box, I.C., P.C.B. etc.

2 Channel Infrared Remote Control Kit (Refer E. A. May '81) Complete kit of parts\$65.00

Sound Level Meter Kit (Refer E. A. May '81) Complete kit of parts for this project including **high quality** electret mic. insert.\$39.50

P.C.B.'s for many other current projects available.

UHF Masthead Amp Kit (Refer E.T.I. April '81) Complete kit of parts including fibreglass boards, OM350, power supply, etc.only \$35.00

P&P CHARGES:

ORDER VALUE	CHARGE \$
\$ 5 - \$9 99	\$1 00
\$ 10 - \$24 99	\$2 00
\$ 25 - \$49 99	\$3 00
\$ 50 - \$99 99	\$4 00
\$100 or more	\$5 50


Jaycar

Shop Hours:

Mon - Sun -
9AM - 5.30PM



380 Sussex St Sydney 2000. Ph 264 6688

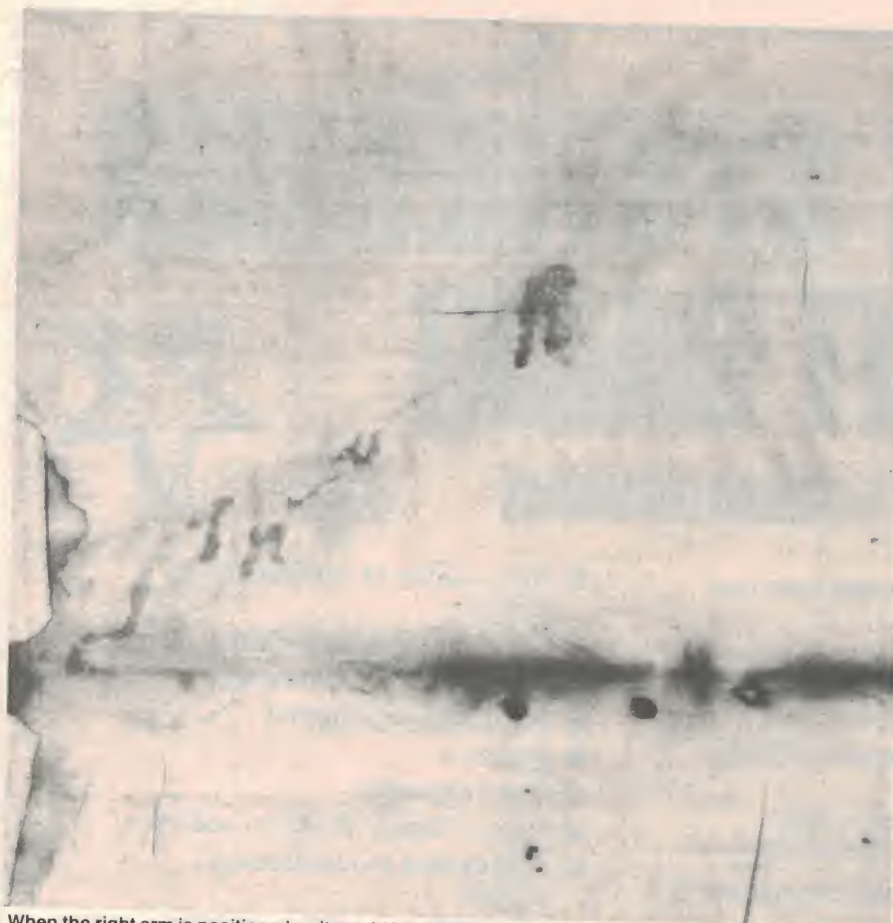

When the right arm is positioned as it would have been during the crucifixion the blood flows are clearly seen to be vertical. Note the wound in the wrist, presumably from being nailed to the cross, not through the hand as traditionally depicted.

© 1978 Barrie M. Schwartz

One important test that has not yet been carried out is carbon dating, which could tell us the age of the cloth to within ± 100 years. This has until recently been resisted by the Church as it would have necessitated large areas of the cloth being destroyed, but now that carbon dating techniques have advanced, minute threads are enough to enable a dating, and the Church has at last given permission for this to take place.

In recent research using image-intensifying and other equipment associated with the American space project, scientists have come to the conclusion that the image must have been created at a distance by some form of emanation, rather than by contact. This was borne out when, using an Interpretation Systems VP-8 Image Analyser, the image was shown to contain perfect three-dimensional information. An ordinary two-dimensional picture or photograph does not contain enough information relating to distance and proportions to be immediately translatable into a meaningful 3-D image. The fact that the Shroud image does must add considerably to the likelihood of its not having been the work of an artist.

The Shroud's history — known and conjectured

The Shroud appeared in Western Europe in the mid-1350s as the property of a chivalrous but poor French knight, Geoffrey de Charny. How it came into his possession has never been explained, but he (or more probably his widow Jeanne de Vergy) was responsible for its first exposition. It passed from him to his son, also Geoffrey, and then to his grand-daughter, Margaret, who finally entrusted it to the keeping of the House of Savoy in 1453. The Shroud was damaged by fire and by the water used to douse it in 1532, and although the triangular patches so evident on all photographs were necessary to repair the cloth after this, the image itself received little damage.

However, it is largely the mystery surrounding its sudden appearance in a relatively humble family in the fourteenth century that has caused so much doubt to be cast on the Shroud's authenticity over the succeeding centuries — apart from the scepticism of those who find 'miraculous' happenings in any case worthy of doubt. In his book *The Turin Shroud*, Ian Wilson has made a highly credible attempt at dis-

covering the history of the Shroud before the fourteenth century and explaining its mysterious reappearance. To do this he largely uses the evidence of art history to substantiate his theory.

There is a legend, substantiated by some ancient writings, of King Abgar V of Edessa (a prosperous town beyond the borders of the Roman Empire) having corresponded with Christ and later, after Christ's death, having been presented by a disciple, Thaddeus, with some kind of holy or miraculous image of Christ's face. When some years later a king who was hostile to Christianity succeeded to the throne, this 'image' was hidden in a bricked-up niche in one of Edessa's city gates — where it remained, hermetically sealed and beautifully preserved, until around the year 525.

By the time of its rediscovery Christianity was well established in both eastern and western Europe, and the image was immediately revered and worshipped as being an image of Christ 'not made by hands'. It was accredited with miraculous protective powers, and many copies were made of it. The strange thing about this image, which came to be called the Mandylion, was that in many details it resembles exactly the face on the Shroud.

There is no account anywhere in the Gospels of what Christ looked like, and until about the sixth century there had been no tradition or consensus of opinion about this in art. However, around the sixth century likenesses of Christ which correspond in too many details for coincidence to the image on the Shroud start to appear in both Byzantine and western art. They date from the discovery of the Mandylion, supposedly an image 'not made by hands', which would therefore be regarded as the definitive true image of Christ — but they are also identical to the image of the Shroud. Wilson draws the obvious conclusion: the Mandylion and the Shroud are one and the same.

His conjecture is further substantiated by the fact that the Mandylion disappeared from Constantinople (where its home had been since 944) during the sack of that city by the Crusaders in 1204, and has never been rediscovered since. Wilson speculates that the Mandylion/Shroud could have fallen into the hands of the Knights Templar, a religious and chivalrous organisation which was finally quashed by Philip the Fair of France. The Templars were reputed to have strange religious and initiation ceremonies which included the worship of a 'head' — an image of some kind. This of course laid them open to the charge of heresy,



The Shroud is removed from the backing board, which it had been fastened to for public display, by two of the Poor Clare nuns who are responsible for care of the Shroud. In rear pictured left to right: Gabriele Porretti (Italian scientific team) and Don Devan (American scientific team). © 1978 Barrie M. Schwartz

and Philip delivered them not unthankfully to the Inquisition whilst pocketing their considerable wealth.

The treasury of the Templars had been at Acre, on the eastern Mediterranean coast (close to the Gospel areas); from there it had moved to Cyprus and thence to Paris, but the 'image' or 'head' they were said to worship was never found. Descriptions of it, however, make it sound distinctly like the image on the present-day Shroud: it was said to be blurry, pale, indistinct, and many of the features, e.g. the forked beard, correspond exactly.

In 1314 the Templars' Master of Normandy, one Geoffrey de Charnay, was burnt at the stake in Paris; some 40 years later the Shroud as we know it turned up in the possession of Geoffrey de Charny. It does not seem unreasonable to conjecture some kind of family relationship — the spelling of the name was irrelevant in those days — whereby Geoffrey de Charny came into possession of the Shroud; it would also explain his family's reluctance to explain where the Shroud came from — de Charny would not wish to be accused of heresy as a Templar.

Whilst this conjectural history of the Shroud is pretty convincing, it must be emphasised that it works from the premise that the Shroud is genuine; if one wishes to look at it another way, the theory also gives us a fair amount of evidence to suppose that the Shroud could be a copy of the Mandylion — if the scientific evidence didn't seem to be against the Shroud's having been the work of an artist.

The question of authenticity

When talking of the Shroud's authenticity, it must be emphasised that we are talking about whether or not it originates from the first century A.D., and whether or not the image was 'made by hands'. Science will never be able to prove or disprove conclusively whether it was Christ's body that caused the image to be formed or not; that must be left to the speculation of religion.

There are, however, many scientific findings which indicate that the Shroud is not fourteenth century artistic forgery: the lack of pigments found, the absence of any penetration of the fibres or the spaces between fibres, the consistency of the weaving and the cotton particles with the Middle Eastern area around the first century, the anatomical evidence of the crucifixion, the pollen samples from Middle Eastern areas, notably around the Dead Sea, as well as from Constantinople and Europe. These pollen samples also substantiate Wilson's theory that the Shroud spent some time in Edessa, which is in the region of the Anatolian steppe.

There is also the question of the means of image formation, the aspect of the Shroud which scientists study with the most interest; even if it was man-made, we still have no idea of the process.

If Ian Wilson's theory of the history of the Shroud is accepted, this would diminish scepticism about its authenticity on the ground of its mysterious appearance. We would therefore seem to be left with only one large stumbling-block to acceptance of the Shroud as an

authentic image of a resurrection: the fact that it's never been seen before or since, and without explanation of the process many people are unable to accept it as a miracle.

How was the image formed?

As stated, this question arouses the main curiosity of scientists; what force could possibly have caused the formation of this negative, three-dimensional image? The word 'force' is used purposely, since it seems more and more apparent from modern research that the image was not caused by direct bodily contact with the Shroud. Attempts at reproducing this 'contact' process with bodily oils, unguents, etc, have failed to produce anything looking remotely like the image on the Shroud. The lack of penetration of the 'blood' or the image into the fibres supports this, as does the three-dimensional information carried by the image.

A more promising suggestion is that the image is some kind of scorch, the colour being the sepia of the first stage of the oxidation process before actual burning. A cloth placed over a heated brass ornament produced an image far more like that of the Shroud than any other experiment yet tried, and spectroscopic laboratory analysis bears this theory out.

What, however, could have caused a dead body to produce a radiance or force sufficient to scorch cloth, acting in so controlled a manner and over so short a period that it dissolved and fused blood flows on to the cloth as well as creating the perfect impression of the body, yet without actually burning the cloth? Some kind of very swift thermonuclear flash, acting in an upward and downward direction with no diffusion, is the answer that has leapt to the minds of many scientists, though they are no nearer to explaining how this could be possible than they were before. However, as experience at Hiroshima has shown, such powerful blasts can cause prints of shadows cast by the light of the blast to be imprinted on buildings, etc. There are even photographs to prove this.

So although scientists now have better access to investigation of the Shroud than ever before, none of their work has yet been conclusive. Research has indicated that the Shroud is unlikely to be an artist's forgery, yet scientists still cannot explain how the image got on to the linen, either naturally or by the hand of man. For this reason the results of the analysis of the scientific tests of 1978 are eagerly awaited to provide more evidence to help unravel the mystery of the Holy Shroud of Turin.

FANTASTIC OFFER!

Playmaster Mosfet **50W** Amp

Including
professionally
designed front
panel & pro-quality
knobs all
for

\$159⁰⁰

Cat. K-3515

Yes - the all new Playmaster Mosfet Stereo Amplifier is here. The genuine kit, as described by Electronics Australia (see Jan 81) complete to the last nut and bolt.

Now's your chance to upgrade your hi fi system to the very latest in audio and semiconductor technology: Power Mosfets. These remarkable devices give incredible performance, very low distortion and offer big advantages over earlier amplifier designs.

Your Dick Smith Playmaster Mosfet Stereo Amplifier kit contains all brand new, prime spec devices, complete with a superb new range of knobs imported specifically for this project. With our professionally designed front panel, your new Playmaster amplifier will look so good ... your friends will never believe you built it.

Features:

- Our exclusive step-by-step instruction manual. If you can solder two wires together, you can build this kit.
- Our Exclusive 'Sorry Dick, it doesn't work' coupon. If for some reason you cannot get the amplifier working you can send the board back to us and, for a small fee, our Service Centre will get it working for you.
- Our Exclusive money back guarantee. Examine the kit in your home for up to seven days. If you think construction is beyond you, return it in original condition and packaging, and we'll give you a full refund.

DICK SMITH
Electronics



Includes
our exclusive
'Sorry Dick it
doesn't work' return
coupon



YES: Please send me the all-new Playmaster Mosfet Stereo Amplifier kit(s) for \$159.00 each including pack & Post (normally \$5.50 extra).

I enclose: cheque/postal order for \$.....

OR please charge my Bankcard No.

496

Exp. Date

Account Name

Signature

Dick Smith Mail Order Centre.
P.O. Box 321, North Ryde NSW 2113.

Name

Address

Postcode

Your Playmaster Amplifier will be despatch within 24 hours of receipt* of this order - please allow normal parcel delivery times. * As long as we have stock!!!

RARE ADDITIONS FROM MARANTZ. SLIMLINE COMPONENTS.



Rare: very valuable.

Additions: the things added.

Ma'raantz: a range of ultra-high performance Slimline Components which blend state-of-the-art engineering with operational versatility.

MARANTZ ST450 AM/FM STEREO TUNER

Electronic Gyro-Touch tuning and digital display enable precise and speedy station selection which can be servo-locked for drift-free operation.

MARANTZ EQ20 STEREO GRAPHIC EQUALIZER

Beautifully styled, the EQ20 provides highly personalised tone control flexibility with its ten detented slide controls per channel – the perfect finishing touch to any high quality audio system.

MARANTZ SC500 STEREO PREAMPLIFIER

Traditional Marantz performance in the all important first stage of amplification. Moving coil cartridge head-amp and different cartridge load inputs are just two of the comprehensive number of facilities.

MARANTZ SM500 DC POWER AMPLIFIER

Perfectly complements the SC500 and delivers 50 watts RMS per channel. Output is displayed on two large, peak responding power level meters.

MARANTZ PM350 INTEGRATED AMPLIFIER

Bass, mid and treble controls and LED power level meters, combined with an output of 30 watts RMS per channel, make this the ideal amplifier for normal listening levels.

MARANTZ SR1100 AM/FM STEREO RECEIVER

Slim, stylish and component width, the 30 watt RMS per channel SR1100 provides a new concept in compact audio sophistication.

MARANTZ SD5010 STEREO CASSETTE DECK

Forerunner to a new generation of superior cassette decks, the SD5010 has soft-touch controls, LED meters, metal tape facility, fine bias control and an electronically controlled linear skating mechanism operating the cassette drawer.

Shown are but a few of the new Marantz Slimline Components. If you see your hi-fi as an investment and, if you demand critical performance standards as well as the best value for money, listen to the future.

Listen to Marantz.

marantz.
Now you're listening.

Distributed by MARANTZ (AUST) PTY LTD.
P.O. Box 604, Brookvale, N.S.W. 2100
Telephone: (02) 939 1900 Telex AA24121
Melbourne (03) 329 7655 Brisbane (07) 446 478
Adelaide (08) 223 2699 Perth (09) 276 2944

A Technics SL10 turntable is shown floating in the air, tilted at an angle. The turntable's platter is black with a yellow label on the right side. The tonearm and tracking arm are visible. The background is a landscape of red, rocky hills under a blue sky with scattered white clouds.

Product of a sup

Introducing the futuristic SL10, Technics' new quartz-locked, AC/DC, direct-drive turntable. Unlike conventional turntables, the SL10 has an electronically-controlled linear tracking arm that doesn't depend on gravity to track a record. All contact with a record is controlled by microcomputer, so the SL10 plays perfectly at any angle—even upside down.

The precise tracking arm control is designed to extract the maximum amount of musical detail from your records.



errior intelligence.

It's the kind of innovative thinking you expect from Technics—who introduced the world's first direct-drive turntable 10 years ago. And yet all this sophisticated technology is contained in a piece of equipment the same width and depth as an LP cover.

The SL10 is part of the highly advanced Technics range. See it at better hi-fi stockists.

We're sure you'll agree it's definitely the product of
a superior intelligence.

Technics
National Panasonic (Australia) Pty Ltd

Expanding the music experience.

Dailey/NPA21

It's a better system, at a better price, and it's Sony. In Sony's new TC-K81 three head cassette tape deck, each head

The new TC-K81 also has microcomputer control and feature-touch operation, and LED Peak Programme Meter,

Sony's 3 head system. It's 3 ways better.

has its own individual casing and suspension system.

You get precise azimuth alignment,* equal record and playback head-to-tape pressure, and reduced magnetic leakage flux.

It's a unique three-head system, with two-motor, closed-loop dual capstan drive with metal tape compatibility.

bias and record level calibration system, and Dolby** NR.

It's an exceptional new system, at an excellent price. And it's Sony.

So in three-head technology, we're three-ways better.

SONY®

*Factory aligned.

**Dolby is a registered trademark of Dolby Laboratories.



AP 3477

Scientific examination of the Holy Shroud

Few archaeological artefacts or religious relics have attracted such intense cross-disciplinary scientific interest as this. Some 50 scientists and technicians spent a week in October 1978 making an enormous variety of measurements and taking samples. Some of the results of this mammoth effort began to appear last year. This is the first review article of the researches yet published. Is the Shroud authentic, or a fake? The evidence is amazing!

Brian Dance

THE HOLY SHROUD of Turin is not only one of the greatest religious mysteries of all time, but this ancient treasure is also posing very intractable scientific problems. These problems are puzzling many of the world's top scientists, who are still unable to explain exactly how such an image could have been produced. Even if the image had no religious significance, the way in which it has been formed would justify extensive study in itself.

The Holy Shroud of Turin is an old, rather yellow piece of linen cloth about 4.3 m long by 1.1 m wide. It bears a faint image of a naked man of about 1.8 m (5'11") in height. One of its strangest features is that the highlights and shadows in this image are reversed as in a photographic negative. The image shows brownish-red stains, these being in the form of a positive image in the regions of the wrists and feet where crucifixion wounds would have been made, and also has stains resembling blood around the head and in the side of the chest, etc. Even stranger is the fact that the image (at least in the face and hands) contains three-dimensional information; scientists are using the computers designed to process the images of distant planets to try to unravel the mysteries of the image on the Shroud.

The Turin Shroud has been a subject of controversy for centuries. Many scientific results tend to support its authenticity, but even as I write this, I hear a report on British radio that Dr. Walter McCrone has found particles of fine grain oxides in samples taken from the Shroud on sticky tape in 1978, which could have arisen from paint used by a mediaeval image faker. In addition, Dr. McCrone was stated to have found 'tempera' in the specimens



(Left to right) Dr. Ray Rogers, Dr. John Jackson (American scientific team) and Professor Giovanni Riggi (Turin, Italy) take their first glimpse of the underside of the Shroud as Professor Luigi Gonella (representing the Archbishop of Turin) looks on.
© 1978 Barrie M. Schwartz

— a material used in ancient paints. However, the results of the recent work seem to show conclusively that the image could not be a painted one.

The image

The brownish-coloured image on the Shroud is that of a nude man probably aged between 30 and 40 years. One half of the Shroud carries an image of the front of the man and the other half of the back, so it seems that the body was laid with the feet at one end of the Shroud and the head at the middle; the other half was then folded over the body.

It was not until 1898 that the image was discovered to be a negative one. Secondo Pia had taken a photograph of the image and realised that the image on his photographic plate was really the positive and the Shroud image the negative. Who would wish to fake the image

of a man as a negative (before photography was known)?

Paintings of crucifixions show nails driven through the hands of the crucified person, but the French surgeon Dr. Pierre Barbet experimented with dead people and found that nails in the palms will not support the weight of the body. He found that a nail in the forearm would do, but it was not until 1968 that the skeleton of a crucified man was found with marks on the arm showing a nail had been driven through the arm. Thus both medical and archaeological evidence indicates that the crucifixion marks on the wrists of the Shroud image are in the correct places, whereas a faker would have put the nails in the centre of the palm as the painters have done.

The apparent absence of thumbs in the Shroud image has been attributed to ▶

the nails driven through the wrists piercing the median nerves and producing an automatic contraction of the thumbs.

Little more scientific knowledge about the Shroud came to light until 1973, when it was found that the image on the cloth is quite superficial, having a depth of only a few micrometres⁽³⁾ on the top of the linen threads. The image is not visible under the microscope inside a thread.

If some form of paint had been used to produce the image on the Shroud, the medium used would have darkened more rapidly than the remainder of the cloth⁽³⁾, but no discolouration of this type is visible. One would also expect the paint medium to affect the flow of water used during the fire through the image region, but this is not found⁽³⁾. Thus if the image had been painted on the linen, it seems this painting must have occurred after the fire of 1532 and this is known to be contrary to fact.


Pollen samples

In the 1973 tests sticky tape was pressed on the Shroud to remove dust and any other particles which adhered to it. It was found that pollen grains were present not only from plants found in France and Italy, but also from those found in Palestine and in saline regions such as the Dead Sea. This may give some general indication that the Shroud had at one time been in the region of Palestine, but it cannot prove this, since pollen can be carried very long distances by various means (birds, winds, etc).

Three dimensions

In 1977 two scientists of the US Air Force Academy, John P. Jackson and Eric J. Jumper, reported that they had found that the density (or darkness) of the image varies directly with the distance that the corresponding part of the body would have been from the Shroud which covered it⁽⁴⁻⁶⁾. Microdensitometer measurements have been correlated with the estimated body-cloth distance and these suggest that the image contains three-dimensional information. The darkest parts of the image, such as the nose, would have been closest to the Shroud.

Jumper and Jackson felt that the image must therefore have been formed at a distance and not by close contact. They carried out measurements on the cloth-to-body distances using a man of similar build in a similar pose with the aid of stereometric photography⁽⁶⁾. Their photographs were processed with a complex image analyser instrument which had been designed to convert variations of image intensity into

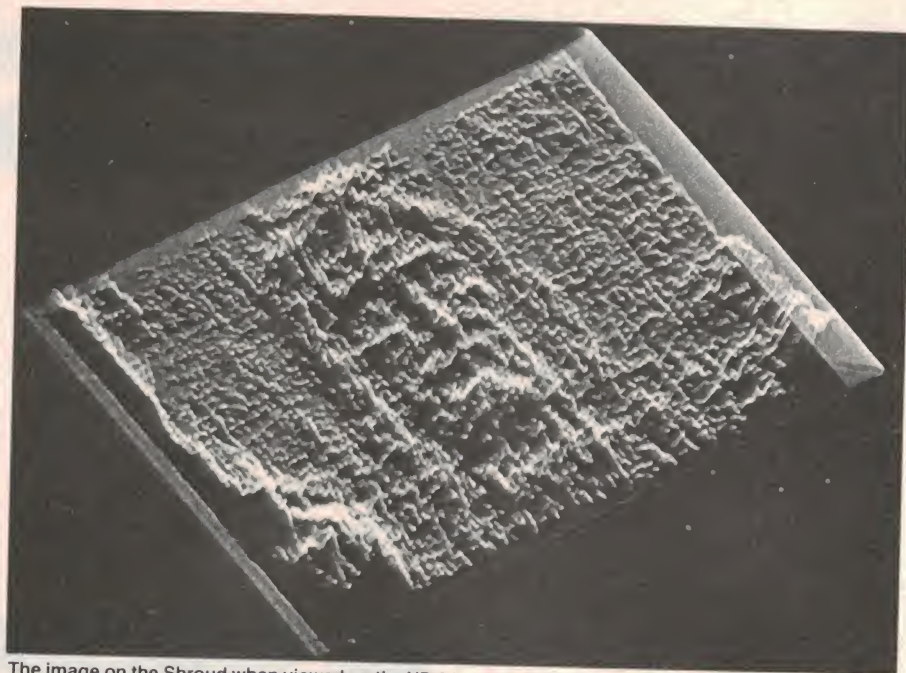

The image on the Shroud when viewed on the VP-8 Image Analyser. (Courtesy JPL).

distance. They found that the Shroud contains three-dimensional information and used a computer to reconstruct a three-dimensional model of the image. This clearly showed that the image of the Shroud is quite unlike any normal photographic image. The smallest feature of the image which can be resolved is 5 mm⁽⁷⁾.

Our discussion so far has been a brief account of the work on the Shroud up to 1978, although many details have been omitted for brevity. For example, we have not considered the attempts made to produce shroud-like images by scorching linen. Neither have we considered the ancient practice of washing cloth in a solution known as 'struthium' (containing the soap weed *Saponaria officinalis*) which not only softens the cloth, but which is toxic to simple living organisms and which therefore inhibits the growth of moulds, mildew, etc.; such a wash may have given the Shroud its fluorescence⁽³⁾.

STURP

It was largely through the interest created by the three-dimensional image work in the USA that a team of 32 specialist US scientists was formed who sought and obtained permission to carry out by far the most thorough scientific investigation ever made on the Shroud.

Some of the scientists call themselves 'sindologists', this name being derived from the Italian word 'sindone' (shroud). They are a largely self-appointed, independent, non-profit-making group of scientists and assistants and do not work under the auspices of any other body. The name STURP (Shroud of

Turin Research Project Incorporated) has been adopted by this group. Previous investigators have been mainly selected by the Archbishop of Turin.

STURP's scientific proposals were submitted to the Archbishop of Turin (keeper of the Shroud) and to Centro Internazionale di Sindonologia in September 1977, and to Umberto II, a former King of Italy and the legal owner of the Shroud; all gave their approval.

The workers were divided into teams to cover the various types of investigations. They worked out their testing schedule and collected and constructed specialised instruments ready for their trip. Basically they were to examine the Shroud with electromagnetic radiation of all wavelengths from the mid-infrared through the visible and ultraviolet to the X-ray region.

A special test frame was constructed to support the Shroud and its backing cloth, which had been sewn to it after the fire of 1532. The frame could be rotated from the vertical to the horizontal⁽⁹⁾ and magnetic strips were used to hold the Shroud. Panels 200 mm wide could be removed from the middle part of the frame to provide optimum access for some X-ray investigations.

Operation STURP

The Shroud was placed on public display in October 1978 to commemorate the 400th anniversary of its arrival in Turin, this being the first public display for 45 years. At the end of this display on Sunday, October 8 1978, the Shroud was removed from its nitrogen-filled case to



A photographic negative of the Shroud facial area shows considerable detail. The image contains three-dimensional information — darkness (brightness here) varying with apparent distance from body to cloth. The most striking evidence of this was produced by Jackson and Jumper, seen in the picture at left, using image analysing equipment at the California Institute of Technology's Jet Propulsion Laboratory. © 1978 Barrie M. Schwartz

the nearby Visiting Princes' rooms of the Palace of the House of Savoy, where it was given over to the scientists for five days.

The main objects of the investigations were to try to establish the nature of the image on the Shroud, to characterise the image spectrally over a wide range of wavelengths, to investigate the nature of the stains on the Shroud and in particular to try to ascertain if they are due to blood, and to study the manufacturing technique of the cloth so as to check whether it is likely to have been woven about the time of Christ. It was also hoped to be able to make recommendations about the optimum conditions of storage to prevent degradation of the image with time. The testing had to be



Transferring the Shroud from its display support board to the Shroud support table. Pictured left to right: Don Janney, Tom D'Muhala, Mark Evans, John Jackson, Don Devan. In background: Riccardo Bissi (Italian team photographer).

© 1978 Barrie M. Schwartz

non-destructive and could only be carried out during this one period.

The team of investigators, almost all from the USA, has agreed to publish all their findings and some of their papers have already appeared. The Church has agreed that it will not interfere with these publications. As the scientists have been working in their spare time, there has inevitably been some delay in the publication of their results. A 'complete' report may appear by 1982.

Scientific work

The work of the scientists included looking for fluorescence under X-ray and ultraviolet irradiation. X-ray fluorescence provides data on the elements present in various parts of the Shroud. In the X-radiography work, low-energy X-rays were passed through the Shroud and were detected by an X-ray film placed at the back of the Shroud. The films were manually processed in a nearby darkroom and were given a preliminary visual examination so that any necessary changes could be made in the exposure of the subsequent films⁽⁹⁾.

In the visible region an extensive series of photographs was made with red, green and blue filters for colour separation so that colour mosaics of the whole surface of the cloth could be built

up at reductions of 5.6:1 and 22:1⁽⁹⁾. The importance of this visual light photographic work becomes obvious if one remembers that the computer work on the image, including three dimensional image work, was carried out with photographs made in 1931⁽¹⁰⁾. The filters were chosen by Sam Pellicori, a physicist employed at the Hughes Aircraft Company's Santa Barbara Research Centre, California, so as to bring out the slight colour differences between various parts of the Shroud. The images underwent further processing by computer programs developed at the Jet Propulsion Laboratory's Image Processing Laboratory for Planetary Studies, which have been especially designed to bring out every possible piece of detail in the images returned by spacecraft from distant planets. The raw images returned by such spacecraft often show little contrast — rather like the Shroud. Over 500 photographs were taken at various wavelengths.


In other work ultraviolet transmitting filters were used for contrast enhancement. Another series of photographs was taken in which the visible spectrum was divided into 10 nm intervals by a series of filters⁽⁹⁾. The Shroud was also examined in infrared radiation to ascertain if any new features became visible, since chemicals containing certain groups of atoms may be identified in this region. Infrared thermographic techniques were employed, since together with micro-Raman spectra these are considered to be the most likely methods for identifying blood components and certain types of burial substances mentioned in the Scriptures⁽⁸⁾.

Minute particles of fibre, pollen, dust, etc. were removed by means of specially prepared adhesive tapes and also by means of a suction device. In the case of the tape, both the adhesive and the tape were made of pure hydrocarbons so that the Shroud was not contaminated — indeed, the scientists wore white gloves when handling the Shroud. The adhesive tape was applied to the Shroud with a specially designed roller; after it had been removed each tape was attached to a labelled microscope slide and placed in a box which was later sealed.

The particles of material removed on the tapes were examined by visual microscopy and by the micro-Raman method. Further work on these particles involved electron spin resonance, electron microscopy, ion microprobe techniques and the scanning electron microscope⁽⁹⁾. It is hoped that scanning electron microscope images at magnifi- ▶



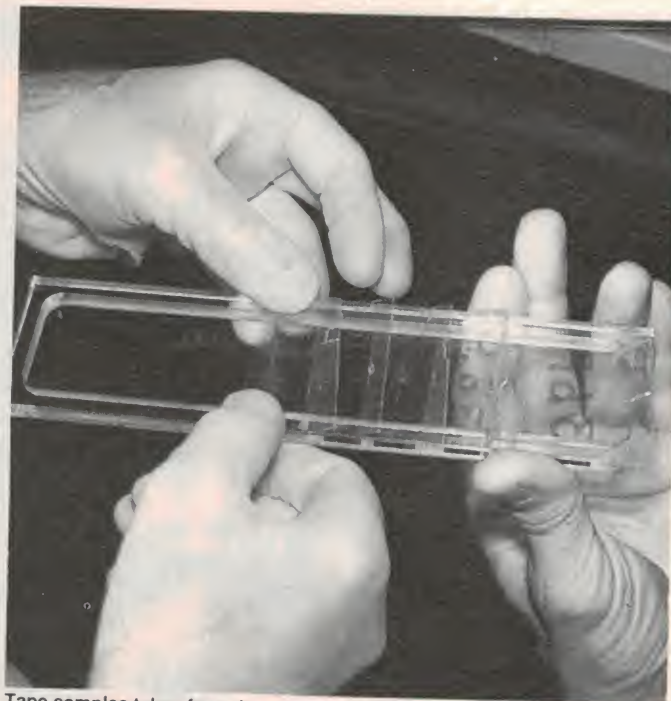(Left to right) Chemist Ray Rogers (American scientific team) looks on as Swiss criminologist Dr. Max Frei takes a tape sample of the Shroud. Rogers took 36 tape samples for the American team. © 1978 Barrie M. Schwartz



Tape samples taken from the surface of the Shroud are placed on specially sterilised glass plates. © 1978 Barrie M. Schwartz

cations of up to 10 000 times will provide data of the image depth and sharpness at different points on the Shroud and this may help us to produce a satisfactory theory of the image formation mechanism⁽⁸⁾.

Even the back surface of the Shroud was examined after parts of the backing cloth (stitched on in the 16th Century) had been loosened. An Italian biologist, Giovanni Riggi, employed fibre optics to photograph the back surfaces, and he also collected particles from it⁽⁶⁾. A few extra threads were taken for later examination.

Now that we have looked generally at the scope of the 1978 investigations, we will consider specific items of the work in more detail, together with the results already published.

X-ray fluorescence

The main aim of the X-ray fluorescence experiment was to estimate the variations in the concentration of the elements in different areas of the Shroud containing 'blood' stains, other parts of the image, the background cloth, the scorch areas and the patches⁽¹¹⁾. Elements with atomic numbers exceeding 16 could be detected with the equipment used.

An X-ray tube operating at 50 pkV and 20 mA and shielded in lead (Figure 1) had its beam directed on to a tin target within the shielding⁽¹¹⁾. This produced the 25.5 keV K-alpha radiation, a 12 µm thick silver foil located over the outlet removing the K-beta

radiation from the tin target. Thus this system produced a beam containing almost monochromatic 25.5 keV X-rays which were allowed to strike the vertical surface of the Shroud at about 45°.

The fluorescent X-rays from the Shroud were detected by a silicon (lithium) semiconductor detector shielded with lead so that an area of 1.3 cm² of the Shroud surface was examined at any one time. The pulses from the detector were amplified and fed to a pulse-height analyser having 512 channels. Each spectrum was transferred to a digital cassette for subsequent analysis.

The X-ray fluorescence workers collected a total of 37 spectra (including background, calibration and Shroud data) and made further calibration measurements after their return to Los Alamos⁽¹¹⁾. The most obvious feature in all of their spectra was a Compton peak formed by the scattering of 25.5 keV X-rays by electrons. However, one can detect elements present in the Shroud by the presence of peaks in the photon energy spectra at less than 20 keV; these peaks are due to the K-alpha radiation of the elements (fluorescence).

A prominent peak due to iron at 6.4 keV (with a smaller peak at 7.0 keV due to its K-beta X-rays) was found in



Scientists eagerly examine the underside of the Shroud, seen for the first time in 400 years. This is the first photograph taken of the underside of the Shroud. © 1978 Barrie M. Schwartz

the 'blood' stained regions and a much smaller iron peak in other areas of the Shroud (Figure 2). This does not prove that the 'blood' stained areas contain blood, since a material such as jeweller's rouge (Fe_2O_3) could have been used as an image-colouring agent. A quantitative comparison between whole blood, rouge stains and the Shroud results was made. Calcium and strontium were found, but the workers suggested that these may have arisen from dust carried from the marble and limestone regions of northern Italy. The absence of heavier atoms, as far as could be detected with the equipment used, indicates that pigments or dyes containing such elements could be present only in small amounts.

The paper concludes by suggesting that radioisotope sources have advantages over an X-ray tube source for any future X-ray fluorescence study⁽¹¹⁾. It is feasible for a future study to look for potassium in the 'blood' stains with equipment of adequate sensitivity, since blood contains appreciable amounts of this element as well as iron.

UV work

The ultraviolet-visible reflectance and fluorescence spectra from the Shroud have been investigated in detail by the husband-and-wife team of Roger and Marion Gilbert, who state⁽¹²⁾ that their measurements were performed as an aid to later analysis of the substances making up the various stains on the cloth and to a possible determination of the manufacturing techniques of the

cloth. They took fluorescence and absolute reflectance spectra on areas of the Shroud not containing markings for possible comparison with other cloth samples. They also recorded fluorescence and relative reflectance spectra of the image, scorched and bloodstained areas, the reflectance being relative to clear areas.

These workers used a 150 W xenon lamp or a 200 W mercury arc lamp with a 1200 line/mm diffraction grating monochromator to provide a beam of 5 nm bandwidth, which illuminated a 6 mm by 3 mm area of the Shroud at an incident angle of 45° ; this angle was chosen rather than 0° in order to reduce the apparent spaces between the threads of the cloth and hence to reduce the contribution from the backing cloth. The beam optics need not concern us. The detection channel was similar to the source channel and contained a second monochromator with an 8 nm bandwidth. The output from this second monochromator was directed onto the photocathode of a photomultiplier tube.

A voltage proportional to the wavelength of the second monochromator was fed to the x-axis input of a pen recorder and the amplified signal from the photomultiplier tube to the y-axis input. Twenty six scans were made over the 250 nm to 750 nm band in the re-

flectance measurements and a scan of magnesium oxide was made; the reflectivity of the latter was assumed to be unity. The xenon lamp was used for these reflectance measurements.

The mercury arc lamp was used in the fluorescence measurements with the source monochromator set at 365 nm and an ultraviolet-transmitting, visible-absorbing filter after the monochromator to reduce stray visible light. An ultraviolet-absorbing filter was placed in the detection channel and the monochromator was continuously scanned from 390 nm to 700 nm.

The relative spectral reflectance of four areas of the Shroud image is shown in Figure 3 and the spectral fluorescence of four similar areas in Figure 4⁽¹²⁾. It can be seen that the lower the reflectance of an area, the lower the fluorescence. At lower fluorescence levels, the peak moves towards longer wavelengths.

These workers noted that the image (without magnification) seems to have the same sepia colouring as the lightest of scorch marks and that the image colour does not seem to come from a particular matter. The image is extremely faint under backlighting, whereas the bloodstains then stand out as dark reddish-brown spots.

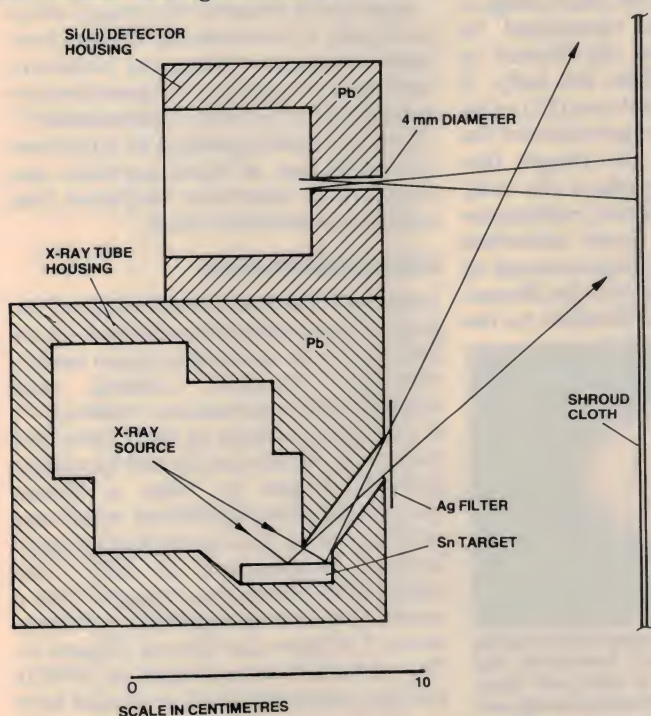


Figure 1. The apparatus used for the X-ray work. (Reproduced from reference 11).

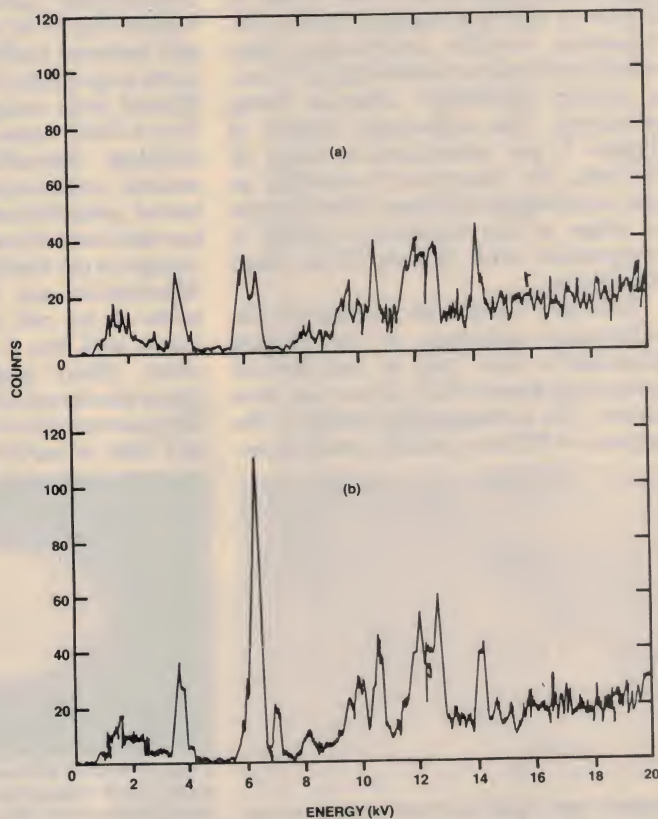


Figure 2. (a) X-ray fluorescence spectrum; (b) similar spectrum taken over the side wound 'blood' region. Note the higher peak at 6.4 keV. (Reproduced from reference 11.)

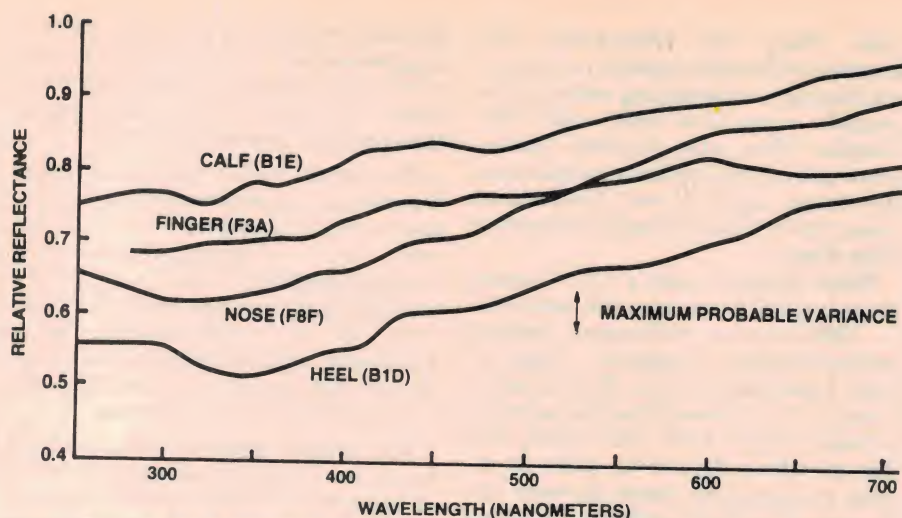


Figure 3. Relative spectral reflectance of four regions of the body image. (Reproduced from reference 12.)

The body image areas seem to have the same spectral reflectance properties as those of the scorched areas together with similar fluorescence characteristics. The stains seem to quench the fluorescence of the cloth and to exhibit a low-level fluorescence of their own in the 600-700 nm region.

Further spectral work

Further work on the spectral properties of the Shroud, mainly in the visible region, has been described in a paper by S.F. Pellicori⁽⁷⁾. His results using a 'quick look' spectrometer are shown in Figure 5; this spectrometer used a continuously variable interference filter wheel to provide a bandwidth of 17 nm, a silicon photodiode detector being employed. The reflectance curves of Figure 5 are normalised to unity at 700 nm, the absorption increasing as the wavelength decreases. The changes in slope of the bloodstains makes a comparison with human blood more definitive.

Pellicori⁽⁷⁾ has also compared the reflectance spectrum of the Shroud bloodstains with that of four-day-old laboratory blood which, in one case, was baked. The corresponding bands in the regions of 550 nm and 625 nm have en-

abled him to say that there is sufficient correlation to decide that the material on the Shroud is blood.

The relative spectral responses of substances that may once have been in contact with the Shroud have been examined before and after baking in air for five hours at 150°C; the baking simulates aging of the cloth and produces a colour similar to that of the clear areas of the Shroud⁽⁷⁾. This colour is due to the formation of double bonds in the cellulose, which results in increasing absorption at shorter wavelengths. Experiments have shown that an invisible deposit of perspiration plus skin oils becomes visible on baking and displays a spectrum closely resembling the Shroud body image. It was concluded that a likely cause of the body image is cellulose degradation stimulated by natural substances on the Shroud or burial preparations from the body. It has also been shown that iron (III) oxide (rouge) is not wholly responsible for the 'bloodstains' nor for the image; this oxide is too red to produce the body image and has a different reflectance curve. Many people have remarked about the decrease in image contrast as the observer comes nearer to the Shroud and this is partly attributable to the

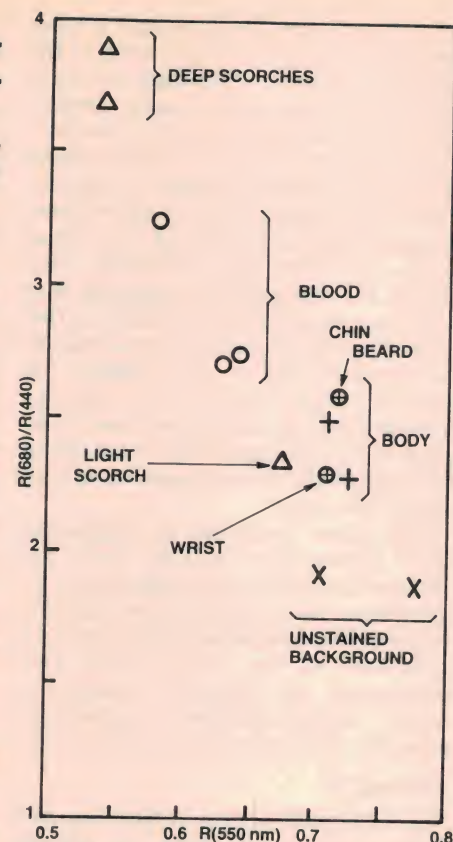



Figure 4. Spectral differences of various details on the Shroud are intensified by taking the ratio of widely separated reflectances and normalising to the absolute R at 550 nm. Notice the grouping by stain type, and that the darker the feature is, the redder it is. The body image points 'Beard' and 'Wrist' contain minute traces of blood.

increased contribution of scattered light into the cone of vision.

In order to preserve the image, which is already of low-contrast, storage in an inert atmosphere (nitrogen) containing some water vapour at temperatures not exceeding 25° has been recommended⁽⁷⁾. Physical handling should be minimised to reduce loss of blood particles, and exposure to ultraviolet radiation from sunlight should be avoided.


Infrared studies

Infrared reflectance spectroscopy of the Shroud was undertaken in the 3 - 5 μ m and the 8 - 14 μ m bands, where readily available detectors coincide with atmospheric transmission windows⁽¹³⁾. A black-body source at 980°C provided radiation, which was focused by sodium chloride lenses to form a 20 mm diameter spot on the Shroud, which was 400 mm away, thus producing an equilibrium temperature of 59°C. The reflected radiation was detected with a mercury-cadmium-telluride detector about 2 m from the Shroud (Figure 6). The radiation was chopped at 500 Hz and the reflected signal processed with a synchronous amplifier to provide background rejection.

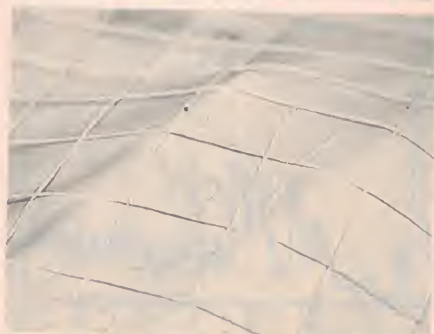

Reflected light close-up of #3 bloodstain on the forehead of the frontal image, with a 6 cm grid placed over that area of the Shroud for size reference.

© 1978 Barrie M. Schwartz

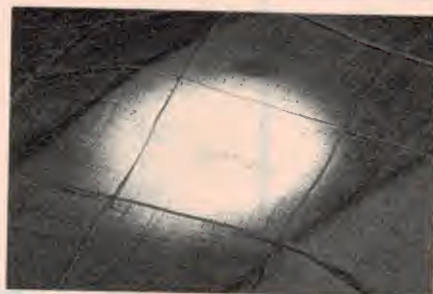

#3 bloodstain of the frontal image of the Shroud viewed with transmitted light. This is the first photograph of the Shroud of Turin with transmitted light, showing the comparative density of a bloodstained area versus image area.

© 1978 Barrie M. Schwartz

The spectral similarities of most of the features observed rendered the results somewhat inconclusive. The Shroud bloodstained areas showed different spectra from known bloodstains both in the shorter (Figure 7) and longer wavelength (Figure 8) bands. It has been suggested that these differences are due to surface effects rather than the chemical composition of the materials⁽¹³⁾.

The same workers carried out imaging experiments in the same two wavelength bands using two 1500 W photographic floodlamps to illuminate the area⁽¹³⁾. No image contrast was observable without this illumination, showing that an increase in the temperature above that of the background was required; without this the differences in emissivity were below the limit of sensitivity of the cameras. Good contrast was found in the 8 to 14 μm band, but no features could be found in

Figure 5. Shroud background linen and modern linen artificially aged by baking. Reflectance of iron oxide to be compared with body image (Figure 7). If Fe_2O_3 were present in a high enough concentration to make up a visible image, its reflectance curve would be quite different from the Shroud's image.

Figure 6. Comparison between Shroud blood spectrum and laboratory blood artificially aged by baking.

Figure 7. Laboratory simulations of body image spectral reflectance characteristics produced by accelerated aging, and Shroud body image included for comparison. P_1 and P_3 are skin oil plus perspiration.

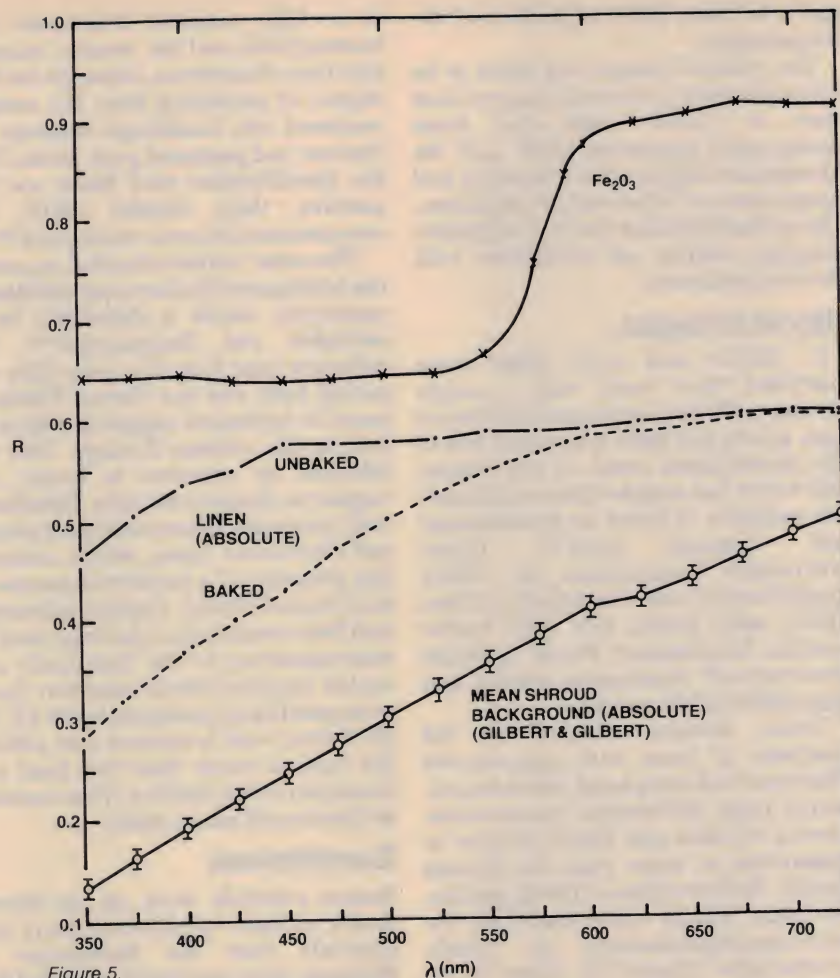


Figure 5.

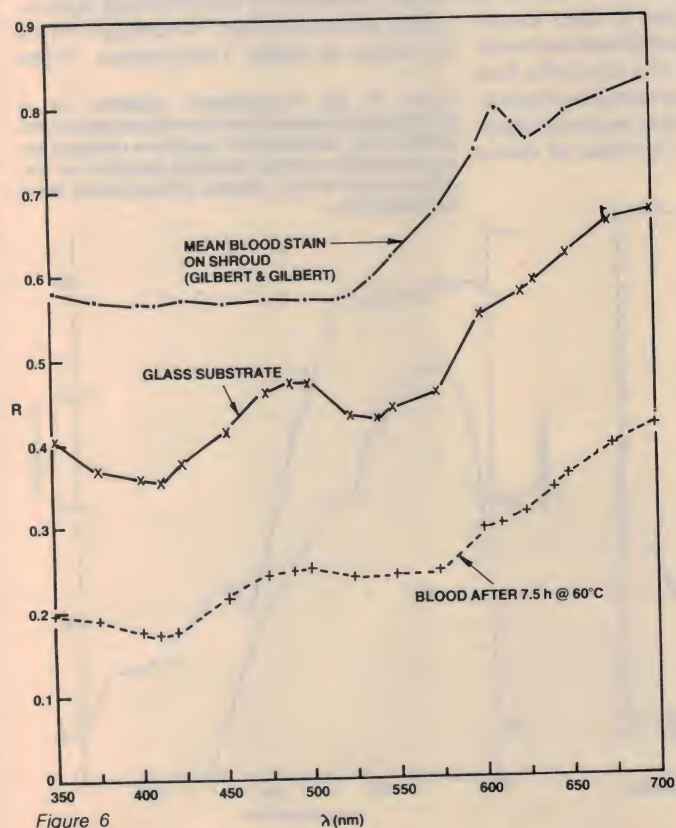


Figure 6

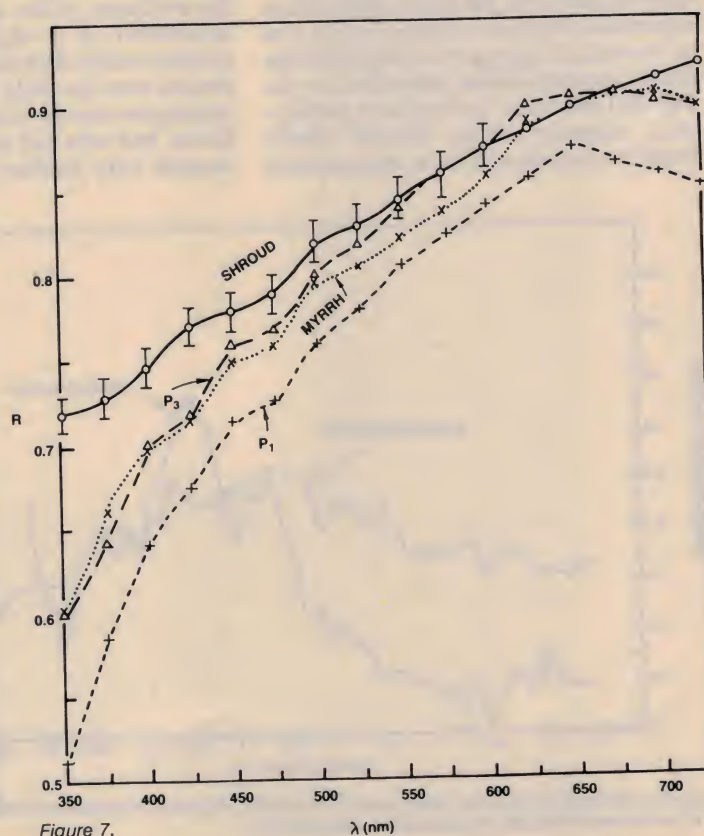


Figure 7.

the 3 to 5 μm band regardless of the illumination.

The infrared image was found to be approximately a reversed image of that seen in visible light, the linen background appearing black and the bloodstains bright, with the scorch and image areas of intermediate brightness. The authors felt that the thermographic imaging results are consistent with their expectations.

Blood on tapes

J.H. Heller and A.D. Adler have described their work with a single 25 mm x 75 mm specimen of adhesive tape which had been pressed on one of the bloodstained areas of the Shroud and which has enabled them to identify the presence of blood by spectroscopic and chemical tests⁽¹⁴⁾. Under microscopic examination at 1000X magnification, some hundreds of linen fibrils were found, less than twelve possible bloodstained fibrils, a single brownish-red translucent crystal and other debris of the centuries.

These workers stained an old specimen of linen with one-year-old blood and took samples of this using adhesive tape. Microscopic examination showed crystals and fibrils similar in appearance to those from the Shroud sample. Both the Shroud fibrils and the simulated fibrils were examined by micro-spectrophotometry at visible wavelengths (Figure 9). There is no specific spectrum for blood, since much depends on its exact chemical state and on its state of aggregation, but all of the fibrils showed intense absorption in the 400-450 nm band, indicating a porphyrinic substance. The Shroud fibrils would be expected to show the spectrum

of a fully oxidised denatured met-haemoglobin and the results indicated this type of spectrum, although the high degree of scattering from the samples rendered the bandshape features less distinct and produced peak shifts. Thus the identification with blood was less positive than desired when this measurement alone is considered⁽¹⁴⁾.

The same workers decided to convert the heme group in the suspected blood to porphyrin, which is detectable by its excitable red fluorescence⁽¹⁴⁾. The adhesive tape from the glass slide was peeled back and the Shroud fibrils exposed to hydrazine vapour to reduce the iron to the valency II stage. This was followed by exposure to formic acid vapour to displace the iron. Irradiation with longwave ultraviolet then showed red fluorescent spots, which indicated the presence of a porphyrin species on the Shroud fibrils. Vapour techniques had been employed in the hope that the micro-spectrum of the chemically converted material would establish that it was specifically protoporphyrin IX, but the formic acid treatment had affected the tape so much that this final confirmation of the identity of the material as blood could not be made.

Conclusions

Recent scientific work on the Shroud seems to have established fairly conclusively that the bloodstains do originate from real blood, provided that the evidence of the various workers is considered as a whole. It also seems almost certain that the Shroud was once draped over the body of a man who had undergone not only the tortures of crucifixion, but who had also received other wounds very similar to those of Jesus

Christ as described in the Gospels (the side wound, the crown of thorns and the beating).

The conclusions on the mechanism of image formation seem less definite. The suggestion of Pellicori that the image was formed by perspiration and oils accelerating the normal degradation and darkening of the cellulose of the cloth seems to be the most promising. It is supported by laboratory evidence in which darkening of cellulose cloths was speeded by baking; body oils, sweat and olive oil (the latter is found in myrrh and aloes used in the burial oils of ancient Palestine) were used in these experiments⁽¹⁵⁾. The images formed in some hours and had some characteristics of the Shroud image when viewed microscopically.

Pellicori's hypothesis suggests the Shroud image was formed by skin contact. Some say this could not explain the three-dimensional effect, but Pellicori⁽¹⁵⁾ feels we do not yet have enough understanding of the image transfer mechanism to answer this point. Not all scientists agree with Pellicori's suggestions. Early suggestions that the body image is light singeing of the cloth with a hot statue seem to be refuted by ultraviolet fluorescence studies, which show that the body image has a different fluorescence from the fire-scorched regions. As regards the work of McCrone (mentioned earlier), the STURP team made extensive tests to detect pigments or their binding agents, using microchemical techniques down to levels of under 1 microgram. None

Figure 9. (a) Transmission spectrum of a brownish-red stained fibril from a blood area of the Shroud. (b) Transmission spectrum obtained by transformation of the reflection spectrum of the blood areas of the Shroud. (Reproduced from reference 14.)


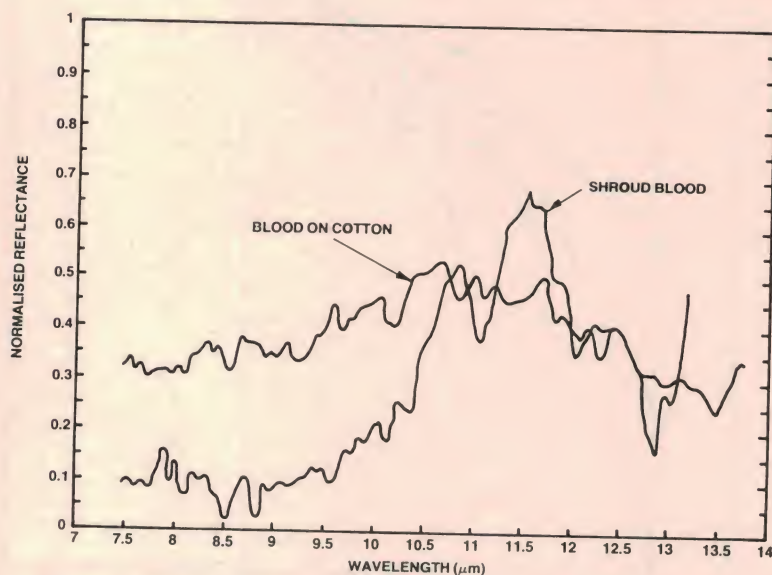


Figure 8. Normalised spectral reflectance of blood-on-cotton and Shroud blood in the 8 to 14 μm infrared band. (Reproduced from reference 13.)

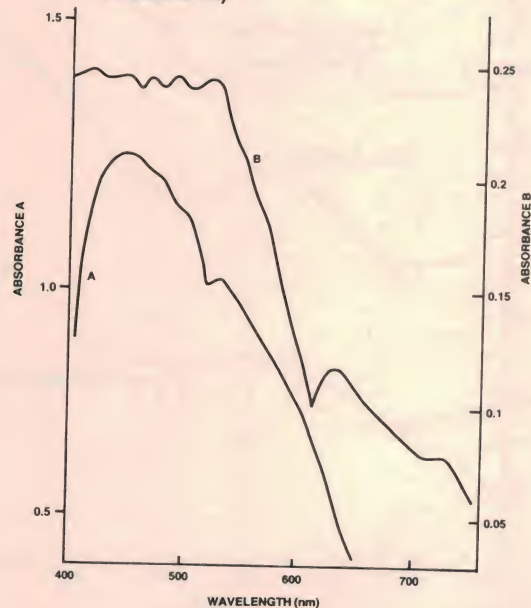

were found and the traces of iron oxide revealed were not only invisible to the naked eye, but equally distributed throughout the image and non-image areas. How could they produce the image, in spite of McCrone's views?

The very detailed tests on the Shroud have given no indication that it could have been a fake — indeed, they indicate the opposite view. Although it might have been possible to prove the Shroud a fake, it seems science can never prove it is genuine, nor whom it covered — although no other suggestion than that it was the body of Jesus Christ seems to have been made. Science's main concern, however, is with 'how?' and not with 'whom?'.

Rev. David Sox (formerly Secretary of the British Society for the Turin Shroud) stated on British Radio that he is still not sure whether the Shroud is a fake. He has been pressing for its carbon dating for many years, but mentioned he no longer considers the Shroud to be important to his beliefs — especially as there is no indication in the Gospels that such a sign would be left for posterity.

Carbon dating

Now that we have considered the published results of the work which has already been carried out on the Shroud, let us consider a long-proposed test which has not yet been performed. If the approximate age of the linen could be established, this might provide additional evidence as to whether the Shroud was made about the time of Christ. The obvious technique is the well-known one of carbon dating developed by Willard F. Libby.

Carbon-14 (a radioactive beta emitter) is formed in the upper atmosphere of the earth when neutrons formed by cosmic radiation interact with nitrogen nuclei. This carbon-14 has a long half-life (about 5730 years), so it becomes well-mixed with the non-radioactive carbon of the earth's atmosphere. Plants take in carbon dioxide from the air, so that the amount of carbon-14 per gram of carbon in a plant becomes equal to that in the air. This amount produces 15.3 radioactive disintegrations per minute per gram of carbon (dpm/g).

If a plant ceases to live, the carbon-14 it contains will continue to undergo radioactive decay but no new carbon-14 is taken in from the atmosphere. Thus after 5730 years the activity of the carbon-14 falls at $15.3/2 = 7.65$ dpm/g. Hence by measuring the activity of a specimen of carbon from a material such as linen which was once a living plant, one can estimate the time at which the plant ceased to be alive. An accuracy of

the order of ± 150 years may be obtained for a specimen aged about 2000 years.

The reason this carbon-14 decay has not yet been used for dating the cloth of the Shroud is that an area of some hundreds of square cm⁽³⁾ of the cloth would have been destroyed by such work through the use of the dating techniques available in the past. If the results were ambiguous, still more of the cloth would be needed. In any case experts feel it would be very surprising if the Shroud cloth has a date before the first century or after the fourth century⁽⁸⁾, so one may well ask whether carbon dating can provide much useful information.

Recently carbon-14 dating techniques have been developed which should be able to give an estimate to within about 100 years using only a few milligrams of the cloth. American workers at the University of Rochester and at the Brookhaven National Laboratory have proposed dating by this new technique, which involves an accelerator and a sensitive mass spectrometer. The Shroud's owner, King Umberto, has already given his assent⁽³⁾ and the matter is still under consideration by the Archbishop of Turin.

Material in the form of a few threads has already been removed for the purpose of carbon dating so that it will not be necessary to open the sealed Shroud container to obtain samples. It seems almost certain that dating will be carried out in the not too distant future with laboratories in the USA and England competing for the work on milligram samples. ●

Acknowledgements

The writer is indebted to The Optical Society of America, Washington, for permission to use material from the Journal *Applied Optics*; to Heyden & Son Ltd, London, for permission to use material from their Journal *X-ray Spectrometry*; and to Dr. H.B. Porter, Editor of *The Living Church*, Milwaukee, USA, for providing copies of material from his Journal and for permission to extract short items from it. Acknowledgement is also made to the Centro Internazionale Di Sindonologia, Turin, for providing copies of their Journal *Sindon*, which is devoted to work on the Shroud. Gratitude must also be expressed to Don Lynn, Jet Propulsion Laboratory (Image Processing), to S.F. Pellicori, Santa Barbara Research Centre, Goleta, California, to Rev. Adam J. Otterbein, President of the Holy Shroud Guild, New York, to David Sox, formerly of the British Society for the Turin Shroud, and to Hughes Aircraft Company, California. Lastly acknowledgement is made to your Editor for suggesting this fascinating subject which involves so many scientific disciplines.

References

1. D. Crispino, 1204: 'Deadlock or Springboard?' *Sindone*, Vol. 22, p. 24, December 1980.
2. I. Wilson, *The Shroud of Turin: The Burial Cloth of Jesus Christ?*, Doubleday & Co., New York, 1978.
3. R.H. Dinegar, 'The Turin Shroud', *The Living Church*, Milwaukee, USA, Vol. 180, No. 6, p. 9, February 10 1980.
4. P. Jackson et al, 'The three-dimensional image on Jesus's Burial Cloth', in *Proc. 1977 U.S. Conf. of Research on the Turin Shroud*, Holy Shroud Guild, New York, 1977.
5. E. Jumper et al, *The Numismatist*, 1349, July 1978.
6. K.F. Weaver, 'The Mystery of the Shroud', *National Geographic*, Vol. 157, No. 6, p. 729, June 1980.
7. S.F. Pellicori, 'Spectral properties of the Shroud of Turin', *Applied Optics*, Vol. 19, No. 12, p. 1913, June 15 1980.
8. R.H. Dinegar, 'Operation STURP', *The Living Church*, Milwaukee, USA, Vol. 178, No. 9, p. 9, March 4 1979.
9. E.J. Jumper and R.W. Mottern, 'Scientific Investigation of the Shroud of Turin', *Applied Optics*, Vol. 19, No. 12, 1909, June 15 1980.
10. J. Hanlon, 'Christ under the Microscope', *New Scientist*, Vol. 80, No. 1124, p. 96, October 12 1978.
11. R.A. Morris, L.A. Schwalbe and J.R. London, 'X-Ray Fluorescence Investigation of the Shroud of Turin', *X-Ray Spectrometry*, Vol. 9, No. 2, p. 40, 1980.
12. R. Gilbert, Jr. and M.M. Gilbert, 'Ultraviolet-visible reflectance and fluorescence spectra of the Shroud of Turin', *Applied Optics*, Vol. 19, No. 12, p. 1930, June 15 1980.
13. J.S. Accetta and J.S. Baumgart, 'Infrared reflectance spectroscopy and thermographic investigations of the Shroud of Turin', *Applied Optics*, Vol. 19, No. 12, p. 1921, June 15 1980.
14. J.H. Heller and A.D. Adler, 'Blood on the Shroud of Turin', *Applied Optics*, Vol. 19, No. 16, p. 2742, August 1980.
15. S. Pellicori and M.S. Evans, 'The Shroud of Turin Through the Microscope', *Archaeology*, pages 34-43, January/February, 1981.

Further reference material

Books (see also references 2 and 4)

- P. Barbet, *A Doctor at Calvary*, Image Books, Doubleday & Co, New York, 1963.
- T. Humber, *The Sacred Shroud*, Pocket Books, New York, 1978.
- P. Rinaldi, *The Man in the Shroud*, Futura Publications, London, 1978.
- R. Wilcox, *Shroud*, McMillan and Co, New York, 1977.
- P. Rinaldi, *When Millions Saw the Shroud*, Don Bosco Publications, 1980.
- P. Jennings, *Face to Face with the Turin Shroud*, British Society for the Turin Shroud, London, 1978. (A series of six articles.)
- Other material**
- The Silent Witness*, Screenpro Films, 4 Meard St, London W1V 3HQ. A 55-minute film giving a good summary of what was known around 1977. Available as 16 mm film for rental or purchase and as video cassette.
- The Holy Shroud*, Don Bosco Films, 148 Main St, New York 10802. A 35 mm film strip or set of 35 mm slides.
- The 1978 Exposition of the Shroud of Turin*, Rev. F. Filas, Loyola University, Chicago. A documentary filmstrip with cassette commentary covering the 1978 public viewing and the scientific investigations. (From ACTA Foundation, 4848 N. Clark St, Chicago 60640.)
- Photographs: Barrie Schwartz Studios, 310 E. Haley Street, Santa Barbara, California 93101.

SOLAR PANELS — SPECIAL OFFER TO READERS OF ETI.

AMTEX ELECTRONICS, solar energy specialists, have available a number of *mil-spec.* solar panels that they are willing to offer to readers of ETI at a special price. These panels, type MB 4310, were manufactured by Sensor Technology (now called Photowatt International Inc.) for a military order and have the characteristics listed below:

ELECTRICAL DATA

Circuitry:	51 cells of 75 mm dia. connected in series with dual, independent connections
Voltage at peak power:	20 V
Current at peak power:	1.2 A
Peak power output:	24 Watt (Measured at a light intensity of 100 mW/cm ² and 24°C)
Electrical insulation to substrate:	2000 Vdc minimum

MECHANICAL DATA

Nominal outside dimensions:	1220 x 290 x 22 mm
Nominal weight:	9 kg
Hail storm:	Hailstones up to 30 mm dia.
Wind loading:	190 km/h
Storage temperature:	-40 to +80 °C



SPECIAL PRICE — \$399

(plus \$10 freight and packing)

This price includes waterproof connector sockets. There are only a limited number of panels, so be early. Offer closes 29 May, 1981.

NOTE: This offer is made by Amtex Electronics and ETI is acting as a clearing house for orders only. Cheques should be made payable to **Amtex Solar Panel Offer** and sent to "Solar Panel Offer", ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011. We will then process your order and pass it on to Amtex, who will send you the goods. Please allow up to four weeks for delivery. Offer expires on 29 May, 1981.

Please supply panels, type MB 4310.

I enclose \$ plus \$10 each freight and packing

TOTAL \$

Name

Address

.....

..... Postcode

Cheque or money order

Signature

Please allow up to four weeks for delivery.

Forging new
frontiers in speaker
performance

Richard Allan

top quality
English speakers
now available

*New Release:—

*CG 12L HI-FI Bass driver
lightweight cone for better
transient and frequency
response.

Also available HP 12B Super, HP 8B, CG 12 Super.
New stocks of Richard Allan speakers
soon to arrive.

Professional advice on all facets of speaker
design and construction available.
Come and inspect our unique
experimental speaker design
facility.



The
**ACOUSTIC
FOUNDRY** Hi Fi

56 King William Road, Goodwood 5034
(08) 2710276.

Please forward me further details
on Richard Allan speakers.
(Trade enquiries also welcome).

NAME

ADDRESS

.....

..... POSTCODE

UHF to VHF TV converter

This project will convert TV station transmissions in the UHF band down to unoccupied channels in the VHF TV band. If your present TV set does not have a UHF tuner and you want to watch programmes on UHF, this project is for you.

Phil Wait

SINCE THE introduction of UHF TV services — first the translator services re-radiating the VHF station signals on UHF channels and then the multi-cultural service on channel 28 — the number of stations and service areas has grown at quite a rapid rate. It's no wonder that we have received many calls and letters from readers asking for projects to solve problems they had in trying to explore what the new services offered. We have already published an antenna design (ETI-728, March '81 issue) and a masthead amplifier (ETI-729, April '81 issue). However, these two projects only cater for those who own a TV receiver having a UHF tuner already built in. Judging from the deluge of requests following the antenna project in the March issue, it seems the biggest demand is for a UHF-to-VHF TV converter. We trust this project satisfies that demand.

Design philosophy

The predominant design requirement for this project was *simple construction* and a *minimum of alignment*. We judged that most constructors tackling a project such as this would not be familiar with UHF circuit techniques. Consequently, the design had to be simple, yet provide good performance — at least as good as the front end of UHF TV tuners used in modern domestic TV sets. We feel those aims have been achieved.

To reduce the requirement of alignment, there is only one adjustment — setting the local oscillator. That isn't even necessary in the tuneable version!

Before proceeding, we should explain that this project can be built in two versions: the *single channel* version and the *tuneable* version. Each has its advantages. If you only have a single UHF channel available in your area, and it's likely to remain that way for some time, then the single channel converter is the one you want. If you have several UHF channels available, then you can either make several single channel converters


and set them up for the different channels, switching between converters, or you can make the tuneable version. If you only have one channel available currently and make a single channel converter, and then more channels become available later, the single channel converter is readily modified to the tuneable version.

The circuit arrangement is fairly conventional. An RF stage employing an OM350 hybrid wideband IC provides some 17-18 dB of gain before signal is applied to the mixer. A two-stage high-pass filter employed between the antenna and the RF amp input provides over 20 dB of attenuation to prevent crossmodulation problems from the high-powered VHF TV signals and other transmissions below 450 MHz. For the mixer, we chose to use a ring-diode balanced mixer circuit, employing wideband input and output matching transformers. This type of mixer provides low noise operation with good crossmodulation performance. In addition, the wideband input and output transformers do away with the

necessity of having tuned circuits which require alignment. The ability to choose any convenient output channel is another advantage.


The local oscillator employs a FET in the familiar Hartley circuit. A parallel-tuned circuit is connected between the gate of the FET and common (ground). The drain is bypassed at the operating frequency and the source is tapped up to the tuned circuit's inductance to provide positive feedback. The tuned circuit inductance (L3) is realised by a length of track on the pc board and a small, low-value trimmer provides the tuning capacitance (CV1). Injection to the LO port of the mixer is provided by inductive coupling from L3 and a short length of 50 ohm stripline.

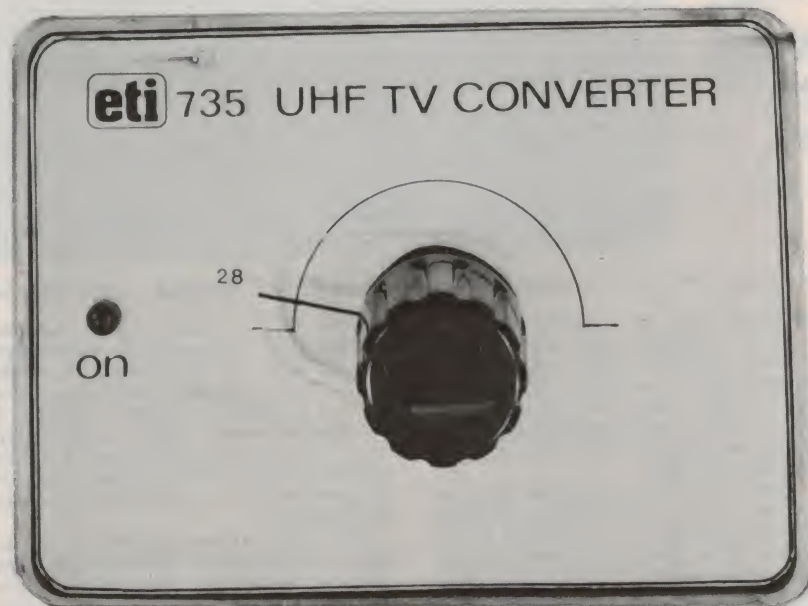The pc board is double-sided to provide a groundplane area for the UHF circuitry. Output to the VHF TV receiver input can be either 75 ohm unbalanced (via coax) or 300 ohm (via ribbon). A regulated power supply is provided on board and the converter may be powered from a 12 Vac, 500 mA plugpack or a conventional trans-



Front panel view of the tuneable version of our UHF converter. Note there are two versions: tuneable and single channel.

Project 735

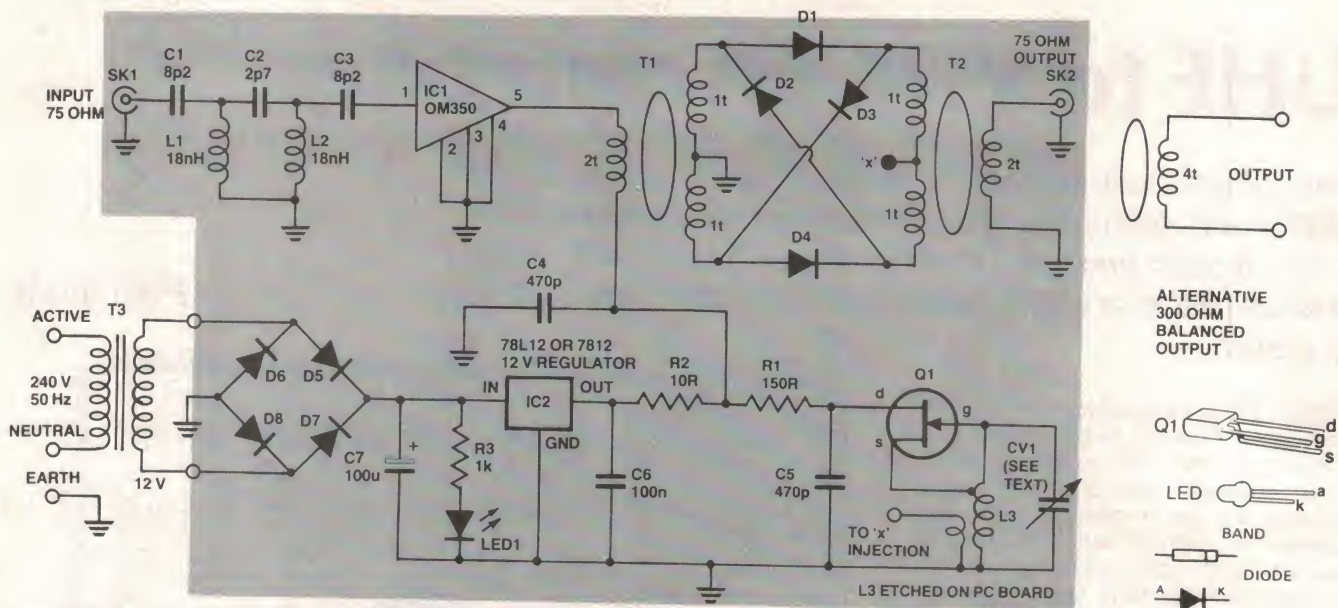

HOW IT WORKS — ETI 735

The converter's format is quite conventional — an RF amplifier drives a mixer, local oscillator injection being provided by a variable frequency oscillator, the frequency of which is set by a small variable capacitor. A full-wave bridge rectifier followed by a three-terminal regulator provides regulated 12 Vdc to power the circuitry.

Signals from the antenna are fed to the input of the RF amplifier stage via a two-stage high-pass filter consisting of L1, L2 and C1, C2, C3. This filter attenuates strong signals in the VHF band (below 300 MHz) from overloading the converter and possibly causing crossmodulation problems. The UHF signals are amplified by IC1, a hybrid wideband amplifier chip which provides a gain of about 18 dB over a bandwidth extending from 40 MHz to 860 MHz. The input filter provides around 10 dB attenuation at 300 MHz, around 20 dB at 200 MHz, and more below that. The gain of the amplifier stage is around 15-16 dB across UHF Band IV and around 17-18 dB across UHF Band V. The gain falls off rapidly above 900 MHz. Noise figure is in the region of 6-7 dB, which is quite a bit better than many commercial UHF TV tuners!

The input and output impedances of the OM350 RF amp IC are quoted as 75 ohms, which is convenient.

The output of the RF amplifier is coupled into the mixer via the primary winding of T1.

The mixer employs four Schottky hot-carrier diodes (D1 to D4) in a double-balanced ring mixer circuit. The input and output transformers, T1 and T2 respectively, are wideband types, providing input and output impedance matching. No alignment is necessary — which is one of the reasons we used this type of mixer. The local oscillator injection is applied at point 'x' (the LO port). This type of mixer provides good conversion efficiency, few spurious outputs and has good strong signal performance so that problems with overload and crossmodulation are minimised.

The local oscillator employs a junction FET, Q1, in a Hartley oscillator circuit. This circuit is simple and reliable. The tuned circuit consists of CV1 and L3. The latter is a length of track on the pc board, a 'printed inductor'. Q1 is operated in the common drain mode, positive

feedback being obtained by tapping the source across L3. The oscillator can be tuned over a range from about 250 MHz to a little above 600 MHz. Injection to the LO port of the mixer is obtained by inductive coupling. A short length of track adjacent to the 'earthy' end of L3 couples a small amount of energy from the oscillator. This is coupled to point 'x' via a short length of stripline running across the pc board.

The mixing process combines the signals amplified by IC1 and the signal provided by the local oscillator to produce a whole range of 'products' at the output. The principal products are the sum and difference of the input and local oscillator frequencies.

Say the input frequency we want to receive is 526 MHz (lower edge of channel 28). This will be amplified by IC1, along with all the other frequencies passed by the input filter, and applied to the input of the mixer. If we set the local oscillator to 470 MHz, the mixer output will be:

$$526 - 470 \text{ MHz} = 56 \text{ MHz}$$

This is VHF TV channel 1. If we tune the TV receiver to channel 1, we will be able to receive UHF channel 28. However, the sum of the input and local oscillator frequencies will also result from the mixing process:

$$526 + 470 \text{ MHz} = 996 \text{ MHz}$$

But the TV receiver will not respond to such a high frequency. A signal from UHF channel 50 (694-701 MHz) may appear at the output too:

$$694 - 470 \text{ MHz} = 224 \text{ MHz}$$

But that's outside the range of the VHF TV receiver. If we set the TV receiver to channel 6 (174-181 MHz), we will be able to receive channel 50 by setting the converter's local oscillator to 520 MHz.

Reception of a UHF station can also be obtained with this converter design by tuning the local oscillator above the channel frequency. For example, to receive channel 28, which occupies 526-533 MHz, assuming we have the TV receiver set on channel 1, the converter local oscillator should be set to 589 MHz:

$$589 - 533 \text{ MHz} = 56 \text{ MHz}$$

But, if there is a signal 56 MHz above the local oscillator frequency (otherwise known as the 'image' frequency), i.e.: $589 + 56 \text{ MHz} =$

645 MHz (UHF channel 43), it will be received equally well — and you'll have terrible interference if there's a station on that channel! With this converter, and the current arrangement of channel allocations, it is best to tune in a station with the oscillator set on the low frequency side of the desired channel. In addition, it is best to use channel 1 (or an adjacent unused channel) to receive UHF stations in Band IV (520-580 MHz) and an unused channel between 5A and 11 to receive UHF stations in Band V.



Power is provided by a full-wave bridge rectifier involving diodes D5 to D8, input being derived from a 12 Vac (nominal) source. An indicator LED (LED1) is driven from the output of the rectifier. Capacitor C7 is the rectifier smoothing capacitor. A three-terminal regulator, IC2, employing either a 78L12 or 7812, provides a regulated 12 Vdc supply for the RF amp, IC1, and the oscillator FET, Q1. The regulated supply ensures good oscillator stability. Capacitor C6 bypasses the output of the regulator, IC2, and prevents it bursting into HF oscillation. Resistor R2 prevents interaction between IC1 and IC2 at low frequencies, and C4 provides an RF bypass for the supply rail to IC1, which goes to the output pin (pin 5) via the primary of T1.

RF bypassing for the drain of Q1 is achieved by C5, and the power supply rail is decoupled via R1.


The output impedance of the mixer can be matched to an unbalanced 75 ohm load or to a balanced 300 ohm load by having a different secondary wound on T2. The impedance transformation ratio provided between the primary of T1 and the secondary of T2 will depend on the square of the ratio of their turns. With two turns on the primary of T1 and two turns on the secondary of T2, the impedance transformation will be 1:1. In this instance, one side of the secondary of T2 is grounded to provide an unbalanced output to match coax cable. If the secondary of T2 is wound with four turns, the output impedance will be given by:

$$75(4/2)^2 = 75 \times 4 = 300 \text{ ohms}$$

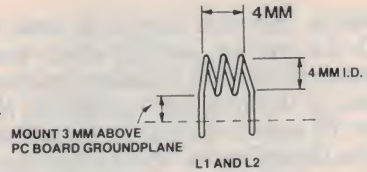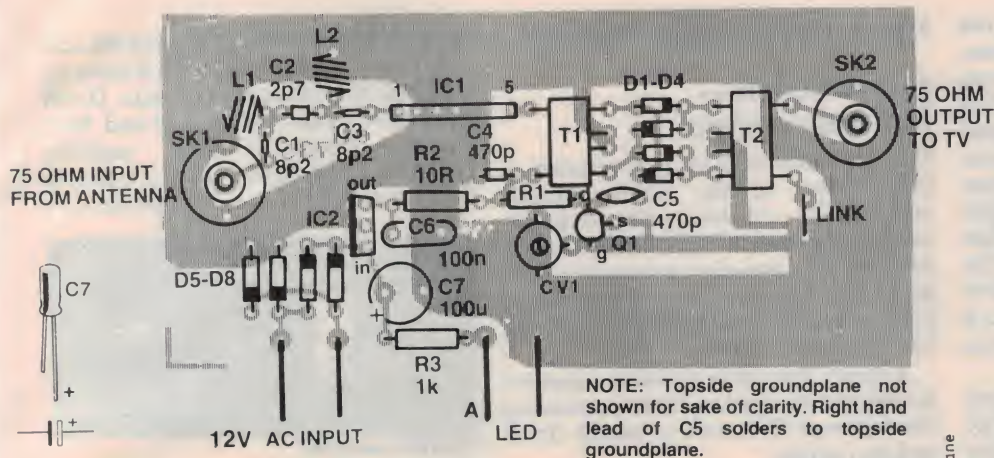Thus, four turns on the secondary of T2 will provide a balanced match to 300 ohms.



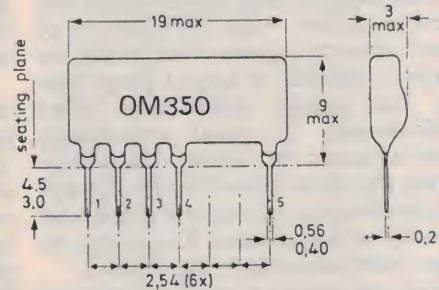L1 AND L2 ARE WOUND WITH 22 SWG TINNED COPPER WIRE, THREE TURNS EACH, ON A 4 MM DIAMETER FORMER, AND SET TO A LENGTH OF 4 MM EACH. MOUNT THEM SUCH THAT THE LOWER PART OF EACH COIL IS ABOUT 3 MM ABOVE THE BOARD GROUNDPLANE.



PARTS LIST — ETI 735

Resistors	all 1/2W, 5%
R1	150R
R2	10R
R3	1k
Capacitors	
C1, C3	8p2 ceramic NPO
C2	2p7 ceramic NPO
C4, C5	470p ceramic
C6	100n greencap
C7	100u/16 V electrolytic
CV1	2-18p miniature film trimmer (see text)
	OR
	2-15p miniature air trimmer with 4.8 mm (3/16") shaft.
Semiconductors	
D1-D4	5082-2800 (four-off) or matched set of 5082-2804 Hewlett Packard hot carrier diodes
D5-D8	1N4001, 1N4002 etc or similar
Q1	2N5245 FET (no substitutes)
IC1	OM350 Philips wideband amp IC
IC2	78L12 or 7812, 12 V three-terminal regulator.
LED1	TIL220R or any suitable LED.
Miscellaneous	
SK1, SK2	Belling & Lee pc-mount coax sockets
L1, L2	see text and diagrams
T1, T2	see text and diagrams
T3	12 Vac, 500 mA plugpack
	ETI-735 pc board (double-sided, fibreglass necessary); pc board stakes; tinned copper wire; hookup wire; vernier drive (for tuneable version); 6.5 mm to 4.8 mm shaft reducer (for tuneable version); box to suit.

former. Overall gain is around 12 dB and the noise figure is around 6-7 dB. This sort of performance is more than adequate for normal service reception of UHF transmissions.

No doubt some readers are curious as to why we didn't design a tuner employing voltage tuned varicaps to tune the local oscillator and/or RF tuned circuits. Firstly, suitable varicaps having the required characteristics for these frequencies were not readily available. We did experiment with a few types that were available, as well as with some common high frequency silicon diodes, but results were very poor owing to the low Q and high losses of the components. Hence, we opted for the circuit design described here.

Construction — single channel version

We shall describe the construction of the single channel version first. The tuneable version is actually just a modification of the single channel version.

The converter is constructed on a double-sided pc board having a fibre-glass substrate. A phenolic substrate board will not work in this application. The top side is predominantly copper, which serves as a groundplane, small areas being etched away where components pass through from the top to the bottom side tracks. The complete converter fits on to the one pc board, including the rectifier and power supply

regulator components.

Construction is best commenced by mounting all the minor components. Leave the input and output sockets, coils and mixer transformers until later. All components should be mounted with the *absolute minimum lead length*. Press them hard down on the board. However, the input high pass filter coils, L1 and L2, are mounted about 3 mm above the board, to avoid the groundplane dampening their Q.

A number of components are soldered on both the top and the bottom sides of the board. These are: the anodes of D6 and D8 (in the rectifier), one lead of C4, plus the earth stake, the centre-tap connection of T1, the earth end of the output link (for 75 ohm output) and the earth ends of L1 and L2.

The OM350 RF amplifier IC must be seated hard down on the board, as should Q1 and the mixer diodes D1 to D4. Watch the orientation of the semiconductors and the rectifier filter capacitor, C7. Note that the OM350 can only be inserted one way, but the local oscillator FET, Q1, has its source lead — the centre one — offset from the others. This lead must be bent over so that the FET can be inserted the right way round. This is necessary to give the correct length of track on the board for the source feedback tap on L3 — which is a printed circuit inductor.

Take care when soldering CV1 in place as conducted heat can distort the body of the component, ruining it.

Having mounted the minor com-

Project 735

ponents, the next step is to wind the coils L1 and L2, and the mixer transformers T1 and T2. Winding details are given in the diagrams on page 38. Note that T2 can be wound in two different ways, depending on whether you choose to have a 75 ohm unbalanced output (coax) or 300 ohm balanced output (ribbon). If you choose a 300 ohm balanced output, the small link near the output socket is left out and the ends of the secondary of T2 connect direct to a length of 300 ohm ribbon, soldered on the underside of the pc board.

The converter may be mounted in any convenient box — but don't put the pc board close to a panel. Use 12 mm (or longer) standoffs to keep it away from the box panels, which may affect performance. To avoid unnecessary terminations, the input and output cables should be taken directly through the lid of the box you use and terminated directly on the pc board. This is why we have used pc-mounted coax sockets.

You can mount a small transformer in the box to power the converter, or you can use a plugpack. The transformer or plugpack should have an output of 12 Vac, rated at about 500 mA. Transformers and plugpacks with this rating are cheap and quite common. While the converter doesn't draw anything like 200 mA, the rectifier output must be several volts above the three-terminal regulator's output voltage. As less than full load is drawn from the transformer or plugpack, its output will be high enough to meet this requirement.

If you choose to use a plugpack, mount a suitable insulated two-pin socket on the box housing the converter. Dick Smith stores stock a suitable ac plugpack, catalogue number M-9555, while Ferguson market a plugpack designed

to power doorbells, model PPB 12/500.


Construction — tuneable version

The tuneable version just requires a modification to the single channel version. To construct the tuneable version, commence by constructing the converter as per the instructions just described, but leave out the trimmer capacitor CV1 (not needed) and Q1 (which must be inserted later).

A small, low value variable capacitor is added to the local oscillator, replacing the trimmer CV1, and a vernier drive and dial added.

For the variable capacitor, we chose an American-made Johnson type with a ceramic base, measuring about 12 x 14 mm, with a threaded spindle and nut mounting. The shaft has the variable plates attached and the mounting spindle also serves as the moving plates connection. This is a common form of construction for small, single-gang variable capacitors for those readers who are not familiar with the beasts. The type we chose to use in the prototype has the moving plates and the fixed plates each milled out of a brass block, which provides excellent mechanical and electrical stability. These capacitors are available in different values and we would recommend you use one with a maximum capacitance of 15 pF. The exact one we wanted was not available when we constructed the prototype so we used one with a maximum capacitance of 20 pF and cut down the fixed plates to obtain the required value. This is visible in the close-up photographs. We purchased ours from General Electronic Services Pty Ltd of 99 Alexander

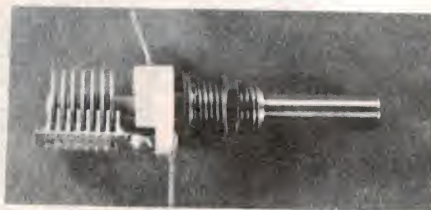St, Crows Nest NSW 2065, but kit and component suppliers may stock them by the time this issue goes on sale. David Reid Electronics (in Sydney and Melbourne) stock a small variable capacitor, type C1604, that is suitable for this project. It is somewhat smaller




The C1604 capacitor.

than the one shown in the prototype, measuring 9 mm square around the base and standing about 17 mm high above the base of the spindle. It comes in three values of 20 pF, 14 pF and 8.5 pF maximum capacitance. The 14 pF model is the one to use here; it costs around \$7.

Each capacitor requires a 6 mm hole to be drilled in the pc board for the spindle. This is drilled through the pc board adjacent to the end of the local oscillator inductor strip (L3), the hole centre being spaced about 9 or 10 mm from the pad at the very end of L3. The capacitor from David Reid Electronics (C1604) could be placed a little closer if you wish. Whichever capacitor you use, it must clear adjacent components. The main requirement is to place the solder tag for the fixed plates connection above the pc board hole for the gate of the local oscillator FET, Q1.

When securing the variable capacitor to the pc board, make sure the nut gets a good grip so that the shaft and spindle are well connected to the groundplanes on the top and bottom of the board. Ensure that the areas of copper on the board surrounding the spindle hole are clean and bright before installing the capacitor.

With the capacitor installed, Q1 needs attention. The drain lead goes in the original hole (see the overlay), but the source lead now goes in the hole where the gate lead went on the single channel version (again, refer to the overlay). Now, pass a short length of tinned copper wire through the hole in the pad on the very end of the local oscillator inductor strip (L3), up to the lug connecting to the fixed plates on the variable capacitor. Solder the wire to the board, then bend the lug on the capacitor down towards the board and solder the free end of the wire to the lug. Take the gate lead of Q1, bend it towards the capacitor lug and solder it in

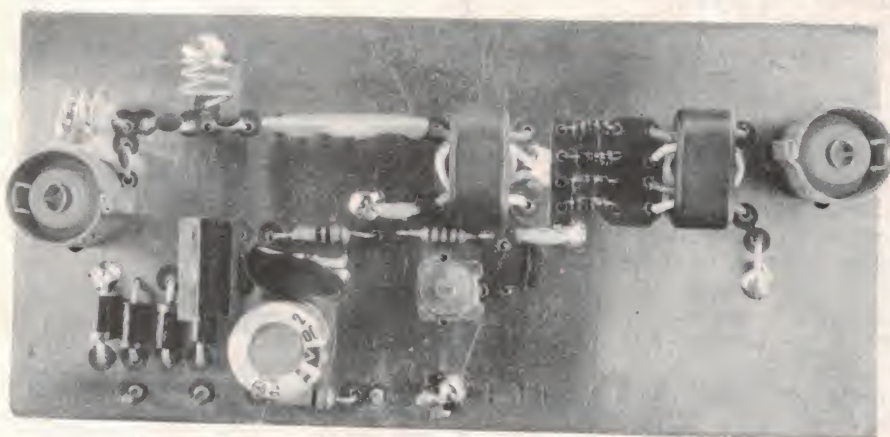


The completed single-channel converter. Topside of the board is largely copper with 'let-outs' where components pass through. Input is on the left, output at right.

place. The one thing to remember here is to *keep all leads as short as possible*. The accompanying close-up photograph shows how we did it.

The converter may now be mounted in a box, so that the vernier drive and dial can be installed. The vernier drive we used is a Jackson dual-ratio type having a 2:1 and a 6:1 action. This is designed to couple to a 6 mm ($\frac{1}{4}$ " diameter shaft. The Johnson capacitor specified has a 4.8 mm ($\frac{3}{16}$ " diameter shaft, while the C1604 capacitor from David Reid Electronics has a 4 mm diameter shaft. You will need an appropriate split-tube shaft reducer to slip over the capacitor's shaft, depending on which particular type you are using.

We mounted our tuner in a small Horwood box, type 34/6/D. This consists of an aluminium extrusion 100 mm wide by 75 mm high and 75 mm deep with a panel in each end secured by self-tapping screws. The converter and dial mechanism are secured to one end panel and the RF input/output and power supply cables are passed through holes in the other. Drilling details to mount the converter and dial mechanism are given in the drawings below. The pc board is secured to the front panel by four 38 mm long ($1\frac{1}{2}$ " 6 B.A. bolts, while the vernier dial drive mechanism is mounted using two 25 mm long (1" 6 B.A. bolts. All six bolts have countersunk heads to permit the front panel transfer (such as Scotchcal) to sit flat on the panel. General construction is visible from the photographs here. The best way to go about the mechanical assembly is as follows: first, carefully mark out and drill the front panel as per our detail drawing. Secure all six bolts to the

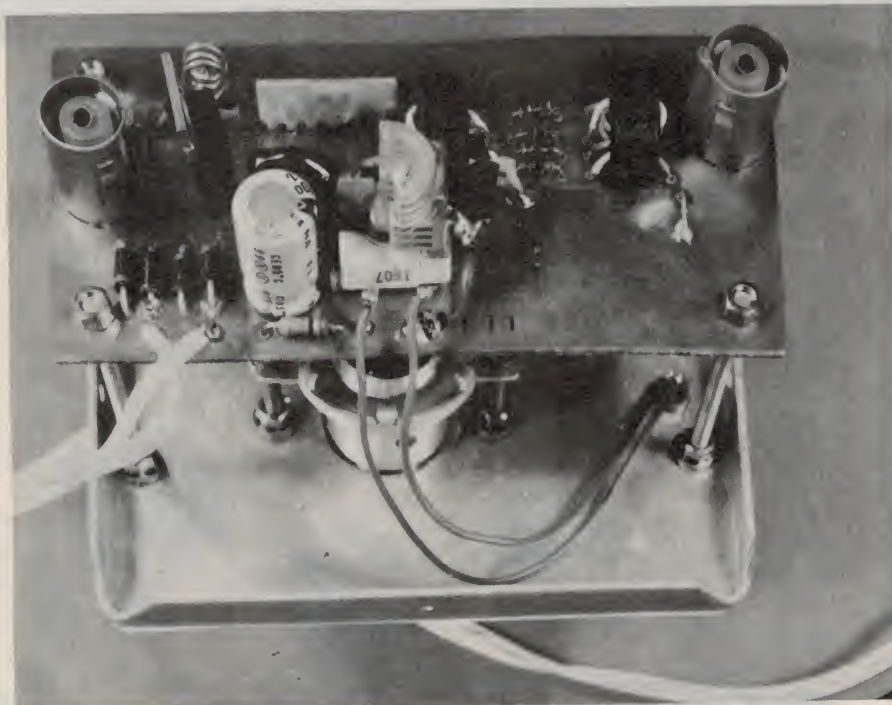

The completed tuneable version showing how we mounted the board and dial mechanism.

panel using washers under each nut. Thread another nut on each bolt. Slip the vernier drive over its two mounting bolts and position the two nuts such that the mounting lugs of the drive are about 15 mm from the panel. Secure the drive mechanism with two more nuts and washers, making sure the drive shaft passes through the panel at a right angle otherwise your dial pointer will not move parallel to the front panel.


Now, slip the shaft reducer over the shaft of the variable capacitor. Assemble the pc board onto the mounting bolts and position the nuts on each bolt so that the board is about 32 or 33 mm from the panel. The capacitor

shaft should line up with the drive coupling. Don't secure the board yet. Tighten the grub screws on the drive coupling to secure the capacitor shaft. Now you can secure the board with four more nuts.

Before you assemble the dial pointer mechanism to the vernier drive, fix the indicator LED in place and then attach the panel artwork. We used a Scotchcal panel, but only general markings are shown, as the exact channel positions (or frequency markings) will depend on which VHF channel you select as the converter's output. With the panel artwork in place you can assemble the dial pointer mechanism to the vernier drive. ▶



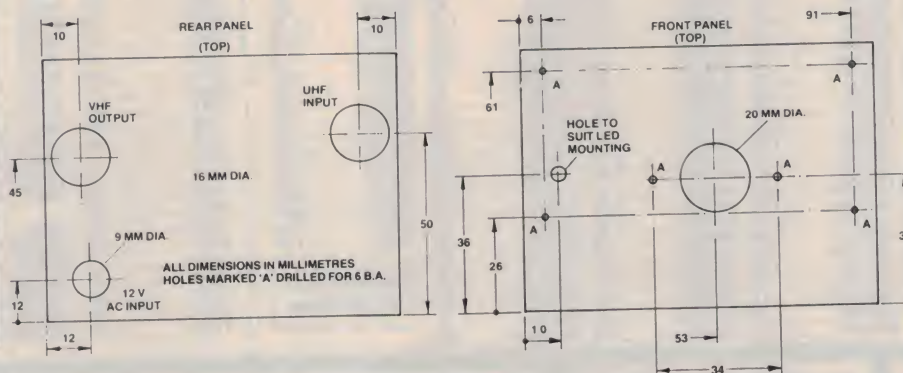Close-up of the FET and tuning capacitor in the tuneable converter, showing where the capacitor is mounted and how the FET's gate lead is bent over to the capacitor's lug. The source lead now goes in the original gate hole.



Panel drilling details for the Horwood box in which we housed the tuneable converter.

TRANSFORMERS

Made in Australia to Australian standards for 240V, 50Hz mains
with secondaries from 1.5V to 115V.

CONVENTIONAL

Rated from 2.5 to 350VA



LOW PROFILE

20, 40 & 60VA ratings with dual secondaries for various output voltage and current combinations. Also multi-tap 20VA version. Compact design.

P.C.B. MOUNTED

Pins located at standard 0.1" PCB grid. Ratings from 2.5 to 15VA with dual secondaries.



MICROPROCESSOR

Specially produced with 8V main secondaries and 12-15V dual auxiliary secondaries. Outputs from 200mA to 10A. Also Computer Line Conditioners.



ENCLOSED TYPES

Includes step down transformers for 115V equipment, soldering irons, mains isolation etc.



POWER POINT ADAPTORS

Available in AC and DC versions with outputs to 6VA AC or 4VA raw DC or 3VA filtered.



POWER SUPPLIES

Fixed regulated 13.8V DC supplies, variable 0-35V DC with current limiting. Battery Chargers up to 20A.



Send for data sheets and rating selection guide.

FERGUSON TRANSFORMERS PTY LTD
331 High Street, Chatswood 2067 Tel (02) 407 0261

TRANSISTORS

AC128.....90	MPSA12.....50	BC639.....40	2N2484.....55
AD149.....2.20	MPSA14.....45	BC640.....40	2N2645.....1.00
AD161.....2.20	MPSA55.....30	BCY71.....69	2N2647.....1.20
AD162.....2.20	MPSA92.....40	BCY72.....69	2N2904.....50
BC107.....35	MPSA93.....55	BD131.....65	2N2905.....50
BC108.....35	PN3564.....24	BD139.....65	2N2906A.....50
BC108C.....39	PN3565.....18	BD140.....65	2N2907.....50
BC109.....35	PN3566.....18	BD234.....1.00	2N2907A.....50
BC109C.....40	PN3567.....18	BD262.....1.20	2N301.....3.75
BC177.....35	PN3568A.....18	BD263.....1.20	2N301.....3.75
BC177B.....65	PN3638.....18	BD647.....1.90	2N3053.....75
BC178.....35	PN3641.....20	BD648.....1.90	2N3054.....1.85
BC179.....35	PN3642.....20	BDV64B.....3.19	2N3055.....75
BC182B.....20	PN3643.....20	BDV65B.....3.19	2N3107.....1.20
BC184L.....25	PN3644.....22	BF115.....65	2N3300.....85
BC212L.....25	PN3645.....22	BF167.....95	2N3302.....60
BC286.....16	PN3646.....22	BF173.....95	2N3638.....25
BC287.....16	PN3693.....29	BF180.....85	2N3642.....30
BC317.....22	PN3694.....29	BF338.....90	2N5210.....30
BC318.....22	PN4121.....35	BF469.....1.00	2N5401.....1.15
BC319.....22	PN4248.....22	BF470.....1.00	2N5458.....50
BC320.....22	2N3702.....20	BF494.....22	2N5459.....55
BC327.....30	2N3703.....30	BFW10.....1.40	2N5461.....90
BC337.....30	2N3704.....30	BFX84.....85	2N5462.....90
BC338.....30	2N3740.....1.60	BFY50.....85	2N5485.....65
BC546.....24	2N3819.....40	BFY51.....85	2N5550.....90
BC547.....19	2N3904.....25	BFY90.....1.50	2N5871.....1.70
BC548.....19	2N3906.....20	BU126.....3.90	2N5872.....2.25
BC549.....19	2N4030.....1.00	BUX80.....9.95	2N5873.....1.70
BC549C.....20	2N4032.....80	FPT100.....1.20	2N5874.....1.85
BC550.....25	2N4033.....1.00	PN4250.....29	2N6027.....1.10
BC556.....24	2N4036.....1.20	PN4355.....29	2N6124.....1.20
BC557.....20	2N4037.....1.30	TIP31A.....65	2N6126.....1.30
MJ802.....4.20	2N4124.....28	TIP31C.....1.60	2N6129.....1.40
MJ2955.....1.10	2N4231.....1.20	TIP32C.....85	2N6130.....1.30
MJ4502.....4.20	2N4234.....2.10	TIP2955.....1.60	2N6132.....1.60
MJ15003.....5.90	2N4235.....1.70	TIP3055.....1.00	2N6134.....1.70
MJ15004.....5.90	2N4238.....1.90	TT800.....1.20	2SJ49.....8.95
MJE340.....1.30	2N4403.....20	TT801.....1.20	2SK134.....8.95
MJE350.....2.10	2N4870.....1.25	2N697.....60	3N201.....1.60
MJE2955.....1.49	2N5086.....25	2N918.....65	40673.....1.40
MPF102.....60	2N5087.....25	2N2102.....82	
MPF131.....1.20	2N5088.....30	2N2219.....50	
MPS3565.....18	2N5089.....25	2N2219A.....65	
MPS3638.....18	BC558.....20	2N2222A.....35	
MPSA05.....30	BC558B.....20	2N2368.....25	
MPSA06.....30	BC559.....20	2N2369A.....65	

Mail Orders, \$1.00
Min. P & P Please.

TTL. 7400.

7401.....35	7483.....1.40	74LS08.....30	74LS164.....1.40
7402.....35	7485.....1.40	74LS09.....30	74LS165.....1.40
7403.....35	7486.....55	74LS10.....30	74LS169.....1.90
7404.....35	7489.....2.60	74LS11.....55	74LS174.....65
7405.....45	7490.....60	74LS12.....30	74LS175.....90
7406.....50	7491.....95	74LS14.....80	74LS190.....1.60
7407.....45	7492.....80	74LS15.....75	74LS191.....1.30
7408.....35	7493.....55	74LS16.....60	74LS192.....1.15
7409.....35	7494.....1.15	74LS20.....30	74LS193.....1.00
7410.....35	7495.....1.00	74LS21.....35	74LS194.....1.20
7412.....40	7496.....1.10	74LS27.....30	74LS195.....1.00
7413.....50	74100.....1.95	74LS28.....35	74LS196.....1.60
7414.....65	74107.....75	74LS30.....30	74LS197.....1.60
7416.....50	74121.....65	74LS32.....30	74LS221.....1.50
7417.....60	74123.....85	74LS37.....40	74LS247.....1.95
7420.....35	74132.....1.30	74LS38.....40	74LS251.....85
7421.....35	74145.....1.50	74LS40.....30	74LS253.....85
7422.....35	74150.....1.50	74LS42.....45	74LS257.....75
7425.....45	74151.....1.40	74LS47.....1.20	74LS259.....3.30
7426.....40	74153.....1.40	74LS73.....60	74LS279.....95
7427.....40	74154.....1.40	74LS74.....40	74LS290.....1.30
7430.....35	74157.....1.40	74LS75.....50	74LS365.....80
7432.....35	74160.....1.70	74LS78.....65	74LS366.....80
7437.....40	74165.....1.70	74LS85.....1.40	74LS367.....90
7438.....45	74172.....1.40	74LS86.....60	74LS368.....65
7440.....45	74173.....2.60	74LS90.....60	74LS373.....2.40
7441.....2.50	74175.....1.20	74LS92.....1.00	
7442.....80	74180.....1.50	74LS93.....85	
7447.....1.00	74192.....1.80	74LS95.....1.00	
7448.....1.00	74193.....1.80	74LS107.....65	
7450.....45	74176.....1.50	74LS109.....50	
7451.....45	74367.....80	74LS113.....50	
7453.....35	74S02.....75	74LS114.....75	
7454.....50	74S74.....1.40	74LS123.....1.50	
7460.....35		74LS125.....70	
7470.....50	74LS.	74LS133.....30	
7472.....55	74LS00.....33	74LS138.....1.10	
7473.....55	74LS01.....30	74LS151.....1.00	
7474.....55	74LS02.....30	74LS155.....60	
7475.....55	74LS03.....30	74LS157.....75	
7476.....55	74LS04.....40	74LS160.....70	
7480.....1.00	74LS05.....50	74LS163.....80	

TASMAN ELECTRONICS

12 Victoria Street, Coburg, VIC, 3058.
Phone (03) 354-5062.

uhf tv converter

We cut a piece of 3 mm thick perspex to shape and put a line on it with black ink.

The rear panel of the box has three holes drilled in it, two to pass the input and output cables and one, which is grommeted, to pass the power supply input lead. Pass the ac supply lead (length of figure-8 flex) through the grommeted hole and the input and output cables through the appropriate holes and then assemble the rear panel to the case. Wire up the ac supply to the pc board and you're ready to roll!

Setting up

Setting up the single-channel version is quite simple. We presume you already have an antenna (see the March issue). Install a short jumper cable from the converter's output to the TV receiver's input. Attach the ac power source to the converter (plugpack or what-have-you), plug in your UHF antenna and switch on.

You will need to select an appropriate unused channel on your TV receiver. For UHF stations in Band IV (channels 28 to 34), VHF channel 1, or an adjacent unused channel, can be used. For Band V UHF stations (channels 38 to 63), select one of the higher VHF channels, such as channel 6 or 8.

First ensure your antenna is pointing in the right direction. Then, using an insulated alignment tool, adjust CV1

for best reception on the UHF channel you want to receive. Start with CV1 set at maximum capacitance so that the local oscillator frequency is tuned *upwards*. It is possible to tune Band IV stations by setting the local oscillator above the channel of interest, but this is not recommended as it may be possible to experience interference from stations on the 'image' frequency. For example, say you have chosen VHF channel 1 (56 MHz) as the converter output frequency. You can receive UHF channel 28 by setting the local oscillator to 470 MHz (526 - 56 MHz). You can also receive channel 28 by setting the local oscillator to 589 MHz. However, a station on 645 MHz (channel 43) may be received equally well. This channel is not occupied at the moment, though.

Setting up the tuneable version is very similar. First, set the dial to the lowest frequency (capacitor plates fully meshed). Attach the antenna and jumper cables and the ac power input from the plugpack, and power up. For the tuneable version, one of the higher frequency VHF channels should be selected on your TV receiver. If you want to go right up to UHF channel 63, you'll have to use VHF channel 11, as the converter's local oscillator in the tuneable version does not go above 600 MHz as it does in the single channel version.




With everything set up, rotate the dial until you obtain good reception of the station of interest. Dial positions of channels can be noted on the panel with a Chinagraph pencil and the channel number put on later with rub-down lettering such as Letraset.

If you find you need to improve reception, experiment with the position and direction of the antenna. If necessary, further improvement can be obtained by using a masthead amplifier, such as our ETI-729, published in the April issue.

Amateur TV use

The converter is eminently suited to amateur TV applications in the 420-450 MHz (70 cm) amateur band. Two 'channels' are used: 425-432 MHz (vision carrier on 426.25 MHz) and 443-450 MHz (vision carrier on 444.25 MHz). The local oscillator range in this converter is more than adequate to cover these two frequency bands, set to either the 'high side' or the 'low side'. However, the input high-pass filter will require some modification. This is simple — squeeze both coils until they're just under 3 mm long! This will bring up the gain around 400 MHz and still provide a reasonable roll-off below 250 MHz to attenuate the strong VHF TV station signals that may bring crossmodulation problems.

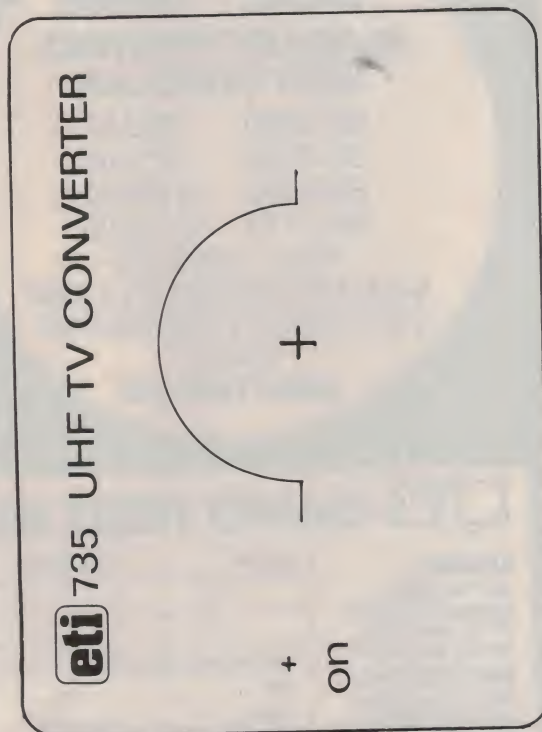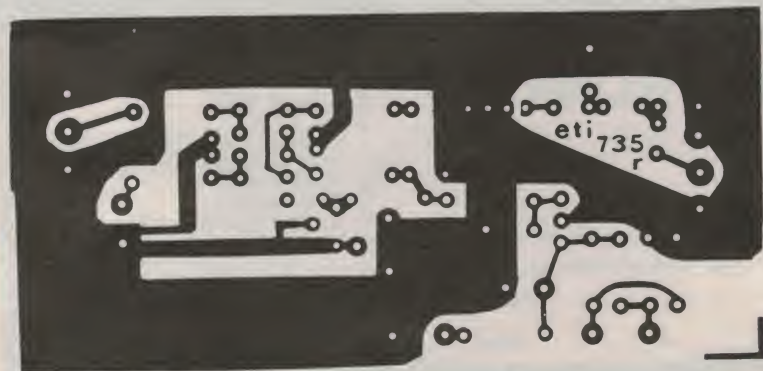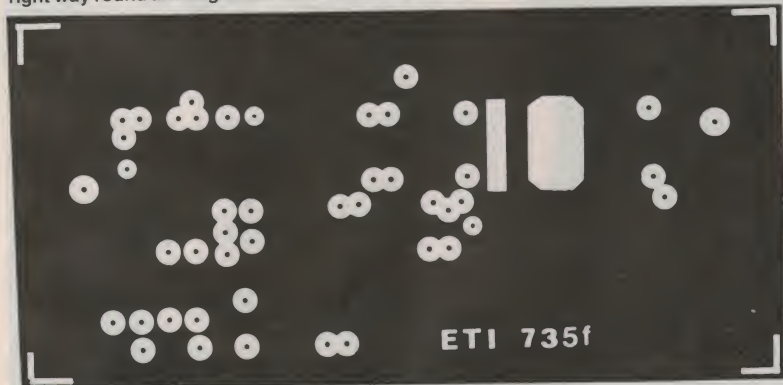Full-size artwork for the front and rear sides of the pc board. Take care to place them the right way round and align them when exposing the resist.



Full-size artwork of the front panel for the tuneable converter.

"MEMORY" SPECIALS

4116's 200ns \$23 for 10
\$2.50 each

2114's LP \$32 for 10
\$3.57 each

2114's LP3 \$34 for 10
\$3.88 each

2716's \$90.00 for 10
\$10.09 each

ALL INCLUDING
TAX

GREAT MAY SPECIAL QUALITY ELECTRIC CAR AERIALS

ONLY

\$14.95

SAVE

\$10.00

WINTER NIGHTS WITH "ATARI" TV GAMES GREAT FAMILY ENTERTAINMENT FOR \$269.00

(INCLUDES "COMBAT" GAME)

FULL RANGE OF GAME CARTRIDGES

AVAILABLE — "SPACE INVADERS",

"INDY 500", "VIDEO CHESS",

"ADVENTURE", "OUTLAW"

PLUS MANY MORE

GET YOURS NOW

NEW "KAISE" DMMs ALREADY PROVING VERY POPULAR

SK 6200 \$69.50

SK 6220 \$79.50

SK 6100 \$108.00

SK 6110 \$118.00

All plus 15 percent tax

• ALL AUTORANGING • 3.5 DIGIT
LCD READOUT • PROFESSIONAL
QUALITY


CHECK THEM OUT

YES! WE'RE STOCKING IT BIFET OP. AMPS

TL061	73c	TL075	\$2.63
TL064	\$2.87	TL080	57c
TL071	90c	TL081	63c
TL072	\$1.51	TL082	\$1.32
TL074	\$1.95	TL084	\$2.42

ALL INCLUDING
15% S.T.

WRITE NOW
FOR FREE CATALOGUE
PRICE LIST

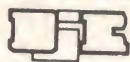

DAVID REID ELECTRONICS PTY. LTD.

SYDNEY:

127 York Street
Sydney 2000 N.S.W.
G.P.O. Box Q103
Sydney 2001 N.S.W.

MELBOURNE:

356 Lonsdale Street
Melbourne 3000 Vic.
G.P.O. Box 1417M
Melbourne 3001 Vic.

Part No.	Description	Quantity	Price	Total
Please print clearly. Date				
Tel.		Minimum Postage/Packing charge 1.00		
Name		Plus Postage/Packing surcharge		
Address		Subtotal		
Postcode		TOTAL		

Enclose your personal cheque, Money
Order or Bankcard Numbers as
specified below:
Check and fill in

☐ Cheque or Money Order Enclosed
☐ Charge to my Bankcard No.
CARD HOLDER'S NUMBER

496

Signature

Card Expiry Date

RADIO DESPATCH SERVICE

869 George Street,
Sydney, NSW. 2000.
(Near Harris Street)
Phone 211-0816, 211-0191.

MAY SPECIALS

Transistors: BC237 or BC23810 for 75c
"Jabel" 3 pole, 2 position rotary switch.....\$1.00
"Altronic" TI-302 soldering iron stand.....\$5.50
CSR-4 Cassette tape module rack.....\$3.40
CA-30 Top Cowel car aerial — 42" ext.\$4.75
"RALMAR" SDH-7D stereo headphones.....\$8.95
"VICTORY" MPT-02 colour TV game unit ..\$78.95
Extra cartridges for TV game\$18.95 ea.
Ni-Cad rechargeable AA Penlite Cell.....\$1.75
"MUFFIN" 240V computer fan\$22.94
"SPRITE" 240V computer fan\$30.36
"LOTRING" 3212 soldering iron 30 watt.....\$12.30
"G.E." SC-151D Triac 400V 15A 1-9.....\$2.00 ea.
10 up. \$1.61 ea.
SC-40 twin speaker control unit.....\$2.50
"FERGUSON" PF2228 transformer,
prime: 240V, sec: 30V-20VA\$5.00

See us for all types of valves
We specialise in:

- PC Boards for ETI and EA projects.
- Scotchcal labels made under order for ETI and EA projects 1979 and onwards.

Texas Calculators

	excl. ST	incl. ST
Ti.59	\$271.29	\$302.00
Ti.58C.....	\$141.11	\$156.00
Ti PC 100C Printer....	\$216.28	\$239.00
Ti.50	\$37.05	\$41.00
Ti.55	\$54.27	\$60.00
Ti.30 Student Pack....	\$20.13	\$22.50
Little Professor	\$17.20	\$19.00
Dataman	\$23.63	\$26.15
Speak and Spell	\$69.53	\$77.00
Ti 1750	\$16.72	\$18.50
Ti BAII	\$41.48	\$45.92

MAIL ORDER CUSTOMERS

Packing.....	\$1.00
Minimum postage.....	\$1.00
Minimum interstate postage.....	\$1.50

OPEN: Mon-Fri 8 am to 5.30 pm.
Thursday night late shopping till
8.30 pm. Saturday 8 am to
11.45 am.

UHF VHF FM

THE ULTIMATE ANTENNAE FOR ANY RECEPTION DISTRIBUTION PROBLEM

NOW SOLE VIC. & S.A. DIST.



**CHANNEL KING
PTY. LTD.**

117 Burwood Hwy
Ferntree Gully
Vic. 3156
(03) 758-5199

GW ELECTRONIC TEST INSTRUMENTS

Best value
Oscilloscope in '81

NOW AVAILABLE
THROUGHOUT
AUSTRALIA

ONLY
\$225



- 130mm LABORATORY CRO
- 6.5MHz Bandwidth
- CRT Calibration

Specifications:

Vertical Deflection:

Sensitivity: 10mVp-p/cm or better
Bandwidth, -3dB: DC to 6.5 MHz;
AC: 2Hz to 6.5MHz

Input Impedance: 1MΩ ± 5 percent within 35PF
Input Control: x1, x10, x100, and fine adjuster
Calibration Voltage: 0.05Vp-p 1kHz square wave

Maximum Input Voltage: 600Vp-p or 300V
(DC + AC peak)

Horizontal Deflection:

Sensitivity: 250mVp-p/cm or better
Bandwidth, -3dB: DC to 500kHz
Input Impedance: 1MΩ ± 10 percent within 35PF
Maximum Input Voltage: 100Vp-p or 50V
(DC + AC peak)

Sweep Frequency: 10Hz to 100kHz in 4 steps
with fine adjuster

Synchronization: Internal — & + , external, line.
Power Supply: AC 240V/50Hz; approx. 15VA

Size and Weight: 250(H) x 180(W) x 415(D)mm;
4kg

Accessories: Test leads and instruction manual.

OTHER GW INSTRUMENTS: Function/audio generators, DMM's, frequency meters, AC millivolt/milliohm meters, AF/RF attenuators, capacitance/leakage meters, puncture/insulation testers, regulated power supplies.



Sole Australian Agent:
**EMONA ENTERPRISES
PTY. LTD.**

CBC Bank Bldg, 661 George Street,
Haymarket, Sydney. (02) 212-4815.



Available from:
NSW Radio Despatch Service, 211-0191. Emtronics
211-0531. David Reid Electronics 29-6601. Radio
House 212-3800. Pre Pack Electronics 569-9797.
Martin de Launay (Wollongong) 28-6020. (Newcas-
tle) 24-741. VIC Radio Parts 329-7888. SA Int. Comm.
Systems P/L 47-3688. QLD Audiotronics 44-7566.
WA Letco Trading Co. 387-4968. ACT Electronic
Components P/L 90-4654. TAS D&I Agencies 23-
2842.

UNBELIEVABLE PRICE BREAKTHROUGH

**Telephone Answering
Machine only \$199⁰⁰**

Answers &
records
24 hours a day.

**DON'T
pay over
\$400!**

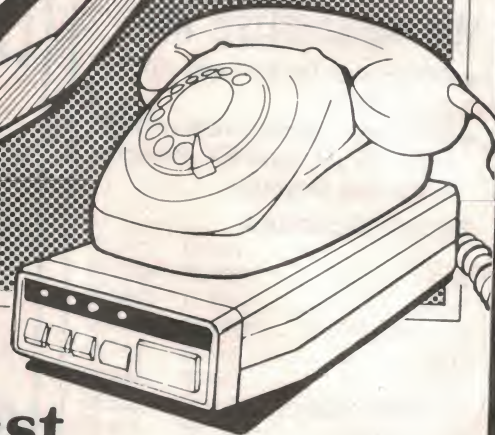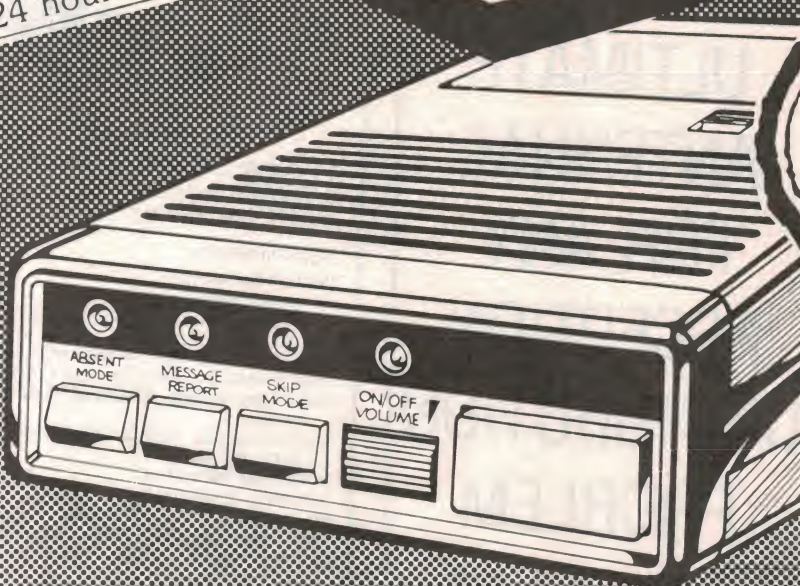

Capture important
calls **WITHOUT**
returning to your
office!



*With this optional remote beeper you can actually dial your number from any other phone & listen to any messages that have been recorded - imagine how handy that would be for busy people on the move. You can capture important calls without having to go to the office.

*Remote beeper
available \$39.00

**Direct
import & latest
microprocessor technology
have halved the cost of
telephone answering
machines from**

DICK SMITH

Huge price breakthrough

Traditional telephone answering units are enormously complex and expensive. In this revolutionary unit most of the components have been replaced by one "microprocessor" (computer) integrated circuit which not only means greater reliability but also vast savings in cost. **To purchase this unit outright you will probably spend less than one years lease payments on competitive units**


NOT AS GOOD.

This unit has some tremendous advantages over competitive units however we must first tell you of one disadvantage. With competitive units selling for \$400-\$500 a sales representative will call, demonstrate and quote you. However, because of the extremely low price of this unit we can only sell it directly "over the counter" or by mail order. The profit we make wouldn't even run a traditional salesman's car for very far!

but far better

Many telephone answering units (including this one) can have remote beepers. This means that when you wish to retrieve a message, you simply 'phone your number, hold the beeper to the 'phone and the telephone answering machine then rewinds to the start of your first message and plays back. However, with most units if you then wanted to erase these messages and rewind, it was either impossible or extremely complicated. This unit solves the problem as you can command the machine to rewind from your beeper at any time.

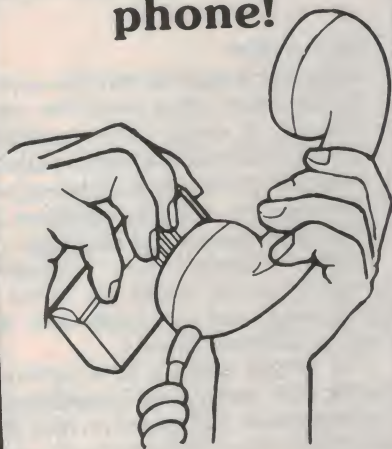Remote control of your machine from any other phone!



easy to install

The telephone answering unit simply plugs into the power and connects to your telephone (Telecom install a socket at a nominal charge). We even supply instructions on how you can easily install it yourself in seconds where Telecom regulations do not apply.

incredibly small

Microprocessor technology has reduced the machine to 25.5 x 15 x 6cm. (your telephone sits on top perfectly) and the unit will record up to 45 messages on the standard cassette tape (many other machines have special tapes costing over \$20.00).

You don't have to pay for special tapes costing \$20 or more!

Features:

- All solid state - non mechanical switches.
- Electronic cassette mechanism (patent pend).
- All functions computer controlled.
- Acknowledges all commands.
- Messages received signal.
- "Fail safe" signal - signals if you forget to insert cassette.
- Uses standard cassette.
- Supplied with pre-recorded cassette tape - unit ready for immediate use.
- Supplied with microphone for personal recording of outgoing message.
- Computerised "Auto Record" - just speak into the microphone and the computer does it all.
- Monitor allows undetected screening of callers.
- Skip mode - automatically jumps to start of next message.
- No listening to outgoing message. Only hear the message received.
- Remote beeper allows you to listen to your messages from any telephone.
- Choice of keeping messages or resetting to fresh start, from any telephone.
- Unit has "No message received" signal on remote call-in.
- Last message received signal.
- Signal for tape fully recorded with incoming messages.
- Book size - fits under your telephone.

no wasted time


With our unit there is a special beep tone that tells you the moment you call in if there's a message. It also tells you if you have finished listening to the last message.

This saves you time and money!

try it yourself- no obligation

We are so confident of this computer controlled marvel that we are happy for you to try it yourself for 14 days and if you are not completely satisfied, simply return it to us in its original condition and we will refund your money in full.

XK-2100 TELEPHONE ANSWERING UNIT

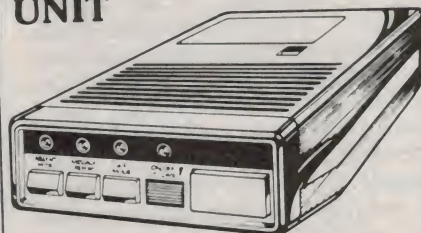

Cat. Y-2173 **\$199⁰⁰**
P&P \$5.50

OPTIONAL REMOTE BEEPER

(Allows you to interrogate machine from another phone).

\$39⁰⁰

Cat. Y-2174
P&P \$3.00

don't miss those important calls

TELECOM APPROVED
(App. No: C80/16/92).

DICK SMITH ELECTRONICS

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS



Electronic humidity meter can double as a controller

Graeme Teesdale


This project can be built to give a readout of relative humidity either on a LED dot-mode display or a conventional meter. In addition it can be used with a following project as a controller to turn on and off a water mist spray in a hothouse, for example.

MEASURING environmental parameters such as temperature, wind speed and direction, etc, are relatively simple problems in electronics. But when it comes to humidity — or relative humidity — a stumbling block arises. The Bureau of Meteorology, and most other agencies or people interested in measuring relative humidity (H_{rel}), employ wet bulb/dry bulb thermometer instruments and a conversion table. Attempts to emulate the wet bulb/dry bulb technique electronically have been tried, using thermistors, in the past but the technique has not met with a great deal of acceptance. It's "fiddly" and offers few advantages — other than a direct readout of relative humidity — over the wet bulb/dry bulb method.

Now, doubtless many an electronics engineer and hobbyist has turned their mind to the problem of a suitable electronic sensor over the years — finally turning to more stimulating things after running up a number of frustrating blind alleys. Not so the Philips organisation. Somewhere along the line they ran up an alley that bore fruit (. . . pomegranates and paw-paws, but that's another story entirely!). In 1979, Philips released a 'capacitive humidity sensor for consumer applications', type number 2322 691 90001. The device characteristics and applications circuitry were described in Philips Technical Note 134, issued 12 September 1979.



The capacitive humidity sensor.

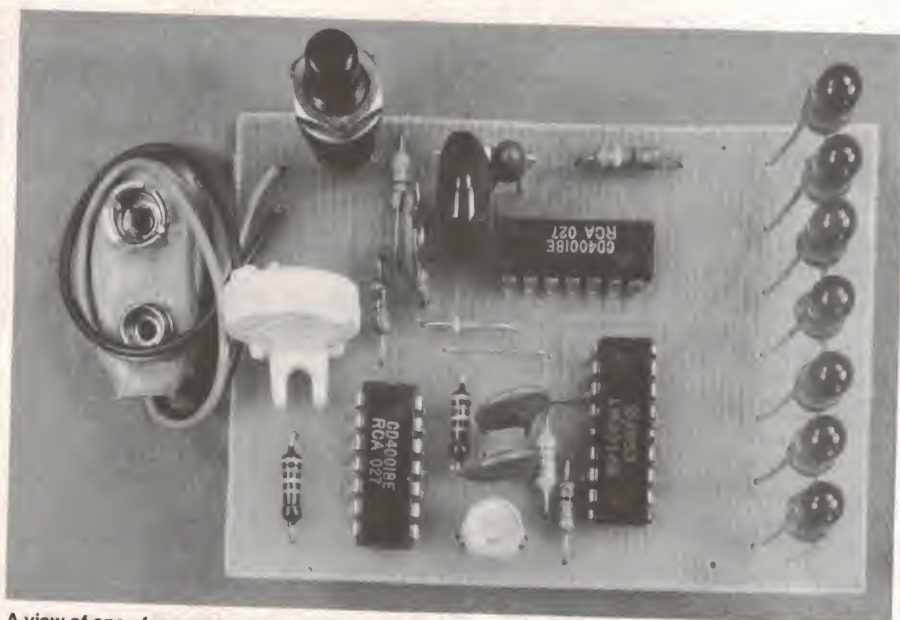

A view of one of our prototype humidity meters featuring the LED display. Note the sensor mounted on the board at the left, adjacent to the battery clip.

This project has been designed to use that sensor and employs a measurement technique described in that Technical Note. To cater for as wide a range of readers' interests and applications as possible, we have designed this project to display the relative humidity reading either on a conventional moving-coil meter or on a dot-mode LED display, using the ubiquitous LM3914 to drive seven LEDs indicating relative humidity over the range 35% to 100%. For those who wish to employ the project in an automatic humidity control system, it can be coupled to our Universal Relay Driver project, ETI-257, also described in this issue.

This project is not intended as a true scientific instrument as accuracy of the sensor is only a few per cent, but for most general domestic applications it should prove more than adequate.

The sensor

A humidity sensor to suit the applications described must meet two major objectives: it must have predictable behaviour and good long-term stability. In addition, the sensor must be ruggedly constructed for reliable operation and be simple to operate and maintain.

Philips claim their capacitive humidity sensor meets the above requirements, and our experience with them would bear this out.

The device consists of a perforated plastic case containing a membrane of non-conductive foil coated on both sides with gold, the membrane and coating forming, respectively, the dielectric and electrodes of a parallel plate capacitor.

Changes in relative humidity cause a change in the sensor's capacitance. With suitable circuitry, this change can be converted into a dc voltage that can

be used to give a direct reading of relative humidity, or to serve as the monitoring signal of an automatic humidity control system.

The sensor is designed to measure relative humidity between 10% and 90% and has the advantage that its long-term characteristics are unaffected by condensation of water on the foil surface.

The relationship between relative humidity and capacitance for the sensor is somewhat non-linear. To obtain a direct indication of humidity, either a non-linear scale must be employed on the readout or the circuitry output signal must first be processed by a linearising circuit.

The sensor will not respond immediately to a very rapid, large-scale change in relative humidity. For example, if the relative humidity jumps from 10% to 43%, it will take the sensor round three minutes to again provide a stable reading, according to the Philips data.

If the relative humidity exceeds 90%, even slight temperature variations can lead to condensation of water on the sensor foil; this will cause measurement errors and a considerable increase in response time. The sensitivity of the sensor is not specified below a relative humidity of 10%, although it would be feasible to measure values below this.

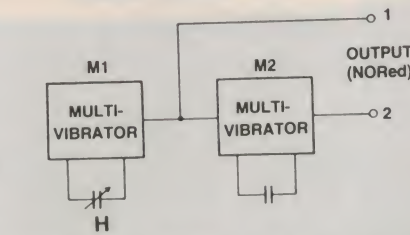


Figure 1. Block diagram of the circuit technique employed in the humidity meter. Two synchronised multivibrators provide an output signal which varies proportional to variations in relative humidity. 'H' is the humidity sensor.

The circuit

We've used a circuit technique suggested in Philips' Technical Note 134. The operating principle is based upon measuring the pulse width differences between two synchronised multivibrators (see Figure 1). M1 is controlled by the capacitive humidity sensor, the output pulse width varying as the humidity varies. The second multivibrator, M2, has a fixed pulse width, set by a fixed capacitor. The output of each capacitor is combined in a NOR gate which produces an output signal that varies in width proportional to the difference between the multivibrator output pulse widths (see Figure 2). This is very convenient as the difference signal will be virtually independent of temperature and voltage,


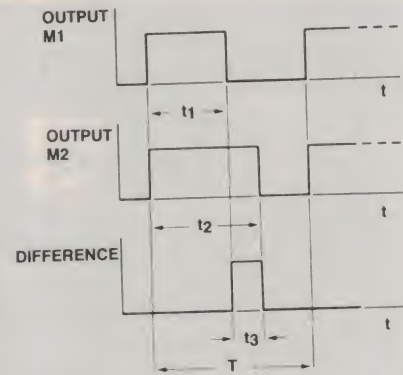



Figure 2. Illustrating how the output signal, t_3 , is obtained. If t_2 is fixed and t_1 varies with variations in humidity, t_3 will vary in direct relation to it.

provided the characteristics of both multivibrators are identical and the fixed capacitor controlling M2 has a temperature coefficient as close as possible to the capacitive humidity sensor. The first requirement is easily met as both multivibrators employ two gates from a 4001 quad NOR gate package.

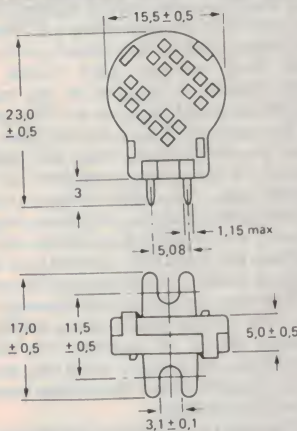To provide M2 with a temperature characteristic closely matching that of the humidity sensor, several positive temperature coefficient ceramic capacitors in parallel are used. A small value trimmer capacitor permits adjustment of this multivibrator to calibrate the



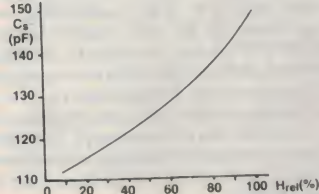The relationship between H_{rel} and C_s (sensor capacitance) can be approximated by:
 $C_s/C_s(12\%) = 0.985 + 0.34(H_{rel}/100)^{1.4}$
 where $C_s(12\%)$ is the capacitance at $H_{rel} = 12\%$.




Relationship between relative humidity, H_{rel} , and sensor capacitance, C_s .

Characteristics of the humidity sensor


Capacitance	$122\text{pF} \pm 15\%$
($T = 25^\circ\text{C}$, $H_{rel} = 43\%$, $f = 100\text{ kHz}$)	
Sensitivity	$(0.4 \pm 0.05)\text{pF}/\%$
($H_{rel} = 43\%$)	
Operating frequency range	1 kHz to 1 MHz
Temperature dependence	$\approx 0.1\%/K$
(over operating frequency range)	
Measuring range	H_{rel} between 10% and 90%
Operating temperature range	0°C to 60°C
Maximum operating voltage	15 V
(ac or dc)	
Dielectric loss ($\tan \delta$)	$< 35 \times 10^{-3}$
(at $T = 25^\circ\text{C}$, $f = 100\text{ kHz}$)	
Response (90% value)	
within the range of $H_{rel} = 10\%$ to 43%	$< 3\text{ min.}$
within the range of $H_{rel} = 43\%$ to 90%	$< 5\text{ min.}$
($T_{amb} = 25^\circ\text{C}$, in circulating air)	
Hysteresis at one cycle	$\approx 3\% (H_{rel})$
($H_{rel} \uparrow 10\% \rightarrow 90\% \rightarrow 10\%$)	

Capacitance of the humidity sensor at four different frequencies (nominal values)

frequency	C_0 (pF)	ΔC (12%)	ΔC (100%)
f (kHz)	($H_{rel} = 0\%$)	(pF)	(pF)
1	116.1	3.6	45.5
10	112.7	3.5	44.2
100	109.0	3.3	42.7
1000	104.6	3.3	41.0

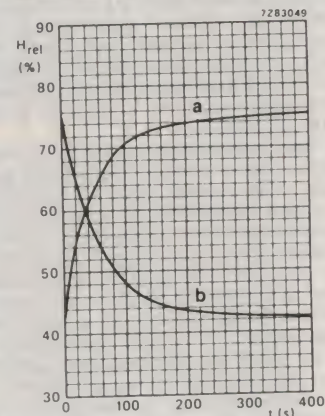


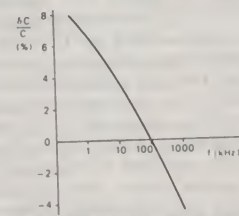Response of sensor to rapid changes in humidity: (a) from 43% to 75%, (b) from 75% to 43%.



Influence of frequency upon sensor capacitance, C_s , based upon a reference frequency of 100 kHz. (Note this curve also represents the influence of frequency on ΔC and C_0 .)

LEDs — TIL220R
OR SIMILAR

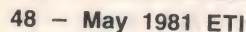

PARTS LIST — ETI 256

Resistors		all ½W, 5%
R1, R2	470k	
R3	4k7	
R4	22k	
R5	4M7	
R6	390R	
R7	1k	
RV1	10k miniature trimpot	
Capacitors		
C1, C2	47p ceramic (see text)	
C3	10u/16 V tantalum	
C4	100n greencap	
CV1	2-40p film or ceramic trimmer	
Semiconductors		
IC1, IC2	4001	
IC3	LM3914	
LED1-7	TIL220R or any suitable LED	
D1	1N914, 1N4148 silicon diode	
ZD1	400 mW or 1 W zener, see text	
Miscellaneous		
H1	Philips humidity sensor type 2322 691 90001	
ETI-256 pc board, pushbutton switch (momentary action); battery clip to suit No. 216 9 V battery.		

read at a glance. The indication is somewhat non-linear; that is, the interval between each LED is not the same, as the linearising circuit is not perfect. The interval decreases with increasing humidity. Between LED1 and LED2, the change indicated in relative humidity is 15%, from 35% to 50%. At the opposite end of the scale, the change indicated in relative humidity between LED5 and LED6 is less than 10%. The reading indicated by LED6 is only accurate to a few per cent in any case. If you want to read the humidity to within 5% over most of the range between 10% and 90%, we suggest you opt for a meter readout. A calibration graph is given in Figure 3. To employ the project as part of an automatic environment control system, the LED readout circuitry is necessary.

Our prototype operates from a No. 216 9 V battery. To conserve battery life, we used a pushbutton switch to operate the unit, and the reading stabilises very shortly after the circuit is switched on.

Construction

The unit is quite easy to assemble. We've not given any details of housing the completed project as this is likely to vary widely according to individual requirements. Generally, the components may be assembled in any order. Take care with the orientation of the three ICs, the LEDs, C3 and the two diodes, D1 and ZD1. The humidity sensor is not polarised and may be connected any way round. Solder its leads quickly to avoid affecting its performance. The photo-

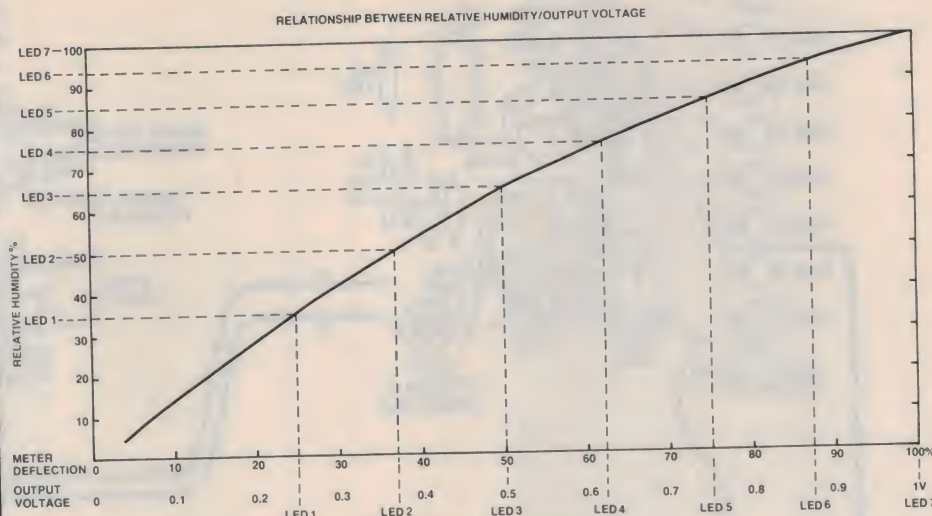


Figure 3. LED display and humidity readings against meter deflection.

graph of our unit shows the sensor mounted on the pc board, but we did this principally for convenience. It can be mounted off the board but it is necessary to keep the leads short and ensure they have little capacitance. We would recommend you mount the sensor no more than about 50 or 60 mm away from the pc board and use 22 gauge tinned copper wire spaced the width of the sensor's pins apart (about 5 mm). A twisted pair of hookup wire is not recommended.

If the unit is to be used in a very humid environment (in a hothouse, for example), mount the electronics in a sealed box with the sensor mounted externally, and pass the sensor's pins through a hole in the box, sealing the box with Silastic or a similar sealing compound so that the humid atmosphere does not affect the electronics.

Note that positive temperature coefficient (PTC) capacitors are specified for C1 and C2. *No substitutes can be*

made without adversely affecting the operation of the instrument. We have given Philips part numbers but other manufacturers do make PTC ceramic capacitors. It is necessary to ensure you purchase capacitors having a positive temperature coefficient of 100 parts per million (i.e. P100) of the nominal capacitance specified (47 pF).


Alignment

To obtain optimum performance, the following adjustment procedure is recommended:


If you are using the LED display, connect a high impedance voltmeter (input impedance of 1M or greater) between pin 5 of the LM3914 (IC3) and 0 V. Set RV1 at minimum resistance.

1) Replace the humidity sensor by a combination of capacitors to make up a value of 118 pF (a 100 pF, 15 pF and 3p3 in parallel). Turn the unit on and adjust CV1 to produce minimum out-

Component overlay. If you want meter readout, leave out IC3, the LEDs and R7, put R4 in place of Link 1 and connect the meter between the pin 5 pad of IC3 (+) and 0 V.

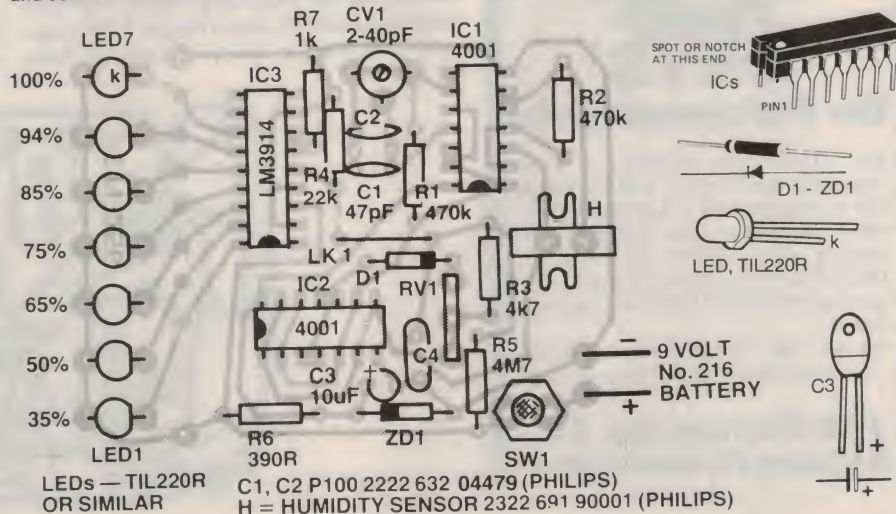

Project 256

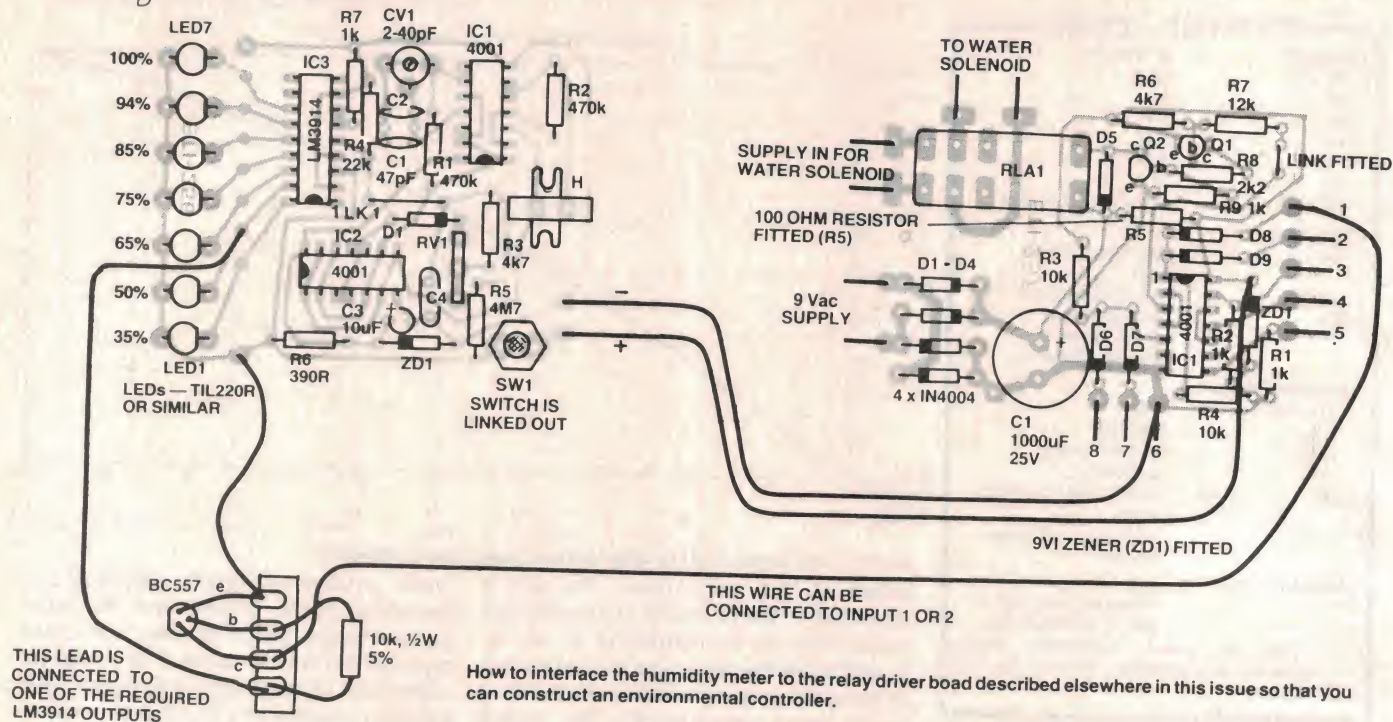

put. You should be able to get this down to about 0.09 V (90 mV). A slight zero offset reading occurs due to the current supplied by R5. Turn the unit off after adjustment.

2) Replace the 118 pF capacitor network substituted for the sensor by one of 160 pF (150p and 10p in parallel). Turn the unit on again and adjust RV1 to produce a reading of one volt on your voltmeter. LED7 should light.

If you are using a 50 uA meter for readout instead of the LM3914 and LEDs, repeat steps (1) and (2), but this time connect your high impedance voltmeter across C4. In step (2) adjust for full-scale deflection on the meter.

As a controller


The humidity meter can be used as a controller in conjunction with the ETI-257 Universal Relay Driver Board described elsewhere in this issue. It is necessary to use the LED display version of the humidity meter. A simple interface circuit, involving a PNP transistor, is used to derive an output from

one of the LEDs on the humidity controller and drive a 'pull high to operate' input on the ETI-257 relay driver board. The accompanying diagram shows how it's done.

The switch on the humidity controller board is not used and the pads on the board are linked. A BC557 is mounted on a tagstrip, along with a 10k, ½W resistor, and this provides the interface between the humidity meter and relay driver boards. The appropriate humidity level is selected by connecting a lead from the cathode of the appropriate LED to the base of the interface transistor, via the 10k resistor.

Power supply for the humidity sensor is obtained from the relay driver board. Don't forget to install Link 1 on the latter board.

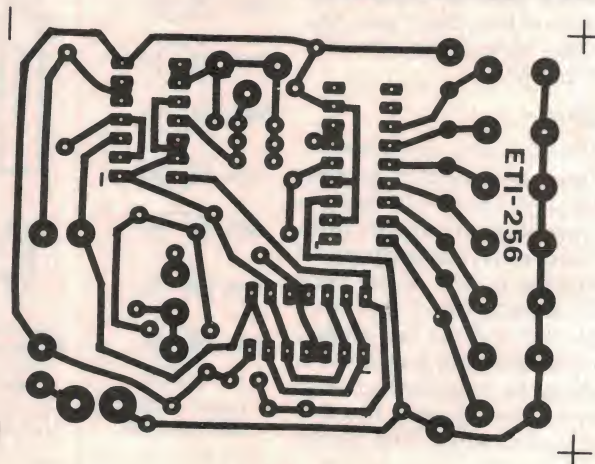In this application the sensor should be placed so that it takes a reading unaffected by the source of water vapour. ●



**DICK SMITH
ELECTRONICS**



NOW OPEN

**7
DAYS***

On Parramatta Rd

Yes! Dick Smith Electronics, your one-stop electronics supermarket, has a branch open 7 days per week! Now you won't be caught short looking for a .001uF greencap to finish a project on Sunday afternoon. Just call into Dick Smith Electronics - Auburn!

*Open 9AM - 5.30PM Mon-Fri, 8.30 - 12 noon Sat & 10AM - 2PM Sunday

**145 Parramatta Rd,
Auburn Ph 648 0558**

HURRY! THESE PRICES JUST CAN'T LAST FOR THESE FULL SPEC. PRIME I.C.'s

2716. 450ns Single 5v Supply	\$7.50
2716. 200ns Single 5v Supply	\$19.50 ea.
2114. 450ns	\$2.50
2114. 300ns	\$3.30 ea.
2708. 450ns	\$5.90 ea.
4116. 200ns	\$2.50 ea.
Z80 C.P.U.	\$10.80 ea.
Z80A C.P.U.	\$11.10 ea.
Z80 C.T.C.	\$9.40 ea.
Z80A C.T.C.	\$11.30 ea.
Z80 P.I.O.	\$6.50 ea.
Z80A P.I.O.	\$8.50 ea.
Z80 S10/0	\$38.60 ea.
Z80A S10/0	\$49.00 ea.
Z80 S10/1	\$38.60 ea.
Z80A S10/1	\$49.90 ea.
Z80 S10/2	\$38.65 ea.

Z80A S10/2	\$49.00 ea.
Z80 S10/9	\$38.60 ea.
Z80A S10/9	\$49.90 ea.

8 BIT MPU'S

6802	\$11.80 ea.
6808	\$10.50 ea.
6809	\$45.00 ea.
6821	\$5.10 ea.
6840	\$7.84 ea.
6845	\$38.94 ea.
6847	\$28.00 ea.
6850	\$4.40 ea.
6852	\$5.50 ea.

Full range of chemicals available.

ALL PRICES PLUS 15 PERCENT SALES TAX IF APPLICABLE

FLOPPY DISC CONTROLLERS

FD 1771	\$25.00 ea.
FD 1791	\$61.00 ea.
FD 1793	\$61.00 ea.
FD 1795	\$65.00 ea.

RISTON 3000 COATED FIBREGLASS BOARD SINGLE SIDED

6" x 3"	\$1.60 ea.
6" x 6"	\$2.25 ea.
9" x 6"	\$3.30 ea.
12" x 12"	\$7.90 ea.

DOUBLE SIDED

6" x 3"	\$2.25 ea.
6" x 6"	\$3.25 ea.
9" x 6"	\$4.05 ea.
12" x 12"	\$9.40 ea.

NEW JIFFY BOXES

New snap-in PCB design. PCB's slide vertically into card guides or larger boards will clip in horizontally. No more expensive spacers etc.

UB1 \$1.65	UB2 \$2.50
UB3 \$1.30	UB5 \$0.80

ALL PRICES PLUS 15 PERCENT SALES TAX

COMPUTER COOLING FANS

Either 115 volts
or 230 volts.

\$18.00

Plus 15% S/T

HIROSE AND ANSLEY RIBBON CABLE CONNECTORS FITTED SAME DAY



SOAR MODEL 501A

4 DIGIT
LARGE LCD
DISPLAY

Send now
for spec's.

Add \$3 P&P
and certified mail.

Plus 15%
sales tax


\$69

QUALITY RITRON HEATSINK (AS FEATURED AUGUST ETI)

HIGH THERMAL CAPACITY		UNANODISED FINISH	
BLACK ANODIZED		HS1	38MM
		HS12	75MM
		HS13	150MM
		HS14	300MM
		HS15	600MM
		HS16	1200MM
BLACK ANODISED	1-4	5-9	10-49
HS1 38mm (1 1/2")	\$1.85	\$1.75	\$1.50
HS2 75mm (3")	\$3.00	\$2.90	\$2.50
HS3 150mm (6")	\$5.80	\$5.40	\$4.90
HS4 225mm (9")	\$8.10	\$7.60	\$7.10
HS5 300mm (12")	\$8.90	\$8.40	\$7.90
HS6 600mm (24")			\$6.50
HS8 900mm (36")			\$4.90
		Price On Application	
		Price On Application	
UNANODISED	50-99	100-499	500+
HS11 38mm	\$1.40	\$1.20	\$1.00
HS12 75mm	\$2.50	\$2.20	\$1.90
HS13 150mm	\$4.90	\$4.50	\$4.00
		\$3.20	\$2.45
		\$2.45	\$2.40

**"For reliable data storage,
you can't beat Shugart's**

Verbatim

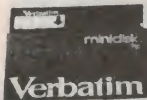

CHECK THESE PRICES

SA400	\$330.00
SA800	\$550.00
SA801	\$550.00

5 INCH \$3-69

8 INCH \$3-90

SPECIAL

Part No.	Sectoring	Application
MD 525-01	Soft Sector	TRS 80 Apple
MD 525-10	Hard 10 Sector	North Star
MD 525-16	Hard 16 Sector	Micropolis
FD32-1000	Hard Sector	Shugart 801R
FD34-1000	Soft Sector	IBM 3740

SUPER SPECIALS

PANEL METERS



All prices plus tax.

MU45 ... 58mm x 52mm
50-0-50µA

1mA fsd
50µA fsd
10A DC
30V DC

All \$6.50
plus tax

MU45 VU meter \$7.60 plus tax

MU65 100mm x 82mm
30VDC
10A DC
1mA DC

All \$9.60
plus tax

Tax exempt customers from Ritronics Wholesale.
(03) 489 7099

2114's	\$3.30 ea	2708's	\$6.90 ea
2716's	\$11.00 ea	2732's	\$23.00 ea
		100 Redleds	\$9.00

ALL PRICES PLUS TAX IF APP

REGISTERED PACK & POST \$5.00



RITRONICS WHOLESALE
425 HIGH ST., NORTHCOTE VIC
481 1923 489 7099 PO BOX 235

Bankcard Mail Orders Welcome

Please debit my Bankcard

Bankcard No

Expiry Date

Name

Signature ETI 5/81

Bill Edge's

ELECTRONIC AGENCIES

Bankcard
welcome here
115-117 Parramatta Road Concord 2137
(Corner Parramatta Rd & Lloyd George Ave)
Tel. 745 3077 (two lines)

open Sundays

what else do we carry?
HARDWARE * TOOLS * WIRE * SEMIS
VALVES * HI-FI * KITS * PA EQUIPMENT
MIKES * SPEAKERS * BOOKS

MAIL CHARGES

\$5-\$9.99
\$10-\$24.99
\$25-\$49.99
\$50-\$99.99
\$100 or more

\$1.00 All heavy or bulky items
\$2.00 (over 20kg) sent 'Freight-on'
\$3.00 through carrier. Bankcard
\$4.00 welcome—by mail, phone or
\$5.50 over the counter.

No crossover
needed with
these

TRADING HOURS
Mon-Fri 9am-5.30pm
Saturday 9am-noon
Sunday 10am-2pm

amazing metal detector

ETI5000 discrimi-
nator. 4 modes.
Ground balance.
Complete kit. Pre
wound search coil.

\$199



\$89
Search head &
handle only.

Some of our popular kits

Cylon voice from EA	K-2375 \$18.95
Le Gong doorbell kit	K-2385 \$15.00
EA Infra-red remote control	K-2393 \$39.00
Light/sound activated flash	K-2340 \$26.95
Fuzzbox EA2/81	K-2350 \$19.50
Musicolor Mk III	K-3140 \$59.50
ETI324 LED Tacho	K-3240 \$29.95
EA Windscreen wiper delay	K-3260 \$19.95
LED Oil Temperature Meter	K-3270 \$15.50
Engine Analyser EA	K-3275 \$53.50
ETI438 LED Level Meter	K-3360 \$11.95
Stylus Timer EA	K-3400 \$47.95
Loudspeaker protector ETI455	K-3420 \$26.00
General purpose Preamp ETI445	K-3427 \$8.50
ETI480 100W amp module	K-3442 \$25.00
ETI466 300W amp module	K-3444 \$63.00
EA 300W amp module	K-3570 \$85.00
Playmaster MOSFET Amp	K-3517 \$169.00

NOW A \$99 Computer!

available
June 1981

Plugs
into any
TV!

ETI 660

No one would have believed it a few years ago. Features include: colour capability, operates from optional 9V plugpack, 1K memory expandable to 3K on-board, single board construction, cassette interface, audio output (play tunes), simple to program (uses Chip-8). Expansion projects coming up include: ASCII keyboard, light pen, games software etc.
Starter Kit (1K RAM, B&W video) \$99.00
9V, 200mA plugpack to suit \$6.50
Colour video option \$8.00
RAM expansion (add to PCB) \$17.00
As with all new kits, please phone first to check stocks. We expect the kit to be in stock some time in June 1981.

"Selectalott"

Why bother thinking up numbers when this great little kit can do it for you? 40 LEDs tells you what to pick. Who knows? You could even win! Great conversation piece (also useful for picking dishes in Chinese restaurants!)

100's sold


\$22.95



pHenomenally popular pH meter only

SHOP ON SUNDAYS
AND AVOID PARKING
PROBLEMS.

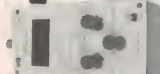The great ETI kit. Includes all parts plus pH probe and both buffer solutions. 3 1/2 digit LCD readout. pHantastic!



\$99.50

Negative Ion generator



Do negative ions make you healthy & happy? Now you can find out for yourself at a price you won't be negative about! Completely safe design from ETI April '81. Commercial units sell for up to \$100!

ONLY \$39

NEW

Infra-red remote control

Controls mains equipment drawing up to 5A from up to 10m away. Transmitter can be carried in your pocket. We don't have to tell you how convenient this could be. Cat. K-2390.



only \$69.00

Special offer! SPEAKER BARGAIN

Limited stock of fantastic Coral 12L40 woofers. 30cm, 80W, Sens. 92dB, Freq. Range 34-3000Hz, Res. 34Hz. Normally \$89.00. Bill's price \$49. Hurry—at this price they won't last.



\$49 SAVE \$40

Piezo tweeters



Famous Motorola Piezo horn tweeters. More high end output than just about anything. The ideal way to get high power, high efficiency, high quality treble in a compact economical package. Three different models. All can be connected directly in parallel with low frequency drivers—no crossover is needed! Can handle up to 100W (25Vrms). Frequency response 3.8kHz to 28kHz.

KSN1005A 85mm square narrow disp.	\$15.00
KSN1016A 145x67mm wide disp.	\$17.50
KSN1025A 180x81mm wide disp.	\$24.00

NEW

3 styles

SELECTASPEAKER

If you're in the market for component midrange & tweeter units, but can't decide which suits you best, come in to Electronic Agencies and try out our range of 40 different units on our exclusive "Selectaspeaker" demonstration system. The "Selectaspeaker" lets you switch between all of our Foster, Philips, Coral & Motorola speakers so that you can actually hear the differences. Don't buy on looks, prices of 'specs' when you can buy on sound.

ETI4000/1 & 2 Speaker kits

Famous ETI4000 speaker systems based on Philips drivers.
4000/1 4 way speaker and crossovers only \$529 pair
4000/1 complete kit with cabinets \$799 pair
4000/2 3 way speakers and crossovers only \$389 pair
4000/2 complete kit with cabinets \$549 pair

ETI5000 Amp kit

with manual



Complete kit for the ETI5000 100W per channel power amp. Includes all parts, deluxe black cast front panel/heatsink and pre-drilled case. Plus our own exclusive detailed assembly manual.

all this for **\$295**

Power Module

Fantastic 150W MOSFET power amp module. As used in ETI5000 amplifier.

\$59

We now have a new kit manager.

& our kits are getting easier and easier to build—in other words—they work!

'Universal' relay driver board

Operating a relay to switch heavy current or mains voltages is a common requirement in electronic control applications. This project permits a relay to be switched in a variety of ways and from a variety of inputs.

Graeme Teesdale


THIS VERSATILE relay driver unit is intended to be used with projects or devices not normally providing a switched relay output. In addition, power for external circuitry can be obtained from the board.

The unit has three groups of 'logic' inputs and a direct input. The relay itself is driven by two transistors, Q1

and Q2, and the direct input goes to the base of Q1 via a resistor (R7). Linking this input to the unit's 0 V rails — via a switch, a transistor which is turned on by a signal (open-collector logic) or a logic gate output — will operate the relay.

The logic circuitry on the board can be implemented by installing Link 1,

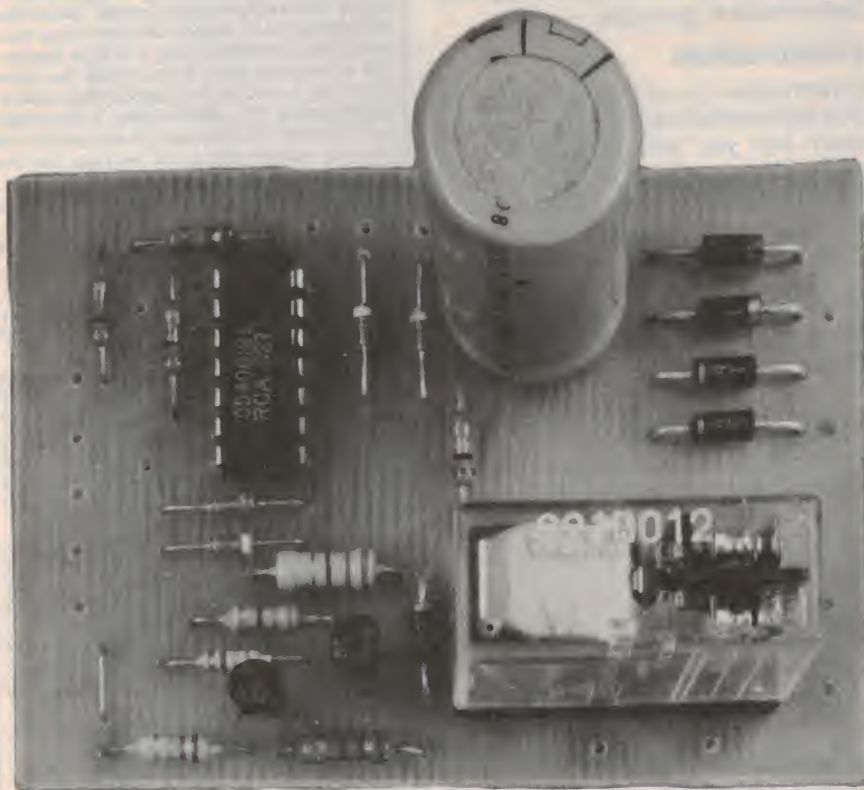which connects the output of the logic circuitry to the direct input. There are two "logic high to operate" inputs (pins 1 and 2). A logic high level — i.e. voltage level above about 2 V — on either of these inputs will operate the relay. There are also two "logic low to operate" inputs (pins 7 and 8). Pulling either of these inputs below logic low — about



The relay driver board is simple, yet versatile. The external input/output pins are located around the edges of the board.

ATTENTION Microcomputer Programmers

Dick Smith Electronics, Australia's most energetic marketers of microcomputers like the highly successful System 80 and Exidy Sorcerer, are currently engaged in an ongoing program to develop truly Australian business software for these machines. To help us with this development, we're looking for further experienced contract programmers.

If you're an experienced microcomputer programmer with a professional outlook and demonstrated track record in completing projects in one or more of the following areas, we'd like to hear from you.


1. Z80 machine language programs
2. Programs in Microsoft Level II BASIC
3. Business applications programming

Please apply initially in writing to:

Mr Jim Rowe
Technical Director,
Dick Smith Electronics,
P.O. Box 321,
North Ryde, NSW 2113

Project 257

The pc board artwork is on page 139.

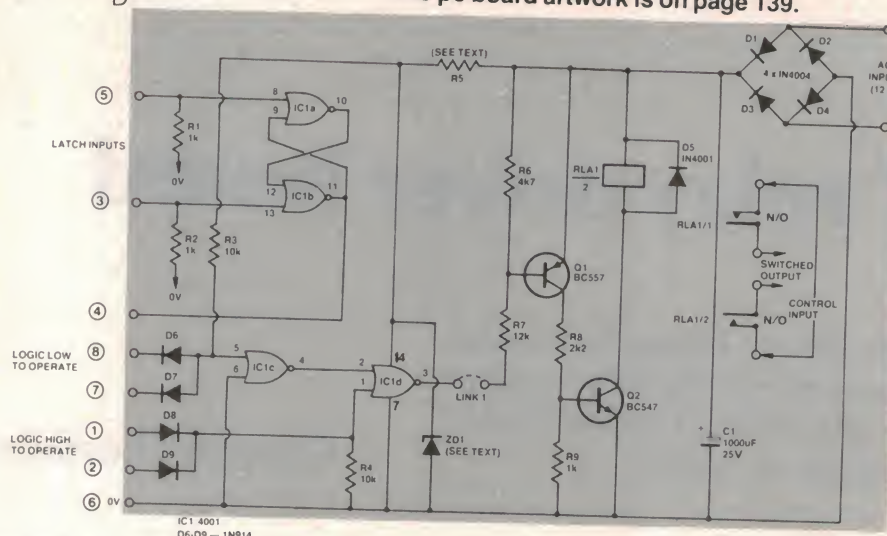

Circuit diagram of the relay driver board. Note that the rectifier diodes may be any of a range of types, such as 1N4001-2-4, etc., or EM401, EM402, etc. A variety of common relays will fit the pc board.

0.5 V — will operate the relay. Note that these input pairs are ORed with diodes and can be linked so that one input inhibits the other. In addition there are two "latch" inputs, pins 3 and 5. Pin 4 is the output of the latch circuitry and latch operation is implemented by linking this pin to one of the other inputs. All the logic inputs are high impedance and can be driven from CMOS circuitry.

This unit is powered from a 12 to 15 Vac source such as a plugpack or 5 VA transformer. Supply for IC1 (and perhaps any off-board circuitry) is obtained from a simple zener regulator circuit. This can be chosen to suit individual requirements. We used a BZY96/8V2 zener (1N4738) to provide an 8.2 V rail for IC1. We used a 220 ohm, 1 W resistor for R5. You can use any convenient zener from 5.1 V to 15 V — but no higher, and we recommend 1 W types run at around 50-60 mA current. You will have to work out the value of R5 according to your choice of zener. For a 15 V zener, R5 could be 47 ohms, for a 5.1 V zener, 270 ohms, or for a 12 V zener, say 100 ohms. There's plenty of latitude and

these values are only given as a guide.

The logic circuitry (i.e. IC1) can be supplied from an off-board source if you wish. To do so, remove R5 and use a 15 V zener for ZD1 to prevent spikes on the external supply line causing damage to IC1. Note also that the logic levels on inputs 1, 2, 3 and 5 should also be no higher than 15 V.

The accompanying drawings illustrate how the unit is used in its four basic modes of operation.

Construction

Construction is very straightforward. The components may be mounted in any order but you will probably find it easiest to leave the relay and C1 until last. Watch the polarity of all the diodes, the transistors and the IC. However, leave out link 1 at this stage.

Once you've got it together and have checked everything, apply 12 V ac to the ac input and check various modes of operation as follows:

- (1) Bridge the free end of R7 to ground. The relay should operate.
- (2) Install link 1, then bridge pin 7 to ground. The relay should operate.

Likewise for pin 8.

(3) Bridge pin 1 to the cathode of the zener. The relay should operate. Likewise for pin 2.

(4) Connect pin 4 to pin 1 or 2. The relay may operate. Apply a pulse to pin 3 or 5 and see that it latches on. A pulse on the other input will drop it out again.

If all is well, your unit is ready for installation!

HOW IT WORKS — ETI 257

The best place to start is right in the middle of the circuit — because that's the 'business' end!

Transistor Q2 has relay RLA1 as its collector load. Diode D5 provides protection for Q2 when the coil current is cut off whenever Q2 is turned off. The base of Q2 is driven by the collector of Q1 via R8 and R9. Base bias for Q1 is obtained from the resistor network of R6 and R7. The 'free' end of R7 can be linked to on-board logic circuitry (IC1) or driven by an external source.

If the free end of R7 is connected to 0 V then base current will flow in Q1, which will turn on. This will turn on Q2 and the relay will operate. In fact, all that is required to turn Q1 on is to 'pull' the free end of R7 about 1 V below the positive supply rail to overcome the 0.6 V base-emitter turn-on voltage of Q1.

Effectively, a 'low' level on the free end of R7 will operate the relay.

Two groups of logic circuitry built around IC1 are included to provide a variety of operating 'modes'. IC1 is a quad NOR gate package. One gate, IC1d, is arranged to provide a 'logic high to operate' mode. Two diodes connected as a simple OR gate have their cathodes connected to pin 1 of IC1d. The output of another gate, IC1c, drives the other input, pin 2, of IC1d. IC1c has one input (pin 6) connected to 0 V, which is thus held at logic low. Pin 5 of IC1c is held at logic high by R3 and thus its output, pin 4, will be high. As this drives pin 2 of IC1d its output, pin 3, will be high. With Link 1 fitted, Q1 will normally be off and the relay not operated.

When a high logic level is applied to either input pin 1 or 2, or both, the diode(s) will conduct driving pin 1 of IC1d high. The output, pin 3, will go low and the relay will operate. The relay will remain operated only while the input remains high.

Two diodes (D6, D7) are connected as a simple OR gate with their anodes connected to pin 5 of IC1c. A logic low on either input pin 7 or 8 ('logic low to operate') or both will pull pin 5 of IC1c low and its output, pin 4, will go low. Pin 2 of IC1d will go low and thus pin 3 of IC1d will go low and the relay will operate. The relay will remain operated only while the input remains low.

The remaining two gates from IC1 are connected as a set-reset (SR) flip-flop. Pin 4 on the pc board provides an output which may be coupled to the other inputs. Assume the SR flip output is initially low. A pulse applied to input pin 3 or 5 will cause pin 4 (pins 9, 11 of IC1a, b) to 'latch' high. A pulse then applied to the opposite input pin will cause the output to go low again, and remain low.

This part of the circuit can be used as a 'switch debouncer' as illustrated.

Power is derived from an off-board 9 Vac or 12 Vac source. This drives a bridge rectifier, diodes D1 to D4, smoothing being provided by C1. A zener diode, ZD1, is used to provide a regulated supply to the logic circuitry (IC1).

PARTS LIST — ETI 257

Resistors

all ½W, 5% unless noted

R1, R2, R9	1k
R3, R4	10k
R5	220R, 1W (see text)
R6	4k7
R7	12k
R8	2k2

Capacitors

C1	1000 u/25 V electrolytic
----	--------------------------


Semiconductors

IC1	4001B
Q1	BC557
Q2	BC547
D1-D5	1N4001, 1N4002 etc
D6-D9	1N914, 1N4148 etc
ZD1	400 mW or 1 W zener, see text

Miscellaneous


ETI-257 pc board; RLA1 — relay, Fujitsu FRL-621D012 or Takamisawa VB 12STAN or Pye 265/12/G2V.

universal relay driver

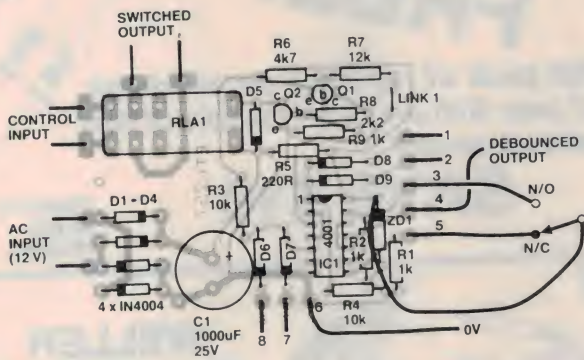


SWITCH DEBOUNCING

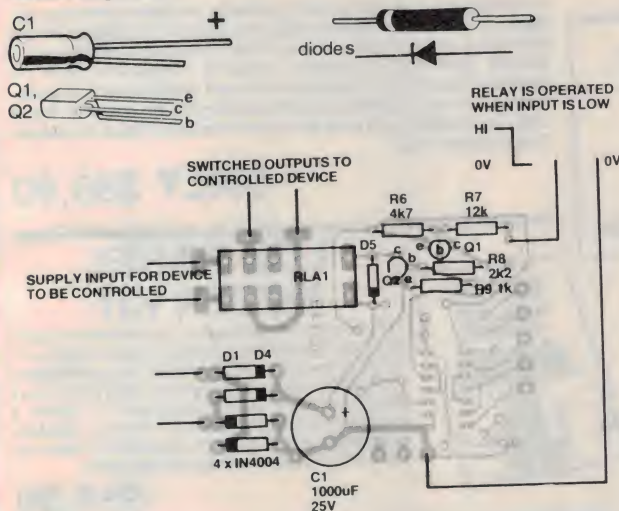The SR flip-flop (IC1a and b) is not electrically connected to the rest of the circuit and may be used in external circuitry — for example, as a switch debouncing circuit.



LATCH OPERATION

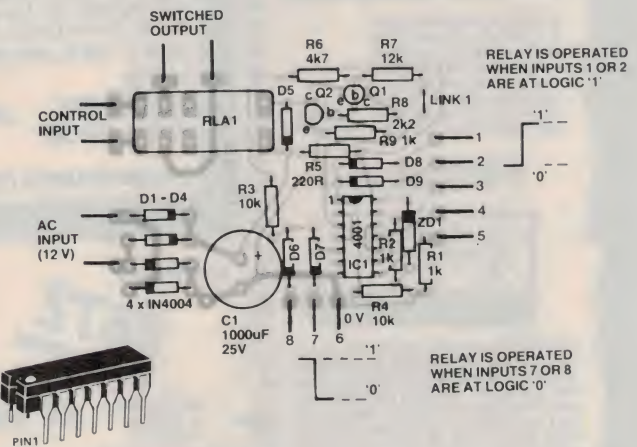Pin 4, the output of the set-reset (SR) flip-flop, must be linked to either pin 1 or pin 2, or pins 7 or 8. A positive-going pulse on pin 3 or pin 5 will cause the relay to latch. A positive-going pulse on the opposite latch input will then cause the relay to unlatch.



DIRECT INPUT

The relay will operate when the input is low (i.e. 0 V) or 'pulled' about 1 V lower than the positive supply rail. Only those components shown are necessary for this mode of operation.

LOW OR HIGH TO OPERATE

The relay will be operated when pins 1 or 2 are held at logic high. To operate the relay from a logic low, pins 7 or 8 must be held at logic low. The inputs are ORed so that up to two input signals can be employed to operate the relay in each mode.

archive
COMPUTER SERVICES
PO Box 13 Clayfield QLD 4011 Ph (07) 2622615

SPECIAL
RECONDITIONED MALIBU 160 \$2200

WE NOW SELL THE COMPLETE
CORVUS RANGE.
HARD DISKS
MIRRORS
CONSTELLATIONS

MORROW 26MEGABYTE HARD DISK
NEC SPINWRITERS
ITHO PRINTERS
8" DOUBLE SIDED DISK DRIVES
TELEVIDEO 912
ARCHIVES BUSINESS COMPUTERS
TRS 80* TO 5100 INTERFACE *TEACH MARK TAMEY
CCS 12 SLOT MAINFRAME COMPLETE

CCS S100 BOARDS ASSEMBLED AND TESTED
280* CPU 4MHz *TEACH MARK 21100
16K STATIC RAM
32K STATIC RAM
64K DYNAMIC RAM 4MHz
12 SLOT MOTHERBOARD WITH CONNECTORS
5" AND 8" DISK CONTROLLER
WITH CPM 2.2
2 SERIAL AND 2 PARALLEL PORTS
4 SERIAL PORTS
4 PARALLEL PORTS

	TAX FREE	TAX INCLUDED
	5100	5656
	3000	3378
FROM	840	923
	725	802
	1190	1340
	6500	7175
	149	166
	499	563

	295	331
FROM	260	294
FROM	555	627
	649	727
	140	157
	399	448
	450	499
	229	337
	285	321
	250	281

SEND FOR OUR FREE 90 PAGE CATALOGUE NOW INCLUDING A TUTORIAL ON BRINGING UP CPM

All prices are F.O.B. and subject to change without notice.

Dealer inquiries invited.

RIT ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE, 3070

FREE!


250 pack of resistors on purchase of over \$10 on presentation of this advertisement.

SAVE \$10

(Normally 4c per resistor)

NEW


AUDIO MIXERS

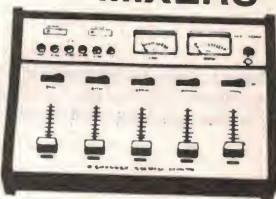

- 2 Hi-Low microphone inputs
- 2 Magnetic/Ceramic phono inputs
- Also tape and tuner inputs
- 2 VU meters
- Stereo or mono
- Independent CUE on each chan
- Compact size, 26 x 20 x 6.5cm
- 9V. battery operation, ext. DC input socket.

\$89

PRO Model

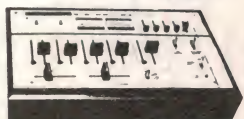

- Facilities for 4 stereo program input and 2 mic. inputs
- Built-in low noise preamplifier for magnetic phono and low or high impedance microphones
- Professional stereo slide controls
- Headphone circuits to monitor each input and output
- Talk switch to attenuate music volume 14db so mic's can be used without readjusting music levels
- 5 channel stereo graphic equalizer section using separate slider controls
- Meters monitor the output of left and right channels independently.

\$169

"Selectalott"

With this great little kit you don't have to bother about thinking up numbers anymore. It features 40 LEDs and tells you what numbers to choose. Great for picking a winner.

\$22.50

CYLON VOICE

Are you sick and tired of that boring voice? Build this delightful little kit and impress your friends with the Cylon Voice.

\$18.50

'LE GONG' door bell kit

Are you sick of ding-dongs? You don't have to spend a fortune to hear a pleasant sounding doorbell. This great little kit does the job simply and cheaply. (pushbutton not included)

\$15.00

8" TWIN CONE SPEAKER

Incredible frequency range from \$7.00 which beats our competitors hands down. Imagine, for a fraction of the cost of the usual pair of hi-fi speakers you can achieve the same gutsy sound. **HURRY! AT THIS PRICE THEY CAN'T LAST!!** 1 only \$7.50, 2 for \$14.75, 10 up \$6.90 each.

2851 240V/12.6C.T. 150MA \$2.50
2155 240V/16.3-15V 1A multitap \$3.85
S.E.C. APPROVED AS WELL.

DON'T TAKE ANY RISKS!

NOW

ANOTHER K.O.!! 2156

only \$6.25

2 AMP VERSION OF THE 2155

INCREDIBLE

6672 TRANSFORMER

240V/15-30V
1A multitap
HURRY!!!!

\$4.90

REED SWITCH AND COIL
NOW THRASHED TO RIBBONS

30c

60c

RACK MOUNTING BOX



from **\$35**


Beautiful fashionable sturdy durable matt black finish

1-4 \$39.95
5 up \$35.00
Standard 19" (48.3cm) stacking

RELAY

- 8-12 V DC operation
- 225 OHM coil resistance
- Silver change over (S.P.D.T.) contacts handle up to massive 2 amps at 24 V DC or 100 V AC
- Mounts directly on to PCB
- Ideal for many applications

SAVE 1's 10's 25 up
\$1.50 \$1.20 \$1.00

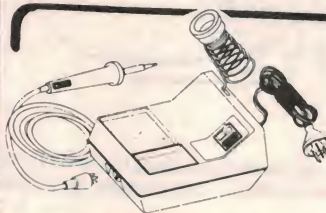

WELLER SOLDERING STATION

A transformer powered soldering station, complete with a low voltage, temperature controlled soldering pencil. The Special Weller features a 'closed loop' which controls maximum tip temperature, thereby protecting temperature sensitive components while the grounded tip protects voltage and current sensitive components. Features: • quick connect/disconnect plug for the soldering iron • extra large wiping sponge • tip tray to store extra tips • 2m flexible 3-wire power cord.

ONLY \$56.90

LCD PANEL METER KIT



This economical evaluation kit features on-board clock and reference, accuracy guaranteed to ± 1 count over entire ± 2000 counts, single reference voltage for ratiometric operation plus many more important features. Kit includes PC Board & hardware, A/D converter, LCD display, resistors, capacitors, wiring diagram, application notes and data sheet (power supply not included).

\$34.50

HARD TO GET JAPANESE TRANSISTORS

2SA683\$0.90c
2SA733P\$0.55c
2SC372\$0.40c
2SC495\$1.80c
2SC710D\$0.80c
2SC735\$0.55c
2SC799\$7.50c
2SC900F\$0.50c
2SC945A\$0.50c
2SC1014\$2.50c
2SC1017\$3.50c
2SC1018\$2.90c
2SC1061\$3.50c
2SC1096\$1.10c
2SC1173\$1.10c
2SC1226A\$1.15c
2SC1306\$2.10c
2SC1419B\$1.25c
2SC1449\$1.50c
2SC1674\$0.45c
2SC1675L\$0.40c
2SC1730\$0.80c
2SC1969\$5.50c
2SC1973\$1.90c
2SC2028\$1.90c
2SC2166\$3.90c
2SC2029\$4.90c
2SD288\$1.40c
2SD325F\$1.10c
2SD350A\$6.10c
2SD525Y\$2.10c
2SK45\$1.20c

QUALITY SPEAKERS
ETI-4001
4-WAY
156W kits
Pair \$579
Cabinets \$190



bankcard
welcome here

Bankcard Mail Orders Welcome

Please debit my Bankcard

Bankcard No

Expiry Date

Name

Signature

ETI 5/81

TO ORDER: Heavy items sent Comet Freight on. Mail Order phone 481-1436. Wholesale Customers phone: RITRONICS WHOLESALE 489-7099 or 489-1923. Mail Orders to P.O. 235 Northcote 3070. Minimum mail order \$2. Add extra for heavy items and registration, certified mail. Prices, spec. subject to change without notice.

Rod Irving Electronics

425 HIGH STREET, NORTHCOTE, 3070

COMING
SOON


FROM THE

THE \$99 COMPUTER

These features as described to us by ETI: low cost, colour capability, plugs straight into TV set aerial, only requires a 9V plug pack to power it, audio output, simple to program and many other features

With standard hex keypad — \$99; With discreet key switches — \$108; Starter Kit (1K RAM, B&W video) — \$99; 9v, 200 mA plus pack — \$6.50; Colour option (add parts to PCB) — \$8; RAM expansion (add parts to PCB) — \$17; Pre-programmed 2716 — \$18.50.

ETI — 256 HUMIDITY METER

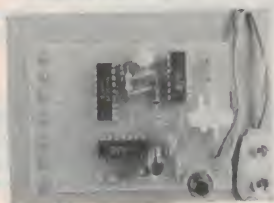

UHF TV CONVERTER ETI — 730



UNIVERSAL RELAY BOARD ETI — 257



LE GONG

Fantastic doorbell using the new Siemens SAB 0600 chip. Kit of parts . . . \$15



INCREDIBLE!!!

E/A has really done it this time. Display your Hi-Fi response on your colour TV. It will really impress your friends. Kit of parts . . . \$99



ETI Digital Clock ETI 564

At last a clock display that can be read at a distance; Kit of parts \$79.50




ETI 262 House Alarm

Kit of parts only \$15.90



New EA Light Chaser

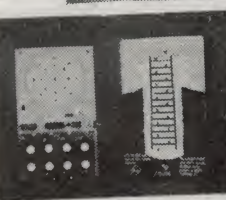Kit \$64.95 Includes Case plus Kit of parts.




LEDS and Ladders

EA August 80 Great game for winter nights. Kit of parts \$18.00 Scotchcal Front Panel to suit 3-25

ETI Digital Car Tacho

ETI 324 . . . Kit of parts \$29.95

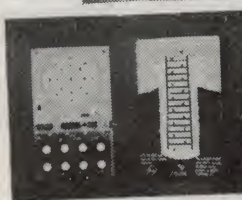

Kit for Exidy Sorcerer EPROM Programmer to be released in August EA Kit price including Scotchcal Front Panel \$75.00

TV PATTERN GENERATOR

Kit of parts as featured in EA JUNE 1980, Dot, Greyscale, Crosshatch, Raster, Check. COMPLETE KIT (including Scotchcal front panel) \$48.49

KIT WITHOUT BOX \$36.90

EPROM PROGRAMMER KIT

Kit of parts as featured in EA JULY 1980 Programs 2708, 2716 & 2532. Usb with TRS 80, Sorcerer & Compucolor Kit does not include connector from the programmer to computer. COMPLETE KIT (inc Scotchcal Front Panel) \$72.49

KIT WITHOUT CASE \$59.99

DIGITAL PANEL CAPACITANCE METER

Kit of parts as featured in EA MARCH 1980 Four Digits. Extremely popular. COMPLETE KIT (inc. Scotchcal Front Panel) \$52.49

KIT WITHOUT CASE \$39.99

TV CRO ADAPTOR KIT (EA MAY 1980)

COMPLETE KIT (inc. Scotchcal Front Panel) \$29.00

(without power adaptor)

POWER ADAPTORS TO SUIT

1. 240V to 6/7.5/9V \$9.50

2. 240V to 9V \$5.95

KITS

ETI SERIES 4000 60W STEREO AMP KIT

Complete Kit Rack Mounting Case \$199.00

Woodgrain Sided Case \$189.00

PARTS AVAILABLE SEPARATELY

Front Panel \$10.90

Rack Mounting Case \$55.00

Wooden Sided Case \$49.00

ETI 471 PREAMP KIT of parts \$45.00

ETI 472 PS KIT of parts \$47.00

(without transformer) \$24.00

ETI 470 60W Kit of parts \$26.50

(without heatsink) \$23.00

ETI 480 50W KIT of parts \$17.50

ETI 480 100W KIT of parts \$22.50

ETI 084 Car Alarm KIT \$11.50

EA TV CRO ADAPTER KIT \$29.00

EA 300W POWER AMP MODULE \$63.50

ETI 466 300W PA MODULE \$63.50

EA DIGITAL CAPACITANCE METER KIT (EA March 1980) \$52.99

AUTOCHIME KIT \$29.75

MK3 Drill Speed Control \$13.50

CAPACITOR DISCHARGE IGNITION \$32.50

MUSICOLOR MK3 KIT \$69.50

DISCO STROBE KIT \$34.50

LEDS & LADDERS (EA August) \$15.75

ETI 149 Two-Tone Generator \$34.90

ETI 563 Nicad Fast Charger \$54.90

DREAM 6802 KIT \$109.00

Power Supply TO Suit \$29.50

Hex Keypad \$24.90

ETI 568 Sound or Light Operated Flash Trig-ger \$25.90

ETI 147 ELECTRONIC DUMMY LOAD KIT \$99.00

SERIES 3000 "MINI" STEREO AMP KIT \$79.90

ETI 561 Metal DETECTOR KIT \$32.50

PLAYMASTER 40+40 AMP KIT \$129.00

PLAYMASTER AM/FM TUNER KIT \$129.00

PLAYMASTER GRAPHIC EQUAL \$99.50

PLAYMASTER GRAPH ANALY KIT \$99.50

EA 79SF9 Sound Flash Trigger \$15.00

ETI 585H Ultra Sonic RX \$15.95

ETI 585T Ultra Sonic TX \$8.95

ETI 576 ELECTROMYOGRAM KIT \$89.00



Bankcard Mail Orders Welcome

Please debit my Bankcard

Bankcard No

Expiry Date

Name

Signature

ETI 5/81

Please note we attempt to have all kits available to our customers. Provided of course we have the required information from the mags in time. Where a component is unavailable we may use a substitute or credit this cost so as to prevent delay.

Post & Pack \$2.50 small kits, heavier kits add extra postage

TO ORDER: Heavy items sent Comet Freight on. Mail Order phone 481-1436. Wholesale Customers phone: RITRONICS WHOLESALE 489-7099 or 489-1923. Mail Orders to P.O. 235 Northcote 3070. Minimum mail order \$2. Add extra for heavy items and registration, certified mail. Prices, spec. subject to change without notice.

Babani Books —

NEW TITLES!

FIRST BOOK OF PRACTICAL ELECTRONIC PROJECTS

Full constructional data, circuits, components lists for many practical projects including audio distortion meter, super FET receiver, guitar amp, metronome, etc. etc.

BP23

\$2.75

GIANT CHART — RADIO, ELECTRONICS, SEMI-CONDUCTOR & LOGIC SYMBOLS

Identify those symbols at a glance. A must for beginners and advanced enthusiasts alike. Professionals can always hide it in their desks! A steal at only...

BP27

\$2.20

FUN AND GAMES WITH YOUR CALCULATOR

Amazing collection of 101 jokes and riddles, several quite mind-boggling games for two or more players and a dictionary of numbers which are words if the calc. is read upside down.

BP38

\$2.75

RADIO STATIONS GUIDE

Eight sections covering: European LW/AM; European, Near East and N. African MW/AM; World-wide SW/AM; European FM/VHF; Broadcast band USA; Broadcast band Canada; Local UK; Wavelength/frequency conversion. Book shows station site, country, frequency, wavelength, effective radiated power and, in some cases, call sign.

BP55

\$6.45

COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS

Well-known author F.G. Rayer features applications and projects using various types of numerical displays, popular counter and driver ICs, etc.

BP67

\$6.10

TRANSISTOR RADIO FAULT-FINDING CHART

How to trace most common faults quickly. Top of chart indicates faults — users then follow arrows indicating checks in correct sequence until fault is cleared. Clever one!

BP70

\$1.85

PRACTICAL COMPUTER EXPERIMENTS

How to build typical computer circuits using discrete logic. This book is a useful intro to devices such as adders and storers as well as a general source book of logic circuits.

BP78

\$6.50

ELECTRONIC PROJECTS USING SOLAR CELLS

Well-known author Owen Bishop has designed a number of projects that benefit from solar power and obviate the problems encountered with batteries, such as weight and bulk, frequency of replacement, and failure when batteries are exhausted.

BP82

\$7.15

AN INTRO TO BASIC PROGRAMMING TECHNIQUES

Ideal for beginners seeking to understand and program in BASIC. Book includes program library for biorhythms, graphing Y against X, standard deviations, regressions, generating musical note sequences, and a card game.

BP86

\$7.15

SIMPLE LED CIRCUITS — BOOK 2

Sequel to BP42. Further light-emitting diode circuits. If you liked BP42 you'll love this one. If you don't know either it's well worth buying both!

BP87

\$5.50

HOW TO USE OP-AMPS

Source book of op-amp circuits. Design notes and applications including basic theory for amps, power supplies, audio circuits, oscs, filters, computers and control engineering. Book is written around the 741 but includes design notes for most common op-amps and comparators. Essential reference for amateur and professional alike.

BP88

\$8.25

HI-FI LOUDSPEAKER ENCLOSURES

Data for building corner reflex, bass reflex, exponential horn, folded horn, tuned port, Klipschorn labyrinth, tuned column, loaded port and multi speaker panoramics. Clear dimensioned diagrams included.

205

\$3.50

PRACTICAL ELECTRONIC SCIENCE PROJECTS

Unusual projects including laser, electronic gas detector, ultra high voltage generator, digital clock, reaction timer, geiger monitor, ultrasonic receiver and transmitter, electroscope etc.

207

\$2.75

DIODE CHARACTERISTICS, EQUIVALENTS & SUBSTITUTES

Includes signal, zener, rectifier diodes etc. Full interchangeability data and characteristics of thousands of diodes of all types with every possible alternative. Includes UK, USA, European, Russian, and Far Eastern devices.

211

\$4.60

ELECTRONIC CIRCUITS FOR MODEL RAILWAYS

Constructional details of a simple model train controller; a controller with simulated inertia, a high-power controller, an electronic steam whistle and a 'chuff generator'. Signal systems and train lighting and RF suppression also covered.

213

\$3.65

BUILD YOUR OWN ELECTRONIC EXPERIMENTER'S LAB USING ICs.

Includes many circuits and designs for constructing test and measuring instruments mostly using modern ICs. Includes AF osc, TTL pulse detector, hi-impedance Vm, square-wave osc/pulse gen, logic probe, lo-range ohmmeter, bridge, signal tracer etc.

218

\$3.10

BUILD YOUR OWN HI-FI & AUDIO ACCESSORIES

Essential for keen hi-fi & audio enthusiasts. Projects include stereo decoder, three channel mixer, FET pre-amp for ceramic p.u.s, mic pre-amp with adj. bass, stereo dynamic noise limiter, loudspeaker protector, voice operated relay etc.

220

\$3.10

28 TESTED TRANSISTOR PROJECTS

Some circuits are new, others are familiar designs. Projects can be split and/or combined for specialised needs.

221

\$4.60

SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS

Design and construction of several solid-state short-wave receivers giving high level of performance yet utilising relatively few inexpensive components. See also 226.

222

\$4.60

50 PROJECTS USING CA 3130 ICs.

The CA 3130 is an advanced operational amplifier capable of higher performance than many others: circuits often need fewer ancillary components. Interesting and useful projects in five groups. Audio projects. RF projects. Test equipment. Household projects. Misc. projects

223

\$4.60

50 CMOS IC PROJECTS

Many interesting and useful projects — multivibrators; amplifiers and oscillators; trigger devices; special devices.

224

\$4.60

PRACTICAL INTRO TO DIGITAL ICs

Introduction to digital ICs (mainly TTL 7400). Besides simple projects, includes logic test set to identify and test digital ICs. Also includes digital counter-timer.

225

\$4.60

direct from ETI

HOW TO BUILD ADVANCED SHORTWAVE RECEIVERS

Full practical constructional details of receivers with performance equal to commercial units. Also 'add-on' circuits of Q meter, S meter, noise limiter etc.
226 \$4.60

BEGINNERS' GUIDE TO BUILDING ELECTRONIC PROJECTS

Enables total beginners to tackle electronic projects. Includes component identification, tools, soldering, building methods, cases, legends etc etc. Practical basic projects are included.
227 \$4.60

ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST

This book supplies hobbyists with background knowledge, tailored for his or her specific requirements and presented in a readable manner with minimum maths. Purpose-designed examples illustrate applications.
228 \$4.60

1ST BOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES

Complete transistor equivalents. Plus 25 000 transistors with alternatives and equivalents. Covers devices from UK, USA, Germany, France, Europe, Hong Kong etc. See also 211 and BP14.
BP1 \$2.25

HANDBOOK OF RADIO, TV, INDUSTRIAL & TRANSMITTING TUBE & VALVE EQUIVALENTS

Equivalents book for amateurs and serviceman. More than 18 000 old and new valves from UK, USA, Europe, Japan et al. CV (military) listings with commercial equivalents included.
BP2 \$2.25

2ND BOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES

Data on devices not included in BP1. This book supplements BP1, i.e. no data is duplicated.
BP14 \$4.05

52 PROJECTS USING IC 741

A must for those interested in any way in this inexpensive and versatile IC. European best seller!
BP24 \$3.50

ELECTRONIC CALCULATOR USERS' HANDBOOK

Invaluable for all calculator users. Presents formulae, data, methods of calculation, conversion factors etc, often with examples. Includes way to use simple calculator for trig functions (sin, cos, tan); hyperbolic functions (sinh, cosh, tanh); logs; square roots, and powers.
BP33 \$4.60

50 CIRCUITS USING GERMANIUM, SILICON & ZENER DIODES

Contains 50 interesting and useful circuits and applications in many different branches of electronics.
BP36 \$2.75

50 PROJECTS USING RELAYS, SCRs & TRIACS

Relays, SCRs and Triacs are used in motor speed control, dimming, heating, timers, light sensitive devices, warning circuits, light modulators, priority indicators, circuit breakers etc. Book gives tried and proven circuits allowing easy modification to suit special needs.
BP37 \$4.60

DIGITAL ICs & PIN CONNECTIONS

Equivalents and pin connections of popular user-orientated digital ICs. Details of packaging, families, functions, manufacturer, and countries of origin. Includes Fairchild, Ferranti, Harris, ITT, Motorola, National, Philips, RCA, Signetics, Sescocem, SGS-Ates, Siemens, SSSI, Stewart Warner, AEG-Telefunken, Texas, Teledyne. Companion volume to BP41.
BP40 \$9.00

LINEAR IC EQUIVALENTS & PIN CONNECTIONS

Similar to BP40 but deals with linear ICs.
BP41 \$10.00

HOW TO MAKE WALKIE-TALKIES

Practical circuitry and construction of transmitters, receivers and antennas. A book of great interest to the licenced operator especially. This book was written with the UK licencing regulations in mind. Some parts may not accord with local regulations.
BP43 \$5.50

IC555 PROJECTS

One wonders how life went on before the 555! Included are basic and general circuits, motor car and model railway circuits, alarms and noise makers plus section on subsequent 556, 558 and 559s.
BP44 \$6.45

PROJECTS IN OPTO-ELECTRONICS

Included are simple circuits using LEDs as well as sophisticated designs such as infra-red transmitters & receivers, modulated light transmission and photo projects.
BP45 \$4.95

LM 3900 IC PROJECTS

Unlike conventional op-amps, the LM 3900 can be used for all the usual applications as well as many new ones. It's one of the most versatile, freely obtainable and inexpensive devices around. This book provides the groundwork for simple and advanced uses — it's much more than a collection of projects. Very thoroughly recommended.
BP50 \$4.95

ELECTRONIC MUSIC & TAPE RECORDING

Shows how electronic music can be made at home with simple and inexpensive equipment. Describes how sounds are created and recorded to build up final compositions. Includes how to build a small studio including mixer and effects units
BP51 \$4.60

LONG DISTANCE TV RECEPTION (TV-DX).

Written by UK authority, the book includes many units and devices made by active enthusiasts. A practical and authoritative intro to this unusual aspect of electronics.
BP52 \$4.60

PRACTICAL ELECTRONIC CALCULATIONS & FORMULAE

For the practical person's workbench. Bridges gap between technical theory and cut-and-dried methods which work but leave the experimenter unfulfilled. There's a strong practical bias. Tedious and higher maths avoided where possible. Many tables included. This one's a beauty!
BP53 \$8.25

ELECTRONIC SECURITY DEVICES

Simple and also sophisticated alarms using light, infra-red and sonics; also gas and smoke detectors, flood alarms, doorphone and baby alarms etc.
BP56 \$5.35

HOW TO BUILD YOUR OWN SOLID-STATE OSCILLOSCOPE

Project divided into sections for builder individually to construct and test — then assemble into complete instrument. Includes short section on 'scope usage.
BP57 \$5.50

50 CIRCUITS USING 7400 SERIES ICs

7400 ICs are freely obtainable, inexpensive and very versatile. Here's 50 interesting and useful circuits using this IC.
BP58 \$4.95

Babani Books

PRACTICAL CONSTRUCTION OF PRE-AMPS, TONE CONTROLS, FILTERS, & ATTENUATORS

How to construct a variety of magnetic tape recording, microphone, and disc pre-amps; plus tone controls, rumble & scratch filters, attenuators and pads etc etc.

BP60

\$5.30

BEGINNERS' GUIDE TO DIGITAL ELECTRONICS

Covers all essential areas including number systems, codes, constructional and sequential logic, analog/digital/analog conversion.

BP61

\$3.50

BEGINNERS' GUIDE TO MICROPROCESSORS & COMPUTING

Introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. Only prior knowledge assumed is very basic arithmetic and an understanding of indices.

BP66

\$6.40

ELECTRONIC GAMES

How to build many interesting electronic games using modern ICs. Covers both simple and complex circuits for beginner and advanced builder alike. Good one!

BP69

\$6.40

A MICROPROCESSOR PRIMER

This small book takes the mystery out of microprocessors. It starts with a design for a simple computer described in language easy to learn and follow. The shortcomings of this basic machine are then discussed and the reader is shown how these are overcome by changes to the instruction set. Relative addressing, index registers follow as logical progressions. An interesting and unusual approach.

BP72

\$6.40

REMOTE CONTROL PROJECTS

Covers radio, infra-red, visible light, ultrasonic controls. Full explanations are provided so that the reader can adapt the projects for domestic and industrial as well as model use.

BP73

\$7.15

ELECTRONIC TEST EQUIPMENT CONSTRUCTION

Describes construction of wide range of test gear including FET amplified voltmeter, resistance bridge, field strength indicator, heterodyne frequency meter etc.

BP75

\$6.40

POWER SUPPLY PROJECTS

Designs for many power supplies including simple unregulated, fixed and variable voltage regulators — particularly for electronics workshops. Also included are cassette power supply, Ni-Cad charger, voltage step-up circuit, and simple inverter, plus info on designing your own supply. All designs are low voltage types for semiconductor circuits.

BP76

\$6.40

RADIO CONTROL FOR BEGINNERS

How complete systems work with constructional details of solid state transmitters and receivers. Also included — antennas, field strength meter, crystal controlled superhet, electro-mechanical controls. Ideal for beginners. Section dealing with licensing etc not applicable to Australia.

BP79

\$6.40

POPULAR ELECTRONIC CIRCUITS — BOOK 1.

Yet more circuits from Mr. Penfold! Includes audio, radio, test gear, music projects, household projects and many more. An extremely useful book for all hobbyists offering remarkable value for the designs it contains.

BP80

\$7.15

ELEMENTS OF ELECTRONICS

This series provides an inexpensive intro to modern electronics. Although written for readers with no more than basic arithmetic skills, maths is not avoided — all the maths is taught as the reader progresses.

The course concentrates on the understanding of concepts central to electronics, rather than continually digressing over the whole field. Once the fundamentals are learned the workings of most other things are soon revealed. The author anticipates where difficulties lie and guides the reader through them.

BOOK 1 (BP62): All fundamental theory necessary to full understanding of simple electronic circuits and components.

BOOK 2 (BP63): Alternating current theory.

BOOK 3 (BP64): Semiconductor technology leading to transistors and ICs.

BOOK 4 (BP77): Microprocessing systems and circuits.

BOOK 5 (BP89): Communications.

This series constitutes a complete inexpensive electronics course of inestimable value in hobby or career.

Books 1/2/3

\$8.25 (each)

Books 4/5

\$10.80 (each)

ORDER FORM

Please forward

Book	Qty	BP1	...	BP50	...	BP69	...
205	...	BP2	...	BP51	...	BP70	...
207	...	BP14	...	BP52	...	BP72	...
211	...	BP23	...	BP53	...	BP73	...
213	...	BP24	...	BP55	...	BP75	...
218	...	BP27	...	BP56	...	BP76	...
220	...	BP33	...	BP57	...	BP77	...
221	...	BP36	...	BP58	...	BP78	...
222	...	BP37	...	BP60	...	BP79	...
223	...	BP38	...	BP61	...	BP80	...
224	...	BP40	...	BP62	...	BP82	...
225	...	BP41	...	BP63	...	BP86	...
226	...	BP43	...	BP64	...	BP87	...
227	...	BP44	...	BP66	...	BP88	...
228	...	BP45	...	BP67	...	BP89	...

PLEASE NOTE: Following titles being reprinted.

Delivery expected within six weeks ... 160, 202, BP39.

Trade enquiries welcomed

Send to: ETI 'Book Sales', 4th Floor,

15 Boundary St, Rushcutters Bay NSW 2011.

Please allow 4 - 5 weeks for delivery.

Post & handling:

1 - 4 books:	\$1.35	11 - 20 books:	\$3.50
5 - 10 books:	\$2.70	over 20 books:	\$5.00

I enclose \$ (inc. p & h.)

Name

Address

..... postcode

Limited Quantity
- Be Quick

AMAZING BOO-BOO

A manufacturer's
mistake means we
can sacrifice these
incredible CRAIG
language translators
at a staggering

**OVER
80% OFF!**
WAY
BELOW
COST

90 DAY WARRANTY

THE CRAIG M100

This unit sold in
Australia for \$250 and
over 200,000 were sold
world wide at similar
prices. The manufacturer
made too
many
and
we
have
scooped
a limited
quantity at WAY
BELOW the
manufacturer's cost!

**WAY BELOW
COST**

SAVE \$180

Normally over \$250!

NOW \$69.50

Cat. Y-1340

Includes
English
Cartridge

**YOU REAP
THE BENEFIT**

How would YOU like to be able to convey
your thoughts, needs and questions in
another language? Well now you can! The
CRAIG M100 enables you to type in a
message and at the touch of a button
translate that message into another language.
It even has whole phrases that can be
called up at the touch of a button and
partial phrases to which you can add your
own ending. A truly remarkable unit that
can calculate (e.g. currency conversions)
and it has inbuilt metric conversions, a
great boon! The Craig M100, a true hand-
held language computer with RAM, ROM
and CPU! Ideal for businessmen on over-
seas trips, students studying languages
etc.

It is recommended that you use 4
Duracells (Cat. S-3280) at \$2.78 or 4
NiCads (Cat. S-3300) at \$2.05 each. If
using the NiCads they can be re-
charged in the Craig M100 by using
the M-9525 battery eliminator which
also serves to power the unit from the
AC. The M-9525 is great value at
\$6.90.

LANGUAGE CARTRIDGES

French (Y-1341):
Japanese (Y-1342):
German (Y-1343):
Italian (Y-1344):
Bar & Wine Guide
(Y-1345) and Calorie
Counter (Y-1346).

**SAVE
60%**

Normally \$35 ea.
ALL AT \$12 ea.

**7 DAY SATISFACTION
GUARANTEE
TRY ONE AND SEE!**


If you are not totally satisfied return the
unit in the same condition as received and
your money will be refunded.

DICK SMITH ELECTRONICS



See our other advertisements
in this publication for a full
list of store addresses, phone
numbers and post details.

TCT S100 PROM

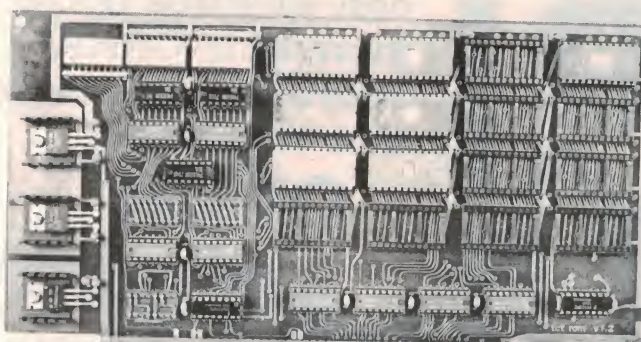


From March 1981 ETI, this is the new S100 ETI-682 PROM board. This feature packed board may be used with no less than four PROM types: the 2708 2758, 2716 (+5V) and 2732. This means the board will not become redundant as PROM prices fall and the 2732 becomes popular.

The board has two banks of eight PROMs each, located on 4K boundaries. Features on this board include:

- * Different PROMs may be used in each bank
- * Dipswitches disable unused PROM sockets
- * Supports phantom and bank select
- * Inserts wait states for slow PROMs

Blank board with manual	\$ 69
Complete kit with manual	\$115

TCT S100 Dynamic

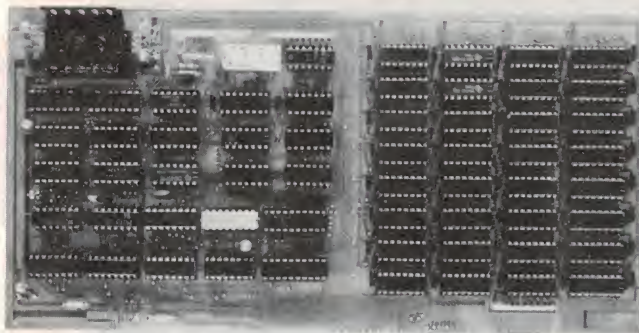

FEATURES:

- * Designed for the S100 bus
- * Expandable from 16 to 64K
- * Does not need halt, wait and reset status signals from bus
- * Optimal arbitration between refreshes and memory accesses
- * All timing derived from 25MHz clock
- * Will run at any speed from zero to 2.5MHz (Z80)
- * Arranged as four 16K banks, with independent write protect and disable
- * Supports bank select and phantom
- * Genuine S100 board size, 5.3 by 10.0 inches
- * High quality solder masked and plated through board
- * Excellent manual, including construction and setting up details and a discussion of testing and memory design techniques.

Unlike most other dynamic boards our's does not use the PSYNC, PWAIT, PHOLD, SM1, RESET, phi 2 and HALTA signals from the bus. Our board uses only one more control signal than most static boards. This means it is easier to interface to virtually any system. We have extensively tested our dynamic board with the DGZ80, Base 2, Jade, Cromenco and SD100 CPU cards. The TCT dynamic board is being used with Versafloppy, Micropolis and Tarbell floppy disk controllers.

KIT PRICES:

	inc. tax	ex. tax
16K bytes	\$279	\$245
32K bytes	\$349	\$305
48K bytes	\$419	\$365
64K bytes	\$489	\$425
8x4116 (200ns)	\$75	\$66

Add \$60 for assembled and tested.

OEM enquires welcome.

Post and packing charges:
\$10 for overnight delivery by courier
\$3 for delivery by post

Allow two weeks for delivery, we will immediately inform of any unexpected delays.

All prices include 15% sales tax

T.C.T. MICRO DESIGN PTY. LTD.
Engineering excellence
P.O. Box 263 Wahroonga, 2076, N.S.W.
Phone (02) 48-5388 A.H.

COMPONENT USERS.

**PHONE YOUR
SEMICONDUCTOR,
RESISTOR &
CAPACITOR ORDERS**

**TO US
BY**
2pm

**IN BRISBANE,
MELBOURNE & SYDNEY
& WE DELIVER
ALL EX-STOCK ITEMS
NEXT DAY.**

Using our on-line computer hook-up from sales office to warehouse, and despatching by Skyroad you get the goods next day.
We stock over 7,000 line items of semiconductors, capacitors and resistors from Motorola, Texas Instruments, Philips and Hewlett Packard.
Try us for service on the widest component range at competitive prices.



**VSI
ELECTRONICS
(AUSTRALIA)
PTY LTD**

THE DISTRIBUTOR OFFERING SOMETHING UNIQUE...SERVICE
Adelaide 51 6483 • Brisbane 52 4261 • Melbourne 877 5311 • Perth 328 8091 • Sydney 439 8622

Lab Notes

Gate, square, sine, modulate — with the 555 & 7555.

Ray Marston

The ubiquitous 555 timer chip, or its modern CMOS counterpart the 7555, can be readily used as a highly stable and cost-effective astable multivibrator. Although often used just as a square wave generator, they're capable of performing some fairly fancy tricks.

THE OLD-FASHIONED 555 IC should be a fairly familiar component to the average hobbyist. It's the 'universal' square wave generator, pulser, gate and timer. But really, it's much more than that if you employ a little ingenuity in circuit design. The modern CMOS version, the 7555, is even more versatile than its predecessor. Apart from a wide variety of gating functions, the 555/7555 can perform tricks like ramp and sine waveform generation.

Astable gate

The 555/7555 astable can be gated on

and off in a variety of ways, to produce different output waveforms. Figure 1 shows the basic connections and the equivalent circuit of the standard 555/7555 astable. It is necessary to understand the operation of this basic circuit in order to appreciate the action of the various gating methods. In the following discussions, a 12 V supply rail is assumed in all circuits.

The first point to note about the Figure 1 equivalent circuit is that the IC contains a three-resistor potential divider, two voltage comparators, a flip-flop, a transistor and an output buffer.

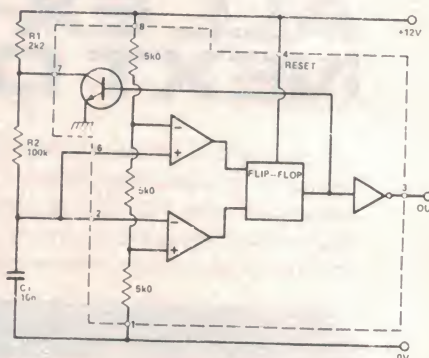


Figure 1b. Equivalent circuit of the 555-type astable multivibrator.

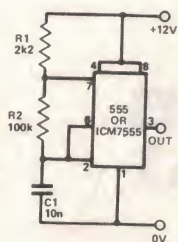


Figure 1a. Basic circuit of the 555-type astable multivibrator.

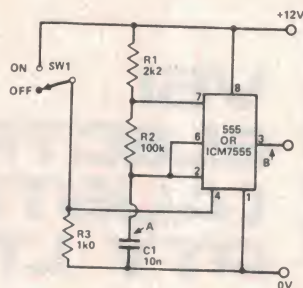


Figure 2. Conventional way of gating the 555 astable, with resultant waveforms.

The divider ratios are such that one-third of the supply voltage (i.e: 4 V) is set on the lower comparator and two-thirds of the supply voltage (i.e: 8 V) is set on the upper comparator. The circuit action is such that, in each operating cycle, C1 first charges up to 8 V through R1-R2, at which point the upper comparator activates the flip-flop and turns

biased and the astable operates in the normal way, but when the circuit is gated off D1 shorts out C1 and pulls point A to ground; in practice, of course, SW1 can be replaced by an electronic switching waveform (the output of a CMOS gate, etc). Note in this circuit that, when the astable is gated on, the first half cycle is again considerably

that of the succeeding half cycles. This is achieved by choosing the R3-R4 values so that the voltage across C1 is only a fraction below 4 V (one-third of supply volts) during the off condition. A substantially different set of waveforms can be obtained by choosing the R3-R4 values so that the voltage across C1 is a fraction below 8 V (two-thirds of supply

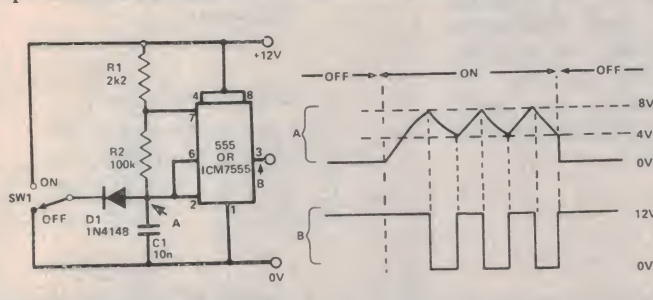


Figure 3. Basic method of gating the 555 astable using C1, with resultant waveforms. Note that the period of the first half-cycle is longer than that of the succeeding half-cycles.

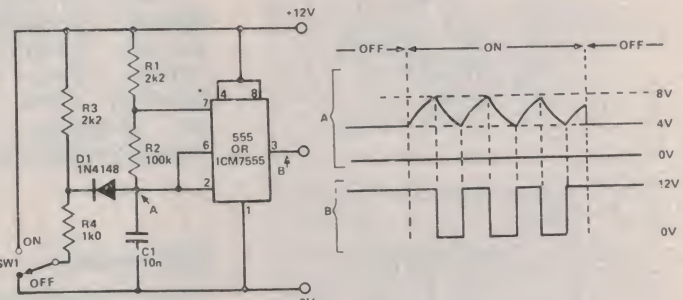


Figure 4. Modification of the C1 gating scheme, giving constant-period half-cycles.

the internal transistor on; the transistor then discharges C1 through R2 until the C1 voltage falls to 4 V, at which point the lower comparator activates the flip-flop and turns the internal transistor off, causing C1 to recharge through R1-R2. The operating cycle is then complete and repeats ad infinitum. A ramp waveform with an amplitude that swings between 4 V and 8 V is generated across C1 and a rectangular waveform is generated at the output, pin 3.

The conventional way of gating the 555/7555 astable is with the pin 4 reset terminal, as shown in Figure 2. When this pin is pulled to ground (by a 1k resistor), the flip-flop output is driven high, thus discharging C1 through R2 and the transistor and also driving the output (pin 3) low. The resulting circuit waveforms are shown in the diagram. Note that, when the astable is gated on, the first half cycle is considerably longer than the succeeding half cycles. Also note that, when the astable is first gated off, the voltage across C1 takes a substantial time to decay to zero. The output is zero during the off condition.

Alternative methods

One alternative method of gating the 555/7555 is shown in Figure 3. Here, when the circuit is gated on, D1 is back-

longer than the succeeding half cycles, but that the C1 voltage falls abruptly to zero at gate-off. Also note that the output is high in the off state, here.

Figure 4 shows how the above circuit can be modified so that the duration of the first half cycle is almost equal to

volts) during the off condition, as shown in Figure 5.

It should be appreciated that the 555/7555 astable can only oscillate if its timing capacitor (C1) is free to swing between the 4 V and 8 V switching levels. This simple fact makes it

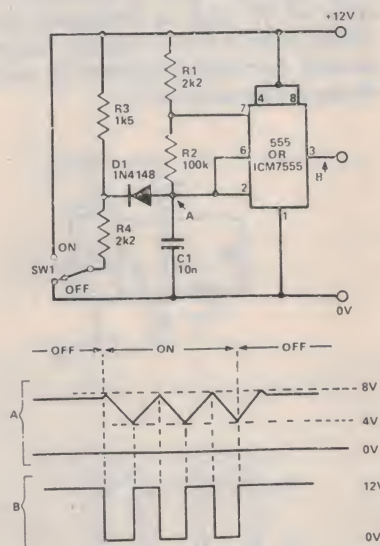


Figure 5. This slight modification of the C1 gating scheme produces a considerable change in the circuit output waveforms.

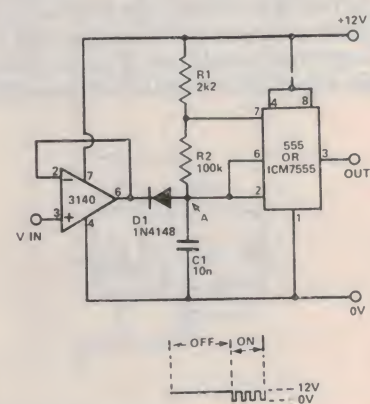


Figure 6. The voltage-controlled astable produces an output only when V_{in} exceeds two-thirds supply (8 V in this example).

possible to voltage-gate the astable by using the circuit of Figure 6. Here, the circuit produces output waveforms only when the input voltage exceeds 8 V. The circuit can be made to trigger at other levels by giving the op-amp an appropriate voltage gain factor.

Lab Notes

Finally, an alternative method of gating the 555/7555 astable is shown in Figure 7. Here, the circuit is gated off by driving the voltage across C1 above 8 V by D1. A feature of this circuit is that its 'B' output is low in the off condition.

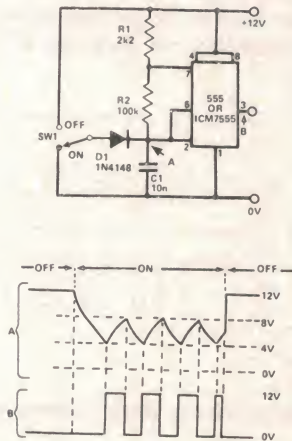


Figure 7. This C1 gating scheme produces a 'B' output that is low in the off condition.

Asymmetrical astables

The basic 555/7555 astable generates near-symmetrical output waveforms, provided that R2 is large relative to R1 (giving near-equal C1 charge and discharge time constants). Figures 8 to 10 show alternative methods of generating

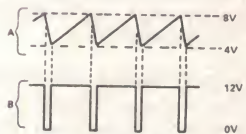
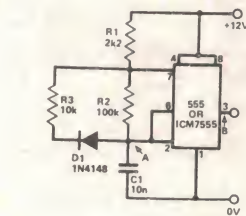


Figure 8. A method of producing a non-symmetrical fixed ratio output from the 555 astable.

non-symmetrical waveforms. In Figure 8, C1 charges through R1-R2 but discharges through R2 in parallel with R3-D1, to produce the waveforms shown. In Figure 9, C1 charges through R1 and R2 in parallel with R3-D1, but discharges through R2 only; this circuit is useful for providing narrow output pulses at the 'B' terminal.

Finally, in Figure 10, C1 charges through R1-R3-D2 and discharges through D1-RV1-R1-R2, to produce narrow output pulses at the 'B' terminal. This circuit is useful for generating variable-frequency constant-width pulses.

Sine waves

Figure 11 shows how a sine wave signal can be obtained from a 555/7555 astable. Here, the symmetrical ramp waveform of C2 is buffered by Q1 and then ac coupled to the R1-R2-D1-D2 divider/limiter network. This network attenuates the ramp signal and then non-linearly removes the ramp's positive and negative peaks, to produce a sine-shaped waveform of about 1 V peak-to-peak amplitude at the output terminal. The distortion level of the resulting sine wave is typically of the order of 3% and its frequency can be varied from a few cycles per minute to several hundred kilohertz by suitable choice of the value of C2.

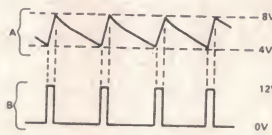
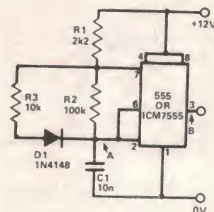


Figure 9. Alternative method of producing a non-symmetrical fixed ratio output from the 555 astable.

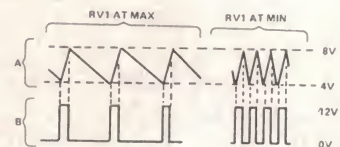
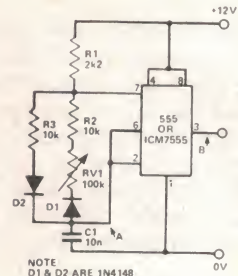


Figure 10. A method of producing a non-symmetrical variable ratio output from the 555 astable.

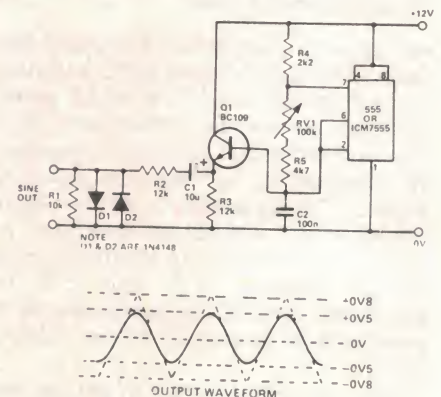


Figure 11. A 555 sine wave generator with a range of 83 Hz to 1.4 kHz (via R1).

AM output

Figure 12 shows how the pin 3 square wave output of the 555/7555 astable can be amplitude-modulated to produce the typical attack-hold-decay envelope of a simple musical instrument or of a special-effects sound generator. The heart of the unit is the diode AND gate, or mixer, formed by D1-D2-R5. One input of this gate is fed from the output of the astable via R3-R4 and the other from across R6. The basic action of this gate is such that (ignoring the diode volt drops) its output amplitude is equal to the lesser of the two inputs.

Thus, when D1 is fed with the square wave output of the astable, the peak output of the unit will be zero when the voltage across R6 is zero, or 5 V when the voltage across R6 is 5 V, etc. In our circuit, R6 is shunted by electrolytic capacitor C2. Thus, when PB1 is pressed, a large voltage is applied to R6 and a large-amplitude square wave output is available. When PB1 is released, the voltage across R6 and the square wave output amplitude decay exponentially to zero (with a time constant of R6-C2), as shown in the diagram. The R3-R4 network is used to apply a slight offset bias to the rectangular input waveform, to ensure a full cut-off of the output waveform after PB1 is released.

Finally, Figure 13 shows how the above circuit can be modified to give extended delay times (via emitter follower Q1) and a buffered audio output (via emitter follower Q2).

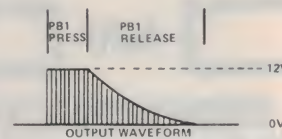
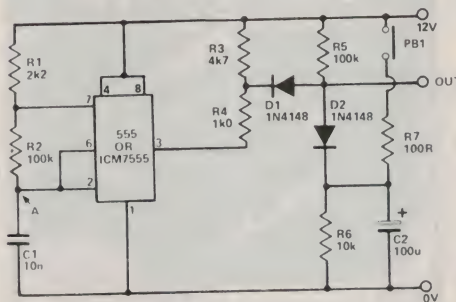


Figure 12. A method of amplitude-modulating the pin 3 output off the 555 astable in music and sound generator applications.

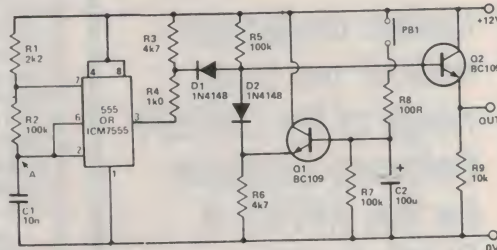


Figure 13. A modification of the Figure 12 circuit to give extended decay times and a buffered output.

**THIS IS
FREE...**



**WITH EVERY
PURCHASE OF THIS**



This Audio Technica light weight headshell is free! In this special offer for mail order purchase only, each Audio Technica AT 11 E cartridge with elliptical stylus is supplied with headshell, AT NO EXTRA COST. All you pay is the regular price of the Audio Technica AT 11 E cartridge at \$31.00 and you have a complete new module that you can simply plug in to your pickup arm. You can discard your old cartridge or keep it as a spare ALL for the price of the cartridge alone.

MAIL YOUR ORDER NOW FOR THE AUDIO TECHNICA 11 E CARTRIDGE AND RECEIVE AS WELL, THE AUDIO TECHNICA UNIVERSAL PLUG-IN HEADSHELL.
THE PRICE \$31.00 MAIL ORDER ONLY

BEST BUYS! CASSETTES, CARTRIDGES, HEADPHONES

Hitachi LN C 60.....\$16.00 pack of 12
Hitachi LN C 90.....\$22.00 pack of 12
Hitachi UDC 60.....\$28.00 pack of 12
Hitachi UDC 90.....\$36.00 pack of 12
Maxell UDC 60.....\$29.00 pack of 12
Maxell UDC 90.....\$37.50 pack of 12

Memorex 8 track 90 min cartridge
(a hard to get item).....pack of 5 \$20
Memorex 8 track headcleaner
cartridges.....\$7.00 ea.
Akai 8 track head
demagnetizer.....\$10.00 ea.

Akai XSE stereo monitoring headphones
C/W Din plug.....\$11.00 a pair
Audio Technica ATH 1 stereo
headphones.....\$32.00 a pair
Raimar stereophones. Top quality, light-
weight. HP44.....\$13.90 a pair

FOR IMMEDIATE DELIVERY OF ANY ITEM, POST YOUR CHEQUE OR MONEY ORDER NOW TO:

M5 MAIL
ORDER
SERVICE

P.O. BOX 345, ARTARMON
2064 N.S.W. Ph (02) 428-3623

GOODS AVAILABLE BY MAIL ORDER ONLY.
All items offered are covered by
manufacturers regular warranty.

COMPUTER COUNTRY PTY LTD

338 QUEEN STREET
MELBOURNE, VIC. 3000
PHONE (03) 329-7533

AND

COMPUTER CITY
600 OLD CLEVELAND ROAD
CAMP HILL (BRISBANE)
QLD. 4000
PHONE (07) 398-6433

Invites inspection
now of our huge
range of the LATEST
Software available
for the APPLE II
PLUS & other
microcomputers.
Names like:-
Adventure
International, Muse,
Softape,
Crystalware,
Automated
Simulations, Avalon
Hill and many others.

ALSO
Ring NOW to
enquire about our
first
NATIONAL
ADVENTURE
TOURNAMENT

AFFORDABLE INSTRUMENTATION

AIM-65, SYM-1 DISC SYSTEM




HDE: Disc system for AIM-65 and SYM-1.
Includes TEAC. (Single density single
sided for high data reliability).

FD50A drives W.D. 1771 based controller
card (KIM 4 bus compatible — plugs di-
rectly into Mother Plus II), file orientated
disc system and Text Editor software, ca-
bles and power supply.

Single Drive System.....\$799

Dual Drive System\$1089

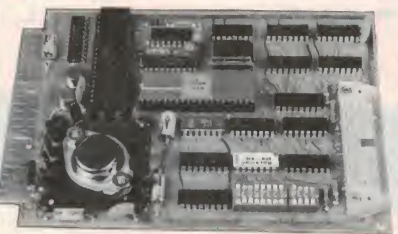Other software available: Dynamic De-
bugging Tool, Advanced Interactive Dis-
assembler, Comprehensive Memory
Test, Disc Basic.



SPECIAL

AIM 65-1K \$429 A&T
SYM-1 \$199 A&T

RAE-1/2.....\$84

BAS-1/2 (2x2332).....\$84

6x2114 for SYM, AIM.....\$19.50

4x2532 (suitable for

DRAM PLUS).....\$63.50

KTM-2.....\$289 A&T

PS1 for SYM 5V, 4A;

± 12V, 0.4A.....\$74.50 A&T

DRAM PLUS 32K RAM, 16K EPROM

SPACE, EPROM PROGRAMMER

2x6522.....\$369

SYM software for Visible Memory and
Music Synthesizer available.

AIM-65 4K, assembler and Basic...\$649

Enclosure with PS1 plus 24V.....\$149

PL 65 on ROM for AIM 65.....\$145

energy
CONTROL

P.O. BOX 6502 GOONDA 4300
PHONE (07) 288-2757
PRICES PLUS TAX IF APPLICABLE

Verbatim®



MINIDISKS

Verbatim, the world's leading
producer of minidisks, makes the
widest range of minidisks availa-
ble for word processing and data
processing applications. Intent
on maintaining this position of
leadership, we constantly strive
to make our minidisks even bet-
ter.

Each Verbatim minidisk is equip-
ped with a hub reinforcing ring to
aid in registration, reduce errors
and give better alignment re-
peatibility. Our dual-sided, dou-
ble density minidisks offer users
higher storage capacity. Our new
plastic box makes our minidisks
easier to use, safer and more
convenient to store. Our testing
standards go beyond the industry
standard because we insist on
Verbatim being the industry stan-
dard of excellence.

**Try new Verbatim disks
for the performance
of a lifetime.**

**"We play it back,
Verbatim"**

**Magnetic Media Services
Pty.Ltd.**

SYDNEY: 5 Apollo Place, Lane Cove,
NSW. 2066. Phone (02) 428-1100. Telex
AA22703.

MELBOURNE: 320 Toorak Road, South
Yarra, VIC. 3141. Phone (03) 240-8288.
Telex AA32127.

BRISBANE: 146 Leichhardt Street, Bris-
bane, QLD. 4000. Phone (07) 229-1941.
Telex AA42367.

CANBERRA: 25 Lonsdale Street, Brad-
don, ACT. 2601. Phone (062) 48-6751.
Telex AA22703.

LOOK AT THESE GREAT KITS



ALL DICK SMITH KITS FEATURE:

- Quality components. . .
- Full, easy to follow instructions. .
- Competitive price. . .

WHY
SETTLE FOR
LESS!

NEW KITS FOR MAY UHF TV Downconverter KIT

UHF TV is here: but only a small percentage of TV's are fitted with UHF tuners. Use any standard VHF TV set with this converter: use for a single channel or make it tuneable.

Cat. K-3235 **\$32⁵⁰**
SEE ETI MAY

UNIVERSAL RELAY DRIVER

SEE ETI MAY

(Printed Circuit Board Only)

How many times have you wanted to control mains, etc, but haven't known how to? This simple interfacing project shows you how to: suits most applications.

Cat. H-8638 **\$3⁹⁵**

HOT CANARY (short form)

SEE EA MAY

A gimmick that will keep any child amused for hours! An electronic bird whistle that sounds just like the real thing.

Cat. **\$14⁹⁵**
K-3395

SPEED SENTRY (short form)

SEE EA MAY

For safer driving. An alarm sounds if you go over a pre-set speed. You set the speed.

Cat. **\$11⁷⁵**
K-3245

INFRA RED REMOTE CONTROL

Control any mains operated (or other) device from across the room. Now you can turn the TV off from your chair - or turn the stereo on.

Cat. K-3380 **\$63⁹⁵**
SEE EA MAY


dB METER

Troubled by noise? Worried about exceeding noise pollution laws? Build this simple dB meter and find out. Easy to build, save \$\$\$ on commercial units.

Easy to build.

Cat. K-3476 **\$34⁵⁰**
SEE EA MAY

CORE BALANCE RELAY

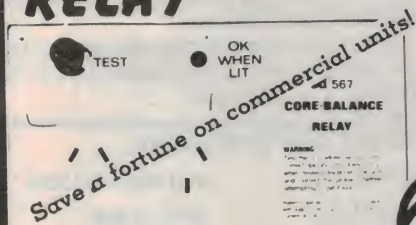

Includes pre-wound coil

This one should be in every hobbyists workshop - it could save your life! Senses any leakage to earth from a mains appliance (e.g. through your body) and shuts off power before it has a chance to electrocute you.

SEE ETI APRIL

\$49⁵⁰

Cat. K-3315

INFRA RED BEAM RELAY

Ideal burglar alarm, door minder, etc. Sounds alarm if beam is cut. Also fantastic for wildlife photography.

SEE EA APRIL



Cat. K-3375

\$37⁵⁰

Improve your health NEGATIVE ION GENERATOR

Completely safe - battery or plug-pack operated. With an incredibly well researched article showing how beneficial negative ions can be!

\$41⁹⁵ Cat. K-3335
SEE ETI APRIL

SERIAL INTERFACE

(For System 80)

Enables your System 80 or TRS-80 computer be used with many of the serial-type devices: teleprinters, etc. A must for the hobbyist buff: gives you the chance to use ex-disposals gear.

Cat. K-3608 **\$57⁵⁰**
SEE EA APRIL

DICK SMITH ELECTRONICS



See our other advertisements in this publication for addresses, phone numbers, post and packing etc.

Ideas for Experimenters

These pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details.

ERRATA

A rather obvious, but potentially dangerous error occurred in the circuit on the top left of page 60 ('Power Monitor') in the March issue. It shows the mains active input connected to the earth at the output. The mains active input should instead go to the fuse. Correct your copy now. Correction slips were inserted in the majority of copies distributed.

Simple anemometer


Having managed to pronounce the heading (an-ee-mom-meter), no doubt you're wondering what it is. It's a wind speed indicator.

The idea comes from 14-year-old Wayne Brown of Dromana in Victoria. Make up an anemometer rotor and attach two small magnets to a mounting on the bottom. A reed switch is then placed under this assembly such that the two magnets operate the reed switch twice per revolution of the rotor shaft.

The reed switch gates on and off a 555, the output of which is rectified and integrated to drive a meter (M1). You can use a meter having a sensitivity up to 150 microamps, but the resistor in series with the 1N914 will have to be selected to suit.

To calibrate it, you will need:
one daring passenger
one car
plenty of road
no radar traps.

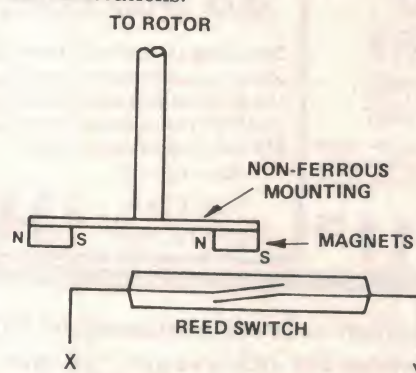With the anemometer's rotor held outside the vehicle (clamped to a roof rack, for example), drive at a variety of speeds for a short distance at each speed. The passenger can then mark down the meter reading against the car's speed so that the meter scale can be later marked with the calibrations.



The ETI-480 amp module — barefoot and bridged.

For many years now, constructors have built the ever-reliable ETI-480 power amp and many people in the industry have used this design in many different ways. Some other variations that have been tried from time to time are listed in the table here, compiled by G.T. Dicker of Parkholme, S.A.

One of the most useful ways to utilise the ETI-480 is by bridging the output stage for increased power into higher load impedances.

This may be done with the 2N3055/2N2955 output stage combination or by utilising the MJ802/MJ4502 or

MJ15004/MJ15003 type transistors in their place.

To bridge two modules, one must first get the modules working to specification, then add a 10k, ½W resistor from the junction of R8 and R9 on module 2 to the output stage, junction of R22 and R21 on module 1. Audio input is then provided to module 1 and output is taken from module 1 and 2 output stages. The input to module 2 may optionally be shorted but in practice makes little difference.

If you feel some of the options tabled look attractive wait and see what will be done with the ETI 466!


ETI-480 TABLE OF OUTPUT POWER FOR VARIOUS CONFIGURATIONS

Supply Voltage	3055/2955	MJ802/4502	MJ15003/MJ15004
±30 Vdc single-ended	35 W - 8 ohm 65 W - 4 ohm	35 W - 8 ohm 65 W - 4 ohm	35 W - 8 ohm 65 W - 4 ohm 100 W - 2 ohm
±45 Vdc single-ended	65 W - 8 ohm	100 W - 8 ohm 150 W - 4 ohm*	100 W - 8 ohm 190 W - 4 ohm 300 W - 2 ohm*
±30 Vdc bridge	150 W - 8 ohm* 75 W - 16 ohm	150 W - 8 ohm 75 W - 4 ohm	150 W - 8 ohm 190 W - 4 ohm
±45 Vdc	100 W - 32 ohm	190 W - 16 ohm	195 W - 16 ohm 355 W - 8 ohm*

*NOTES: Not recommended, unless for home hi-fi.

At output powers above 100 W RMS extreme heatsinking and/or forced air cooling is recommended. Not all configurations are necessarily safe for continuous output power operation.

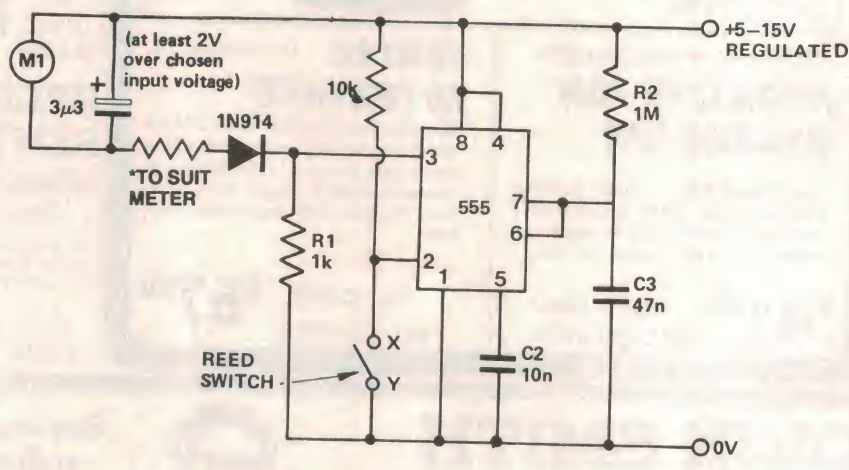When MJ802/MJ4502 or MJ15003/MJ15004 are used supply fuses F1, F2 must be changed to 5 amps.





Australia's Resistor House

"BIG SAVINGS!"

Carbon Film Resistors

$\frac{1}{4}$ watt 5% tol.

50¢

100
in 100 lots*

40¢

100
in 1000 lots*

Metal Film Resistors

$\frac{1}{4}$ watt 1% tol. 50 P.P.M.

\$2

100 in lots of
1000*

\$2.50

100 in
lots of 100*

*Plus sales tax if applicable.



VSI
ELECTRONICS
(AUSTRALIA)
PTY LTD

VSI, the distributor offering something unique — Service.

Adelaide 51 6483; Brisbane 52 4261; Melbourne 877 5311; Perth 328 8091; Sydney 439 8622

LAST CHANCE!!

LOOK AT THESE

CRAZY SAVINGS

25W 8Ω 3WAY

SPEAKER KIT SALE!
WALNUT finish, ready-made boxes, black speaker cloth.

8 WOOFER + 5 MID-RANGE + 3 TWEETER + X'OVERS
+ wire and Innerbond + screws!
PER PAIR \$69
KITS ASSEMBLED & TESTED **\$109**

Speakers Separately: 8" Woofer \$7.50 ea
5" Mid-range 500Hz-12KHz \$5.95 ea
3" Tweeter 5KHz-18KHz \$4.50 ea

POWER SUPPLIES
INPUT: 110v to 235v 50Hz
OUTPUTS: +5v 15A, -12v 8A,
+24v 8A, +26v 4A, -26v 4A.
Very low ripple, circuit
breakers on all outputs, **\$50 EA.**
size approx 300x330x37mm

PLUS LOTS MORE!

• 3-100 PIV 35A RECTIFIERS ON 4"x2" HEATSINK only **\$6**
• ASST. TO-3 POWER TRANSISTORS, Some Germanium, Some Silicon **25c**
• 5-3055 EQUIV. ON 6"x4" HEATSINKS Great for 10A-15Amps **\$10**
• SUPPRESS SPIKES, INTERFERENCE, ETC.
• ALSO RECT. AND SCR'S TO 100AMPS, RELAYS AND CIRCUIT BREAKERS, TRANSFORMERS AND CHOKES, MOTORS, PCB'S, ETC. ETC.

600PIV 25AMP RECTIFIERS
by International Rectifier
Automotive, Industrial.
45c EA

3055's
10 FOR \$4.99

OR YOU CAN BUY AT 69c EACH.
New, full specifications, only 3,000 avail.

NEW MINIATURE LAMPS
LOW VOLTAGE
5v 20mA
6v 60mA
12v 40mA
14v 80mA
24v 30mA
28v 40mA
50c EA
TAKE YOUR PICK!
ACTUAL SIZE

BUY 10+ 40c EA OR 100+33c
LONG LIFE, DEPENDABLE, SMALL SIZE 13mm

TRANSFORMERS
MAINS 120v PRIM.
12-0-12 VOLT
500mA Secondary
MAIL PER PAIR
ORDERS \$1 extra P/P
2 for \$3.95
Series primaries for 240v use!

- 20 Triapots 1K OR 2K OR 5K OR 10K OR 25K.....\$1
- 10 Multiturn cermet triapots, assorted values.....\$1
- 3 metres 3 core mains cable grey.....\$1
- 1 Mono turnover phono cartridge, Xtal.....\$1
- 2 LED red bezels 2.2V.....\$1
- 1 mini m.o. reed switch + 12V coil.....\$1
- 2 In-line std 3AG plastic fuseholders.....\$1
- 2 1A 200 PIV silicon bridge rectifiers.....\$1
- 2 2N6027 PWT transistors.....\$1
- 2 2N5459 (MPF105) FET transistor.....\$1
- 4 Insulated terminals, 2 red, 2 black.....\$1
- 10 mini crocodile clips, 5 red, 5 black.....\$1
- 1 48v mini PCB atg, high speed relay.....\$1
- 2 470pf OR .0047uf OR .047uf ceramic caps.....\$1
- 25 .001uf OR .1uf ceramic capacitors.....\$1
- 10 .001uf OR .0022uf feedthrough capacitors.....\$1
- 4 1uf OR 2uf speaker X'over capacitors.....\$1
- 3 WAF ferrite balun for RF transformers.....\$1
- 4 4-20pf or 6-30pf trimmer capacitors.....\$1
- 1 100pf air-spaced ceramic trimmer capacitor.....\$1
- 50 3/4" plastic knob-spacers, pot washers, etc.....\$1
- 5 7pin or 9pin PCB valve sockets.....\$1
- 1 7M-1000 OR GR-911 0-9 nixie tube.....\$1
- 10 82X79 22v zener diodes 350uA.....\$1
- 1 DC filter choke for power supplies 1A.....\$1
- 4 linear pots 500 OR 1K OR 2.5K OR 10K OR 100K.....\$1
- 4 log pots 25K OR 50K OR 1M ohms.....\$1

Great value buys!
HIGH OUTPUT BUZZERS
6v 12v 30v
9v 12v \$2 ea
EACH

- 200 1W resistor assortment.....\$2
- 250 1/2, 1W resistor assortment.....\$2
- 500 1W resistor assortment.....\$2
- 50 1/2 precision resistors.....\$2
- 100 assorted ceramic capacitors.....\$2
- 50 assorted mica 2.5K hi-stab capacitors.....\$2
- 30 various Greencaps.....\$2
- 6 assorted ferrite rods, aerials.....\$2
- 6 assorted tuning gags PVC ains.....\$2
- 20 assorted potentiometers.....\$2
- 25 assorted preset pots.....\$2
- 30 3.5, 7, 10 watt resistors.....\$2
- 40 radio/TV knobs.....\$2
- 50 assorted tagstrips.....\$2
- 45 assorted electrolytics.....\$2
- 20 RF/IF/OSC coils assorted.....\$2
- 20 assorted VOR's and instructions.....\$2
- 12 assorted switches, slider, etc.....\$2
- 15 tantalum capacitors, 3 ea. 5 values.....\$2
- 12 assorted trimmer capacitors.....\$2
- 30 assorted chokes, RF, video, etc.....\$2
- 1 CB/car stereo noise filter.....\$2
- 1 permeability tuner, 3 coils.....\$2
- 1 transistor radio repair kit.....\$2
- 1 de-soldering wick in dispenser 1 metre.....\$2
- 1 car speaker fader, dual 250ha pot.....\$2
- 8" ceiling sprk grille for background music.....\$2
- 6 PCB offcuts, assorted, handy sizes.....\$2
- 20 18M computer boards, assorted.....\$2
- 1 12v car cassette head demagnetizer.....\$2
- 1 220uf 350VW insulated can electro.....\$2
- 1 560uf .47uf 160VW can electro.....\$2
- 1 3300uf 63VW insulated can electro.....\$2
- 1 1K309K 5V 1.5A Motorola reg. T03.....\$2
- 1 400V 25A std SCR C370.....\$2
- 1 4" Magnavox 15ohm speaker.....\$2
- 1 6" x 4" Plessey 15ohm speaker.....\$2
- 1 pair autimeter test leads.....\$2
- 2 250V chromed red bezel, miniature.....\$2
- 4 1,000uf 25VW PCB electros.....\$2
- 3 3AG standard panel fuseholders, black.....\$2
- 10 DPDT PCB mounting slide switches.....\$2
- 1 PL-259 plug to 2 x PL259 plugs on lead.....\$2
- 10 assorted triaxer capacitors, miniature.....\$2
- 3 neon bezels, std panel atg 220-260V.....\$2
- 1 8 way DIL (16 pin) mini switches.....\$2
- 100 Molex IC socket pins, make your own.....\$2
- 1 mono cassette tape erase head.....\$2
- 2 2N777 germ. power trans. 40V, 15A, 150W.....\$2
- 4 5N7490 OR 5N7473 TTL integrated circuits.....\$2
- 10 asst. slide switches SPDT, DPDT, etc.....\$2
- 4 2 pin din plug/socket set, (8 pieces).....\$2
- 3 5 pin din plug/socket set, (12 pieces).....\$2
- 6 3.5mm plug/socket sets, (12 pieces).....\$2
- 20 asst general purpose equipment knobs.....\$2
- 2 metres 16 strand rainbow cable.....\$2
- 6 2.1mm OR 2.5mm DC plug and socket sets.....\$2
- 1 24V DC heavy duty 10A 3% plug-in relay.....\$2

YOUR CHOICE

\$1 EACH

- 2 18 way edge connectors 0.25" spacing.....\$1
- 5 DPDT mini slide switches PCB atg.....\$1
- 2 NKK paddle switches (ON)-OFF-(ON) DPDT.....\$1
- 2 NKK paddle switches (ON)-ON SPDT.....\$1
- 10 0.68uf 35VW tag tantalum capacitors.....\$1
- 8 2.2uf 35VW tag tantalum capacitors.....\$1
- 4 15uf 35VW tag tantalum capacitors.....\$1
- 10 47uf 6.3VW tag tantalum capacitors.....\$1
- 10 22V 400uM 82X79 zener diodes.....\$1
- 4 36V 1W 1R5Z368 zener diodes.....\$1
- 1 7824 24V 1A pos. voltage regulator T0-220.....\$1
- 10 metres speaker cable, colour-coded.....\$1
- 12 metres assorted colours hook-up wire.....\$1
- 10 NE-2 neons, 90V working.....\$1
- 8 6.3V MES dial lamps.....\$1
- 3 8" x 3/4" diameter ferrite aerial rods.....\$1
- 1 2" (57mm) diameter speaker 8 ohms.....\$1
- 12 pot-nuts and washers.....\$1
- 3 magnetic earphones for radio.....\$1
- 5 0.22uf 250V ACE miniprint capacitors.....\$1
- 4 0.47uf 250V Greencaps.....\$1
- 20 0.047uf 100V poly capacitors.....\$1
- 12 0.082uf 100V Greencaps.....\$1
- 12 0.082uf 100V Greencaps.....\$1
- 15 (5 each) 0.0047, 0.0056, 0.0068 Greencaps.....\$1
- 20 0.015uf 100V poly capacitors.....\$1
- 12 0.022uf 250V Phillips metal poly capacitors.....\$1
- 10 0.1uf 400V Oucan poly capacitors.....\$1
- 6 0.1uf 630V Greencaps.....\$1
- 3 1.0uf 400V poly capacitors.....\$1
- 25 100pf OR 0.001uf OR 0.047uf ceramic caps.....\$1
- 4 0.056uf 1KV poly capacitors.....\$1
- 5 0.47uf 400V poly capacitors.....\$1
- 8 0.58uf 250V poly capacitors.....\$1
- 3 470uf 50VW PCB OR P/I electros.....\$1
- 20 100uf 16VW PCB electros.....\$1
- 100 1W resistor assortment.....\$1
- 1 1TL-305 LED display.....\$1
- 30 PVC main terminal blocks.....\$1
- 2 finned heatsinks for TO-3 transistor.....\$1
- 5 3.5mm earphone plugs and sockets.....\$1
- 3 20V 1A selenium bridge rectifiers.....\$1
- 4 transistor radio PVC tuning gangs.....\$1
- 4 5K transistor radio volume controls.....\$1
- 10 assorted 1/2 shaft volume control knobs.....\$1
- 1 edge connector 0.156" kit, to 80 way.....\$1
- 1 value output transformer, G.P.....\$1
- 5 metres single shielded cable.....\$1
- 3 metres twin shielded cable.....\$1
- 7 9V battery clips for E/R 216.....\$1
- 10 Fuses 3AG standard 1A to 20A.....\$1
- 3 metres 16G 60/40 core solder.....\$1
- 2 240V 2 core mains power leads.....\$1
- 1 1.5K 1W IRC AM pot.....\$1
- 4 SPST pressure contact switches.....\$1
- 1 MURATA 5.5MHz 2 element ceramic filter.....\$1
- 4 keyboard push switches, no caps.....\$1
- 20 assorted low voltage lamps.....\$1

CRAZY PRICES!

DON'T MISS THESE BARGAINS!

WEATHERPROOF ANTENNA BASES

For all Australian made HF communications aerials - ensures good ground contact - rugged and reliable - easy to install on cars, boats, etc. Usually \$4.50, now \$3

- 37 pin mini plug/socket (panel) set.....\$3
- 1 Morse code kit for beginners.....\$3
- 2 pair speaker terminals on recessed panels.....\$3
- 1 12V DPDT 1K ohm Siemens cradle relay.....\$3
- 1 12 channel Sharp TV tuner, 9 biscuits.....\$3
- 1 strobe tube and trigger transformer.....\$3
- 1 lock-down car aerial.....\$3
- 1 dual stereo headphone adaptor for aaps.....\$3
- 1 AY3-8500 TV games I.C. chip.....\$3
- 1 1.2V ni-cad pencil batteries 500mAh.....\$3
- 2 3,300uf 50VW electrolytic cans.....\$3
- 1 metre brown speaker grille cloth.....\$3
- 2 12V mini PCB relays, 8-15V range.....\$3
- 1 transformer 6.3V-0-6.3V 150mA.....\$3
- 1 transformer 6V-9V-12V 100mA.....\$3
- 2 0.01uf PCB etch resist pens.....\$3
- 5 assorted mini toggle switches, SPDT, SPST.....\$3
- 1 2" (57mm) Philips Tweeter 8 ohm 20W.....\$3
- 1 5" twin-cone ams loudspeaker 8 ohm 7W.....\$3
- 1 60W electronic mains lamp flasher.....\$3
- 1 1" reel/reel tape splicer.....\$3
- 1 alternator noise suppressor.....\$3
- 1 generator noise filter.....\$3
- 1 pair CB radio Xals, west channels.....\$3
- 1 25,000uf 10VW ex-computer electro.....\$3

NE 555 40 1M 741 30
10+ 35c ea 10+ 25c 10+ 30c

CHEAP SEMICONDUCTORS

- 1N4004 400v 1A rect. 10c
- 1N4007 1Kv 1A rect. 15c
- 1N5404 400v 5A rect. 30c
- 1N5408 1Kv 5A rect. 40c
- 1N914/1N4148 diode 10c
- RED LED 5mm 10c
- RED LED 5mm 15c
- GREEN LED std 5mm 15c
- ORANGE LED std 5mm 35c
- LM380 2watt IC \$1.50 \$1.30 \$1.20

LM340T-12 \$1 EA
(7812) 12V 1A REG. 10+90c

NE555 \$1 EA 10+ 90c EA

DUAL TIMER LIMITED QTY. AVAIL.
BFX88 UNF 35c
TIC44 40V-6A SCR 25c
UA709 OP-AMP 25c
AY6109 AUDIO OUT 90c PR.

LIGHT DIMMER KITS OR MOTOR SPEED CONTROL
700 watt capability WITH RFI SUPPRESSION
\$4.95
OR 2 FOR \$9.00

LOOK PL-259 PLUGS
with in-built reducer etc
NEW TOP QUALITY
PUSH ON TYPE 40 OR 10
Importers sacrifices stock!

SAVE OVER \$4 SOLAR PANEL
WITH REFLECTORS
R.R.P. \$24.50
3v, 6v, 9v 50mA only **\$19.90**
at full sunlight
Size 104x144x13mm without reflectors!

STEREO COMMANDER
Ultrasonic remote volume control for home, car or boat, Hi-Fi system, connects to tape in/out sockets, 12V operation, hand-held remote unit, limited quantity!
Only **\$59**
Save \$40 was \$99

MEL-12 SCOOP PURCHASE PHOTO-DARLINGTON TRANSISTORS
NEW PRIME SPECS. **\$1 EA**

EHT TRANS.
NT3100 AU \$4.50
NT3101 NEW ONLY
NT3122

PHILIPS TRIPLERS
FOR COLOUR TV QTY. 641-444 1-3 **\$12 EA**
As used in Pyle, Philips, Kruller etc and most German colour TVs. 10+ \$10 EA


DPDT MINI 10+ SLIDE SWITCH
DE-LUXE BE-LINE CHROME **20c**

WERE \$12 \$10
100,000uf 16vW QUALITY ELECTRO'S
New Siemens \$9 EA

FM WIRELESS MIKE
NEW!
88-106MHz
ELECTRET CONDENSER
SALE \$23.90

PRE-PAK Electronics
P.O. Box 43, CROYDON 2132
1a West St. Lewisham, N.S.W.
Ph: 569-9797 A/POST 10% ORDER VALUE
Phone or MAIL BY **bankcard**

Ideas for Experimenters

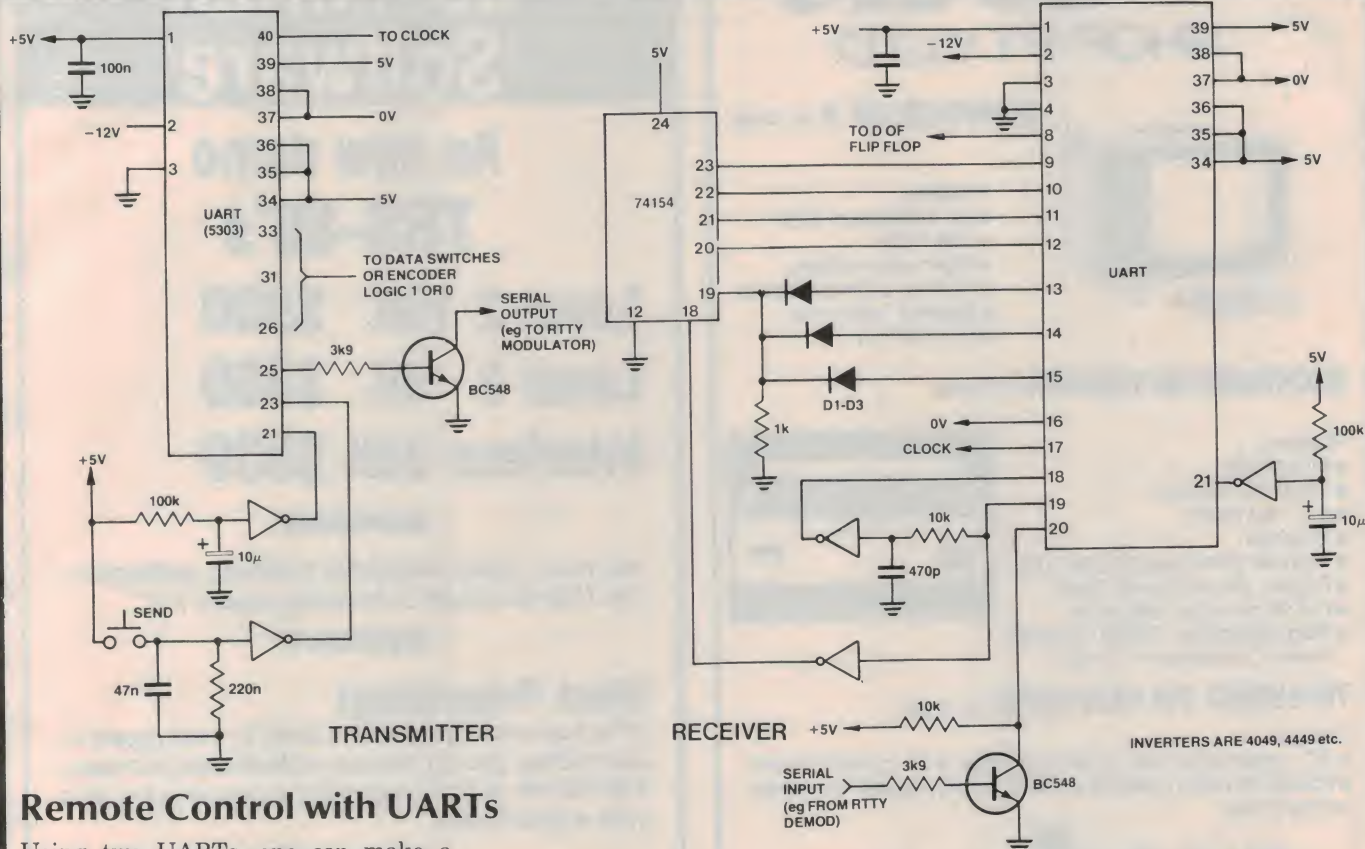

Remote Control with UARTs

Using two UARTs, one can make a simple remote control system as **Ralph Youie of Oakleigh in Victoria** shows here. One UART is used as the transmitter and sends a binary word of, say, five bits. This word may be transmitted by radio, ultrasonics, infra-red etc. The receiver then converts the serial data into parallel data which can be decoded by logic devices, such as a 4-16 line decoder (74154). Each output of this decoder can be connected to the clock input of a 'D' type flip-flop, and the fifth bit can be connected to the 'D' input. Thus, a five-bit word programmed on the transmitter can control 16 flip-flops and hence 16 devices in two states. With a little more logic, one could control 16 devices in 16 states, 128 devices in two states, 64 devices in four states etc., using eight-bit words.

The circuit shown is just one possibility as many factors could be changed, such as clock rate, modulation system, word size, parity and transmission method to name a few. In the circuit, D1-D3 form an OR-gate which prevents the 74154 from operating if an error is found in the word received. Ralph used an RTTY system for the mod-demod and slide switches to program the code word

on the transmitter. However, a refined system could use a keypad with encoder.

Possibilities include remote control of television, hi-fi, solenoid tape decks, lights, garage doors etc... limited only by imagination.

UART pin connections:

1: Vss 2: Vgg 3: Vdd 4: RDE 5: RD 7
6: RD 6 7: RD 5 8: RD 4 9: RD 3 10: RD 2
11: RD 1 12: RD 0 13: RPE 14: RFE 15: ROR
16: SWE 17: RCP 18: RDAR 19: RDA 20: RSI
21: MR 22: TBMI 23: TDS 24: TEOC 25: TSO
26: TD 0 27: TD 1 28: TD 2 29: TD 3 30: TD 4
31: TD 5 32: TD 6 33: TD 7 34: CS 35: NPB
36: NSB 37: NDB 38: NBD 1 39: POE 40: TCP

RDE Receive Data Enable (tri-states data line)

SWE Status Word Enable

RCP, TCP clock input

RPE, RFE, ROR parity, frame, and receive overrun errors.

MR master reset

NSB 1 or 2 stop bits

POE odd or even parity



RSI, TSO serial input, output

TDS send transmit data

NPB parity inhibit

NDB no of data bit 5, 6, 7 or 8

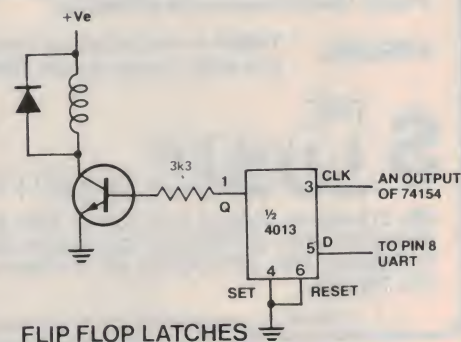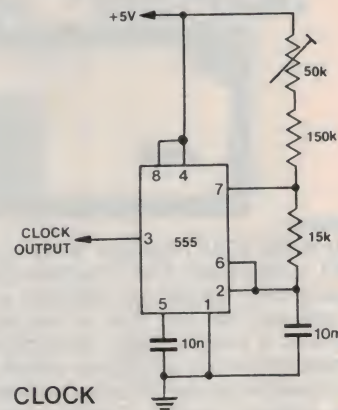RDA, RDAR Received data, Received data reset



\$ THE LOGIC SHOP PTY. LTD.



COMPUCOLOR II ex stock


Features:

- Up to 32K user RAM
- 16K ROM
- Eight colour display
- 32 lines at 64 characters
- Inbuilt 5" disk drive
- RS-232 Port

MICROLINE 80 PRINTER ex stock

Features:

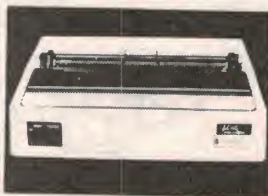- 80 char/sec
- 40/80/132 char/line
- 9 x 7 dot matrix
- Graphics
- Long life print head (200,000,000)
- Friction, pin and tractor feeds
- Full 96 character ASCII set
- Plug compatible: TRS80, Sorcerer, Apple, Compucolor II, TI 99-4



TELEVIDEO TVI 912B (VDU) ex stock

Features:

- 12" screen • 24 lines at 80 characters • 75 to 9,600 Bauds
- RS-232 or 20MA interface • Printer output Port • Microprocessor controlled.

NorthStar HORIZON



Features:

- North Star Z80A Processor. • North Star RAM memory board (64K). • North Star Disk Controller Board (4 drives). • Quad capacity drives (360K bytes per drive). • S-100 motherboard with 12 slots and real time clock. • Two serial and one parallel I/O interfaces. • A power supply more than adequate to power a full complement of 12 S-100 boards. • North Star Software — BASIC, Disk Operating System (DOS), and Monitor on diskette. • Applications software: Debtors, Creditors, General Ledger, Inventory, Payroll, Word Processor, Mail Manager.

SPECIAL

Trader — An integrated invoicing, accounting and stock control system. **NOW AVAILABLE**

\$ THE LOGIC SHOP PTY. LTD.

VIC: 212 High St, Prahran, 3181. (03) 51-1950. **NSW:** 91 Regent St, Chippendale, 2008. (02) 699-4919. **QLD:** Shop 16, Civic Arcade, Adelaide St, Brisbane, 4000. (07) 31-2330. **WA:** 454 Williams St, Perth, 6000. (09) 328-7345.

TRS-80 is a registered trademark of Tandy Electronics.

SALE — SALE — SALE

de Forest Software

**As new demo
TRS-80's**

Level 2 16K \$900

Level 2 4K \$850

Interface 32K \$530

We have totally interactive business software for the TRS-80 Model 2 (Including stock)

Word Processing!

Why buy a word processor, when in most cases for less money you can have a sophisticated computer that will not only do your word processing but also your accounts etc.

"TRS80 Disk and other Mysteries"
Don't Boot-Up without it!
The 'How To' book of TRS-80 data recovery.

- 130 page, 8½ x 11 sortcover
- Actual memory maps, samples
- Detailed recovery instructions
- Recover lost programs, DOS errors
- Fix parity, gat and hit errors
- Recover from unreadable directory
- Fix Electric Pencil file errors
- Recover lost or killed files

JUST \$22.50

Get it and unveil the many disk mysteries.


TRS-80 IS A REGISTERED TRADEMARK OF TANDY CORP.

**26 Station Street, Nunawading Melbourne
3131 (03) 877-6946**

write or phone for our Catalogue.


Don't let technology pass you by!

Learn Microprocessor Programming and Application techniques

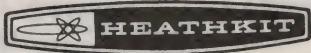with the  **HEATHKIT**
Microprocessor Self-Instruction Program.



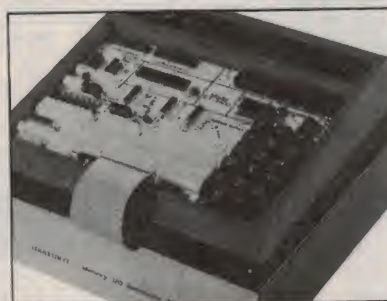Microprocessor Trainer for EE-3401 Program



Functioning as a miniature digital computer, the ET-3400 Microprocessor Trainer is essential for the experiments in the EE-3401 self-instruction program. After completing the program, the ET-3400 is ideal for breadboarding, prototyping and system design.

If you're involved in scientific or electronic pursuits, microprocessors are becoming a way of life and a dominant factor in your success or failure. The EE-3401/ET-3400 self-learning program and accompanying computer trainer is the easy, effective way to learn about these powerful devices. The program uses Heath's proven self-instructional techniques including programmed instructions and audio-visual aids to teach computer programming, microprocessor operation, interfacing and related topics.

This self-instruction program covers microprocessor basics, computer arithmetic, programming, interfacing and much more.

The microprocessor course is organised into 10 learning units as follows: 1: Number Systems & Codes, 2: Microcomputer Basics, 3: Computer Arithmetic, 4: Introduction to Programming, 5: The 6800 Microprocessor—Part 1, 6: The 6800 Microprocessor—Part 2, 7: Interfacing—Part 1, 8: Interfacing—Part 2, 9: Programming Experiments, 10: Interfacing Experiments. Each unit is complete with introduction, unit objectives, activity guide, experiment, examination and examination answers.

The EE-3401 is complete with 62 electronic components required to complete the experiments. These components include two 2112 256 x 4-bit RAM's, 6820 PIA interface chip, 1406 d/a converter, 741 and 301 op amps and a variety of other microprocessor-oriented devices. The ET-3400 Computer Trainer is required for the experiments in the Microprocessor Course.

Course EE-3401

\$155.00

The ET-3400 features a built-in 1K ROM monitor program for controlling unit operation; 6-digit hexadecimal 7-segment LED display for address and data readout; 17-key hexadecimal keyboard for entering programs and data. Has 256 bytes of random access memory (RAM) built-in, expandable to 512 bytes with the RAM's supplied in the EE-3401 program. Also has 8 buffered binary LED's for display of breadboard logic states, 8 SPST DIP switches for binary input to breadboard circuits, a breadboarding socket for prototyping, interfacing and memory circuits.

All microprocessor address, control and data busses are buffered and terminated on the front panel for ease of connection to prototype circuits. There's also provision for a 40-pin external connector to extend memory and I/O capacity. Built-in +5, +12 and -12 volt power supplies.

Kit ET-3400

\$347.00

Microprocessor Trainer Accessory

The ETA-3400 gives you the additional I/O and memory you need to turn your ET-3400 Microprocessor Trainer into a complete, personal computer system. It provides an audio cassette interface so you can store programs on convenient cassettes. It also provides an additional 1K bytes of memory so you can run longer and more sophisticated programs through the ET3400. The memory can be expanded to 4K bytes with the optional 3K chip set (ETA-3400-1). A serial I/O with EIA 20mA loop format provided in the ETA-3400 accessory lets you hookup a video terminal.

A tiny BASIC interpreter is provided in ROM to let you do actual programming using the BASIC language.

Kit ETA-3400

\$270.00

ETA-3400-1, Optional 3K Chip Set

\$ 86.00

ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please rush me the Heathkit of my choice. My cheque for \$..... is enclosed plus \$7.00 for package and post.

Name

Address P/Code

Send to: W. F. Heathkit Centre

220 Park St., South Melb. 3205. Phone 699 4999.

WF 737/80

☐ Course EE-3401

☐ Kit ET-3400

☐ Kit ETA-3400

☐ ETA-3400-1

☐ I'd like to know more about the full range of Heathkit Training Programmes and Prices. Please send to me, without obligation, my FREE catalogue and price list.



Credit Card No:


--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Bankcard

Expiry Date Signature

minimum \$50

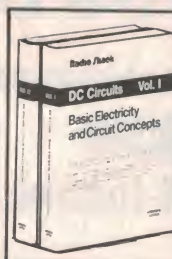What's The Advantage Of Having Tandy Electronics In Your Workshop?




Basic Electricity
695 Each

SAVE \$3.02

Both For **10⁸⁸**

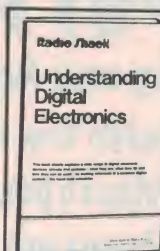Volume I introduces electricity and circuits and Volume II expands on electronic devices.
60-2019/20




Understanding Digital Electronics

295

Explains all you need to know about digital electronic devices, circuits, systems and more.

62-2010

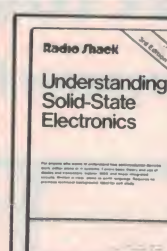

Solid-State Electronics

295

A 12-lesson self-teaching course in semi-conductor theory. 62-2035

Audio Output Transformer



Miniature size, 1000-ohm centre tapped primary, 8-ohm secondary. 1.9x1.5x1.5cm. 273-1380

169

Power Transformers

Type	Volts	Current	Size in Cm	Cat. No.	Each
Miniature	6.3	300mA	5.2x2.5x3.0	273-9006	6.99
Standard	6.3	1.2A	3.1x4.9x3.9	273-9003	6.99
Standard	12.6CT	1.2A	5.0x6.0x3.8	273-9004	7.99
Heavy-Duty	12.6CT	3A	6.9x5.7x5.0cm	273-9010	16.95
Heavy-Duty	25.2CT	2A	6.9x5.7x5.0	273-9011	16.95
Heavy-Duty	18CT	4A	10x5.0x6.3	273-9013	22.95
Clock Module	10/6/5	500mA	5.2x2.8x3.4cm	273-9530	9.95

150 Ceramic Discs



1295

50WVDC. Contains 15 .005uf, 10 each of 100, 220, 470pF; .001, .002, .01, .02, .05, .1uF; 5 each of 5, 47, 68, 330pF; 25 other assorted styles. Sealed construction. Real value! 272-601

Archer-Pak Parts and Semiconductors only \$2.99 each!



Tandy's Greater Efficiency and Value Make Our Parts and Components Stand Out From the Rest!

- | | | | |
|--|----------|---|----------|
| 1. 50 Silicon switching diodes | 276-1620 | 9. Asstd. Mini reed switches | 275-1610 |
| 2. 12 Potentiometers, trimmers. Asstd. | 271-1605 | 10. 15 General purpose transistors | 276-1603 |
| 3. 15 2N2222 general-purpose transistors | 276-1617 | 11. 25 Assorted zener diodes, 250 mW to 5 watts | 276-1629 |
| 4. 20 LED's Asstd. red, green and amber | 276-1622 | 12. 100 Disc capacitors, asstd. types | 272-801 |
| 5. 10 LED readout displays, asstd | 276-1627 | 13. Pair LED digits common cathode | 276-1647 |
| 6. 12 Asstd. switches in many styles | 275-1601 | common anode | 276-1648 |
| 7. Asstd. electrolytic capacitors | 272-802 | 14. 8 Opto-isolators. For logic circuits | 276-1628 |
| 8. Asstd. voltage regulators | 276-1608 | 15. 25 Block-type polystyrene capacitors | 272-803 |
| | | 16. 15 Amplifying transistors, type 2N3906 | 276-1604 |

Available at all Tandy Stores and Participating Dealers Around Australia

TANDY ELECTRONICS

Mail Order Department
P.O. Box 229, Rydalmere,
N.S.W. 2116.

Shoparound

THIS PAGE is to assist readers in the continual search for components, kits and printed circuit boards for ETI projects. If you are looking for a particular component or project — check with our advertisers if it is not mentioned here.

First of all, readers requiring Scotchcal panels for the projects in this issue, or past projects of recent vintage, should enquire with Rod Irving Electronics and All Electronic Components in Melbourne and Radio Despatch Service in Sydney. Printed circuit boards for all this month's projects and almost every project we've done in the past can be supplied by (apart from specific suppliers mentioned) RCS Radio, 651 Forest Rd, Bexley NSW; Radio Despatch Service, 869 George St, Sydney NSW; and All Electronic Components, 118 Lonsdale St, Melbourne Vic.


For subscribers in South East Asia we have news that Jemal Pty Ltd of Welshpool W.A., who stock most ETI pc boards and front panels, have appointed a distributor in Singapore. For your pc board and front panel requirements, contact Applied Digital Systems, 326 3rd Floor, Far East Shopping Centre, 546 Orchard Road, Singapore.

ETI-735 UHF TV converter

The OM350 wideband amp chip used in the RF stage was also used last month in the ETI-729 Masthead Amp. So far as we were aware at time of going to press, the following suppliers were stocking the OM350: in Melbourne — All Electronic Components, Ellistronics, Rod Irving Electronics and Tasman Electronics; in Sydney — Jaycar and Radio Despatch Service. Dick Smith has it listed in his latest catalogue as Z-6185.

For the tuneable version of the converter, there are two sources of suitable tuning capacitors, as mentioned in the article. The C1604 capacitor is sold by David Reid Electronics stores — get the 14 pF type. It costs around \$7. The 15 pF Johnson capacitor is available from General Electronic Services of 99 Alexander St, Crows Nest NSW 2065. However, some kit suppliers may well be stocking this item, so check your favourite supplier first.

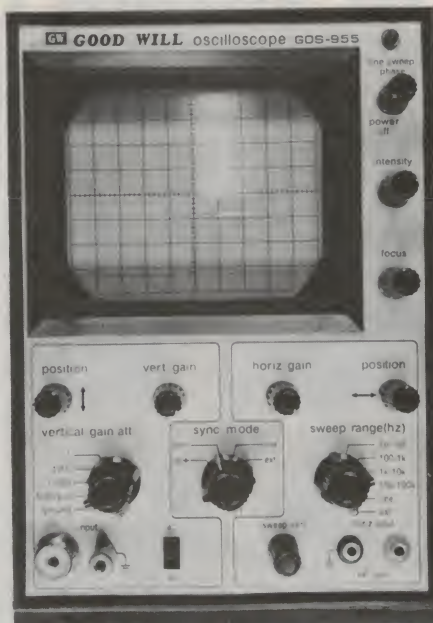Note that this project requires a fibreglass pc board.



Emona Enterprises, who recently gained the Good Will instruments agency, has released a 5" (130 mm) CRO featuring 6.5 MHz vertical amp bandwidth, 10 mV/div sensitivity, horizontal sweep from 10 Hz to 100 kHz, internal voltage and frequency calibration oscillator, and low cost. Called the Good Will GOS-955, it costs only \$255 (plus tax). The two-tone front panel has large, clear markings for the controls and is well laid out. Vertical input connector is an SO239 socket. We found the unit easy to use, with good synchronisation and trace brightness. It held lock on signals well beyond the bandwidth and would be worth considering for the 'serious' hobbyist. We hear the latest shipment sports a 7 MHz bandwidth. See Emona, Suite 208/661 George St, Sydney NSW 2000. (02)212-4815.

ETI-256 humidity meter

This unique, versatile little project is built around the Philips capacitive humidity sensor type 2322 691 90001. This is distributed by Sycom (offices in Sydney and Melbourne). At the time of going to press Radio Despatch Service in Sydney and All Electronic Components in Melbourne said they would be stocking the humidity sensor.

The two 47 pF positive temperature coefficient capacitors (100 parts per million — P100) will also be stocked by these two firms. All other components are widely stocked.

ETI-257 relay driver board

There's nothing out of the ordinary in this project and pc boards and components should be readily available. The board was laid out to accommodate the various popular double-pole relays available and you can fit the Fujitsu FRL621D012 (distributed by IRH Components), the Takamisawa VB 12STAN (distributed by Associated Controls) or the Pye 265/12/G2V.

Series 5000 heatsink panels

At time of going to press, the following firms had ordered or had in stock the front panel/heatsink for the MOSFET amplifier presented in the January, February and March issues: in Sydney — Electronic Agencies and Jaycar; in Melbourne — All Electronic Components, Rod Irving Electronics and Tasman Electronics.

Readers may also order the unit through the magazine. The cost is \$42.50, post paid within Australia. Send your cheque or money order to cover the number you require to:

Series 5000 Heatsink/Front Panel
ETI Magazine
15 Boundary St
Rushcutters Bay NSW 2011

Please allow up to four weeks for delivery.

Project price estimates

As some information on component pricing and availability could not be obtained until very late, we have not included the price estimates with the projects this month. As this page is usually the last to be done, we've included it here. Note that these prices are estimates only and not recommended prices. A variety of factors may affect the price of a project, such as quality of components purchased, type of pc board (fibreglass or phenolic base, tinned tracks, etc), type of front panel (if used) supplied, etc — whether bought as a kit or separate components.

ETI-735 UHF TV converter	
• single channel version	\$35 - \$40
• tuneable version	\$52 - \$58
(plug pack not included)	
ETI-256 humidity meter	\$21 - \$27
ETI-257 relay driver	\$10 - \$12

How many of these kids are equipped for the electronic world of tomorrow?



This century has seen remarkable advances in electronics. Advances which are now a part of every day living. As this continues into the next century, there will be the need for more education in electronics. A good basic knowledge of electronics is essential for those children who are to become our future technicians, programmers and so on. Without this knowledge, your child could be left in the dark, perhaps without a future career.

You can give your kids a head start in electronics; knowledge which is essential to the future of your children.

DICK SMITH'S FUN WAY INTO ELECTRONICS

can provide that
essential knowledge-
& what's more it's FUN!

DICK SMITH
Electronics



Give your child a start for \$4⁹⁵

**DICK SMITH'S
Funway Vol 1.**

Contains useful
& educational
projects.

Cat. B-2600

\$4⁹⁵



**DICK
SMITH'S
Funway Vol 2.**

Increase your
knowledge. Fun &
educational.
Cat. B-2610

\$6⁹⁵



**Great kits from
FUNWAY VOL 1.**

Has all you need to make any
of the projects described in
Volume 1.

Projects 1-10 \$6⁹⁰

Cat. K-2600

Projects 11-20 \$7⁵⁰

Cat. K-2610



**FUNWAY VOL 2 kits
from only \$2⁷⁵**

Build many fascinating
& worthwhile projects.
There are many to choose
from!

**Drop in today & pick up
your FREE kit catalogue
for more details!**

**SEE OUR OTHER ADS FOR
FULL ADDRESS DETAILS**

LETTERS

Sir,

In your March issue, you presented a 'Short Circuit' of a Guitar Sustain, the active component of which was a Motorola MC3340P voltage controlled amplifier.

Having an immediate application for such a unit, I consulted the catalogues of Australia's two largest component retailers, to find neither stocked this vital component. In order to find a supplier, I contacted both Motorola agents. Neither had any stocks, and neither could suggest alternative sources.

Consequently, I contacted your office by phone, and was given the name of two Melbourne stockists, whom you "had been told" carried stocks. Neither did. In desperation, I contacted eleven Sydney component retailers. Not one had current stocks, and only two ever carried stocks; one was just out of stock (around ten weeks' wait) and another was trying to find stocks.

Sir, I find it absolutely incredible that a reputable magazine such as yours could publish a circuit using an essentially unavailable component. Your claim is that 'Short Circuits' are tested, but how could it be tested if the component is unavailable? Surely you have a responsibility to your readers to ensure components for your projects are available — if not, then the circuit should be altered to use a readily available component!

I am confident many other people were annoyed by this lack of planning on your part, and I for one will only continue to read your magazine because limiting my reading to your opposition alone will not allow me to keep up with new developments.

Edwin Humphries
Rockdale NSW

Firstly, the unavailability of the MC3340P was not due to "lack of planning" on our part. More likely, it was brought about by the swift action of other readers! However, I must commend your determination and resourcefulness in attempting to find a source of supply.

It is our standard practice whenever a project or Short Circuit is scheduled for a particular issue, to check the availability of components specified. With projects in particular, we often go to a great deal of trouble to ensure that, with components which are not standard stock lines, dis-

tributors and/or retailers will have them in stock by the time the issue goes on sale and for some time thereafter. We retain a freelance correspondent in Melbourne to assist us in this task. Our publishing schedules are such that the contents of a particular issue are finalised about three months ahead. This means that the Guitar Sustain item was readied for production in December and artwork was prepared in January. In mid-January I rang suppliers and distributors to check on availability of components scheduled for projects etc. in the March issue. From memory, some three suppliers indicated they had stocks, so the Guitar Sustain was considered a 'goer'. Now, consider that there is a period of some six to seven weeks from the time the check is made to the time an issue goes on sale. It is just not feasible to check component availability and alter the contents of an issue if supplies of an item dry up, any closer to the publishing date than that. It seems that what stocks there were of the MC3340P had sold out in the interim or very shortly after the March issue went on sale.

As you would appreciate, although we can advise suppliers that particular components will appear in the magazine, we have no control over their stocking policies. You would also appreciate that they are in the component marketplace 'taking a punt' as it were on how many units of each device stocked they will sell to obtain a reasonable return over a period of time. If there is a sudden upsurge in demand and their punt on sales was well below that demand, then clearly their stocks will rapidly run out. The same applies to distributors — in fact, their planning and setting of stock levels is generally much more rigid than that of retailers. For this very reason, we recently introduced a scheme — at the request of several major distributors — to advise distributors up to four months in advance of semiconductors and 'special' components planned for projects in forthcoming issues. We hope this scheme will go a long way towards alleviating such problems as you found.

Returning to your letter, in your fourth paragraph you say you find it "absolutely incredible" we could publish a circuit "using an essentially unavailable component". According to our usual pre-publication check, the component was available! As you can see from the

foregoing explanation, we take our responsibility to readers seriously with regard to component availability.

Perhaps I can throw the ball back in your court in finishing. Semiconductors are readily and speedily obtainable from overseas if you find them in short supply in Australia, and many resourceful hobbyists use this avenue when necessary (some as a matter of course!). For example, recent issues of English electronics hobbyist magazines (available locally in many newsagents and technical book stores) — Wireless World, for example — carry advertisements which list the MC3340P for sale at 120 pence. Two advertisers I'm looking at as I write this are: Watford Electronics, 33/35 Cardiff Rd, Watford, Herts, UK, and Technomatic Ltd, 17 Burnley Rd, London W10, UK. An international money order or bank draft in pounds sterling for about \$3 would secure one by return airmail — accompanied by a flyer or catalogue, like as not!

Australia represents a very small market in the electronic component business, despite generally good representation by local firms. For those components which are not consumed in relatively large quantities — unlike 1N914s and 555s, for example — the local stock level is likely to be quite small and supply delays quite long. When there's a 'run' on such components, there'll be disappointed and frustrated customers (or ex-customers!), and there's not a great deal we can do to prevent it, apart from the advance notification and checking system we already employ.

As of 20 March, VSI advised that stocks of the MC3340P were expected in six weeks but they were holding no back orders. Soanar advised that their Melbourne head office had 50 units and that more were expected in around four to five weeks.

If you're desperate to build a guitar sustain unit, I would recommend our Project 454, published in the April 1980 issue — which is a combined fuzz and sustain unit to provide sustain alone, fuzz alone or fuzz and sustain. The pc board, semiconductors and suitable other components for this project are normally stocked by Radio Despatch Service in Sydney, while All Electronic Components in Melbourne stock a kit.

Roger Harrison
Editor

Sir,

Your eminent correspondent "Depresst C-Ber" (ETI, Jan. 1981) has most aptly demonstrated the reason why CB is known as the 'Cretins' Band'. Enough said.

"V.K."

Buy YAESU from DICK SMITH and you get a full 12 MONTH GUARANTEE, the benefit of Australia's LARGEST YAESU SERVICE CENTRE plus friendly and helpful service of over 20 stores throughout Australia. But that's not all!

WE WILL MATCH OR BEAT ANY GENUINE ADVERTISED YAESU PRICE!*

Why would you buy from anyone else?

*** OUR POLICY ON YAESU PRICES:**
If you produce a copy of a current advertisement appearing in the national media, with a Yaesu price below our advertised price AND the advertiser has the goods in stock, Dick Smith Electronics guarantee to match or better that price. Verbal or written quotations are not acceptable.

NOTE: This offer does not apply to companies, distributors or re-sellers of Yaesu equipment or their representatives.

FRG 7700SW

Ask for a copy of our brochure showing you what the FRG-7700 can do for you!

\$495
INC. BONUS 12V CONVERSION KIT!



D-2841

FT-7B

BASE/MOBILE HF

FT-7B is ready when you are! All current HF bands, output 50W & the option of AM, CW or SSB. Choice of VFO or crystal locked channels. Great for novices.

ONLY \$599



FT101ZD

INCLUDES NEW WARC BANDS

Remember the famous 101 series? Check these features: variable IF bandwidth, RF speech processor. With 180W input (SSB/CW) & AM/CW/SSB. You're ready to take on the crowded bands... and win.

ONLY \$889

D-2859

CREDIT TERMS AVAILABLE

DIGITAL VFO

FV 707
You lucky FT707 owners! Has 12 memories, up/down scan in 10 Hz steps & receiver offset tuning.
ONLY \$295
D-2896




D-2869

POWER IN A SMALL PACKAGE FT 707

240W DC SSB, 80W AM.
What a performer! This small wonder contains all HF & WARC bands. You also get digital display, LED S/power meter, push button operation. It's great for mobile use & makes a superb base station.

ONLY \$785

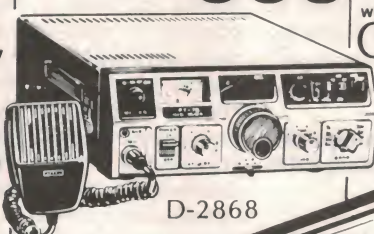

D-2868

GO MOBILE WITH THE FT480R

Yaesu call this their 'total performance VHF computerized transceiver'. You get FM, SSB & CW, over the full 2 metre band. If you want the best, you want the remarkable FT 480R!

D-2887



\$575

YOU CAN AFFORD THE ULTIMATE! FT107M

Yaesu's newest & finest transceiver. Packed with heaps of features and more. All mode, 240W pep output.

D-2871



\$1278
INC. DMS & PS.

P&P EXTRA

DICK SMITH Electronics



SEE OUR OTHER ADS FOR FULL ADDRESS DETAILS

COMMUNICATIONS



More VHF TV channels sought

F.A.C.T.S. seek the facts

The Federation of Australian Television Stations hosted a seminar in mid-March aimed at examining the avenues available to TV broadcasters who are seeking to expand or continue to provide the range of programme choices now enjoyed by the majority of Australians.

In introducing the seminar, the first in a proposed series, **FACTS** said, "There has been a lot of discussion during the past couple of years about the future possibilities for television ... some ... proposals will put further pressure on available frequencies whilst others may tend to alleviate the problem."

"Considered with the adoption of the 1974 McLean Report recommendation to allocate Band II (88-108 MHz) to FM sound broadcasting and an obligation to vacate channel 5A at some future date, the 13 channels determined in 1961 by the Huxley Committee have been effectively reduced to 9 or 10.

"It seems reasonable to assert — and it can be proven — that more than 9 (or 10) VHF channels are needed to continue to provide the programme choices now enjoyed by the majority of Australians and which are more or less promised for everyone.

"In the knowledge that new services would be possible — by satellite distribution, as one factor — and that the General World Administrative Radio Conference (WARC '79) held in Geneva in late 1979 would provide an opportunity for Australia to put its frequency allocations house in order, **FACTS** began pressing the Government for action in June 1978.

"The consistent request, repeated many times since then, has been for an enquiry to determine the future needs of the Australian public for broadcasting services — not just to allocate frequencies for a defined

number of services, but to look at social, economic, political, demographic and technical aspects of the question.

"Nothing has happened."

That provides some background to the efforts of **FACTS** to catalyse some discussion on the question. Basically, what is sought is a 12-channel system in VHF Bands I and III. A variety of proposals were put and discussed at the seminar. Proposal 'a' for Band I involved moving channel 0 down by 1 MHz (putting the 6m amateur band between 51 and 53 MHz) and channels 1 and 2 down by 3 MHz, plus adding a channel above channel 2, between 67 MHz and 74 MHz. Apparently, many tuners will not cope with this. Proposal 'b' for Band I left channel 0 in place, added a channel between 52 MHz and 59 MHz (eliminating the amateur 6m band — oh, horror!) and moving channels 1 and 2 up 3 MHz. Same problem as Proposal 'a'. Proposal 'c' left Band I alone but required the retention of 5A. Jim Wilkinson of the Australian Broadcasting Tribunal put the kibosh on that by announcing that the Prime Minister had decreed that 5A was to go. Full stop. No time scale was proposed, though. Proposal 'd' left 5A out, but added channel 3, to be allocated on a regional basis, so as not to interfere with FM broadcasting.

In Band III, the proposal put it that two extra channels could be gained (channels 12 and 13). Firstly, if the present fixed and mobile and DME stations between 202 MHz and 208 MHz were removed, channel 13

could be placed here if channels 10 and 11 were moved up 1 MHz. Secondly, by clearing 223 MHz to 230 MHz of the current DME and government services, channel 12 could be placed in this region. Most current and past TV front ends could cope with this, it seems.

A number of hitherto unpublished problems with both VHF and UHF broadcasting came out at the seminar. Firstly, Band I (channels 0, 1, 2) stations have many problems. Channel 0 especially has propagation, reception (antenna) and interference problems. All Band I stations will have difficulty with Teletext transmissions owing to propagation distortion causing errors which are unacceptable. Indeed, the ABC (channel 2) is running trials with the French Antiope system in an effort to overcome the problem.

To provide appropriate signal levels and coverage similar to that of VHF stations, UHF stations have to run around three times the e.r.p., it seems. Also, capital cost of a UHF station is around four times that of a

VHF station, as is the running cost.

Roger Harrison

* Stop Press! *

Announcing the start of ABC trials of the French Antiope data broadcasting system on April 6, the Minister for Communications, Mr Sinclair, said it would enable comparison with the UK Teletext system.

"It is important to try as many systems as possible before deciding on the most suitable system for Australia," the Minister said.

"Factors which must be taken into consideration include the reliability of the system, its cost to the consumer and operator, and its suitability for providing captioning for the hearing impaired."

He re-affirmed Mr Tony Staley's February 1980 statement that the system would be reviewed at the end of three years.

"Anyone purchasing decoding devices suitable to one of the systems being tested over that period should realise that there is no guarantee at this stage that their decoder will suit the system finally agreed on."

Fortnightly propagation predictions

George Jacobs, well-known US radio amateur and propagation expert, offers a propagation prediction service.

Available on subscription for US\$25, the publication, *Mail-a-Prop*, is published and distributed every two weeks. Enquiries should be directed to George Jacobs, *Mail-a-Prop*, Box 1714, Silver Spring, Maryland USA MD20902.

George also has his new book for sale, *Shortwave Propagation Handbook*, for US\$7.95. Enquiries to address above. We've not seen it.

stocked locally.

Don't forget that the NSW Division of the Wireless Institute of Australia includes a weekly propagation report and forecast in its Sunday morning broadcasts at 11 am EAST on the 3.5 MHz, 7 MHz, 28 MHz, 52 MHz, and 144 MHz bands and via relay stations on other

500 MHz quartz crystals!

A technique for producing quartz crystals so thin that they vibrate at a fundamental frequency of 525 MHz has been put into pilot production by the Compagnie d'Electronique et de Piézo-Électricité (CEPE).

A Thomson-CSF subsidiary, based in Sartrouville, near Versailles, the firm starts with quartz slices lapped to a thickness of some 33 μ m, equivalent to a 50 MHz fundamental, and then thins them down by ion bombardment to about 3.2 μ m and a 525 MHz fundamental — the highest yet, says CEPE.

Though chips as thin as this are still experimental, the French firm expects to produce industrial versions with fundamental frequencies of 400 MHz.

MR BUSINESSMAN!

here at last from DICK SMITH is a

STOCK CONTROL & PRICING SYSTEM

especially designed
for Australian
conditions

program suits
DICK SMITH
SYSTEM 80
micro computer



No, not just another software package imported from overseas, but one that has been written (at great expense) *by Australians for Australian businesses*

In fact it has been modelled closely on the Stock Control and Pricing System used so successfully by Dick Smith Electronics.

The original system runs on an IBM computer costing more than \$50,000 — but you can have the same benefits for less than one tenth of this cost (yes, for both the computer hardware and the software!)

While you're in one of our stores why not check out the many features of the System 80 and its peripherals?

You, and your business can benefit from this amazing system for less than you think!

HERE ARE JUST SOME OF ITS OUTSTANDING FEATURES

Cat X-3750


- Capacity for up to 1200 stock lines!
- Machine-language sorting for FAST operation!
- Ability to print out price lists as well as stock status reports and other listings (all dated!)
- Fast stock and financial status reports on the screen!
- Simple "menu-driven" operation — no special training required!
- Prints out stock count sheets for stocktaking, then gives you a printed analysis of all discrepancies!
- Special Australian Sales Tax feature (optional)!
- Easily expandable — so you're not forced to change to another system as your business expands!

\$275!

(Program & Data Disks with comprehensive User Manual)

The full Dick Smith business computer system includes computer, monitor, disk-drives, expansion interface, large memory, cables, etc. — costs just \$3,480.00. So with SCAP you can have a superb operating system for well under \$4,000!!!

DICK SMITH
Electronics

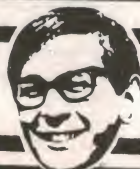

SEE OUR OTHER ADS FOR
FULL ADDRESS DETAILS




HAS THE TASTE STOPPED
GETTING THROUGH?

If your present tobacco just doesn't deliver the
satisfaction you want, then roll a Cannon.
A rich new blend of medium dark cigarette
tobacco that's just a little bit stronger.
Cannon, for the taste you're missing out on now.

CANNON.
SLIGHTLY STRONGER.



Sooner or later you'll need a Gregory's.

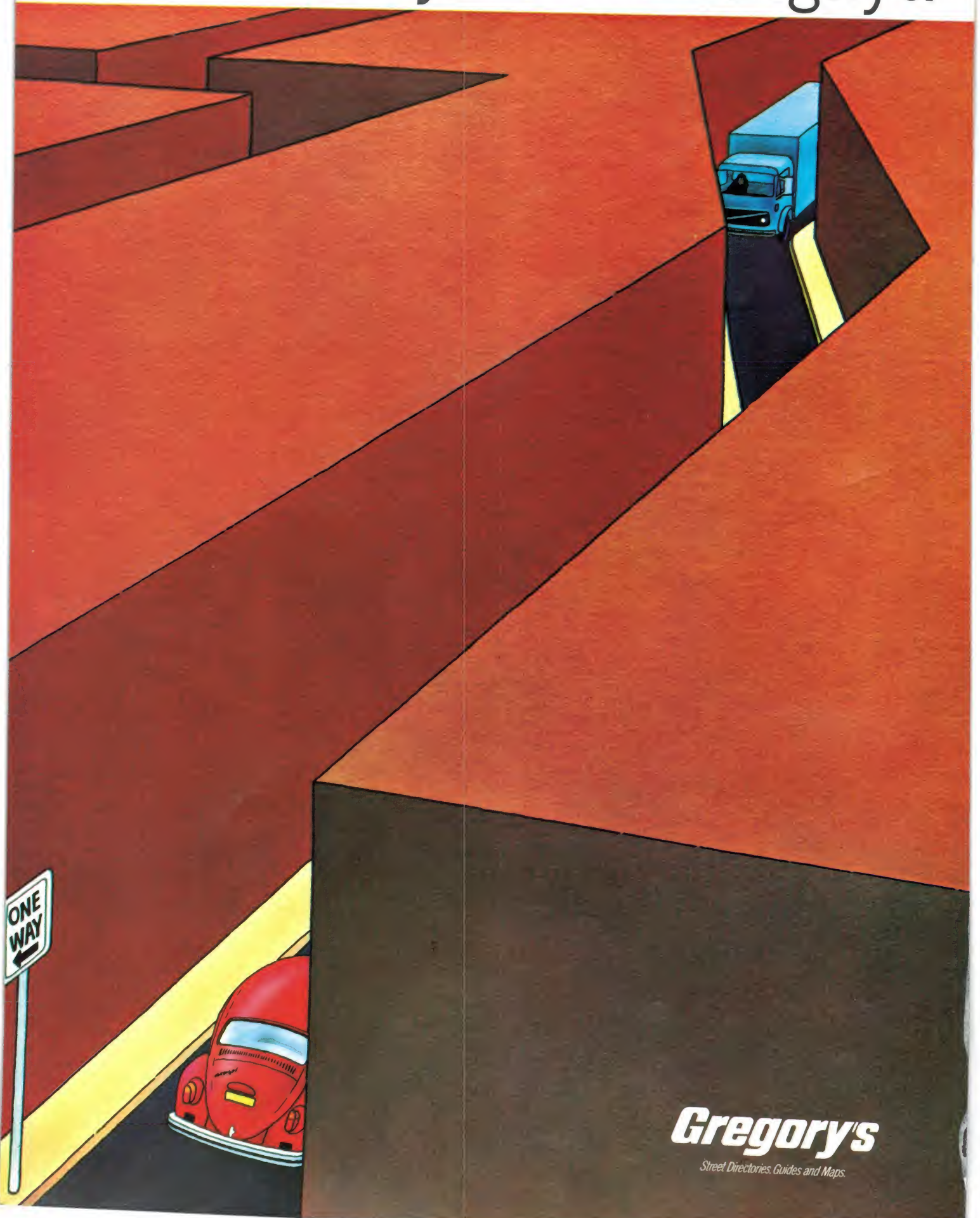

Gregory's

Street Directories, Guides and Maps.

COMPUTING TODAY

Say it again, RAM!

The DT1000, a fully assembled circuit board containing all the components necessary to output speech upon demand, is now available from National Semiconductors.

The DT1000 evaluates the operation and application of the Digitalker speech synthesis chip, in either an end or stand-alone product, and requires only a 9 V power supply and an inexpensive speaker for operation.


It contains National's speech processor chip, two speech ROMs containing 138 individual words, output filter, audio amplifier, keyboard and a COPS microcontroller and EPROM that contain stored data programmed to provide the various functions of the board.

The two speech ROMs enable the user to link words consisting of numbers and letters of the alphabet, assorted useful nouns, verbs, tones and silence durations into phrases

and sentences. The speech quality reproduced is claimed to be very realistic, even sounding much like the original person's voice.

The Digitalker is claimed to have the unique function of reproducing inflection and intonation of the original speech, not just the words spoken; the speaker is even said to be clearly recognisable. This feature is regarded as important in applications where the general public is listening to speech produced by the system — in telecommunications, instruments, control systems, appliances, and even in toys and games and car dashboards!

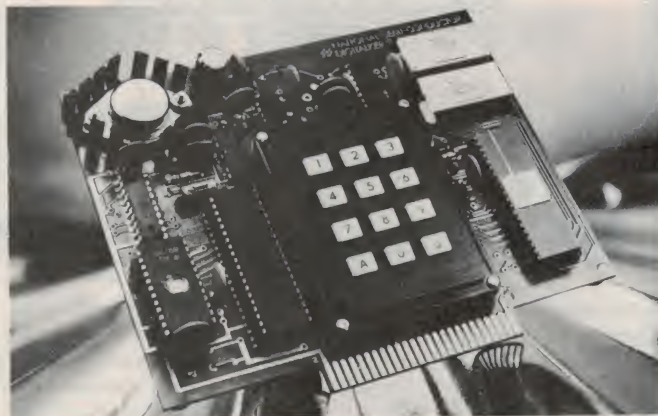Contact National Semiconductor Australia Pty Ltd, cnr. Stud Rd and Mountain Highway, Bayswater Vic. 3153, (03)729-6333, for more information.



Crusading Computercamp

May 9-16 1981 has been scheduled for the third Computercamp, where high school students from Years 10-12 can learn to program computers and computer applications.

Computers of the table-top variety have been made available in various computer houses and educational institutions, and in the past some students have even brought along their own machines.

Newcomers to computing are taught how to program in BASIC in a series of graded exercises. After only one week's camp some students have been able to produce quite sophisticated programs, such as motor trajectories, dodging of random land mines, Hammurabi, and many others.

The camp, run by the Crusader Union of NSW, has a Christian

emphasis and seeks to present the Christian message in an environment which is up to date with the latest technology and will also allow students to pursue an interesting and challenging activity.

Set in a bushland site at Galston, the camp also provides for such activities as outdoor games, hikes and barbecues. Numbers will be limited to 40 (possibly 20 boys and 20 girls), and 13 of last year's campers have already reapplied. The camp caters for all grades from beginner to expert.

Enquiries should be directed to Mr A. Potter, (02)95-6926.



Z80 and Pascal-100 marry on S100 buss

The Pascal-100, a new two-board central processing unit, combines a Z80-type microprocessor and Western Digital's Pascal Microengine to yield five to ten times faster execution times than a Pascal-programmed Z80 alone.

The CPU is compatible with the S100 computer buss and, according to its developers, Digicom Research Inc, Ithaca, New York, may be the first 16-bit microengine to be combined with another microprocessor — in this case an 8-bit unit.

A key advantage of the dual-

processor system is compatibility with existing applications software written for 8-bit Z80- or 8080-based systems or those using the CP/M operating system, as well as with new software like UCSD Pascal, which accesses the 16-bit processor's larger address space.

The Pascal-100 costs US\$1485.

Low cost Commodore

Trying to bridge the gap between the hobbyist and small-business computers, Commodore Business Machines introduced a US\$300 colour graphics computer at the January US Consumer Electronics Show.


Called the VIC 20, it contains a video interface chip that allows it to display material on an ordinary TV set through an external RF modulator. However, the display is limited to 23 lines of 22 characters each.

The VIC 20 uses Pet BASIC.

RIE ROD IRVING ELECTRONICS

425 HIGH ST., NORTHCOTE

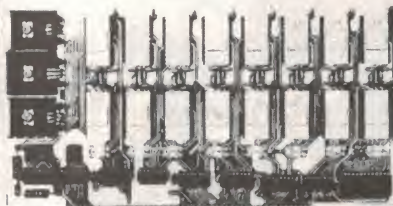**S100 COMPUTER PRODUCTS
16K EPROM CARD-S 100 BUSS**



**\$89.50
KIT**

**FIRST TIME OFFERED!
BLANK PC BOARD - \$39**

USES 2708's!


Thousands of personal and business systems around the world use this board with complete satisfaction. Puts 16K of software on line at **ALL TIMES!** Kit features a top quality soldermasked and silk-screened PC board and first run parts and sockets. Any number of EPROM locations may be disabled to avoid any memory conflicts. Fully buffered and has WAIT STATE capabilities.

**OUR 450 NS 2708'S
ARE \$8.95 EA. WITH
PURCHASE OF KIT**

**ASSEMBLED
AND FULLY TESTED
ADD \$36**

16K STATIC RAM KIT-S 100 BUSS

**KIT \$249
A&T \$279**

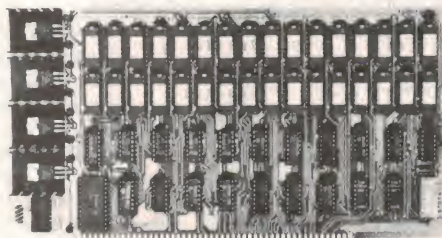

KIT FEATURES

1. Addressable as four separate 4K Blocks
2. ON BOARD BANK SELECT circuitry (Cromemco Standard!) Allows up to 512K on line!
3. Uses 2114 (450NS) 4K Static Rams.
4. ON BOARD SELECTABLE WAIT STATES.
5. Double sided PC Board, with solder mask and silk screened layout. Gold plated contact fingers.
6. All address and data lines fully buffered
7. Kit includes ALL parts and sockets
8. PHANTOM is jumpered to PIN 67
9. LOW POWER under 1.5 amps TYPICAL from the +8 Volt Buss
10. Blank PC Board can be populated as any multiple of 4K.

**BLANK PC BOARD W/DATA \$49
LOW PROFILE SOCKET SET \$19
SUPPORT IC'S & CAPS \$27
ASSEMBLED & TESTED-ADD \$30**

**OUR #1 SELLING
RAM BOARD!**

ITOH Model 8300 PRINTER. \$810 plus 15 percent sales tax.

This 80-column printer provides quiet operation, making it suitable for use in offices, classrooms and homes. Specifications include 125 cps, 60 lines per minute, paper loading from bottom or rear and Centronics-compatible parallel interface. A bi-directional, dot matrix impact printer with a print head designed for 100 percent duty operation, assuring a print life that exceeds 100 million characters. The precision sprocket-fed mechanism permits printing forms from 4 1/2 to 9 1/2 inches wide. A 96 ASCII character set prints in upper and lower case with the added capability of producing double-width fonts in bold face. The vertical format unit provides preprogrammed/programmable tab positions, top of form and bottom of form for complete formatting capabilities.

ETI636 7-SLOT MOTHERBOARD WITH ACTIVE TERMINATION

Kit of Parts \$79.00. Assembled and tested \$105.99 (inc. tax), RITRON COMPUTER GRADE POWER SUPPLY: 5V Reg, 10A, 16V Unreg. Kit of parts \$79.95 inc. tax. A&T \$99.95 inc. tax. Write for list of other power supplies. Tax free prices also available.

JUST WRAP KIT — JWK-6 \$39.50.

50ft ea. blue, white, red, yellow wire. Just Wrap Tool. Unwrap Tool

Please debit my Bankcard
Bankcard No.
Expiry Date
Name
Signature

ETI5/81

**Australia's first
under \$300 COMPUTER..**

Sinclair ZX80

FEATURES:


Includes leads etc Basic on board in PROM unique basic interpreter affords single key functions up to 26 string handling powerful editor high resolution graphics. All documentation included single ROM contains basic interpreter cha gen, operating system and monitor less RAM required due to large PROM expandable to 16K small compact size connect your TV direct and cassette recorder and you're away.



\$295

**INCL ZX80 BASIC
MANUAL**

32K S-100 EPROM CARD **NEW!**

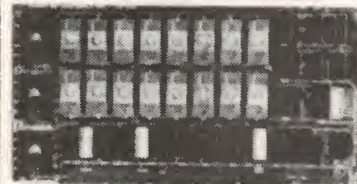

\$99.95

**KIT USES 2716
Blank PC Boards — \$45
ASSEMBLED & TESTED
ADD \$30**

KIT FEATURES:

1. Uses +5V only 2716 (2Kx8) EPROM's
2. Allows up to 32K of software on line.
3. IEEE S-100 Compatible.
4. Addressable as two independent 16K blocks.
5. Cromemco extended or Northstar bank select.
6. On board wait state circuitry if needed.
7. Any or all EPROM locations can be disabled.
8. Double sided PC board solder masked silk-screened.
9. Gold plated contact fingers.
10. Unselected EPROM's automatically powered down for low power.
11. Fully buffered and bypassed.
12. Easy and quick to assemble.

SPECIAL: 2716 EPROM's (450 NS) are \$11 ea. with above kit.

16K STATIC RAM SS-50 BUS


PRICE CUT!

\$229

**FULLY STATIC
AT DYNAMIC
PRICES**

**FOR SWTPC
6800 BUS!**

**ASSEMBLED AND
TESTED — \$30**

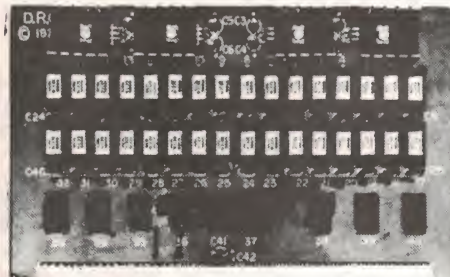

KIT FEATURES

1. Addressable or 16K boundaries
2. Uses 2114 Static Ram
3. Runs at full speed
4. Double sided PC Board, solder mask and silk-screened layout. Gold fingers
5. All parts and sockets included.
6. Low power under 1.5 Amps Typical

BLANK PC BOARD — \$45 COMPLETE SOCKET SET — \$19 SUPPORT IC'S AND CAPS — \$45

AVAILABLE AGAIN

- 16K Dynamic Ram Board
- Fully Expandable to 64K
- Assembled, tested and guaranteed
- S100 compatible

16K Dynamic RAM, Board assembled and tested: Special \$269 plus tax (2mHz), \$299 plus tax (4mHz). This must be the best offer available on quality tested dynamic RAM Boards.

32K Assembled and tested \$309 plus tax (2mHz); \$339 plus tax (4mHz).
48K Assembled and tested \$349 plus tax (2mHz); \$379 plus tax (4mHz).
64K Assembled and tested \$389 plus tax (2mHz); \$419 plus tax (4mHz).

General enquiries (03) 489-8131. Mail order enquiries (03) 481-1436. Ritronics Wholesale (03) 489-7099.

Prices current till June 7, 1981. Heavier items add additional postage. Extra heavy items sent Comet freight on. Prices subject to change without notice. Send 60c and SAE for free catalogues. MAIL ORDERS PO Box 135, Northcote, Vic 3070. Minimum pack and post \$1.

ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE VICTORIA. Ph. (03) 489 8131.

NEW PRODUCTS



JUST WRAP

- 30 AWG wire
- 0.025" square posts
- Daisy chain or point-to-point
- Built-in cut off
- Includes 50 ft. wire
- No stripping or slitting required—just wrap

Part No.	Wire Color	Price
JW-1-B	Blue	\$24.99
JW-1-W	White	24.99
JW-1-Y	Yellow	24.99
JW-1-R	Red	24.99

JUST WRAP Replacement Wire

Part No.	Color	50 ft. roll	Price
R-JW-B	Blue	50 ft. roll	\$4.99
R-JW-W	White	50 ft. roll	4.99
R-JW-Y	Yellow	50 ft. roll	4.99
R-JW-R	Red	50 ft. roll	4.99

SCOTCHCAL FRONT PANELS FOR ETI & EA PROJECTS:

ETI 452 Guitar Practice Amp	\$4.80
Series 4000 Any colour	\$12.50
MOVING Coil Pre Amp	\$2.00
577 Power Supply	\$2.00
455 Loud speaker protector	\$2.70
Variable power supply	\$2.70
Linear ohmmeter	\$2.50
Muscle activity meter scale	\$1.40
ETI 576 Electromyogram	\$2.80
561 Metal Detector	\$2.50
EA Capacitance meter	\$3.50
EA Flash exposure meter	\$4.25
EA Sound triggered flash	\$3.50
EA Slave flash	\$1.20
EA Playmaster graphic analyser	\$8.50
EA Metal Detector 79md9	\$3.90
EA Pulse generator	\$4.80
EA Square wave oscillator	\$2.50
EA RF Z Bridge	\$3.25
EA Thyristor tester	\$2.40
EA Quartz frequency ref	\$2.70
EA Multi monitor	\$1.90
EA Experimenters Supply	\$2.80
EA Quiz master	\$3.70
EA Variable wiper delay	\$1.10
EA Playmate stereo Amp	\$4.50

ALL FRONT PANELS AVAILABLE FROM DAY OF RELEASE OF MAGAZINES WHEN ORDERING FRONT PANELS. SPECIFY COLOUR OF LETTERING FIRST. THEN COLOUR OF BACKGROUND

10 TURN POTENTIOMETERS

Stock resistance values

50R, 100R, 200R,
500R, 1K, 2K, 5K,
10K, 20K, 50K,
100K

Spectrol model 534 1/4" shaft.
Price 1—9 \$8.50
10 + values may be mixed \$7.90

EPROM PROGRAMMER KIT

Kit of parts as featured in Electronics Australia July, 1980. Programs 2708, 2716 and 2532. Use with TRS80, Sorcerer, and Compucolor. Kit does not include connector from the programmer to computer.
Complete Kit \$72.49
Kit without case \$59.99
Pack and post \$2.50

DIG CAPACITANCE METER

Kit of parts featured in Electronics Australia March, 1980. Four digits.
Complete Kit \$52.49
Kit without case \$39.99
Pack and post \$2.50


COMPONENTS

4116 RAMS	\$3.00
2114 RAMS	2.90
2708 EPROM	6.90
741's 10 up	2.50
555's 10 up	2.90
BD139 10 up	5.50
BD140 10 up	5.50
SC141D 10 up	11.00
SC151D 10 up	21.10
RED LEDS 10 up	1.40
RED LEDS 100 up	11.00
YELLOW LEDS 10 up	2.30
8 PIN I/C SKTS 10 up	2.00
BC548	0.15 ea
BC549	0.19 ea
MJ802	3.60
6.800/50V CAPS (LUG)	4.50
5.600/40V CAPS (PCB)	1.90

KITS & CIRCUIT BOARDS

ETI SERIES 4000 AMP

- Complete Kit \$199.00
- Quality front panel to suit above 10.90
- ETI 470 kit of parts 22.50
- ETI 480 kit of parts 100w (incl bracket) 19.75
- ETI 470 PS kit of parts 19.50 (includes relay, not transformer)
- Transformer to suit 22.90
- ETI 471 pre-amp 45.50
- ETI 585R ultra sonic RX 15.95
- ETI 585T ultra sonic TX 8.95
- EA 79 SF9 sound flash trigger 15.00
- All parts available for DREAM computer project
- P C B's (all quality fibreglass boards)
- ETI 574 disco strobe 2.80
- ETI 549A metal detector 2.75
- DREAM circuit board 10.90

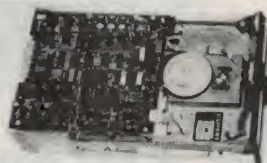

SCHUGART SA 400

5in Minifloppy Drive
\$399.00 Tax Inc
\$347.00 ex

RITRON COMPUTER GRADE P/S
+5V reg 10a 16V unreg @ 1A
KIT \$79.95 inc
Built and tested \$99.50

ETI636 MOTHERBOARD

7 Slot Motherboard \$90.00
Built and Tested \$120.00
ACTIVELY TERMINATED

INTERSIL LCD 3 1/2 DIGIT PANEL METER KITS

Build a working DPM in 1/2-hour with these complete evaluation kits. Test these new parts for yourself with intersil's low cost prototyping kits complete with A/D converter and LCD display (for the 7106) or LED display (for the 7107). Kits provide all materials including PC board, for a functioning panel meter ICL7106EV (LCD)

COMPUTER COMPONENTS


Attention Sorcerer & TRS 80 owners. Memory expansion kits available. We also offer full service on the popular computer projects and systems.

SPECIAL 4116 RAM OFFER
8 OFF PRIME SPEC 4116 I/Cs \$23.00
16 4116s for \$40.00

STATIC RAM KIT 16K S-100
2114 \$2.90; 2716 \$11.00; 2708 \$6.90

DIP PLUGS

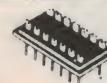Ideal for use with flat ribbon cable or to mount components on
14 pin \$1.20
16 pin \$1.40



24 pin \$1.20

COMPUTER COOLING FANS

Muffin fan 4 1/2" square
110V \$39.50
240V \$26.50

Range of larger fans available. Send for details

POWER TRANSFORMERS

SPECIALLY DESIGNED FOR MICROCOMPUTERS

- Good regulation electrostatic shield
- RI 810
8V @ 10A 2 x 15V @ 1A \$24.50
- RI 820 8V @ 20A 15V @ 1A \$35.50
15V @ 3A

20 TURN CERMET TRIM POT



SPECTROL 43P ACTUAL SIZE

STOCK RESISTANCE VALUES
10R, 20R, 50R, 100R, 200R, 500R, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 200K, 500K, 1M, 2M.
1—9 \$1.40
10—99 \$1.30
100 \$1.20
Values may be mixed.

Hexadecimal Keypad

\$24.50/each



19-key pad includes 1—10 keys ABCDEF and 2 optional keys and a shift key.

Ideal for dream project

MULTIDIALS



Dials to suit 10 T Pots
Model 21 1 8" dia \$16.50
Model 16 9" dia \$12.50
Model 18 1" x 1.75" dia \$20.60

P.C. EDGE CONNECTORS



\$100 gold plated wire wrap \$8.50
\$100 solder tail \$6.90
D2 Motorola bus
43/B6 solder tail \$8.50
43/B6 gold plated wire wrap \$10.50

HAVE YOU BUILT A DREAM YET!

ELECTRONIC AUSTRALIA MICROCOMPUTER PROJECT

Kit for main board (including programme 2708) \$109.00
Also available re-designed
6802 PCB \$11.90
PCB (Fibre glass) only \$10.90
2708 programmed \$15.50
Key Pad 19 Keys \$24.50
Kit (less key pad) \$94.00
PCB for power supply \$3.50

HEAVIER ITEMS ADD ADDITIONAL POSTAGE EXTRA HEAVY ITEMS SENT COMET FREIGHT ON
PRICES SUBJECT TO CHANGE WITHOUT NOTICE. SEND 60c & SAE FOR FREE CATALOGUE

MAIL ORDERS: PO BOX 135, NORTHCOTE, VIC 3070. MIN PACK & POST \$1.00

Print-out

In 1981, it's the ZX81 !

Sinclair Research has done it again — only this time around, a little more refined. In April, their newest 'personal' computer hit the market — the amazing ZX81.

This new machine is a much-upgraded version of the ZX80, incorporating an 8K BASIC ROM, higher speed Z80A processor and using a mere four chips compared to the ZX80's 21!

The ZX81 retains the one-touch key word entry feature of the ZX80 plus the graph-drawing and display facilities. The ZX81 will do animated graphics, though, according to the information from Sinclair Research. It also includes a 'randomise' function (as per the ZX80) which is said to be useful for games amongst other things. With the ZX81 you can LOAD and SAVE named programs on cassette.

The ZX81 is priced at around STG£70, which probably translates to \$200 here.

But there's more! Sinclair has announced they will have their long-awaited ZX Printer available sometime around mid-year for a price around STG£50. The ZX81 can drive it directly, while you'll need the 8K drop-in BASIC ROM in your ZX80 to drive the ZX printer.

We await the arrival of these goodies with a great deal of interest.



The Sinclair ZX Printer, designed for use with the ZX81, offers full alpha-numerics across 32 columns and highly sophisticated graphics. A COPY command prints out exactly what's on the TV screen.

APF 1M-1 for Australia

The Radio Parts Group of Melbourne and Calculator Discounts, also of Melbourne, are the joint Australian importers of this little four-colour wonder that comes from Hong Kong.

The APF 1M-1 has already taken on very well in the American market, and for the price of \$995.00 (including sales tax) should do very well in Australia; it is certainly some of the best value for money seen to date.

For your \$995.00 you get:

MP 1000 microprocessor programmable TV game. Plays on black and white or colour TV. Has two remote hand-held controls with keyboards and joysticks for various types of games.

MPA10 computer module companion. Converts MP-1000 to full user programmable personal computer. Full typewriter keyboard, cassette

deck. We hear that those clever Chinese have solved all the loading problems sometimes associated with the low end of the computer market. **TV Monitor.** A 13-inch colour unit that gives excellent colour resolution for graphics and games.

Probably the best feature of this new computer is that it can be added to with a number of peripherals. Peripherals available to date include:

BB-1 expansion unit with printer interface.

80-column printer (approx. \$575).

BB-s expansion unit with mini-floppy interface.

R-8K RAM memory expansion.

D100 disk drives.

All these peripherals are of moderate price, and a complete system is available for use at schools and in business for \$3049.

Watch ETI for coming review — we're looking forward to getting our hands on this one.

64K CMOS static RAM a first from Toshiba

Toshiba may be the first chip maker to introduce a complementary MOS 64K static random-access memory.

Now in development is an 8K-by-8-bit 28-pin device with cells that measure 15 by 19 micrometres on a 4.6 by 6.55 mm (46 700 sq. mil.) die.

Power dissipation is 50 mW active and just 100 microwatts on standby. Wafer steppers and 2-micrometre features have been used for the first pass on the RAM, which has no redundant elements.

The 64K static RAM is over a year away, but this year the Japanese company will supply samples of the 8049 single-chip microcomputer, also in CMOS. With 3-micrometre rules, that chip will measure 22.8 mm² (35 350 sq. mil.) and draw 50 mW for active operation and only 50 to 500 microwatts while idling.

Later this year, Toshiba will also be in production with a 64K erasable programmable read-only memory — in n-MOS — with a pin-out that matches Intel's.

New store for AED

AED Microcomputer Products recently announced the opening of their new store at 130 Military Road, Guildford NSW 2161.

This new store is only seven doors away from their old establishment, but they say it is eight times larger and boasts a large, airy showroom, administration offices, workshops, development laboratories, design offices and a seminar room.

AED handle what they believe to be the largest range of S100, CP/M and related products in Australia. Complete computers range from the Sorcerer to 'Rolls Royce' 4 MHz S100 machines. Epson Base 2 and Iton dot matrix printers are available, together with TEK and the NEC Spinwriter daisy wheel units.

AED are S100 and CP/M specialists, from complete computers through add-on disks, S100 cards, etc. to prototype equipment and parts. Available software covers all areas of microcomputing, including word processing and business applications.

A full range of magazines is always available, and special parts or software, not normally available in Australia, can be imported to the customer's order.

For further information contact Acoustic Electronic Developments Pty Ltd on (02)632-6301 or (02)632-4966.

New floppy disk system

AED Microcomputer Products of Guildford, NSW, have just released a new floppy disk system for S100 computers.

Priced about midway between the usual single and double-sided systems, AEDisk is a double-sided, double density 8" system using YE data drives. These are housed in a polished timber and vinyl-coated steel case that matches the "VN-Serial" terminal.

The controller used is the latest version of the tried and proven Morrow (MR IEEE S100) disk jockey 20. Drives and controllers are available separately, although the complete package includes CP/M 2.2, and a special version is also available at no extra charge.

Capacity per disk is a maximum of 1.2M (DS, DD), but the system will still handle single-sided, single

density disks, for example for software installation, etc. Both single and dual drive systems are in fact available; in the latter case the drives may be supplied in separate cases or in a single case, either side by side or stacked.

Up to four floppy drives can be accommodated on the one controller, and the system integrates perfectly with the Morrow 10M and 26M hard drive systems.

For information on these and other S100, CP/M and related products, contact Acoustic Electronic Developments Pty Ltd, 130 Military Road, Guildford NSW 2161. Phone (02) 632-6301, (02) 632-4966.



Bubble cassettes

Although at present more costly than other magnetic media, bubble memory technology offers microprocessor-based systems a unique combination of non-volatility, long-term reliability, and data integrity, even in harsh environments. Now National Semiconductor is adding several other dimensions to the technology with the development of a magnetic bubble memory cassette system.

Designated Bublset, the new system consists of a read-write unit, less than 3 by 4 by 6 in. in size, that automatically accepts magnetic bubble cassettes ranging from about 100K to 1M in capacity.

According to Frank Stempiski, product marketing manager for magnetic bubble products, the system was developed in response to the need for a removable, non-volatile solid-state memory in such applications as numerical machine-tool control, data loggers and recorders, portable terminals and intelligent test equipment, and military systems in harsh or dirty environments.

Bubble-based storage systems have no moving parts and thus are not subject to the mechanical failures of tape and disk storage.

The Bublset's temperature range of -20° to +70°C extends well below that of most competitive media, which are limited to 0°C, Stempiski states. The lower range is needed on oil-well data-logging systems and on power-demand meters located outside buildings, as well as in many shipboard and airborne applications, such as flight-management recording systems.

The Bublset cassette has no function or coil drivers and no sense amplifiers — it contains only the

bubble memory and temperature-sensing circuitry. "The design avoids the data loss typically due to powering up or down or from removing a magnetic tape cassette during operation," says George Reyling Jr., manager for magnetic bubble memory systems.

The bubble memory controller detects and corrects errors automatically. It has built-in self-test features as well as an automatic write-protection feature.

The system comes with two selectable ports — an RS-232-C serial interface and a byte-wide parallel port for interfacing with microprocessor-based systems. Its +5 V and +12 V power supply requirements and the low power consumption typical of bubble memory technology increase its suitability for portable applications, Stempiski notes.

National will make the Bublset available in the general marketplace in the second half of this year. For industrial-grade versions, the Bublset will be priced in the US\$1000 range in small quantities. The price includes the read/write system and a minimum-capacity (100K) bubble memory cassette. Prices of the cassettes will vary with capacity. Militarised and more rugged versions will be available next year.



CISA

The one-stop Microcomputer Shop for total service to TRS-80* users

*TRS-80 is a registered Trademark of Tandy Radio-Shack

NOW AVAILABLE CISA DISK PASCAL

Executes up to 60 times faster than DISK BASIC.
HAS FULL DISK I/O FEATURES and many facilities not available on languages costing many hundreds of dollars.
DO NOT CONFUSE WITH CHEAP CASSETTE-BASED 'TINY' PASCALS.

Systems overlays and developments will be available to registered users at a nominal charge.
Includes the fastest and most powerful screen editor we have seen.
Will edit PENCIL, SCRIPSIT and ASCII files.
PASCAL is much easier to manipulate than ASSEMBLY, and is practically as efficient as it compiles into a true-optimized machine-code.

More efficient than currently available BASIC COMPILERS selling for twice the price.
We honestly believe that this Australian written PASCAL to be the fastest, most sophisticated and powerful high-level language available anywhere in the world for the TRS-80 Model I.

RELEASE 1.0 \$99.00

(numbered copies to registered single-users only)

Early purchasers will be offered upgrades at no cost penalty.

CISA HARDWARE AND MODS

HEAVY DUTY POWER LINE FILTER
Absolutely essential for enthusiast and business user.\$65.00

CISA LIGHT PEN AND DEMO SOFTWARE
Don't be fooled, this includes both. Compare prices elsewhere\$19.95

CISA DATA DIGITIZER, Vers. 2
Now accepts most types of cassette player. Essential for use with HISPED. No internal modifications\$57.50

16K UPGRADE KITS
Both keyboard and i/face.
Kit\$75.00
Fitting Charge.....\$20.00

GREEN PHOSPHOR TUBES
Not a cheap plastic overlay. We fit a genuine professional standard VDU tube with 1/4" armoured front glass panel (sorry no kits).....\$99.00
(Can fit to all current VDU's and monitors.)

CISA RS232 PRINTER-DRIVER
Operate any RS232 or 20MA serial printer with this Australian made unit. Includes software.....\$54.75

VIDEO STABILISER CRYSTAL
Totally removes shimmer and wobble on your video. Highly recommended for Green Tube.
Kit\$19.95
Fitted\$39.95

TRS-80 SOFTWARE

AIR TRAFFIC CONTROLLER L2/16K
Supervise a large area of air-space in real time.....\$9.95

SPACE GAMES L2/16K
Five brilliant games in the classic space series.....\$14.50

STRATEGY GAMES L2/16K
Four fascinating games to test your judgement and logic.....\$14.50

ADVENTURE SERIES L2/16K
Adventure-1, The Count, Voodoo Castle.
Each.....\$14.95
Z-CHESS

A fast and exacting opponent. 6 levels of play.
L2/16K.....\$19.95
Disk 32K.....\$24.95

DISASSEMBLER IN BASIC L2/16K only
Disassembles ROM and high memory machine language routines.....\$9.95

TAPECHECK L2 16K plus
Checks and verifies every millimetre of a cassette tape. Also useful as cassette I/O diagnostic\$9.95

FLOPPY DOCTOR 32K/DISK
This is the most comprehensive and exacting series of memory and disk I/O tests we have seen.

THE SIMUTEK SERIES.....each \$14.95
1. Invasion Warg, Star Wars, Space Target, Saucers. Full of action and surprises!

2. Checkers, Poker Face, Tanglemania, The Psychic, Word Scramble. Games of skill and logic.

3. Poetry, Electric Artist, Galactic Battle, Wordmania, Air Command. A good value mix of game type.

4. Life, Planetary Lander, Pharaoh, Robot Hunter, Greed. A more exacting package of games and amusements.

5. Super Horseace, Maze-Mouse, Amobic Killer, Logic, Submariner. 5 games to test your skill and logic.

6. 20 Home Finance Programs. Every calculation you will ever need for your building society or hire purchase deposits or loans.

7. Backgammon, Speed Reading, Yhatzee PT109. Your favourite historical games now on the TRS-80.

These seven packages are excellent value for any TRS-80 owner.....\$14.95 ea.
Plus many, many more.

BASIC EXTENSIONS
Single step through a BASIC programme. Enable/disable BREAK key, plus many other de-bugging aids.....\$9.95

NEW CISA SOFTWARE

BASIC EXTENSIONS by G.J. Howe.
Absolutely essential for every BASIC Programmer, novice to professional. Single steps through every BASIC statement. Full HEX-ASCII memory dump. Enable/disable BREAK key. 2-kit SCREEN-PRINT command dumps video to printer.....\$9.95

MCMOM by M.J. Dinn of 80-Software.
MCMOM provides all the facilities needed to write, run, debug and save machine level programs. Single step through ROM, RAM indefinitely or until a pre-set break-point is reached. Displays all register contents at every step. Immediate switching to Z80 mnemonics display, if required. Many other features.
Level II 16-48K.....\$19.95

Disk version available soon.
Exclusive to CISA and authorised agents.

MICROPOLIS DRIVES FOR THE TRS-80*

For the enthusiast: 192K bytes per drive.

SINGLE 77 TRACK.....\$699.00

A professional disk drive for the business user:

TWIN 77 TRACK 385K.....\$1499.00

Both complete with heavy-duty case and inbuilt power supply and free dospatch to TRSDOS.

Requires cables — 2 drive \$30, 3 drive \$40, 4 drive \$50.

MIX 'N MATCH with any 35 or 40 track drive.
SHOP WHERE YOU CAN BE SURE OF SERVICE
BACK-UP AND YOUR WARRANTIES HONoured.
We copy 35 or 40 track disks onto 77 track disks for \$1.00 each plus the cost of the diskette.

CISA REPAIR, UPGRADE AND MAINTENANCE FACILITIES

Yes, we are now in a position to undertake any repair of any nature (except plastic cases) to any Tandy Model I or Model II equipment or any of our own peripherals. No fancy surcharges if you have any previously fitted mods.

CISA HIRES BOARD

This totally Australian designed and manufactured unit has many features which we truly claim are unique in the world. Every character is now programmable into a 6 x 12 grid, giving you the highest resolution of virtually any microcomputer. Includes full lower case driver to printer and video. Ends many hidden errors in BASIC lines. 90 days full guarantee parts and labour on your system if we install it.

HIRES BOARD.....\$225.00
Fitting.....\$25.00

System 80 version.....\$275.00
(As it is an extremely complex task to fit this to the System 80, no boards will be sold separately.)

Lower case is not fully implemented in the System 80 as the essential ingredients are just not there.

PHONE OR CALL AND BROWSE. TRADE ENQUIRIES INVITED

Trading Hours: 9am to 6pm Monday-Friday, 9am to 12.30pm Saturday.


All the above fine products are available at or can be ordered from:

NSW: SOUTH COAST COMPUTING SERVICES The Village Centre, 90 Worrige Street, Nowra, 2540. (044) 25-552. **CONQUEST ELECTRONICS** 212 Katoomba Street, Katoomba, 2780. (047) 82-2491. **ACT: COMPUTER WORLD** Shop G71, Woden Plaza, Canberra, 2601. (062) 81-1368. **COMPUTER BUSINESS AIDS** PO Box 99, Kambah, 2902. **QLD: SOFTWARE 80** 200 Moggill Road, Taringa, 4000. (07) 371-6996. **UNIVERSAL SERVICES** Cunningham Street, Dalby, 4405. (074) 23-228. **ALLIANCE COMPUTER PRODUCTS** 11 Cracknell Road, Chardons Corner, Annerley, 4000. (07) 392-1152. **OUTBACK ELECTRONICS** 71 Barkley Highway, Mt. Isa, 4825. (077) 43-3475. **TAS: H.S. ELECTRONICS PTY. LTD.** 104 Charles Street, Launceston, 7502. **WA: WACB RADIO CENTRE** 129 Fitzgerald Street, Perth, 6000. (09) 328-6254. **VIC: W.D. LESLIE PTY. LTD.** 363-375 Raymond Street, Sale, 3850. (051) 44-267. **NT: RADIO PARTS (DARWIN) PTY. LTD.** PO Box 515, Darwin, 5790. (089) 818-508.

CISA MICROCOMPUTING PTY. LTD.

159 KENT STREET, SYDNEY, NSW 2000. PHONE: (02) 241-1813.

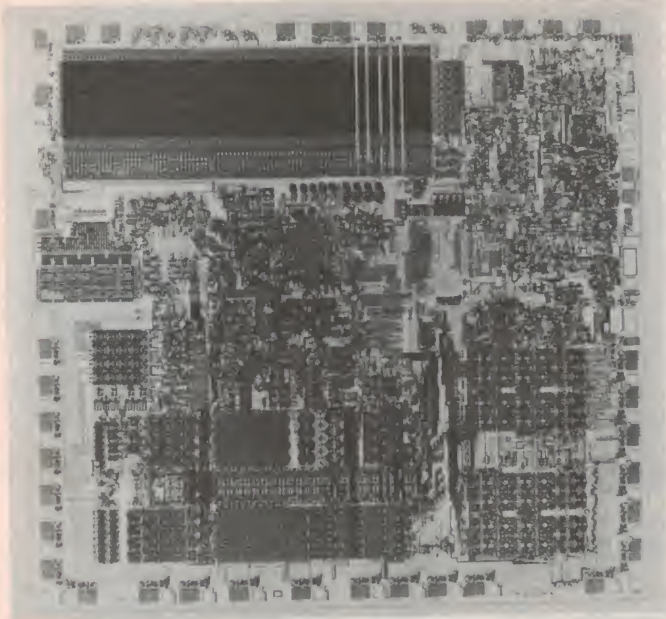Orders under \$100 add \$2.00 p and p. Over \$100 post free. For repairs and mods to systems — send by carrier — you pay, we pay return carriage.



National Semiconductors unveils 16-bit micro


The first wafers of the NS16032 microprocessor were produced in December last year at National's Utah factory, and evaluation and debugging of the complex 16-bit micro are now being carried out.

According to National, the 16000 family offers virtual memory, high level language support, symmetric register set, memory-to-memory operations, powerful addressing modes, numerous data types, symmetric instruction set, memory management and large, uniform addressing, plus unique modular software support and a slave processing facility.

The family supports a wide variety of system configurations, extending from a minimum low-cost system to a powerful 16M system. It will be

fully supported by a complete family of development systems, compilers, operating systems and board level products.

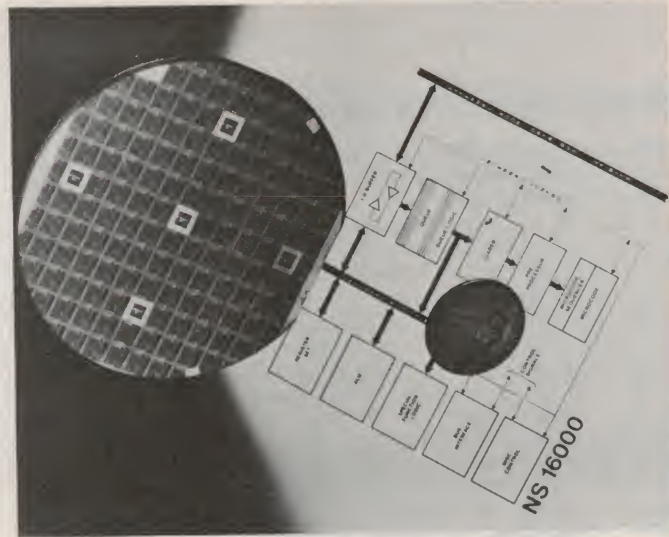National also announced an agreement with Fairchild Camera and Instrument Corporation to second source the NS16000 family. Under the agreement there will be an exchange of mask-making data for the NS16032 CPU and systems-oriented devices with data on Fairchild's dedicated peripheral circuits.



Here's lead in your pencil!

An 'electronic blackboard' that will allow users to write directly on special pressure-sensitive screens has been developed by Sanyo Electric Inc., a US division of the Japanese company.

The blackboard employs a light screen permits the user to select pen and a screen. When the light from 16 colours by touching the pen touches the screen, a signal is sent to an internal microprocessor which generates a video display.

Thus you draw on the screen in the same manner as you would draw on a blackboard.

A display at the bottom of the

The completed drawing can be transferred to a floppy disk for storage and future use. A printer can be attached to provide hard copy.

Powerful desktop computer system

The DSD 880 Winchester/floppy disk storage system can be used to configure a compact and powerful desktop computer system in partnership with the DEC VT-103 intelligent terminal, according to its suppliers, Anderson Digital Equipment.

The DSD 880 is said to be fully compatible with DEC hardware, software and media, and can be used with any system based on the popular DEC LSI-11 processor.

Ideal for any application where space is at a premium, the DSD 880 combines an eight-inch Winchester and an eight-inch floppy in a compact 5¼" high package.

The Winchester provides 7.8M of formatted capacity; the floppy gives an additional 1M and accepts all combinations of single-sided/double-sided and DEC single density/double density diskettes. In most applications the Winchester is the primary on-line storage due to its higher capacity and per-

formance, and low-noise operation. Users may obtain software and diagnostics directly from DEC on floppy disks.

DSD 880 users can move readily from one DEC operating system to another, and can expect to remain compatible with future releases of DEC software. Developers of systems incorporating the DSD 880 can use DEC diagnostics for debugging.

The DSD 880 costs \$7450 in single quantities, and further information may be obtained from Anderson Digital Equipment Pty Ltd, P.O. Box 322, Mt Waverley Vic. 3149. (03)543-2077.

VDU to take Australia by storm?

The TVI-950, manufactured by Televideo and released in Australia by Anderson Digital Equipment, is confidently expected by them to take the Australian market by storm, as it is said to have done in the USA.

The detachable keyboard has 11 special function keys (22 functions with the shift key) that can be programmed to the user's requirements using 256 bytes of on-board RAM. In addition keys, key functions and even keyboard locations can be changed, and other features include advanced editing with wraparound, split screen with line lock, smooth scrolling, and a 25th status line.

Fifteen special characters for powerful line graphics are available as a standard.

The TVI-950 will sell at \$1595 plus tax for one-off, with quantity discounts available on request. Contact Anderson Digital Equipment Pty Ltd, P.O. Box 322, Mount Waverley Vic. 3149, (03)543-2077, for more information.

Super Text 2 for all those little Apples

Muse Software of Baltimore, USA, have announced the release of a new word processor, called Super Text 2, which is compatible with all species of Apple.

Super Text 2 displays either with the normal character set or with the set provided by the 'Dan Paymar Lower Case Adaptor', and according to Muse will enable anyone "to be writing, saving to disk and printing professional-quality copy within minutes of opening the manual". Later sections of the manual are said to teach the user to do tricks and variations on standard letters and files, and the system also has the capability of completing direct mathematical calculations, calculations on numbers in a file, column totals, etc, as well as normal word processor functions. Slave disks may also be copied, even if sectors of them have been damaged.

Muse will be providing add-on facilities to enable Super Text 2

users to have the Form Letter Module, Terminal Module, and the Virtual Memory Assembler.

Unlike most other word processors, the Super Text 2 uses the shift key to call upper case in the way a normal typewriter would; there is no need to use the 'escape' key to obtain upper case displays and printouts.

Seahorse Computers are offering the Super Text 2 for \$149, and if you wish to trade in your old word processor, they will give \$90 credit on a Super Text and \$50 on an Apple Writer, Easy Writer, or Apple Pie.

More details of the Super Text 2 are available from Seahorse Computers, P.O. Box 47, Camden NSW 2570, (046)66-6406, from whom Super Text and the Dan Paymar Lower Case Adaptor are also available ex-stock.

A rolling bubble gathers no MOS

Bubble memory shipments will increase 65% a year, from US\$18.4 million in 1980 to US\$100 million in 1983 and US\$226 million in 1985, according to Venture Development Corporation in the US.

First major applications have been in areas such as numerical control of machine tools, where dust and chemicals in the atmosphere make moving magnetic media unsuitable, and in portable terminals where resistance to shock is important.

Small computers and word processors will be increasingly important applications.

As prices of bubble memories decrease with larger volumes and more experience in producing them, the use of bubbles will shift from specialised areas such as adverse environments to more general memory applications.

New bubble units pose a threat to fixed head disk drives but not to Rockwell.

floppy disk systems. Fixed head disk drives will be displaced by bubbles when the price drops to 15 cents/Kbit in 1984, says the Corporation.


Meanwhile, Rockwell has dropped out of the bubble memory market. It is believed that Motorola's decision not to second-source Rockwell's 256K-bit bubble memory and instead produce its own 1M device was a serious setback to Rockwell.

The price erosion in semiconductor memory devices, particularly in 64K RAMs, slowed the development of the bubble memory market, according to Robert Anslow, EDD

world-wide sales director for

New address for Sorcerers

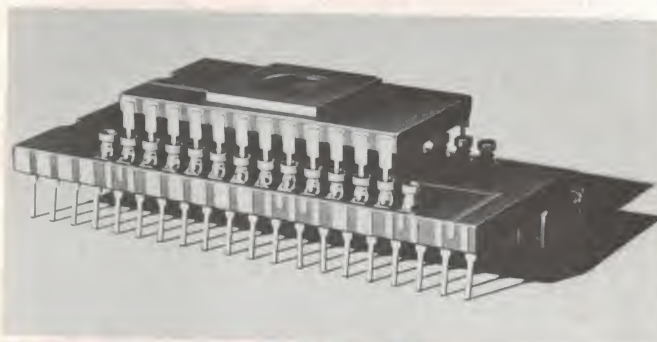The Sorcerer Users' Group in Victoria, which has been established for over two years and has a current membership of over 400, now has a new postal address. Contact them via The Secretary, Sorcerer Computer Users of Australia (SCUA), P.O. Box 144, Doncaster Vic. 3108.



Mostek's new piggyback processor, the MK38P70.

RAMs, chips and cables

Amtron Tyree recently released three new products designed to expand their computing range.

• The Mostek 'Bytewide' RAM was designed to be completely compatible with the most popular industry-standard ROMs and EPROMs, so that memory boards may be configured to accept any mixture of RAM, EPROM and/or ROM. By using PROM or EPROM devices to decode addresses and two wire jumpers per memory chip, a designer can now design a universal memory board upon which both page boundaries and memory type (RAM, ROM or EPROM) may be varied at will, according to Amtron Tyree. Mostek is also committed to compatibility between today's memories and future generation devices.

• The new Mostek MK38P70 can 'piggyback' any one of five popular EPROMs, producing a highly versatile single-chip microprocessor said to be very suitable for low-volume

Australian market conditions. The MK38P70 family features include: 1K, 2K or 4K of EPROM, programmable timer, external interrupts and single 5 V supply.

• The 57F series is a flat cable version of the well-known Ampenol 57 series micro ribbon connector. It is currently available in 36 and 50-way versions, with 14 and 24 to be coming soon. Features include positive spring, latches, 20 000 insertions and withdrawals, and simple and reliable termination to 0.05" flat cable. These connectors are interchangeable and intermateable with the 57 series solder or micro-pierce insulations displacement connectors for intercabinet or flat-to-round cable transitions.

Further information on all these products can be obtained from Amtron Tyree Pty Ltd, 176 Botany St, Waterloo NSW. (02)698-9666.

Zilog cuts price of Z8000

With the introduction of the Z8002 and Z8001 MPUs in plastic packages instead of ceramic DIP, Zilog has cut prices drastically.

The Z8002 will now be priced at US\$19.90 in quantities of 1000; formerly it was US\$45. The Z8001 MPU and the memory management unit (Z8010) is being offered as a kit in plastic packages at US\$49.50 each at the 1000-piece level, compared with a former price of US\$139. The ceramic prices for the Z8001 and Z8002 have not changed.

Zilog is aiming the Z8002, a non-segmented MPU which addresses 64K bytes of memory, at applica-

tions such as printer controllers. The Z8001, a segmented MPU addressing eight bytes of memory, is aimed at medium- to high-end performance applications.

When contacted for comment on Zilog's price reduction, the general manager for Intel's microprocessor operation said, "It is a belated move on their part to make the processors competitive with the 8086 and 8088." He disclosed that Intel is also planning to offer these two MPUs in plastic, and is reviewing its pricing on them.

MOST WANTED



INSTRUCTOR 80:

Ideal starting package. Uses DGZ80 CPU, DG640 VDU, RCA Keyboard and comes complete with manuals and programming course. S100 based system needs no special interface to expand to any configuration. Don't be fooled with single board imitations, the Instructor 80 is fully software supported with basic, assembler, games and even Pascal and CP/M!

IN-Z80-K INSTRUCTOR 80 KIT **\$399.00**

DGZ80 Z80/S100 SINGLE BOARD COMPUTER:

Most popular Z80/S100 SBC in Australia. Features Z80 CPU, PIO, CTC for powerful I/O and timing, 2K ROM/2K RAM on board, 2 or 4 MHz operation. With DGOS Monitor in ROM the DGZ80 needs only a keyboard and DG640 VDU for minimum system.

DG-Z80-2K 2MHZ DGZ80 KIT **\$199.00**

DG-OS-1.4-DGOS MONITOR IN ROM **\$40.00**

DG640 VISUAL DISPLAY UNIT:

This super functional S100 PCB is an industry standard. Generates 64 characters per line, 16 lines per page, full upper/lower case and graphics. Built in crystal time base locks onto TV sync. Watch out for outdated "El Cheapo" 32 character/upper case only displays, they just don't suit most software requirements...

DG-640-K DG640 KIT **\$149.50**

TCT PCG HIGH RESOLUTION GRAPHICS:

Need high resolution graphics and programmable characters? The TCT PCG option connects to the DG640 to produce 512x256 bit resolution. Supplied with StarWars and table tennis programs on cassette and has built in joy stick interfaces.

PCG KIT **\$140.00**

AT16K ECONOMY 16K STATIC MEMORY:

Just released, the AT16K uses proven 2114 static memory chips to produce a 16K block locatable ram module with write protect and bank select (port or switch controlled). AT16K is supplied burned-in and tested ready for years of trouble free service!

AT-16K-4A ASSEMBLED/TESTED AT16K (450NS) **\$199.00**

S100 MICROMODULES: AFFORDABLE, COMPATIBLE, EXPANDABLE...

TCT 16K BLOCK LOCATABLE RAM:

This versatile 16K ram module is configured in four independent 4K blocks each with write protect and independently locatable at any location in 64K address space. The board is fully socketed and includes dip switches for easy location.

TCT-16K-K TCT16K IN KIT FORM **\$209.00**

2650/S100 SINGLE BOARD COMPUTER

Released at last this top class design now brings the 2650 to the S100 bus. Feature laden board contains 2650 CPU, 8255 PPI, serial and parallel ports, on-board ram (to 4K), on-board rom and bank select facility to address up to 512K. The 2650/SBC is available in kit form or as a PCB with manual and control ROM.

SBC-2650-K 2650-SBC KIT WITH MANUAL **\$209.00**

SBC-2650-SK 2650-SBC PCB/MANUAL/ROM **\$80.00**

SCVT S100 SERIAL VIDEO TERMINAL

Described in EA Oct 1980, the SCVT uses the Thomson-CSF VDU Controller to produce this versatile serial terminal. Features on board UART with BAUD rate generator (50 to 1200), cassette interface, RS232 ASCII encoded keyboard to output to 64 characters/16 lines and attributes include reverse or flashing characters, cursor addressing and hardware scrolling. With a keyboard such as the Clare C70, and a suitable TV set, the SCVT becomes a cost effective "Dumb" terminal suitable for many microprocessor applications.

SCV-T100-K SCVT TERMINAL KIT **\$189.50**

Full product descriptions and specifications are detailed in our 1981 catalog (see ETI March 1981). Note that prices quoted include sales tax. Please add \$4.00 to cover packaging and registered postage.

APPLIED TECHNOLOGY -PTY. LTD.

MAIL ORDERS TO:

PO Box 355, Hornsby 2077.

Please add \$2.00 per order towards cost of post and packing.

AND NOW AT GOSFORD -


1 Debenham Road, West Gosford (behind the Pizza Hut) 043.24 2711

OFFICE/SHOWROOM

1a Pattison Avenue, Waitara 2077.

Hours: 9-5 Monday to Saturday

Telephone: 487 2711

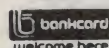

Are you going to let a Yank tell you how to run your Australian business?

Most computer ledger systems are designed for American businesses & tailored around American taxation. So why settle for a hand-me-down?



THE DICK SMITH GENERAL LEDGER WAS DESIGNED FOR AUSTRALIAN BUSINESSES *& suits SYSTEM 80 or TRS 80 computers with S-100 expansion*

There are numerous General Ledger Systems available in Australia today. Most are based on programs written in the USA for American businesses. It took Bob Petersen — ex EDP manager for Woolworths months of hard work to find the best advantages of every system and to incorporate them in this fabulous program suitable for small Australian businesses. To run the General Ledger, you require: System 80 computer, 32K, video monitor, expansion interface, disk drives, printer and cables.

2 program Disks and 1 Data Disk
with Comprehensive User Manual

All this for only


Credit terms available to approved applicants

\$299

Cat. X-3752

Compare these features

- Well-defined chart of accounts. General Ledger comes complete with 200 accounts which will suit most businesses and yet flexible enough so that accounts may be deleted, altered or new accounts added.
- Up to 1,975 accounts with 5 account groups and unlimited account sub-groups
- Up to 315 entries per session and 2,730 entries per month.
- Check digit security — computer generates a check digit so that typing errors for ledger entries are virtually impossible.
- Password security — 3 password levels to enable different access to records. Accounts can now be kept as confidential as you like.
- Batch posting for well-defined audit trails
- Automatic 'Out of Balance' detection.
- Automatic Entry Totalling.
- Automatic document balancing.
- Comprehensive manual complete with illustrations, working samples, reports and glossary — written for the person who knows nothing about computers or accounting.
- Reports generated — trial balance, profit and loss statement balance sheet, chart of accounts, posting summaries, transaction reports, account details. Titles may be provided for reports.
- Fully interactive with Accounts Payable. (Coming soon).

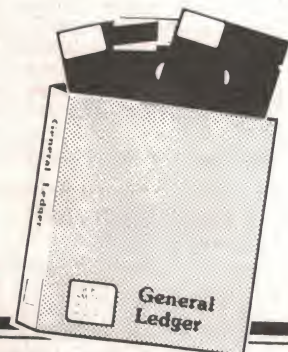

**DICK SMITH
Electronics**



**SEE OUR OTHER ADS FOR
FULL ADDRESS DETAILS**



MENSA COMPUTERS

Suite 3, 454 St. Kilda Road, Melbourne, 3004. Telephone: (03) 26-5683, 26-6150.

FINDEX, The Real Computer



THE WORLD'S FIRST PORTABLE MICROCOMPUTER

Battery or mains operated

RAM 48K to 2 megabytes, bubble memory to 2MB, gas plasma display, optional audio, printer, mass storage mini floppys to 800K bytes, hard disk to 195 megabytes, acoustic coupler, S-100 bus, battery optional, CPU with real time clock. For dynamic businessmen on the move. Ideal for real estate agents, insurance brokers and accountants.



Powerful, multi-purpose microcomputer systems.

BUSINESS SYSTEMS

Priced competitively from as low as \$45.00 p.w. lease cost including sales tax and software.

TYPICAL APPLICATIONS

Debtors ledger and statements, creditors ledger and remittances, general ledger and trial balance, order entry/invoicing, sales analysis, payroll/wages, enquiry, word processing, mailing, record keeping, ledger card, doctors office, real estate, agency accounting, hotel/motel accounting, branch office accounting.

Also:

Facilities management consulting.
Software and computer sales.
Computer data preparation.

INTRODUCING

MENSA G.F. 1000

BASIC SPECIFICATIONS

CPU 8080 and Z80 operating at 4MHZ. 64K bytes Dynamic RAM expandable to 2MB storage bytes of unformatted data on two double density drives. Optional external hard disk storage can be connected using the optional S-100 Bus. Floppy Disk. All modules mounted to base. CRT in a rigid aluminium frame. Disk Drive assemblies are mounted into special brackets for ease of servicing.

WINCHESTER DISK


26MB of Winchester Disk complete with controller and easy backup. Disk has special capacity to only back up files accessed during the last period. Disk operating system CP/M.

OPTIONAL SOFTWARE

FORTRAN, COBOL, BASIC.

Application packages. Extensive software development tools are available from leading software vendors, including software for the following applications: payroll, accounts receivable, accounts payable, inventory control, general ledger and word processing.

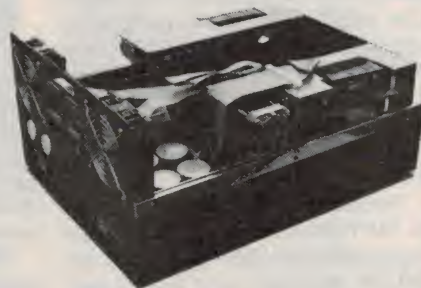Mensa computers provide a service network throughout Australia at major service centre locations to minimise response time to service calls. To ensure that equipment will operate at peak performance, engineers and technicians are trained to ensure the highest possible standard of service.




Want to get into microcomputing without boiling your brain cells or breaking the bank ?

Part 1

We often receive letters from readers that say "... I want to get into microcomputing but can't afford hundreds of dollars and don't have an engineering degree". When approached with this project, we knew that here was an answer. This project is not a 'toy' or anything like an 'evaluation kit', yet is inexpensive and simple to build and get going. It was designed by Hugh Anderson and developed for publication by Graeme Teesdale, both of whom hail from the land of the kiwi and the great white cloud.

SINCE MICROPROCESSORS appeared, the concept of having a personal computer to do one's bidding has firmly taken hold in many people's minds. Electronics enthusiasts generally have a different motivation in that they're interested in the technology as well as what it will do. But the price of getting involved is generally pretty high and the level of knowledge required up front is generally pretty high too. Whilst you can buy an up-and-running computer for around \$300 (the Sinclair ZX80), involvement with the hardware is minimal and many enthusiasts seek to build a computer from a kit. We've described computer projects in the past and it's possible to make up a functioning system from our ETI-680 CPU board with the addition of some peripheral hardware; the cost is around \$400 but this presents a barrier to many otherwise interested enthusiasts. There are other kits around, but the price is much the same or can extend to two or three times that.

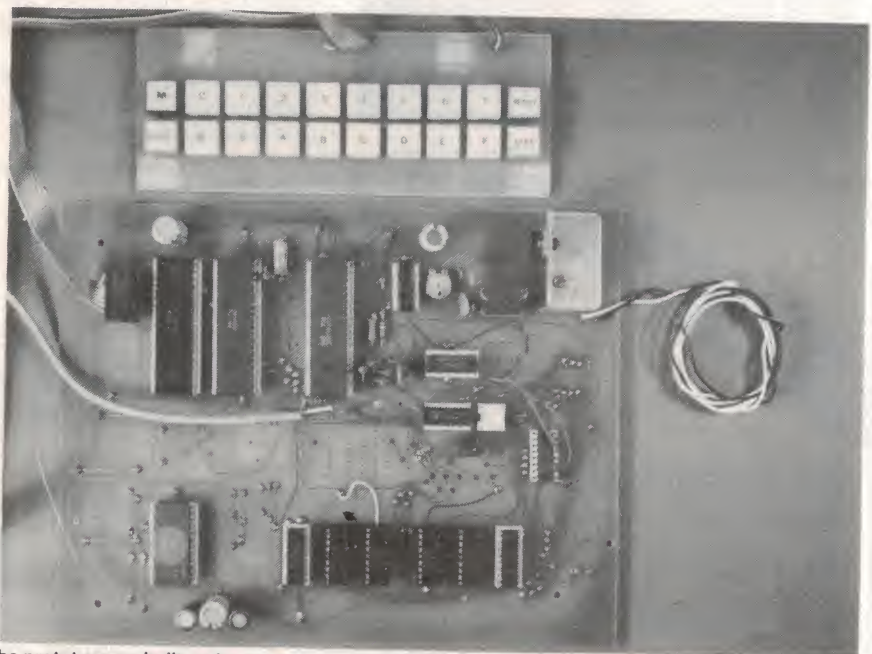The 'evaluation kits' marketed by various microprocessor manufacturers are a less expensive alternative, but are intended for engineers and technicians and a certain level of knowledge and experience is assumed in their presentation. They also have a number of other limitations that cause many enthusi-




The prototype we built up for evaluation, debugging and further development. At top is the re-arranged hex keyboard designed to make data and program entry easy — it's also great when playing games! The final unit has a somewhat larger pc board which includes an RF modulator.

asts to shy away from them.

This project is aimed at people wishing to make a start in the microprocessor field, but who have no real idea where to begin. That 'dream' computer is here. The basic unit is constructed on a single pc board, but

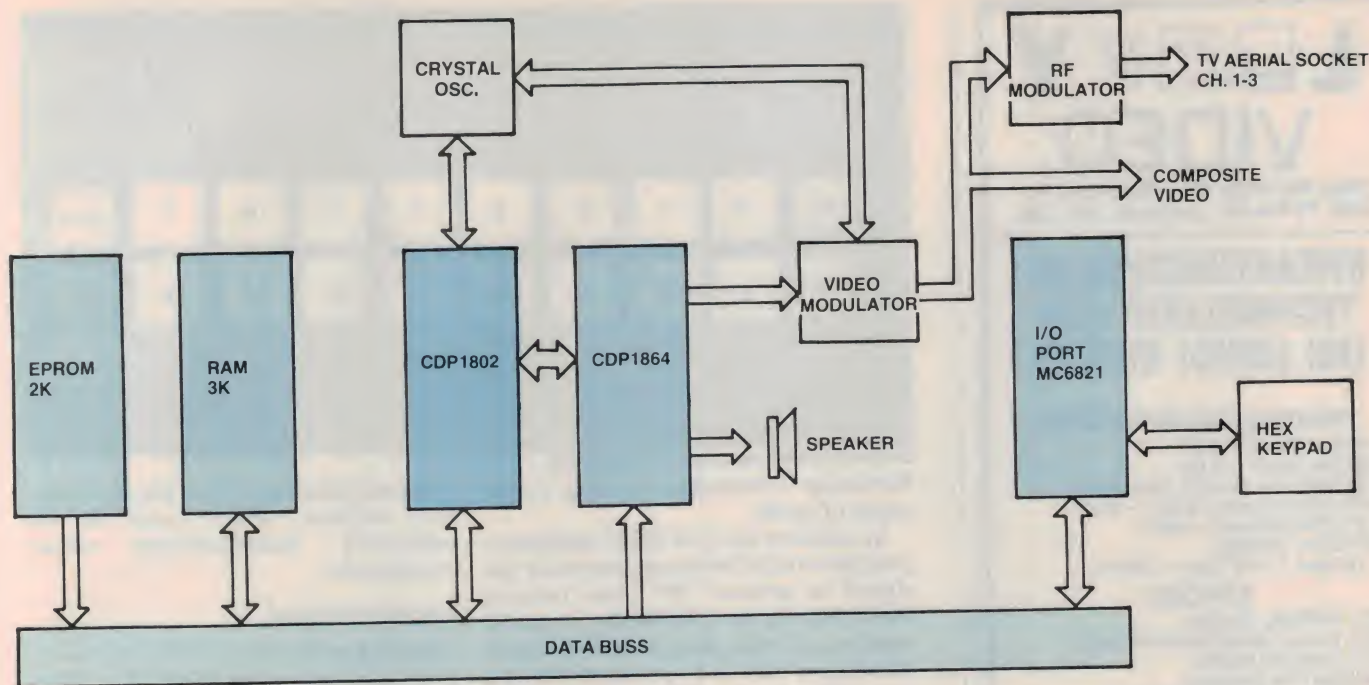provision for expansion units — such as additional memory, standard keyboard, etc — has been included. The basic unit provides for data and program entry from a hex keypad and either a standard type or one we've especially designed for user convenience may be used. Video



can be taken direct to a monitor, or RF output from an on-board modulator can be plugged directly into the antenna of a TV set tuned to channel 1. A cassette interface is provided on board and any standard cassette recorder and tape may be employed to permanently save programs. Colour video can be obtained with the addition of further components to the basic board. An audio output, via a small speaker, is provided and is used to give an audible 'prompt' when operating the keypad. In addition, it is possible to play tunes and provide games sound effects.

Following is a general technical explanation and description of the project.

The microprocessor

The Computer is a versatile single-board mini-computer using an LSI COS/MOS CDP1802 microprocessor. This is one of two produced by RCA and is an eight-bit register-oriented central processing unit. Its main advantages are low power consumption and a wide operating voltage range of 4-10 volts.

However, one of the side effects of the low power consumption is its slow-speed machine cycle; the oscillator input frequency is 1.773 MHz to the CDP1802, machine cycle duration being approximately 4.5 μ S. However, this apparently slow speed is counteracted by efficient software design.

The CDP1802 has a total of 91 easy-to-use machine code instructions, and to speed up writing programs a resident CHIP-8 language interpreter is located in EPROM.

A saving on hardware is achieved by

locating the monitor and CHIP-8 interpreter in memory location 0000 to 0400. To start the monitor program running the on-board RESET button is depressed; when it is released the processor resets some of the internal registers and looks to address 0000 for the next instruction. There is thus a saving in the hardware necessary to bootstrap the processor to some other area of the memory map, e.g.: 8000 to 81FF, as in some other systems. The following is a memory map for this computer:

0FFF	— additional user RAM
0C00	
0BFF	— additional user RAM
0800	
0700	— program storage area in RAM
0600	
0500	— video display memory — variables and scratchpad
0400	
0300	
0200	— monitor and CHIP-8 interpreter located in EPROM
0100	
0000	

The user RAM is standard 2114 RAM, the final design being expanded to 3K RAM and 2K of EPROM on board. The

● This project was originally developed by Hugh Anderson for Kitparts N.Z. and known as the 'HUG 1802'. Graeme Teesdale, working in ETI's laboratory, has further refined it in conjunction with advice from Hugh, and prepared it for presentation as an ETI project, number ETI-660.

use of the more expensive CMOS 2114 RAM will result in a lower total power consumption, and using a total of 3K standard RAM and other COS/MOS devices the total load current for the complete project is around 400 mA. This low power consumption allows the use of a simple power supply driven by an ac plug pack — no lethal 240 V mains to connect up!

Using the cheaper 2K 2716 EPROM only a single 5 V supply is required. Only 1K of the 2716 is used at this stage, but a 'tiny BASIC' is at present under evaluation.

Features

RCA produce a wide range of buss-compatible devices for use with the CDP1802. For this project we have selected the CDP1864C, an LSI CMOS colour or black and white PAL-compatible video controller. The CDP1864C generates vertical sync, horizontal sync and composite sync. These signals combined with the RED, BLUE, GREEN, BURST and BACK-GROUND output signals can be used to generate a composite video signal for a video monitor or into our RF modulator to your TV aerial inputs. The DMA (Direct Memory Address) feature of the 1802 is used for direct data transfer of luminance information for display refresh.

The completed toy computer with additional components added to the motherboard and under program control will produce limited background and foreground colours, but sufficient ►

LO-KEY VIDEO

Shop: 418 Bridge Road, Richmond, Vic.
Mail: PO Box 347, Richmond, 3121, Vic.

BREAKTHROUGH IN TECHNOLOGY FOR OSI (OHIO) SII/C1P

PRINTED CIRCUIT BOARDS

1. Mother Board — 8 Slot
2. Mother Board — 5 Slot
3. 8K RAM Exp. Board & Connector
4. 8K RAM Expansion Board — plain
5. 8K EPROM Board — plain
6. PASCAL Compiler
(on tape, 5" & 8" Disc — Soft/w.)

EPROMS

- EP.1. PASCAL Compiler
- EP.2. Cursor Control/Single Key Basic
- EP.3. Extended Monitor
7. Floppy Disc Controller
4 Drives, Single sided, 8" or 5¼"
8. Programme Generator
9. Dual V.I.A.

Drilled Boards extra.

Assembled & Tested \$15 extra.

Component Packs available from \$6-\$50.

See previous adverts for over 100 items of software or buy our catalogue \$3.50 plus \$1.00 P&P.

This ad was printed entirely on the NDK S-4000 wordprocessing printer using

Spellbinder

THE LATEST WORD IN WORDPROCESSING.

Spellbinder can operate the NDK fully proportionally with variable character widths, can print '...'scripts or ...scripts with both underlines and wide characters. And it will print around 200 of them every second!

Spellbinder

will drive any precision printer such as Diablo, Qume, Spinterm, etc. And Spellbinder will operate on almost any CP/M-based microprocessor - Sorcerer, TRS80, System80, Apple (with 280 card), Vector Graphic, Superbrain, etc. Full mailing-list facilities, mail-merge, boilerplate, forms-handler, alpha and numeric sorting, multi-column printing, line-numbering, etc.

And the system that printed this ad does our accounts and keeps our books, types our letters (as well as our letterheads!), keeps mailing-lists, does stock control and even corrects our spelling mistakes! It costs around \$8500 all up. And that's the top of the range! Contact us for a full demonstration.

Software Source

Spellbinder

AUSTRALASIAN DISTRIBUTORS

DEALER

ENQUIRIES WELCOME

po box 364 edgecliff 2027
australia phone (02) 33 4536



Close-up of the re-arranged hex keyboard.

flexibility is available to satisfy a wide range of needs.

In addition the CDP1864C contains a programmable frequency generator designed to produce 256 tones ranging from 107 Hz to 13 672 Hz. A small speaker is driven from the AUD output, allowing a tone to be produced when a key is depressed and the computer is in the tape load/dump routine. This generator can be used with suitable software in users' programs.

To produce the correct line and vertical sync pulse periods, a crystal frequency input of 1.75 MHz is required to the CDP1802; conversely, to produce the correct colour phase angles, a reference of twice colour-burst frequency is required by the colour modulator circuitry. Considerable attention was given to this area in an effort to reduce the crystal count to one. The frequency of the colour burst is far more important than the line or vertical frequencies, and most video or TV receivers have at least a 5% catching range about their nominal frequencies. A decision was therefore made to use the more commonly available 8.86 MHz crystal, which was divided by five to produce a frequency of 1.773 MHz. The error when compared to the original 1.75 MHz is slightly over 1%, and results in a vertical sync frequency of 50.6 Hz and a line frequency of 15 820 Hz. The only effect on screen is the 0.6 Hz beat pattern on the picture if an older monochrome receiver with a poorly filtered power supply is used. In modern colour TV receivers the effect is not noticed due to the improved power supply designs. The cost saving of not having the additional crystal and TTL oscillator outweighs any disadvantages encountered.

In practice it is difficult to obtain a symmetrical output divide-by-five to drive the clock input of the CDP1802. We experimented with different circuits until we discovered that the CDP1802 would accept an inverted non-

symmetrical output from the divide-by-five sections, which saved us the additional pulse-doubling circuit components.

Input/output

The most commonly used I/O port is the RCA support device CDP1852, which has the disadvantage of not being software programmable to be input or output; the CDP1851 does not have this disadvantage but is more expensive. The more commonly available Motorola MC6821 Peripheral Interface Adaptor (PIA) was therefore chosen for the I/O port. The basic system uses only one of the two eight-bit bi-directional ports, the other being user-available, although only using machine language programming.

The PA0-PA7 section of the PIA is used to interface the hex keypad to the CPU, the other PB section not being initialised in the monitor program. The 6821 PIA is normally memory-mapped in the 6800 system, a combination of the decoded address lines and the 1802 encoded 'N' lines being used to select it for software programming.

The PIA allows a high degree of flexibility, but does require some initialisation software in the monitor for it to act as a keypad reader. Our design is arranged so that no load key is required in conjunction with the keypad to debounce keys. An audible tone is an indication of a key being depressed.

Whetted your appetite?

Construction details of this brilliant little computer will commence next issue, so clean up your soldering irons and clear a space on the workbench, kitchen table, etc. Following the construction we intend to present an article or two on programming along with a few already-developed programs that you can play with. Now you can learn about the ins and outs of microprocessing without boiling your brain cells or breaking the bank. Don't go away! ●

Introducing

THE HUG 1802 MICROPROCESSOR

Introducing

Developed by our parent company in New Zealand to allow the hobbyist to get into microprocessors at minimal cost.

This simple single board microcomputer has already become the top selling micro kit in New Zealand — thoroughly tested and proven over the last 8 months.

And for those wishing to expand, there are many add-ons already under development.

CLUB

We have established a club for 1802 users to swap software and interesting applications. Club members are eligible for discount on software and peripherals purchased through us.

Club members will be given first (and possibly the only) opportunity to purchase anticipated new innovations as we develop them.

Membership is free ONLY to those who purchase the original HUG 1802 kit from Kit Parts (Aust.) Pty. Ltd.

Write now for **FREE** details to:

**KIT PARTS (AUSTRALIA)
PTY. LTD.,**

**PRIVATE BAG, NOOSA HEADS,
QLD. 4567.**

New Zealand customers please write to:

**Kit Parts Ltd.,
PO Box 6544,
216 Cuba Street,
Wellington.**

NEW SOFTWARE FBN "SMART KEY"

AN INTELLIGENT KEYBOARD
PROGRAM FOR ALL CP/M COMPUTERS
— ONLY FROM AED!

- User can redefine the logical layout at the keyboard e.g. define as single keys common control characters.
- Otherwise unavailable characters can be programmed onto unused keys.
- Keys can be defined to generate the strings of characters e.g. for use in a Basic program a key can generate "for I =", another "next I".
- Definitions can be saved on disk and called up and used or altered on demand.

There is nothing like "SMART KEY"

\$50 on 8" disk with full manual
(\$55 for Micropolis II 5¼" disk with manual)

NEW HOBBY COMPUTER

Announcing the AED "Stanten System"

A new concept in hobby computers. A computer to a high standard at a reasonable price. Using S100 card with guaranteed trade in values when the time comes to upgrade.

Standard Specifications

- 4 MHz Z80 CPU • 64 x 16 video display with chunky graphics
- 8-slot actively terminated Mothercard • Attractive and strong case with 10 amp power supply • Programmable I/O set up for Centronics style printers • Dual cassette interface • 16K of static RAM with room for another 16K on the same board • Basic on tape
- Powerful MONAED monitor in EPROM • B&W TV style video monitor.

Obvious Upgrades

Guaranteed trade-in of 80 percent of original purchase price when customer decides to upgrade to 20A power supply, 12-slot bus, 80 x 24 video, or green Phosphor video monitor.

Available in kit form or assembled and tested. Prices range from \$1731 for tax free kit to \$2173 for tax paid assembled.

This computer may be easily expanded to disk operation (from \$1285 plus extra 16K of RAM) and onto the ultimate in IEEE S100 computing.

- PRINTERS
- MONITORS
- S100 CARDS



- HARD DISK
- FLOPPY DISK
- CASSETTE

MICROCOMPUTER PRODUCTS

1981 CATALOGUE

The AED 1981 Catalogue is too large to insert in a copy of ETI (unfortunately). So send an 80c A4 SAE for:

- 16 pages of S100 cards • 4 pages of cases and power supplies • 10 pages of keyboards, video monitors, printers and disk systems • 13 pages of complete computers — Sorcerer, AED "Stanten" and AED "Eclipse" business and engineering computers • 14 pages of CP/M compatible software • 3 pages of books and magazines • 10 pages of parts • 4 pages of furniture • plus data on S100, RS232, IEEE 488 and Centronics Standards • You need the 1981 AED Catalogue.

There isn't room to tell it all, so see us at:

130 Military Road, Guildford, NSW 2161

Phone (02) 632-6301

Telex AA70664

Trading Hours 9am — 6pm Monday to Saturday

Acoustic Electronic Developments P/L reserve the rights to vary prices and specifications without notice.

CAN YOU AFFORD NOT TO SUBSCRIBE TO MICRO-80?

MICRO-80 is a monthly magazine dedicated to users of SYSTEM 80 and TRS-80 microcomputers. Owned and produced entirely in Australia, each issue of MICRO-80 contains at least six programs, articles, useful hints and answers to readers' problems; all designed to help YOU get the most out of your SYSTEM 80 or TRS-80. Since MICRO-80's first issue in December 1979, we have published over 80 major pieces of software and 10 hardware projects. Most of the programs and articles are written by our readers to whom we pay publication fees thus enabling them to make their hobby pay. MICRO-80 readers can save money by buying Tandy products at 10% discount from an authorised dealer — for details see any issue of MICRO-80. Our sister business, MICRO-80 PRODUCTS, sells Australian designed and produced software and high quality, imported goods at low, sensible prices. We repeat, if you own a SYSTEM 80 or TRS-80,

CAN YOU AFFORD NOT TO SUBSCRIBE TO MICRO-80? 12 month subscription delivered to your door, only \$25.00

CASSETTE EDITION only \$60.00 for 12 months

If you do not have enough time at the keyboard to type in the program listings which are published in MICRO-80 each month, then you need a cassette subscription. As well as MICRO-80 magazine, you receive a cassette each month containing all the programs listed in the magazine.

SPECIAL OFFER TO ALL NEW SUBSCRIBERS TO MICRO-80


A FREE cassette containing 6 programs (3 Level I + 3 Level II), together with complete documentation, will be sent to every new subscriber to MICRO-80.

Suspicious of mail order? Then send \$2.50 for a single copy of MICRO-80 and see for yourself that this is the magazine for you!

Daisy Wheel Typewriter/Printer

MICRO-80 has converted the new OLIVETTI ET-121 DAISY WHEEL typewriter to work with the TRS-80 and SYSTEM 80 or any other microcomputer with a Centronics parallel port (RS 232 serial interface available shortly). The ET-121 typewriter is renowned for its high quality, fast speed (17 c.p.s.), quietness and reliability. MICRO-80 is renowned for its knowledge of the TRS-80/SYSTEM 80 and its sensible pricing policy. Together, we have produced a dual-purpose machine: an attractive, modern, correcting typewriter which doubles as a correspondence quality Daisy-wheel printer when used with your micro-computer.

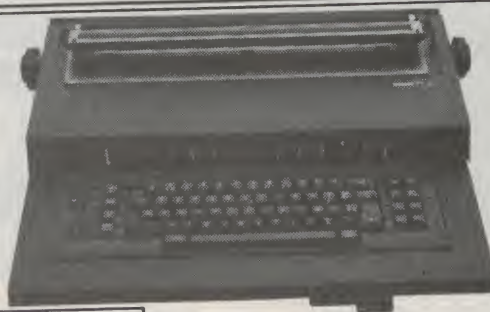How good is it? - This part of our advertisement was typeset using an ET-121 driven by a TRS-80. Write and ask for full details.



ONLY \$1995 INC. S.T.

MPI DISK DRIVES

MPI is the second biggest manufacturer of mini floppy disk drives in the world. They produce a family of high quality 5 1/4" drives with super-fast track-to-track access times (5ms!)

40 TRACK SINGLE HEAD \$339
40 TRACK DUAL HEAD \$449
80 TRACK SINGLE HEAD \$499
80 TRACK DUAL HEAD \$599

Dual head drives use both sides of the disk and occupy two drive positions — it is like having two drives for little more than the price of one!

Prices quoted are for bare drives. Add \$10 per drive for a cabinet and \$30 per drive for a power supply.

DISKETTES FOR TRS-80

NASHUA 40 track single side . . . \$4.50 ea
VERBATIM 40 track double side . . \$5.90 ea
VERBATIM 77 track single side . . \$5.90 ea

THE FABULOUS NEWDOS 80 IN STOCK NOW!

ND-80 \$149

The disk operating system that gives:

- New basic commands that support variable record lengths up to 4095 bytes long.
- Mix or match disk drives — supports any number of tracks from 18 to 80. Use 35, 40 or 77 track 5" mini disk drives or 8" disk drives, or any combination.
- A security boot-up for basic or machine code programs. User never sees "Dos-ready" or "Ready" and cannot "break" clear screen or issue any direct basic statement including "List" . . . and much, much more

77 TRACK DISK DRIVES DOUBLE YOUR CAPACITY

DD-7S \$775

Metropolis Floppy Disk, 77 Track, 100% larger capacity than most mini-floppy drives, complete with cable, power supply, chassis, and includes NEWDOS '80.

SYSPAND 80 FOR THE SYSTEM 80 \$119.00

SYSPAND 80 is a self-contained module which connects to the expansion port on your SYSTEM 80 and gives you a CENTRONICS parallel port to drive a printer PLUS the TRS-80 40 line bus. SYSPAND 80 allows you to connect all Tandy peripheral, including the expansion interface, disk drives, MICROTEK MT-32 memory expansion unit and the fabulous EXATRON STRINGY FLOPPY.

TRS-80 MEMORY EXPANSION UNIT MT-32 . . . \$149.00

The MT-32 is manufactured by MICROTEK Inc., USA. It provides a CENTRONICS printer port and sockets for up to 32K of dynamic RAM. It comes complete, ready to plug into the expansion port of your Level II 16K machine. (Will also work with your SYSTEM 80 via SYSPAND 80).

MT-32A without RAM \$149.00
MT-32B with 16K RAM \$204.00
MT-32C with 32K RAM \$249.00

16K MEMORY EXPANSION KIT

ONLY \$30 incl. p & p

These are prime, branded, 200 ns (yes, 200 ns!) chips. You will pay much more elsewhere for slow, 350 ns chips. Ours are guaranteed for 12 months. A pair of DIP shunts is also required to upgrade the CPU memory — these cost an additional \$4.00. All kits come complete with full, step-by-step instructions, no soldering is required. You don't have to be an electronic type to instal them.

DISK DRIVE HEAD CLEANING DISKETTES

\$29.00 plus \$1.20 p & p

Disk drives are expensive and so are diskettes. As with any magnetic recording device, a disk drive works better and lasts longer if the head is cleaned regularly. In the past, the problem has been, how do you clean the head without pulling the mechanism apart and running the risk of damaging delicate parts. 3M's have come to our rescue with SCOTCH BRAND, non-abrasive, head cleaning diskettes which thoroughly clean the head in seconds. The cleaning action is less abrasive than an ordinary diskette and no residue is left behind.

To: MICRO-80

P.O. Box 213, Goodwood, S.A. 5034

Please rush me the items checked below:

- ☐ 12 month subscription to MICRO-80 and my free software cassette \$24.00
- ☐ 12 month subscription to MICRO-80 and the cassette edition, plus my free software cassette \$60.00
- ☐ The latest issue of MICRO-80 \$2.50

PLUS THE ITEMS LISTED BELOW

DESCRIPTION	PRICE
TOTAL ENCLOSED	

Name

Address

Post Code

☐ bankcard welcome here No

Please debit my Bankcard \$

Expiry date

Signature ETI

MICRO 80 PRODUCTS

(08) 272 0966

433 MORPHETT STREET,
ADELAIDE S.A. 5000

AUSTRALIAN SOFTWARE

We have a wide range of Australian software available. Send for a free catalogue

TRS 80 and SYSTEM 80 OWNERS TRS 80 and SYSTEM 80 OWNERS

THE AFFORDABLE HOME COMPUTER



When the System 80 was first introduced to Australia, the response was overwhelming! The Computer World was **ASTONISHED** at the **QUALITY**, as well as the **PRICE**. In fact, the System 80 has more features than the TRS-80, but with a price tag that is substantially less!

Microsoft's Level II BASIC and 16K Memory.

Another reason for all the commotion is that the System 80 uses the same, easy to learn, **LEVEL II BASIC** language that the TRS-80 uses! What does this mean? It means that the System 80 can run most of the 1000's of programs that have been written for the TRS-80 Level II, 16K computer! This means that you have scores of games, educational programs, business programs, simulations etc, that can be used with the System 80.

The System 80 is Expandable!

Your System 80 is ready to grow with your needs. The S-100 Expansion Interface enables lots of other "goodies" to be interfaced to the System 80. For example, you can control up to 4 disk drives, there is a full Centronics-type parallel printer port, RS-232C serial communications port plus two vacant S-100 card sockets. All of this for \$499 (X-4010) plus if you want further RAM memory you can get a 16K card for only \$199 (X-4016) which has provision for a further 16K to be added for only \$59.95 (X-1186).

IS NOW ON SALE

Comparison Chart

Parameter	Syst. 80	TRS-80
CPU Type	Z-80	Z-80
Speed	1.7MHz	1.7MHz
S-100 Compatible (with expansion unit).	Yes	No
RAM (basic computer)	16K	16K
Built-in Cassette Recorder	Yes	No
Built-in Video RF Modulator	Yes	No
Capacity of BASIC ROM	12K	12K
Cassette Recorder Ports (basic machine).	2	1
Motor Control for Cassette Recorders.	Yes(2)	Yes(1)
Cost of basic unit with 16K RAM, video monitor & cassette recorder *	\$899.50*	\$1169

* The Basic System 80 costs only \$750. As this computer can connect direct to your TV set a video monitor, as a separate entity, is not required: making the saving on TRS-80 prices even greater!

WHY SPEND MORE AND GET LESS! SYSTEM 80 - THE AFFORDABLE COMPUTER. . .

Also available for the System 80: Disk Drives (X-3230 for \$379); Printers from \$495 (X-3252) to \$1995 (X-3265); Light pen (X-3645 at \$9.95); Add sound to your computer with "Sound Off", X-3648 at \$14.50 plus a host of cassette based software from system utilities to games - a full support of peripherals for your System 80.

Save Money! Use your own Television!

The System 80 has a built in RF modulator so you can use your black and white or color TV for a **VIDEO MONITOR!** A simple hook-up to your television's antenna socket.

Here's what you get:

The System 80 microcomputer with 16,000 characters of "In Computer Memory", Microsoft's Level II BASIC (built into the computer), a cassette player for storing or retrieving programs or data (cassette player is built into the computer!), an RF modulator for connecting the System 80 to your TV set (can also be connected directly to a video monitor, see our X-1196 @ \$149.50), complete instruction manual, learning manual and owners manual so you can begin to write programs straight away, plus a demonstration cassette with 5 programs (Cost Analysis, Graphics, Statistics, Biorhythm, and Star War).

ORDER TODAY!

4K RAM Cat. X-4003

\$695

16K RAM Cat. X-4005

\$750

DICK SMITH ELECTRONICS



See our other advertisements in this publication for address details, phone numbers, post and packing etc.

Universal logic: more potential in the chip

C.L. Boltz

Will we see the thousands of logic chips shrink to one small 'universal' set? If Dr Stanley Hurst of the University of Bath can translate his theories into practice a revolution in logic circuit design may well be sparked off.

MOST SILICON CHIPS are cheap because they embody conventional circuits of the sort generally needed in electronic equipment and are mass-produced. Many others are needed for special applications, but making small batches of chips designed to do specific, less commonplace jobs is complicated and expensive. A new approach to this problem, based on what is called universal logic, is a design for a chip with the potential of virtually any kind of computer-logic circuit and which can be used as a 'universal' building block in electronic systems.

A new and highly original line of development in microelectronics is being pioneered by Dr Stanley Hurst, a senior lecturer in the school of electrical engineering at the University of Bath, in the west of England. Dr Hurst's early work in universal logic, as it is called, was supported by the UK Science Research Council; now the Wolfson Foundation has made a grant of STG£127 000 (A\$254 000) to turn the theory into practical devices.

Closely associated with this research, but with its own money, is Silicon Microsystems, a small microelectronics company based 30 or so kilometres away in Malmesbury. The company's part is the practical and commercial aspects of design. Dr Hurst says that one aim of the partnership is eventually to become a national centre for designing microelectronics devices of the sort that will not be sold in the usual vast numbers.

Microprocessors (computer control processors on tiny slivers of silicon) are cheap and plentiful, but they are so only because of immense sales. The range available from the world's manufacturers is relatively inflexible, which means that users have to surround the microprocessor with other integrated-circuit devices to get the operation they require. So there is already a market, one which will increase in the 1980s and

onwards, where makers of equipment need *specific* digital microelectronics devices designed to their individual needs. The difficulty here is that the cost of designing a silicon-chip device is enormous, involving many highly skilled scientists and engineers over a very long time, even with computer-aided design, and needing very complex and expensive equipment. This huge cost is quickly recovered when there are large, world-wide sales, but such a project cannot be considered by an equipment manufacturer who needs but one or at most a few types of special digital devices designed for his particular application.

Dr Hurst and Silicon Microsystems are not the only ones to see this. The British firm of Ferranti has already won a Queen's Award for technology for what it calls its uncommitted logic array, based on blocks of conventional circuits already incorporated in each chip but not connected to each other until the customer's needs are known.

Dr Hurst's approach is quite different. Though, as he says, there has been and will continue to be tremendous development in designs and manufacturing techniques, there has not been much "evolution or revolution at the fundamental level". If there were a general-purpose basic design, needing only the final masking procedure for arranging the interconnecting links to

make a device to suit a specific purpose, the small-quantity market could be satisfied economically. So he has researched what he calls his Universal Logic.

In this context, logic is the application of Boolean algebra to a digital process using binary arithmetic. Boole was an English logician and mathematician who wrote a paper on the mathematical analysis of deductive reasoning in 1847, a paper re-discovered in 1938 and applied first to relays and switches. It was seized on in the mid-1940s for electronic computing. It is a sequence of decisions of 'go' or 'not-go', or 'on' or 'off' or, in the language of Boole, 'true' or 'false'. A computer and any similar digital device is an immense multiplicity of electronic switches, known as 'gates', which pass on binary information (that is, a 0 for 'off' and a 1 for 'on') from one or more input signals.

Orthodox gates

Among the orthodox gates used in all digital computers and circuits employing logic there are four that are by far the most common. The simplest is probably the AND gate. In this, if there are two inputs, A and B, when both are 'on' or represent 1 in binary arithmetic the output is also 1. If either A or B is not on (that is, represents a 0) the output is a 0. Another is the OR gate. In this, if there are two inputs, A and B, the output

Inputs		All possible output functions $f(x_i, x_j)$															
x_i	x_j	f_0	f_1	f_2	f_3	f_4	f_5	f_6	f_7	f_8	f_9	f_{10}	f_{11}	f_{12}	f_{13}	f_{14}	f_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Table 1. Functions which can be obtained from various gates with two inputs. For three input variables there are 256 possible output functions.

BUILD YOUR OWN COMPUTER FOR LESS THAN \$200!

Who but
DICK SMITH
could offer this value?

**COMPATIBLE
WITH ZX80
SOFTWARE**

Connect
to your
tv* & you're ready
to go!

The MicroAce is not just another personal computer. Apart from the exceptional low price it offers two uniquely advanced components; the powerful BASIC interpreter plus the simple teach-yourself BASIC manual.

Comes complete with everything you need to build your personal computer at home — PCB with IC sockets for all IC's, case, leads for direct connection to cassette recorder and television etc.

FEATURES:

- BASIC language
- Exceptionally powerful edit facilities, allows modification of existing program lines
- Randomise function, useful for games and secret codes etc.
- High-resolution graphics with 22 standard graphic symbols
- All characters printable in reverse under program control
- Lines of unlimited length

**INCLUDES
ATTRACTIVE CASE
& KEYPAD**

**Why pay
\$\$\$ or more?**

Complete
kit including
UHF Modulator
(connects to your UHF TV)

ONLY \$199
Cat. K-6500
P&P \$5.50

*If you want to operate
with a VHF TV we have
a VHF modulator for
\$4.96 Cat. K-6040
Power supply to suit
Cat. M-9560 \$12.95

DICK SMITH ELECTRONICS

NSW: 145 Parramatta Rd **AUBURN** 648 0558; 613 Princes Hwy **BLAKEHURST** 546 7744; 818 George St **BROADWAY** 211 3777; 531 Pittwater Rd **BROOKVALE** 93 0441; 147 Hume Hwy **CHULLORA** 642 8922; 162 Pacific Hwy **GORE HILL** 439 5311; 30 Grose St **PARRAMATTA** 683 1133; 125 York St **SYDNEY** 290 3377; 263 Keira St **WOLLONGONG** 28 3800; 171-173 Maitland Rd, Tighes Hill **NEWCASTLE** OPENING SOON; **ACT:** 96 Gladstone St **FYSHWICK** 80 4944; **QLD:** 166 Logan Rd **BURANDA** 391 6233; 842 Gympie Rd **CHERMESIDE** 59 6255; **SA:** 60 Wright St **ADELAIDE** 212 1962; **VIC:** 399 Lonsdale St **MELBOURNE** 67 9834; 656 Bridge Rd **RICHMOND** 428 1614; Cnr Dandenong & Springvale Rds **SPRINGVALE** 547 0522; **WA:** 414 William St **PERTH** 328 6944; Cnr Wharf St & Albany Hwy **CANNINGTON** 451 8666
Mail Order Centre: PO Box 321, North Ryde, NSW 2113, Ph. (02) 888 3200



**The name for value
in computers and
peripherals**

Credit terms available
to approved
applicants

is 1 if either A or B is 1, or if both are 1. There is also an inverter or negator gate which inverts a single input, so that a 0 becomes a 1 and a 1 becomes a 0. Combining an inverter with an AND gate makes a NAND gate; an inverter with an OR makes a NOR gate. Generally speaking, for reasons of electronics, NAND and NOR gates make up the bulk of the logic of a digital system.

Lacking power

From the evidence of digital computing it must be agreed that these gates have been very successful, but analytically they do not satisfy Dr Hurst. In his words, they lack logical power. It is easy to see that there is an ambiguity in each gate. With an AND gate, for example, accepting inputs A and B, we can say that when one input is in the off state and the other in the on state the output is 0, but it does not indicate which one of A and B is off or on. With three inputs things are even more ambiguous. To put it another way, the output of an NOR gate is unique only when all inputs are 0, and of a NAND gate only when all inputs are 1.

The practical outcome of this lack of logical power is that quite a number of gates have to be combined to give a specified result. For example, in one simple device adding numbers there are 16 gates. A straightforward decoder (which translates from binary to ordinary decimal numbers, among other tasks) needs 50 gates to do its basic job. A circuit to compare one number with another has 33 gates. (These figures are taken from a random look at some published circuits.) In a microprocessor there may be at least 3000 gates.

The inefficient way orthodox gates operate Boolean logic has set more than one microelectronics engineer or scientist thinking of possible better circuits, but large manufacturers have had such enormous success in getting thousands of gates on a silicon chip, making it a cheap device, that they are interested only in competitive technological improvements in getting more and more on less and less. There is no reason why they should be interested in fundamental changes in logic. In the market for small-quantity, custom-built chips things are different.

Mathematical

The approach of Dr Hurst and his colleagues is fundamental yet unconventional. In trying to find out whether one could get a basic circuit that would do whatever logical step was needed, according to the connections and the programming, their thinking was

	ULG2	NAND	NOR
Total number of cells or gates to realize all 256 functions	683	1118	1124
Average number per function	2.67	4.36	4.39
Maximum number per function	4	7	7
Average number of cell/gate connections per function	10.68	17.44	17.56

Table 2. Comparison between the capabilities of ULG2 cells and those of orthodox gates. The table shows that the ULG2 is roughly twice as powerful as a NAND or a NOR gate.

primarily mathematical: it made use of esoteric techniques such as set theory, Walsh functions and so on. They were able to show that a universal logic gate was indeed a possibility. With two input variables there are 16 possible output functions (see Table 1, which is an exercise to see what functions could be obtained from various gates). For three input variables there are 256 possible output functions. Could a single circuit cope?

Calling the circuits ULG2 (universal logic gate for two input variables) and ULG3, Dr Hurst has shown that an array of ULG2 gates will do all the logical steps possible even for three input variables and that one ULG3 will be capable of realising all 256 outputs — not all at once, of course, for the result depends on which input terminals are used and how the circuit internal wiring is connected.

The number of ULG2 cells needed to realise all the 256 functions of three input variables has been calculated and compared with the equivalent figure for orthodox gates. The results are shown in Table 2. We can see that the ULG2 is roughly twice as powerful as a NAND or a NOR. Incidentally, it should be noted that although a ULG2 may have only two independent variables as input, there may be three or four physical connections. Figure 1 shows a circuit for a ULG2. It has two transistors, two diodes, and three resistors. Though there are but two input variables, there

are three input connections. This is to do with the set-theory mathematics of the device and need not concern us.

The electronics of the circuit need not be considered in detail. A gate is made of transistors, diodes, resistors and, sometimes, capacitors. Up to now most logic gates have depended on bipolar technology, that is, transistors with two possible states. This is the one represented in the diagram. A newer technique is based on MOS (metal-oxide-semiconductor) devices, which involve far fewer states in manufacture and avoid the 'cross-talk' between adjacent conductors. Silicon Microsystems is very much committed to MOS technology and Dr Hurst considers that bipolar methods will die out in the next decade and be replaced by MOS circuitry.

The practical problem is concerned with how big an area of silicon is used up in a ULG as compared with orthodox gates. It is easily seen that a ULG3 would occupy much more space. So is it better to use an array of identical ULG2s or rely on a ULG3? These are the questions being looked into at Bath now. The answer may be a compromise. When such matters are decided there will be available a set of universal logic gates which can be supplied as units. All that the designer then has to do is produce a suitable mask, a task made simple by computer-aided design, which will deposit the appropriate interconnections on the chip. The cost of design for a custom-made device will therefore be drastically reduced, even if the ULGs are themselves more expensive than orthodox gates — another question being researched.

Furthermore, as Dr Hurst has said, a considerable amount of special logic design in ULG form can be undertaken and a library of standard interconnection details built up, ready for individual customer requirements. It is a long-term research development programme for which full-time staff will be recruited. It could lead to a commanding position in the ever-growing use of silicon chips for specific purposes. ●


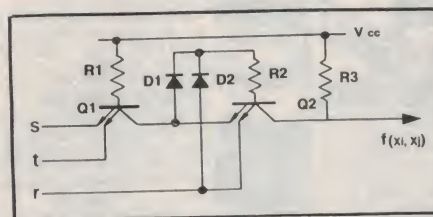


Figure 1. Basic circuit of a ULG2, comprising two transistors, two diodes and three resistors. Although only two input variables are applied, three input connections (s, t and r) are provided. This is to do with the set-theory mathematics of the device.

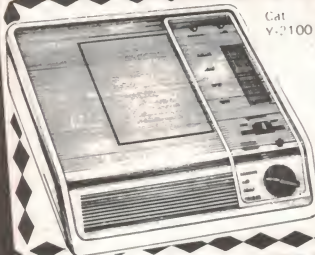

Cat Y-2100

HEY EXPERIMENTERS... LOOK AT THIS!

Amazing 'CALL JOTTER' Telephone Answering Machine

YES, you can afford this one! This is the affordable answering machine that can be connected to any phone and comes complete with its own AC power supply. BUT IT'S MORE THAN AN ANSWERING MACHINE:

- As a phone monitor
 - As a dictation/transcriber for the business person.
 - As a tape recorder - play your favourite cassettes on it!
 - Uses standard cassettes!!!
- And with all these features, it'll GET YOUR MESSAGES THROUGH TO YOU! NOTE This machine is not Australian Telecom Approved. See catalogue for our other answering machine which is approved.

ONLY \$99.50

DROP IN & CHECK OUT OUR GREAT

THROW THOSE TOYS AWAY...

Now's the time to use a PROFESSIONAL METAL DETECTOR with a discrimination feature that indicates treasure from rubbish! It's professionalism is only offset by the fact that it's easy to use. So now you can learn to master the detector quickly. The latest in microprocessor technology is employed but that's not all - look at my price!


Cat Y-1065

Just \$149

WHO KNOWS...IT COULD LEAD YOU TO A FORTUNE!!!

THEY'RE TURNING GREEN!

When they look at my price for this fantastic GREEN SCREEN MONITOR! Compare the others against ours & you'll find us on top. Features an ultra high resolution (not found in other more expensive units) and it's absolutely complete and ready to go. Great for hobbyists, etc. who want to build their own computer console. This would also be the PERFECT MONITOR for use with our NOVA 80 computer kit. Hurry - there is only a limited number in stock! Cat. X-1199

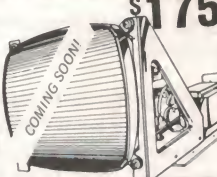

\$175

FOR SAFE KEEPING...

Cat. D-1102

\$49.50

BUDGET KEY

For the novice or anyone who wishes to learn the code. Spring tension adjusts. As used in the Morse Practice kit in Dick Smith's Funway kits. Cat. D-7105

\$1.75

LEARN THE CODE

Teach yourself Morse. Learn Morse the easy way. These tapes will teach you in the convenience of your own home (or shack). Speeds from 5wpm to 15wpm in graduated steps. Ideal for Novice licence or 2nd calls. GIVE IT A GO!!! Cat. D-7106

\$7.90

TEACH YOURSELF MORSE THE EASY WAY

FULL NOVICE STANDARD

COLOURED GLOBES

Great 100W par 38 floodlights in 4 colours:
Yellow S-3850
Red S-3852
Blue S-3854
Green S-3856



PARTY TIME!

Get your party going with this versatile Muscular kit. Accepts an audio input from almost any amplifier and uses the information to control 3 channels of light. Easy to build. It will provide endless enjoyment to you and your friends. Cat. K-3140

\$69.50

\$7.95 EA

holders: \$3.50 ea.

YOU ASKED FOR IT - YOU GOT IT!

The new 3.5MM STEREO PLUG & SOCKET!!!

These new plug & socket are much sought after by proper builders and experimenters. Both plug and socket are extremely versatile where space is a problem. The plug suits our micro-sized cassette recorder headphones (see catalogue). PLUG P-1140 75c. SOCKET P-1240 95c.

COMING SOON!

HOT TRANNIES?

Our heatsinks will give the best heat transfer for your money! And you'll save even more on bulk purchases!

HI EFFICIENCY POWERSINK

For those big jobs. Mounting surface temp. rise above ambient 60°C @ 30W heat diss.

75mm H-3422 \$3.50 ea.

225mm H-3426 \$9.50 ea.

TO-3 POWERFIN

Best possible heat diss. in smallest possible space. Thermal rating approx. 5°C/Watt. Cat. H-3400 \$1.25 ea.

UNIVERSAL POWERSINK

Universal hole pattern allows mounting of almost all power semiconductors. Cat. H-3401 98c ea.

MINI ALUMINIUM

Ideal PCB mounting suits transistors, SCR's, Triacs etc. Cat. H-3402 75c ea.

VERSATILE POWERSINK

Mount flat or end on. Has side groove fins for multiple connection. Accepts 2 x TO-3's. Un drilled H-3460 \$5.50 ea. Drilled H-3461 \$5.95 ea.

OUR SWITCHES ARE BEST!

Our most popular switches. Low in cost, high in quality. Ideal for many applications.

DPDT Sub Mini Slide Sw. S-2010 40c ea.

SPDT Toggle. 240VAC 1.5A S-1173 \$1.45

SPMT Push Button. Nor open S-1102 45c

DPDT Toggle Sw. 240VAC 3A S-1393 \$2.75

We have micro switches, pushbuttons, rotary switches, illuminated switches, PCB DIL switches & MUCH MORE! Compare our prices. You'll save even more if you buy in bulk!

DROP IN & SEE OUR HUGE RANGE!

TEST IT!

Tests bipolar transistors, FET's, diodes & even SCR's & PUT's. Easy to build & is ideal for beginners, servicemen & schools. A valuable piece of test equipment! Cat. K-3052 \$19.75

ONLY A FEW LEFT!

Cat. Y-9000 \$85

12V FLUORO \$12.50

Take anywhere portable fluoro light comes complete with cigarette lighter plug. Use as a map reading light, for the caravan, boat, garage etc. Well...not very versatile and quite, but this inexpensive unit can mix 4 signals (mic, tuner, T, table etc) into 1 signal for amp or recorder. Cat. F-2272 \$14.95

'MIX' MASTER

Learning has never been so enjoyable...

SPEAK & SPELL

It actually talks! Develop your child's skills in spelling, pronunciation & reading. The unit pronounces the word while the student keys in the spelling. It tells you if you're right or wrong & even keeps a score! Has a vocabulary of over 200 most commonly miss-spelt words. Complete with 32 page guide. Cat. Y-1300 \$79.00

SPEAK & READ

Develop your child's vocabulary, word meaning & reading comprehension. Offers 6 games & activities to play. Use alone or with friends. Makes it ideal for migrant English education! Complete with 64 page book. 'You can Read!' Cat. Y-1313 \$99.00

SPEAK & MATH

The microprocessor IC in this unit can generate over 100,000 math problems & talk to you, giving you a problem & telling you if you're right or wrong. Added games make learning fun. Supplied with 32 page book 'Math Talk'. Each unit has a battery saver device. Cat. Y-1310 \$89.00

SWITCH IT! \$11.75

With this 3-way antenna switch, your problems are over! Use up to 3 antennas for your CB, Ham radio. Handles 150 watts at 30MHz. Ideal for base or mobile use! Cat. D-5206 \$6.50

COAXIAL ANTENNA SWITCH \$6.50

You may be annoying your neighbour by interfering with his TV set! Save yourself the hassle (& perhaps a broken nose) with this low pass filter. 30MHz cut off, low loss. 50 ohm

FILTER IT! \$6.50

Save yourself the hassle (& perhaps a broken nose) with this low pass filter. 30MHz cut off, low loss. 50 ohm

PARTS FOR NEW KITS

See also our advert elsewhere in this magazine with new kits since our last catalog.

HOT CANARY (See EA May)
Complete kit, inc. inst. K-3395 \$14.95
PCB only H-8396 \$2.25

SPEED SENTRY (See EA May)
Complete kit, inc. inst. K-3245 \$11.75
PCB only H-8399 \$1.95

INFRA RED REMOTE CONTROL (See EA May)
Full kit, inc. inst. K-3380 \$63.95
PCB only H-8397 \$6.95

dB METER (See EA May)
Complete kit, inc. inst. K-3476 \$34.50
PCB only H-8398 \$2.35

UHF TV DOWNCONVERTER (See ETI May)
Full kit, inc. inst. K-3235 \$32.50
PCB only H-8637

UNIVERSAL RELAY DRIVER (See ETI May)
PCB only H-8638
(All parts for this kit are normal stock lines)

SYSTEM 80/TRS 80 SERIAL INTERFACE (See EA April)
Full kit, inc. inst. K-3608 \$57.50
PCB only H-8394 \$7.95


INFRA RED BEAM RELAY (See EA April)
Full kit, inc. inst. K-3375 \$37.50
PCB only H-8395 \$3.95

CORE BALANCE RELAY (See ETI April)
Full kit, inc. inst. K-3315 \$49.50
PCB only H-8635 \$4.50

NEGATIVE ION GENERATOR (See ETI April)
Complete kit, inc. inst. K-3335 \$41.95
PCB only H-8634 \$3.95

(Above prices & dates are from magazine estimates only. We cannot guarantee that the articles will appear when specified. * Price unavailable at time of going to press.)

NEW NICADS

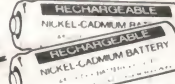

Want to save a heap on batteries? Try these value-packed NiCads! They're cheaper at the start, but you can charge them over and over again! And now we have 'C' & 'D' size NiCads, too, at bargain prices! So why not up-date now and start saving!

NOTE: 'C' & 'D' NiCads come in packs of two; 'AA' size NiCads are supplied individually.

'C' SIZE 1.2Ah Cat. S-3302 Pk 2: \$7.50
'D' SIZE 1.2Ah Cat. S-3304 Pk 2: \$7.95
POPULAR 'AA' size Cat. S-3300 Each \$2.05

Save more if you buy in bulk!!!

NICAD BATTERY CHARGER

Great for charging anything up to 12 volts! Will charge from six to ten 1.2 Volt batteries at a time. The current automatically adjusts FULLY APPROVED and it's only Cat. M-9517

\$11.50

WOULD YOU LIKE TO WORK WITH US?

Dick Smith Electronics is expanding - if you've been watching your local press you'll probably have noticed this already!

Opening new stores requires new staff. Good staff. Electronics enthusiasts who can be trained to become professional sales people and managers.

If you're talented and enthusiastic, we offer good wages and conditions. If you're above average, promotion can be very rapid. (One of our salesmen became general manager three years later!)

No matter what area you live in, if you'd like to work with us, drop us a line. When we open a store in your area, we'll be in touch...

Send your application to:
The Personnel Manager,
Dick Smith Electronics Pty Ltd
PO Box 321,
North Ryde, NSW 2113

WOULD YOU LIKE TO BE A DICK SMITH RE-SELLER?

How would you like to join the hundreds of successful Dick Smith re-sellers, spread right across Australia? If you're interested, why not give our wholesale division a call - Sydney (02) 888 3200, 9AM - 5.30PM weekdays. It could be the start of something big...


A NEW GENERATION IN UHF CB...

The deluxe Apollo 40 ch UHF Transceiver


Until now, you've really had no choice in buying a UHF transceiver. With the new Apollo AP400 you'll surprise your contacts with a good clear sound - standing out from the crowd. This amazing breakthrough in UHF technology makes it ideal for small business or rural applications. Great for use in the car on the way to work or as a home installation. On air signal is strong and clear while the powerful receiver has a high selectivity to eliminate cross channel interference.

Just look at these features:

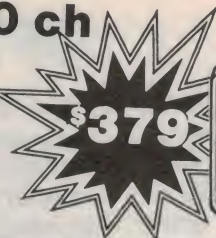- Large illuminated SRF meter.
- Delayed action squelch circuit.
- RF gain control.
- Tone control.
- Green LED channel indicator for sharp image - even in daylight!
- Dimmer switch.
- Performance you just couldn't find in less expensive equipment.



Cat D-1802

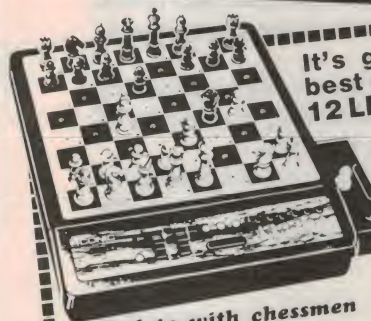

It's got to be the best ever so far... 12 LEVEL CHESS COMPUTER

This magnificent and attractive unit has 12 different levels of skill enabling you to learn gradually. It even plays against itself! A must for any professional or serious chess player. You'll have to see for yourself the number of incredible features it has.

Cat. Y-1256
Don't pay \$1000 or more - our price is only:

\$245.00

Complete with chessmen and power supply!

Learning to play Chess?

Improve your skills with this Chess Master learning aid. You can soon play like a professional! Solve problems in the least number of moves. Play alone or with others and experience the different tactics and checkmates etc. Complete with 7 booklets each containing 50 moves - that's 350 moves to play!

\$35.00

Cat Y-1257



Did you miss out?

Last month EA & ETI included our FREE 1981 catalogue packed with goodies for the eager enthusiast. If you missed out don't worry. Just send 75c (P&P is free) to our Mail Order Centre. Address below. INCLUDES 30 PAGE DATA SECTION!!!



PROTECTION... COMMUNICATION...

Too many intruders? This unit won't let them pass the door. If they try, they'll encounter a piercing siren. Also features pleasant ding-dong sound - so you don't scare your friends. The 15 buttons enable you to pick your own secret code, so you can switch it off when you get home. Take with you anywhere. VHF receiver. Has 6 bands including AM, FM, CB, AIR, POLICE, TAXI & much more. Its unique tuning meter also acts as a battery indicator. Comes complete with earphone jack & VHF listening guide. Cat. D-2833



\$29.50

Cat L-5100

OOPS!

Catalogue Correction

Due to an oversight, the price and catalogue number for a discontinued printer were shown on page 6. The correct catalogue number for our new low-cost printer is X-3252 and the price is \$495.00. Our apologies for any inconvenience caused.

Dick Smith & Staff

WHOLESALE MAIL COMPETITION PRIZE WINNERS

Thanks to all who entered our 'Wholesale Give-away' competition for a fabulous System 80 computer and other great goodies. We received thousands of entries.

Congratulations to:

Graeme Ryder, Jindabyne NSW - 1st prize: Dick Smith System 80 16K personal computer.

Stephen Morton, Nightcliff NT - 2nd prize: Dick Smith Telephone Answering Machine complete with remote beeper.

Colin Laidley, Coffs Harbour NSW - 3rd prize: Sanyo Stereo Cassette Deck with Dolby Noise reduction.

PLUS 100 FUNWAY VOLUME 2 BOOKS GIVEN AWAY!!!

Once again, thanks to all who participated.

Dick Smith & Staff

FOR THE LOVE OF BOXES!



Superbly made folded aluminum cases in a variety of sizes, fitted with rubber feet and have ventilation slots. Look really great!

SIZE	CAT	1-9	10 up
102 x 56 x 83	Cat H-2741	\$2.75	\$2.55
150 x 61 x 103	Cat H-2742	\$4.35	\$3.95
150 x 76 x 143	Cat H-2743	\$4.90	\$4.40
184 x 70 x 160	Cat H-2744	\$5.45	\$5.00

DICK'S ZIPPYS ARE BEST!

Dick Smith zippy boxes are unique: they're the ones with slotted sides allowing for easy mounting of PCB's etc. Insist on them!

SIZE	Cat No	1-9	10 up
150x90x50	H-2751	\$2.50	\$2.00
196x113x60	H-2752	\$3.75	\$3.00
130x66x41	H-2753	\$1.95	\$1.60
85x54x28	H-2755	\$1.50	\$1.20

Our 2nd Perth store is NOW OPEN

Hey you lucky Western Aussies, you've got another store! You'll find the same reliable & friendly service and a wide range of goodies for the electronics enthusiast and professional. We're just a short walk from the 'Carousel' shopping centre at the corner of Albany Highway and Wharf St. Ph 451 8666. SEE YOU THERE!



DICK SMITH ELECTRONICS



- NSW**
- AUBURN: 145 Parramatta Rd. 648 0558.
 - BLAKEHURST: 613 Princes Hwy. 546 7744.
 - BROADWAY: 818 George Street. 211 3777.
 - BROOKVALE: 531 Pittwater Rd. 93 0441.
 - CHULLORA: 147 Hume Hwy. 642 8922.
 - GORE HILL: 162 Pacific Hwy. 439 5311.
 - PARRAMATTA: 30 Grose Street. 683 1133.
 - SYDNEY: 125 York Street. 290 3377.
 - WOLLONGONG: 263 Kiera Street. 28 3800.

DICK SMITH MAIL ORDER CENTRE:
PO Box 321, North Ryde, N.S.W. 2113. Ph: (02) 888 3200.
SERVICE CENTRE: LANE COVE & WATERLOO RDS. NORTH RYDE NSW 2113. PHONE (02) 888 3200. 9AM TO 5PM. MONDAY TO FRIDAY ONLY

MAJOR DICK SMITH RE-SELLERS:

- ATHERTON, QLD:** Tableland Radio Service
2 Dick Street. Phone 912 017
- BENDIGO, VIC:** Summer Electronics
95 Mitchell Street. Phone 431 977
- BLACKHEATH, NSW:** Goodwin Electronics
123 Station Street. Phone 878 379
- BROKEN HILL, NSW:** Crystal TV Rentals
66 Crystal Street. Phone 6897
- CAIRNS, QLD:** Thompson Instrument Services
79-81 McLeod Street. Phone 512 404
- COFFS HARBOUR, NSW:** Coff's Harbour Electronics
3 Coff's Harbour Place, Park Ave. Phone 525 684
- DARWIN, NT:** Kent Electronics
42 Stuart Highway. Phone 814 749
- DOUBRO, NSW:** Selekt Sound.
31 Talbeger Street. 826 979
- EAST MAITLAND, NSW:** East Maitland Electronics.
Cnr Lewis & High Streets. 337 327
- FAIR MEADOW, NSW:** Trilogy Wholesale Elect.
40 Princes Hwy. Phone 831 219
- GERALDTON, WA:** KB Electronics & Marine
361 Main Terrace. Phone 212 176
- GOSFORD, NSW:** Tomorrow's Electronics & Hi Fi
68 William Street. Phone 247 246

- HOBART, TAS:** Aero Electronics
123a Bathurst Street. Phone 348 232
- KINGSTON, TAS:** Kingston Electronics & Records
Channel Court. Phone 296 802
- LAUNCESTON, TAS:** Advanced Electronics
55 The Quadrant. Phone 317 075
- LISMORE, NSW:** Decro Electric
Magellan St & Brunner Hwy. Phone 214 137
- MACKAY, QLD:** Stevens Electronics
42 Victoria Street. Phone 511 723
- MARYBOROUGH, QLD:** Keller Electronics
218 Adelaide Street. Phone 214 555
- MORUYA, NSW:** Coastal Electronics
43 Vulcan Street. Phone 742 545
- MT GAMBIER, SA:** Hutcheson's Communications
5 Elizabeth Street. Phone 256 404
- MUSWELLBROOK, NSW:** Silicon Chip Electronics
Suite 3, 98 Bridge Street. Phone 43 1096
- NAMBOUR, QLD:** Nambour Electronic Shop
Shop 4, Lower House, Ann St. Phone 411 604
- NEWCASTLE, NSW:** Elektron 2000
181 Wharf Road. Phone 262 644

- ACT**
- Fyshwick: 96 Gladstone Street. 80 4944.
- QLD**
- BURANDA: 166 Logan Rd. 391 6233.
 - CHERMSIDE: 842 Gympie Rd. 59 6255.
 - ADELAIDE: 60 Wright Street. 212 1962.
 - MELBOURNE: 399 Lonsdale Street. 67 9834.
 - RICHMOND: 656 Bridge Rd. 428 1614.
 - SPRINGVALE: Dandenong & S'vale Rds. 547 0522.
 - PERTH: 414 William Street. 328 6944.
 - CANNINGTON: Wharf St & Albany Hwy. 451 8666

SHOP HOURS: 9AM TO 5.30PM MONDAY TO FRIDAY; NOON SATURDAY (Brisbane stores half hour earlier). Some stores are open on late shopping nights: please phone your local store to check before coming in!

PRICES CORRECT FOR MONTH OF PUBLICATION OR WHILE STOCKS LAST.

Listed below are re-sellers who stock a large proportion of our range. However we cannot guarantee that they will have any or all of the items, or at the same prices, as those shown here.

- ORANGE, NSW:** M&W Electronics
48 McNamara Street. Phone 626 491
- ROCKHAMPTON, QLD:** Purely Electronics
15 East Street. Phone 21 058
- SOUTHPORT, QLD:** Amateur's Paradise
121 Nerang Street. Phone 322 644
- TAMWORTH, NSW:** Sound Components
78 Brisbane Street. Phone 661 363
- TOOWOOMBA, QLD:** Hunts Electronics
18 Neil Street. Phone 326 944
- TOWNSVILLE, QLD:** Tropical TV
49 Fulham Rd. Vincent Village. Phone 791 421
- TRARALGON, VIC:** Power N Sound
147 Argyle Street. Phone 743 638
- WAGGA, NSW:** Wagga Wholesale Electronics
82 Forsyth Street
- WINDSOR, NSW:** Hawkesbury Electronic Centre
111 George Street. Phone 773 411
- WODONGA, VIC:** A & M Electronics
78a High Street. Phone 544 588
- WHYALLA, NORRIS, SA:** Mellor Enterprises
Shop 2, Forsythe Street. Phone 454 764

BUYING BY MAIL?

ORDER VALUE:	P&P
\$5 (min) to \$9.99	\$1.00
\$10.00 to \$24.99	\$2.00
\$25.00 to \$49.99	\$3.00
\$50.00 to \$99.99	\$4.00
\$100 or more	\$5.50

NOTE: These charges apply to goods sent by post in Australia only. Large and bulky items cannot be sent by post.

If you prefer, we will despatch your order by Comet Road Freight to anywhere in Australia for only \$7.00 - that's below what it costs us! Large and bulky items are normally sent by Comet unless you specify differently (eg by rail or air - you pay freight on delivery).

COMPUTER HOTLINE

Want to know more about our computers? Or maybe you're having problems and need advice. For friendly, helpful information on System 80 or Sorcerer computers, or on any of our peripherals, phone our Computer Hotline:

Monday - Friday, 9 - 5.30 on Sydney (02) 888 2002

Dear Customers,

Quite often, the products we advertise are so popular they run out within a few days. Or unforeseen circumstances might hold up goods so that advertised lines are not in the stores by the time the advert appears. Please don't blame the store manager of staff; they cannot solve a dock strike on the other side of the world, or even locate a shipment that has gone astray.

What we are trying to say is that if you are about to drive across town to pick up a particular line at a Dick Smith store, why not give the store a ring first (addresses and phone numbers opposite) just in case. Thanks

Dick Smith and Staff

There's a re-seller near YOU!

NDK S-4000

SAMPLE PRINTOUT

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{RMS} = \sqrt{4KTR(f_2 - f_1)}$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$



$$W_{xy}(f) = \int_{-\infty}^{\infty} \psi_{xy}(\tau) e^{-j2\pi f\tau} d\tau$$

$$L = \int_0^{\pi} \sqrt{\left(\frac{dx_1}{d\theta}\right)^2 + \left(\frac{dy_1}{d\theta}\right)^2} d\theta$$

$$\psi_{xy}(f) = \tan^{-1} \left[\frac{P_{xy}(f)}{C_{xy}(f)} \right]$$

$$\begin{cases} a_1x + b_1y = c_1 \\ a_2x + b_2y = c_2 \end{cases}$$

$$x = \begin{vmatrix} c_1 & b_1 \\ c_2 & b_2 \end{vmatrix} \div \begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix} = \frac{c_1b_2 - c_2b_1}{a_1b_2 - a_2b_1}$$

$$S = \sum_{j=1}^n X_j$$

$$\Delta f_{\text{max}} \tau_{\text{max}} \leq 0.3$$

$$|W_{xy}(f)| = \sqrt{C_{xy}^2(f) + Q_{xy}^2(f)}$$

$$\Psi_{xy}(\tau) = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T f_x(t) f_y(t+\tau) dt$$

PRINTER

\$3,190 C.O.D.

STAND\$160

SALES TAX\$390

OPAL 2000C

The OPAL 2000C is an 8 slot S-100 system conforming to the new IEEE standards. The system uses a 4Mhz Z80 CPU and has 3 serial RS232c serial and 3x8 bit bi-directional parallel ports. The disk controller, is California Computer Services' multi-mode model (able to control both 5" and 8" disk drives).

Memory is provided by a 4 MHz 64k dynamic RAM Board by Measurement Systems and Control. The memory board is fully bank selectable and is designed for upgrading to a multi-user system.

Disk drives are 2x8" QUME double density, double sided disk drives with a total on line capacity of 2.4 megabytes (1.2 megabytes per 8" disk).

The system is mounted in an attractive pressed Aluminium housing with a cast front panel fitted with reset button and key operated on/off switch. The power supply is equipped with a line filter.

The operating system software is CP/M version 2.2. An extensive monitor is included. The OPAL 2000C will read and write on any of the following formats or exchange information between any combination on A and B drive:

IBM 3740 Single Density single sided disk.....	240k
Double Density Single sided disk.....	480-600k
Single Density Double sided disk.....	480k
Double Density Double sided disk	1.2 mbytes

Introductory Price: \$4,975.00 plus \$600.00 sales tax.

LIFELINES

Lifelines is a monthly software newsletter published by Lifeboat Associates.

Although Lifelines contains features and columns dealing with new software products on the market, product comparisons, the CP/M Users Group and other items of general interest, the principal role of the periodical is to provide timely notice to owners about their software. Each month, new revisions are reported, together with information on the purpose for each such release, be it for the correction of "bugs" or the addition of features and facilities.

The software products distributed by Lifeboat Associates are frequently both complex and costly. We recommend that all serious users of software should take out subscriptions to Lifelines, ensuring that they are automatically informed about the current state of their software tools and thus get full value for their purchase.

Subscription Costs:

\$36.00 for 12 issues. Price includes postage for anywhere in Australia. \$5.00 each for back issues. Price includes postage for anywhere in Australia.

All orders must be prepaid.

Prices and specifications are subject to change without notice.

Send \$1.00 for our Hardware Catalogue which describes our complete range of NDK printers, OPAL systems and contains a summary of CP/M software.

The SOFTWARE OMNIBUS (\$5.00) contains a complete description of all Software retailed by John F Rose Computer Services Pty Ltd together with user feedback and information about software versions.

FMS-80

FMS-80 is a comprehensive file management system, designed for use by everyone from novice to advanced programmers. It is the first complete data management system for CP/M, MP/M or CDOS. The program is completely menu-driven using a set of interactive integrated component programs.

FMS-80 leads you interactively through defining file and record descriptions, making additions, deletions and corrections and generating reports from your data files. FMS-80 will help you define selection criteria, to extract information for your reports by upper and lower limits, specific values for fields, relative values among fields, across multiple files, etc.

For example: All employees between the ages of 40 and 50 who received an annual salary greater than \$20,000.00. With FMS-80, selection criteria can include logical connections between fields or among groups of fields. Reports and printed summaries are easy to produce. FMS-80 leads you interactively through its report generation program; asking questions and producing reports only with the information you request, placing data in any format on a page or across multiple pages. Thus you can fill in prepared forms and create reports to fit your own unique specifications. Using the report generator's math functions, summaries, price extensions, etc., are all readily available at print time.

File definition allows you to interactively tell the computer how to keep track of desired data. Each record of information can contain up to 255 fields with each field containing up to 255 characters. Altering field size or addition and deletion of fields allow data files to grow and change with your needs. Duplicate data entry is eliminated.

FMS-80 allows you to specify which field or fields constitute a Master key or various secondary keys. The system uses these keys to build indexes for rapid retrieval of any record in a file when performing updates or queries. Any field may be used by record selection, even though it was not previously selected and defined as a key field. Data files can be recorded into various sequences to allow display of data ordered to your specifications.

FMS-80 selection features allow you to extract data from a file using your own specifications. Data can be selected by a range of values, conditions (equal or unequal), or relations to other fields. After a record has been selected using your specifications, the data can be summarized, stored in another data file, or printed. Regardless of complexity, selection never requires more than a single pass of the file. Using the advanced features of FMS-80, program like commands allow data selection and extraction from multiple files.

FMS-80 can specify the format on the screen for data display and collection. A complete form can be outlined on the screen to ease data entry. If your data collection requirements will not fit on a single screen, you can define multiple screens in each screen definition. Through the extended file maintenance (EFM) feature, data from multi-

ple record and multiple files can be displayed simultaneously on a single screen. In addition to the normal error checking of alphabetic and numeric type data, EFM allows specific data entry validation.

Using FMS-80 application programs or other non-related programs can be executed. Not only can a single program be invoked, but a series of programs can be linked and executed by selecting a single menu entry. (for example WORDSTAR/MAILMERGE, General Accounting Package (GAP), DATASTAR, etc., can be called from a single master menu). Application programs could be written in CBASIC (or BASIC-80) and run using FMS-80 files.

FMS-80 allows 3 methods of generating printed reports. The simplest method allows the system to format printed data in columnar fashion. With the FMS-80 report generator you can define the format of the data printed for such things as cheques, statements and order forms, or simply arrange the data the way you want it to look. Any number of "header" or "footer" lines can be defined as well as page length and width. Multiple records can be placed on a page or a single record can fill a page or multiple pages. FMS-80 will paginate, fitting the correct number of entries on each page. Using the contents of the data fields, a variety of functions can be controlled. "Header" or "Footer" substitution, new page control, math functions performed, or summary lines can all be accomplished. The most powerful report generation is accomplished through EFM. In addition to the above features, data can be drawn from multiple sources, including the terminal or multiple files.

The QUERY function allows online browsing of a data file. Any previously built indexes and/or screen descriptions may be used when retrieving data.

FMS-80's Extended File Maintenance (EFM) brings the full capability of FMS-80 under full control. EFM allows you to develop applications faster than programming in BASIC or other languages because all the complex screen and report handling functions are handled for you. Split screen formatting, multiple data file access and generation and selection are some of the features provided. Additional EFM capabilities include:

- Processing up to 20 files at a time.
- Reformatting and expanding data records and files.
- Combining multiple input files along with terminal input to produce one or more output files, printed reports or terminal display.
- Math functions including addition, subtraction, multiplication and division on fields containing numeric data.
- Control statements available when creating an EFM request include CALL, IF-THEN-ELSE, SWITCH/CASE and GOTO.
- End of file and on error conditions for the file input/output are supported.
- Extensive screen handling and printer handling are available.

Price: \$950.00 (Quantity discounts are available).

Formats: Micropolis Mod II (Q2), Northstar Single/Double/Quad (P2), 8" IBM. (a1).

JOHN F. ROSE COMPUTER SERVICES PTY. LTD.

33-35 ATCHISON STREET, ST. LEONARDS, N.S.W., 2065, AUSTRALIA.
TELEPHONE: (02) 439 1220 TELEEX: AA 27901

Wordsquare — a game for the TRS80

A. Lacy

Simpler than Scrabble, cheaper than crosswords and more humane than Hangman, we present Wordsquare, your very own cure for insomnia.

THIS PROGRAM is designed to run on a Level II TRS80 equipped with a printer, and it occupies under 4K bytes. It accepts a list of words and then constructs a word puzzle of the type you have, no doubt, seen for sale in newspapers.

I find this program very useful; the puzzles it produces keep my family occupied for hours on end while I am at the keyboard! It is designed to be used by 'non-computer' people, and this is the reason for the emphasis on input error trapping and the 'chatty' style of the prompts.

Many of the statements are special features of the TRS80, notably CLS, which clears the screen, and INKEY\$, which is a single keyboard scan and does not need the 'ENTER'. I believe the PET has a similar statement called 'GET'. Only one PEEK is used and this is not essential to program operation

anyway, which should please some readers.

The wordsquare and the word list to be used are represented by string arrays S\$(n,m) and W\$(n) respectively. The program attempts to find vacant areas or matching letters in the array S\$(n,m) and put in the words from W\$(n). It will try all directions, including backwards and diagonally, and a fair amount of string handling takes place. Not surprisingly, the program can take several minutes to run; in fact it will sometimes appear to 'hang' and won't even respond to the break key. This is due to the fact that the TRS80 has to reorganise its string storage areas occasionally and ignores the keyboard while it is doing this. (This is called Garbage Collection.)

When the puzzle has been constructed it will first be displayed on the screen without the usual jumble of random letters; you can cheat at this point if you

wish. The video display section is included for debugging and checking purposes; if you wish to remove it then delete lines 730-800. There is an option for suppressing the usual list of words which are included in the puzzle, which makes it much more difficult, the only clues given in this case being a list of dashes corresponding to word lengths. I have included an example of each option; I am sure readers will find them trivial!

The word list W\$(n) is sorted into words of descending length because this reduces execution time by allowing the longest words to be put into a nearly vacant array first, the shorter words then being fitted around and through them.

The randomising methods used ensure that no two puzzles are similar even though they may contain the same words.

SALTY

```
F P U Y Y Y O K R V B Z F L L PERIWINKLE
V P E R I W I N K L E E Y X N SEASHELL
X E R U M E Q S L E S S U M C STARFISH
Z C L A M W H S I F R A T S N SCALLOPS
N S B S L O N E S L I M P E R ABALONES
K L E H W C S O B R O Z A R U COCKLES
E U C H I D C E C O Y S T E R COWRIES
P C O N C H A A A O L Y L J O MUSSELS
K T W R H I L F T S C R Z E Y OYSTER
T R R T Q P L S S J H K A X E LIMPET
N D I J F K O T X Y X E L E B RAZOR
V N E H I M P K R X S X L E P CONCH
S H S C Z N S B Z G S N G L S WHELK
M S F P S O X C Q L T U A G U PEARL
W P L M S C B S K L J Y T O Z MUREX
                                CLAM
```

BYTE THIS

```
Z C L O A D Y X L N U W Y N C
Q T U Y A H D U O A D D G O B
F I T A R F E X W O N W W I E
E E W S T A R P M A I G K T N
Y J E N S W N E T Z F B M U C
Y A D O T G N I T U P M O C H
T I N T E G E R B N R Q T E M
M S O F T W A R E T I X W X A
I I N T E R R U P T Z R B E R
G M I C R O S O F T P P P W K
B H E X A D E C I M A L F K S
H B L R E N I T U O R B U S D
M H T I R O G L A Q U U R Q X
B C K R Y O L S G U B E D Z P
C P J Q D D R L E D J K K E W
```

Two specimen "Wordsquares" as produced by the program.

Variables used

A,C,D,G,P,X,I	Counters temporary storage integers.	Q\$	Temporary storage for single letter replies.	S\$(n,m)	The string array representing the wordsquare.
C(n)	List of shuffled vertical coordinates.	R(n)	List of shuffled horizontal coordinates.	T\$	Title.
C1,C2	Temporary storage for vertical coordinates.	R,R1,R2	Temporary horizontal coordinates.	W\$(n)	List of inputted words.
D(n)	List of shuffled directions.	S\$	Temporary storage inputted words.	W1,W2	Pointers into W\$(n).
				X1,X2	Used in row and column shuffle.

Program listing

```

10 REM WORDSQUARES
20 REM
30 REM INITIALISE
40 CLS
50 CLEAR 400
60 DEF INT A-Z
70 DIM C(15),R(15),D(8),W$(16),S$(15,15),R2(15),C2(15)
80 PRINT TAB(20) "WORDSQUARES"
90 PRINT TAB(20) "YOU WILL NEED A PRINTER
FOR THIS PROGRAM. TYPE IN A LIST OF UP TO 16 WORDS OR TYPE
'@' IF YOU WISH TO USE LESS. THE MAXIMUM NUMBER OF LETTERS
IN A WORD IS 15, BUT IF YOU"
100 PRINT "USE TOO MANY LONG WORDS THE PROGRAM WILL TAKE
AGES TO RUN. IN FACT IT MAY NOT BE ABLE TO FIT YOUR WORDS IN
AT ALL! IF SO IT WILL TELL YOU (EVENTUALLY)"
100 REM**SHUFFLE COORDINATES
120 FOR A = 1 TO 15:C(A) = A:R(A) = A:IF A < 9 THEN D(A) = A
130 NEXT
140 FOR A = 1 TO 15
150 R1 = RND(15):R2 = RND(15):X1 = R(R1):X2 = C(R2):R(R1) = R(A):
C(R2) = C(A):R(A) = X1:C(A) = X2
160 NEXT
170 REM**INPUT WORDLIST
180 PRINT"NOW TYPE IN YOUR LIST"
190 FOR W = 1 TO 16
200 INPUT S$:IF S$ = "@" THEN 280
210 IF W = 1 THEN CLS:PRINT@2,S$
220 W$(W) = S$
230 REM**TEST THE WORD FOR LENGTH AND CONTENT, S IS ERROR
FLAG
240 S = 0
250 GOSUB 1030
260 IF S = 1 THEN 200
270 NEXT
280 W = W-1
290 CLS:PRINT@590,"THIS COULD TAKE ME A FEW MINUTES";
300 REM**SORT WORDS, LONGEST FIRST
310 GOSUB 1190
320 PRINT@590,CHR$(30);
330 REM**CHOOSE THE NEXT WORD
340 FOR W1 = 1 TO W
350 REM**RANDOMISE DIRECTIONS
360 FOR A = 1 TO 8:R = RND(8):X = D(R):D(R) = D(A):D(A) = X:NEXT
370 REM**CHOOSE A COORDINATE
380 FOR R = 1 TO 15
390 PRINT@600,"THINKING";
400 FOR C = 1 TO 15
410 R1 = R(R):C1 = C(C)
420 REM**CHOOSE A DIRECTION
430 FOR D = 1 TO 8
440 REM**CAN IT BE FITTED?
450 FOR I = 1 TO LEN(W$(W1))
460 ON D(D) GOSUB 1090,1100,1110,1120,1140,1150,1160,1170
470 REM**OFF THE EDGE?
480 IF R2 > 15 OR R2 < 1 OR C2 > 12 OR C2 < 1 THEN 580
490 S$ = MIDS(W$(S1),I,1)
500 IF S$(R2,C2) < > "" AND S$(R2,C2) < > S$ THEN 580
510 R1 = R2:C1 = C2:R2(I) = R2:C2(I) = C2
520 NEXT I
530 REM**OK WE HAVE A WORDFIT SO PUT IT IN THE ARRAY
540 FOR I = 1 TO LEN(W$(W1))
550 S$(R2(I),C + (I)) = MIDS(W$(W1),I,1)
560 NEXT I
570 GOTO 700
580 NEXT D
590 REM**MUST HAVE FAILED TO FIND FIT SO TRY ELSEWHERE
600 PRINT@609,"HARD!";
610 NEXT C
620 PRINT@600,CHR$(30);
630 NEXT R
640 REM**TO GET HERE MUST HAVE FAILED FOR ENTIRE ARRAY
650 CLS:PRINT"SORRY, I CAN'T COPE WITH '";W$(W1);"' , DO YOU
WANT TO START"
660 PRINT"AGAIN (PRESS 'S') OR PRINT OUT THE PARTLY DONE
WORDSQUARE ANYWAY (PRESS 'P')"
670 Q$ = INKEY$:IF Q$ = "" THEN 670
680 IF Q$ = "S" THEN RUN ELSE CLS:GOTO 730
690 REM**GET THE NEXT WORD
700 NEXT W1
710 REM**PRINT OUT THE ARRAY TO SCREEN
720 PRINT@600,"GOT IT!!!!";CHR$(30);:FOR A = 1 TO 800:NEXT:CLS
730 FOR R = 1 TO 15
740 PRINT
750 FOR C = 1 TO 15
760 IF S$(R,C) = "" THEN PRINT". ";:GOTO 780
770 PRINT S$(R,C);" ";
780 NEXT C,R
790 PRINT"PRESS A KEY";
800 IF INKEY$ = "" THEN 800
810 CLS
820 REM**PRINTER STATUS CHECK (OPTIONAL)
830 GOSUB 1260
840 REM**PRINT TO PRINTER
850 PRINT"TYPE IN A TITLE FOR YOUR WORDSQUARE THEN PRESS
ENTER"
860 PRINT
870 INPUT T$
880 PRINT"BY THE WAY, DO YOU WANT THE WORDLIST PRINTED AS
WELL? (Y OR N)"
890 Q$ = INKEY$:IF Q$ = "" THEN 890
900 IF Q$ < > "Y" AND Q$ < > "N" THEN 890
910 LPRINT TAB(25)T$
920 LPRINT TAB(25)STRINGS(LEN(T$),".");:LPRINT
930 FOR R = 1 TO 15
940 FOR C = 1 TO 15
950 IF S$(R,C) = "" THEN LPRINT CHR$(RND(26) + 64);" ";ELSE LPRINT
S$(R,C);" ";
960 NEXT C
970 IF Q$ = "N" THEN LPRINT TAB(48)STRINGS(LEN(W$(R1)),".");ELSE
LPRINT TAB(48)W$(R)
980 LPRINT
990 NEXT R
1000 IF Q$ = "N" THEN LPRINT TAB(48)STRINGS(LEN(W$(R1)),".");ELSE
LPRINT TAB(48)W$(R)
1010 FOR X = 1 TO 4:LPRINT:NEXT:RUN
1020 REM**INPUT TESTING
1030 IF LEN(W$(W1)) > 15 THEN S = 1:PRINT"THIS WORD IS TOO LONG. TRY
AGAIN":RETURN
1040 FO A = 1 TO LEN(W$(W1))
1050 S$ = MIDS(W$(W1),A,1)
1060 IF S$ < "A" OR S$ > "Z" THEN S = 1:PRINT"LETTERS ONLY
PLEASE.":RETURN
1070 RETURN
1080 REM**HORIZONTALS AND VERTICALS
1090 R2 = R1 + 1:RETURN
1100 R2 = R1 - 1:RETURN
1110 C2 = C1 + 1:RETURN
1120 C2 = C1 - 1:RETURN
1130 REM**NOW THE DIAGONALS
1140 R2 = R1 + 1:C2 = C1 + 1:RETURN
1150 R2 = R1 + 1:C2 = C1 - 1:RETURN
1160 R2 = R1 - 1:C2 = C2 + 1:RETURN
1170 R2 = R1 - 1:C2 = C2 - 1:RETURN
1180 REM**WORDLENGTH SORT
1190 S = 0
1200 FOR W1 = 1 TO W - 1
1210 IF LEN(W$(W1)) < LEN(W$(W1 + 1)) THEN S$ = W$(W1):W$(W1) =
W$(W1 + 1):W$(W1 + 1) = S$:S = 1
1220 NEXT
1230 IF S = 1 THEN 1190
1240 RETURN
1250 REM**PRINTER CHECK TO PREVENT SYSTEM HANG
1260 IF PEEK(14312) <= 127 THEN RETURN
1270 PRINT"PRINTER NOT READY!! PRESS 'P' WHEN THE PRINTER IS
READY OR 'S' TO START AGAIN"
1280 Q$ = INKEY$:IF Q$ = "" THEN 1280
1290 IF Q$ = "S" THEN RUN
1300 IF PEEK(14312) <= 127 THEN 1270
1310 IF Q$ = "P" THEN CLS:RETURN
1320 GOTO 1280

```


PICK YOUR PERIPHERALS CAREFULLY

Can you be SURE of getting unbiased advice
about what you really need?

We stock a range of products including:

COMPUTERS:

IMS International
Exidy Sorcerer

TERMINALS:

IMS International
Televideo
Soroc
Visual Technology

PRINTERS:

Datasouth
NEC
Qume
Impact Data
MPI — New 88G (Graphics)
Malibu — New 200
Centronics (new 737)
IDS — Paper Tiger
Texas Instruments
Howard — Olivetti

SOFTWARE:

Micropro: Wordstar, Supersort, Datastar.
Digital Research: MP/M, CP/M,
MVT, EFamos & Basic.
Davidson Accounting Packages,
— Australian designed and produced.
Microsoft: Fortran-80, Cobol-80, Basic-80.

S-100 SPECIAL BOARDS:

Calendar Clock
Microangelo Graphics Boards

SPELLGUARD
WORD
PROCESSOR
DICTIONARY

Dealer and OEM discounts available where appropriate,
CAN YOU AFFORD NOT TO CHECK WITH US???

S.I. MICROCOMPUTER PRODUCTS PTY LTD

GPO BOX 72 SYDNEY 2001 92 PITT ST SYDNEY (02) 2314091 232 6804
Melbourne (03) 26-5522. Brisbane (07) 52-8455. Hobart (002) 28-6288.

INTRODUCING

S100 MULTIUSER SYSTEMS

Microtrix continues to present state-of-the-art microcomputer products. Our extremely popular single-user system can now be easily expanded to cater for two, or up to five, users.

This has been made possible by a new intelligent multiuser input/output board. Known as the MPC-4, it provides four serial I/O channels with individual baud rate selection, and an input and output buffer for each port. Data transfers are efficiently handled by interrupt driven techniques.


An on-board Z-80 Microprocessor controls the functions of the MPC-4, freeing the main CPU to complete other tasks. This creates a more efficient and higher performance system.

But that's not all! The hardware is backed up by a sophisticated multiuser operating system: COSMOS. CP/M compatibility is maintained, but file protection is greatly enhanced. Both global and local files are supported. An editor, Z-80 assembler, linker, loader, CBASIC 2, and a full set of utility programs are provided. These, together with a time-of-day clock, make the system appear like more expensive minicomputers. And COSMOS will also support a hard disc when required.

The MPC-4 and COSMOS are available separately, or complete systems can be configured to suit your requirements.

So, for the latest in microcomputer technology, contact us now.

DEALERS REQUIRED AUSTRALIA-WIDE

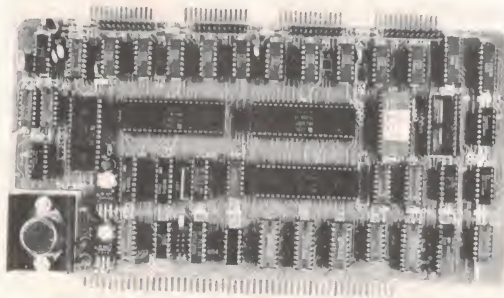

SYSTEM PRODUCTS

SBC 200 Single Board Computer	\$400 kit	\$470 A/T
Versafloppy 2 Double density controller	\$425 kit	\$485 A/T
Expandoram 2 Dynamic RAM 16K	\$360 kit	\$420 A/T
Expandoram 2 Dynamic RAM 64K	\$600 kit	\$660 A/T
VDB8024 Video card with Z-80	\$450 kit	\$520 A/T
PROM 100 PROM programmer	\$245 kit	\$295 A/T



MICROTRIX


PO Box 158, Hurstbridge, Victoria 3099
Phone (03) 718-2581

A complete catalogue of all our products is available for the asking.
Please add 15 percent sales tax to the above figures if applicable.
Postage on any single board is \$3.



Dot Matrix Printer
less than \$500!

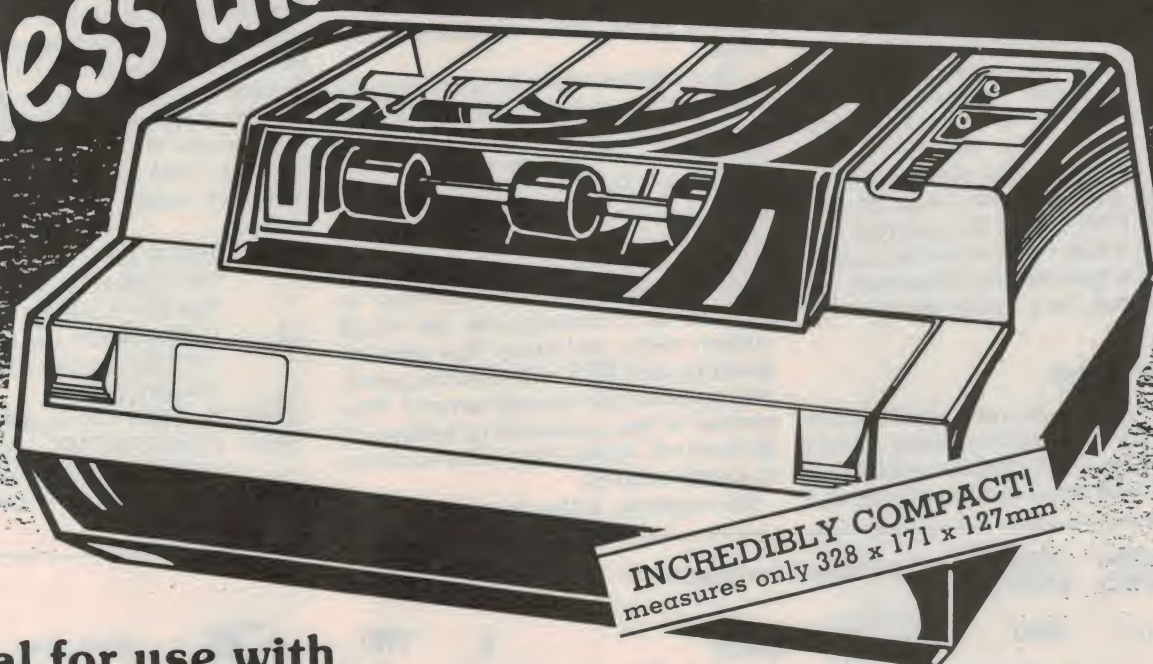who else but
DICK SMITH
could offer
value like this?



INCREDIBLY COMPACT!
measures only 328 x 171 x 127mm

Ideal for use with System 80, TRS 80, Sorcerer & other computers

Up until now you would expect to pay around \$1,000 for a dot matrix printer. We've changed all that with the release of this compact 80 column tractor-feed impact printer. If you're into computers, then this is the printer for you!

NB: Wrong catalogue No. and price shown for this item in our 1981/82 catalogue.

look at these features:

- Full 80-column printing
- Tractor-feed as standard
- Printing at 30 characters/second
- High-resolution graphics printing
- Standard Centronics-type parallel interface
- Compact size: only 328 x 171 x 127mm



Credit terms available
to approved applicants

Optional cable required for connection of printer to computer.
Type depends on computer.

all this for only
\$495
Cat. X-3252
P&P \$5.50

Fan Form Paper

2,000 sheets continuous fan
form paper to suit printer
Cat. X-3254 \$27.50


Replacement Ribbons

Cat. X-3253
\$6.95

BE EARLY — WE EXPECT DEMAND TO BE HEAVY!

DICK SMITH ELECTRONICS

NSW: 145 Parramatta Rd **AUBURN** 648 0558, 613 Princes Hwy **BLAKEHURST** 546 7744, 818 George St **BROADWAY** 211 3777, 531 Pittwater Rd **BROOKVALE** 93 0341, 147 Hume Hwy **CHULLORA** 642 8922, 162 Pacific Hwy **GORE** 211 3777, 531 Pittwater Rd **BROOKVALE** 683 1133, 125 York St **SYDNEY** 290 3377, 263 Keira St **HILL** 439 5311, 30 Grose St **PARRAMATTA** 683 1133, 125 York St **SYDNEY** 290 3377, 263 Keira St **WOLLONGONG** 28 3800, ACT: 96 Gladstone St **FYSHWICK** 80 4944, QLD: 166 Logan Rd **BURANDA** 391 6233, 842 **Gympie Rd** **CHERMSIDE** 59 6255, SA: 60 Wright St **ADELAIDE** 212 1962, VIC: 399 Lonsdale St **MELBOURNE** 67 9834, 656 Bridge Rd **RICHMOND** 428 1614, Cnr Dandenong & Springvale Rds **SPRINGVALE** 547 0522, WA: 414 William St **PERTH** 328 6944, Cnr Wharf St & Albany Hwy **CANNINGTON** 451 8666
Mail Order Centre: PO Box 321, North Ryde, NSW 2113, Ph. (02) 888 3200

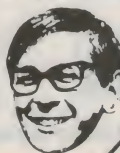

**The name for value
in computers and
peripherals**

PET Talk — double density

Paul Williams

Double the plotting capacity of PET with this routine.


THE FOLLOWING simple program listing allows plotting of characters on an 80 by 50 grid on the PET screen, thus enabling more precise graphs and pictures to be drawn. The first two lines of the program (lines 1 and 2) should be included at the beginning of the program that is to use the double-density feature; they initialise the two arrays required. The plotting section (the last two lines) can be called by a GOSUB 1000 during the program run, after an x and y value has been specified. The x value should be between -39 and 39, and the y value between -24 and 24.


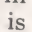
Where to go

Assigning 0 to both x and y will produce a dot in the centre of the screen: -39 for x and 24 for y will produce a dot in the top left-hand position of the screen, and

39 for x and -24 for y will be in the bottom right-hand corner of the screen. Thus the positions radiate as for a normal graph from the centre of the screen.

The program works by arranging the codes for the sixteen different double-density graphics in such a way that if the position of the code already on the screen is ORed in binary with the position in the array of the code that you want to put on the screen, the resulting position will give the code containing both the characters that you want to plot. Array S contains the list of all sixteen codes, and array T is used for decoding the PEEK code from the screen into a position for use with array S. This method is best explained by looking at the array S. Table 1 shows the contents in graphical form.












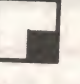
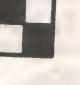

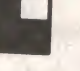

For example, if the character  was

on the screen, and the character  wanted to be added, the position of the first character, 0 0 0 1, is ORed with the position of the second character, 0 1 1 0; the result obtained is 0 1 1 1, which, in the table, is the character , which is the one required to POKE on to the screen. Line 1010 of the subroutine does this, as well as calculating which character needs to be added to the screen.

```

1  DIM S(15),T(255):FOR T=0
   TO 15:READ S(T):
   T(S(T))=T:NEXT T:T=0
2  DATA 32,123,126,97,108,98,
   127,252,124,255,226,236,225,
   254,251,160
1000 S=33267+(X/2)-INT(Y/2)*40
1010 POKE S,S(T(PEEK(S)) OR
   (2*((X/2-INT(X/2))*4+
   ((Y/2-INT(Y/2))*2)▲2)))
   RETURN

```

POSITION IN ARRAY	BINARY POSITION	DECODED CHARACTER					
0	0000		SPACE	8	1000		SHIFTED <
1	0001		SHIFTED ;	9	1001		RVS SHIFTED ?
2	0010		SHIFTED >	10	1010		RVS SHIFTED "
3	0011		SHIFTED !	11	1011		RVS SHIFTED ,
4	0100		SHIFTED ,	12	1100		RVS SHIFTED !
5	0101		SHIFTED "	13	1101		RVS SHIFTED >
6	0110		SHIFTED ?	14	1110		RVS SHIFTED ;
7	0111		RVS SHIFTED <	15	1111		RVS SPACE .

© COPYRIGHT MODMAGS Ltd

Table 1. The block graphics characters and their binary and character key designations for producing the double density effect.

Commodore Computer Users...

Put this on your reading list.


The new Commodore computer magazine is out now.

Prepared specially for Australia, there are up-to-the minute details on Commodore hardware. Reviews on Software. New product releases.

Programming information and service tips.

RAM and ROM maps for all Commodore computers.

Plus much more.

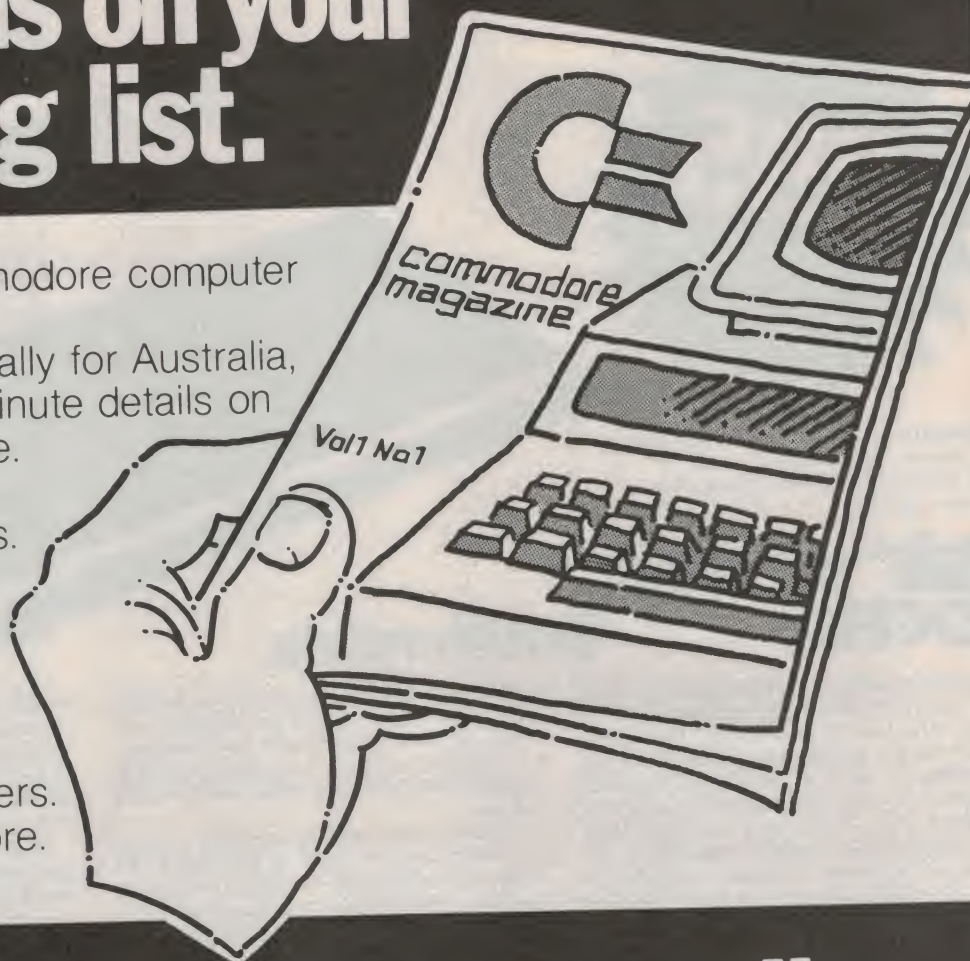

And put this in the mail.

If you send us this coupon with a cheque or money order for \$30 (your annual subscription for 8 copies) you'll be saving 25% on the normal cost of Commodore Magazine.



Yes I'd love to save \$10 on my subscription to Commodore Magazine. Enclosed is my full payment of \$30:

NAME _____

ADDRESS _____



commodore

Commodore Magazine, PO Box 336,
Artarmon NSW 2064.

Australia's first under \$300 COMPUTER...

\$295

INCL. ZX80 BASIC
MANUAL

Remember — all prices shown include sales tax, postage and packing.

N.B. Your Sinclair ZX80 may qualify as a business expense.

Sinclair ZX80

-British made.



Until now, building your own computer could cost you around \$600 — and still leave you with only a bare board for your trouble. The Sinclair ZX80 changes all that. For just \$295 you get **everything** you need including leads for direct connection to your own cassette recorder and television. The ZX80 really is a complete, powerful full-facility computer matching or surpassing other personal computers costing much more. The ZX80 is programmed in BASIC and you could use it for anything from chess to running a power station.

Two unique and valuable components of the Sinclair ZX80: the Sinclair BASIC interpreter and the Sinclair teach-yourself BASIC manual. The unique Sinclair BASIC interpreter: offers remarkable programming advantages — unique 'one touch' key word entry. The ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST etc) have their own


single key entry. Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately, preventing entry of long and complicated programs with faults only to discover them when you run.

Excellent string handling capability — takes up to 26 string variables of any length. All strings can undergo all rational tests (e.g. comparison). The ZX80 also has string input to request a line of text; strings do **not** need to be dimensioned. Up to 26 single dimension arrays. FOR/NEXT loops nested up to 26. **Variable names** of any length. BASIC language also handles full Boolean arithmetic, conditional expressions, etc.

Exceptionally powerful edit facilities, allows modification of existing program lines. **Randomise function**, useful for games and secret codes. **Timer under program control**. PEEK and

POKE enable entry of machine code instructions.USR causes jump to a user's machine language sub-routine. **High resolution graphics** with 22 standard graphic symbols. The Sinclair teach-yourself-BASIC manual 96 page book free with every kit.

Fewer chips, compact design, volume production means MORE POWER FOR YOUR DOLLAR! The ZX80 owes its low price to its remarkable design: the whole system is packed onto fewer, newer more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer because the ZX80's brilliant design packs the RAM so much more tightly. (Key words occupy just a single byte). You can add to the memory via the expansion port, giving a maximum potential of 16K.

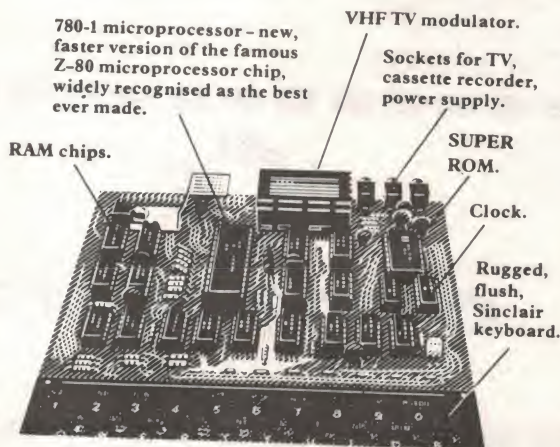

ORDER FORM:

SINCLAIR EQUIPMENT (AUSTRALASIA) PTY. LTD.
308 High St., Kew 3101, Vic. Tel. 861 6224.

308 High St., Kew 3101, Vic. Tel. 861 6224.

308 High St., Kew 3101, Vic. Tel. 861 6224.

308 High St., Kew 3101, Vic. Tel. 861 6224.

308 High St., Kew 3101,

More POKEing on your ZX80

M.E. Bryant

Last month we showed you the basics of using screen POKEs on your ZX80. This month we round it all off with an example program.

Graphic Example

Just for fun, here is a simple program that demonstrates the features discussed in the last article. It just fits in the 1K ZX80. The computer prints up a display consisting of black and grey squares in a pattern determined by a number input at the beginning of each series of games. The object of the game is to get the "woodworm" (an asterisk), which first appears at line 8 column 1, to eat its way across the screen to column 32 in the least number of moves. The snag is that the black squares represent a particularly tough kind of wood and each time one is eaten a penalty of 5 moves is incurred. Numerals 6, 7 or 8 are input as pseudo-cursor controls to move the insect down, up, or forwards respectively. The computer keeps track of the number of moves taken to reach column 32 and displays the total at the end of each game together with the best performance in the present series. Pressing NEWLINE after a game sets up another game in the same series. Entering a character starts a new series.

```

2 LET Y = 32000
4 INPUT R
    No. of moves -- best so far!
    Seed for random number
    generator

8 LET P = 0
10 LET W = 0
12 LET B = 1
14 LET A = 8
16 LET Z = -1
18 LET M = 0
20 RANDOMISE R
    Assign variables prior to PEEK
    and POKE

24 FOR N = 1 TO 32
26 LET D = 9
28 IF X = 1 THEN LET D = 128
    Set seed for random number
    generator

    Print eleven lines with black and

```

```

30 PRINT CHR$(D);
32 NEXT N
34 GOSUB 500
36 POKE W + 232, 20
38 LET Z = Z + 1
40 INPUT C
42 GOSUB 500
44 LET M = W + (A - 1)*33 + B
46 POKE M, 0
48 IF C = 6 AND A < 11 OR C = 7 AND
   A > 1 THEN LET A = A - 2*C + 13
50 IF C = 8 THEN LET B = B + 1
52 LET M = W + (A - 1)*33 + B
54 IF PEEK(M) = 128 THEN LET Z = Z + 5
56 POKE M, 20
58 IF B = 32 THEN GOTO 62
60 GOTO 38
62 IF Z < Y THEN LET Y = Z
64 PRINT "END OF GAME IN ";Z;"
   MOVES"
66 PRINT "BEST SO FAR ";Y;" MOVES"
68 INPUT X$
70 CLS
72 IF X$ = " " THEN GOTO 8
74 RUN
500 LET P = PEEK(16397)
510 IF P > 127 THEN LET P = P - 256
520 LET W = PEEK(16396) + P*256
530 RETURN

```

grey squares at random. Pattern determined by R.

Locate display-file
Insect in initial position
Count No. of moves
Which way?
Locate display-file

Put a space where insect is
Set A and
way and make sure we don't
POKE off-screen

Set M to next insect location
address
If there's a black square in the
way, add penalty
Put insect in next location
Watch for end of game
Next move
Set Y to best so far

NEWLINE for another game
Any character for another series

Subroutine for setting W to
address of start of display-file

DON'T BUY A PERSONAL COMPUTER!

until you have checked Seahorse Computer's prices on APPLE & COMMODORE systems.

e.g. • 16K APPLE'S from \$1306.95 + S.T. • 8K COMMODORES from \$722.00 inc. tax.

- We talk to our customers
- We service what we sell
- We support our sales with Australia's most comprehensive Range of High Quality Software

Personal callers welcome
We Mail Order all over Australia.

— Personal cheques — Bankcard
— Visa — Mastercharge

*APPLE, Reg. T.M. of APPLE INC., Cupertino, CA, U.S.A.
COMMODORE, Reg. T.M. of COMMODORE INC., U.S.A.




SEND FOR OUR FREE COMPREHENSIVE CATALOGUE
OF HARDWARE & SOFTWARE FOR:— APPLE,
COMMODORE, SORCERER & TRS-80

SEAHORSE COMPUTERS

33 MITCHELL STREET,
CAMDEN 2570

PHONE (046) 66 6406

P.O. BOX 47
CAMDEN 2570

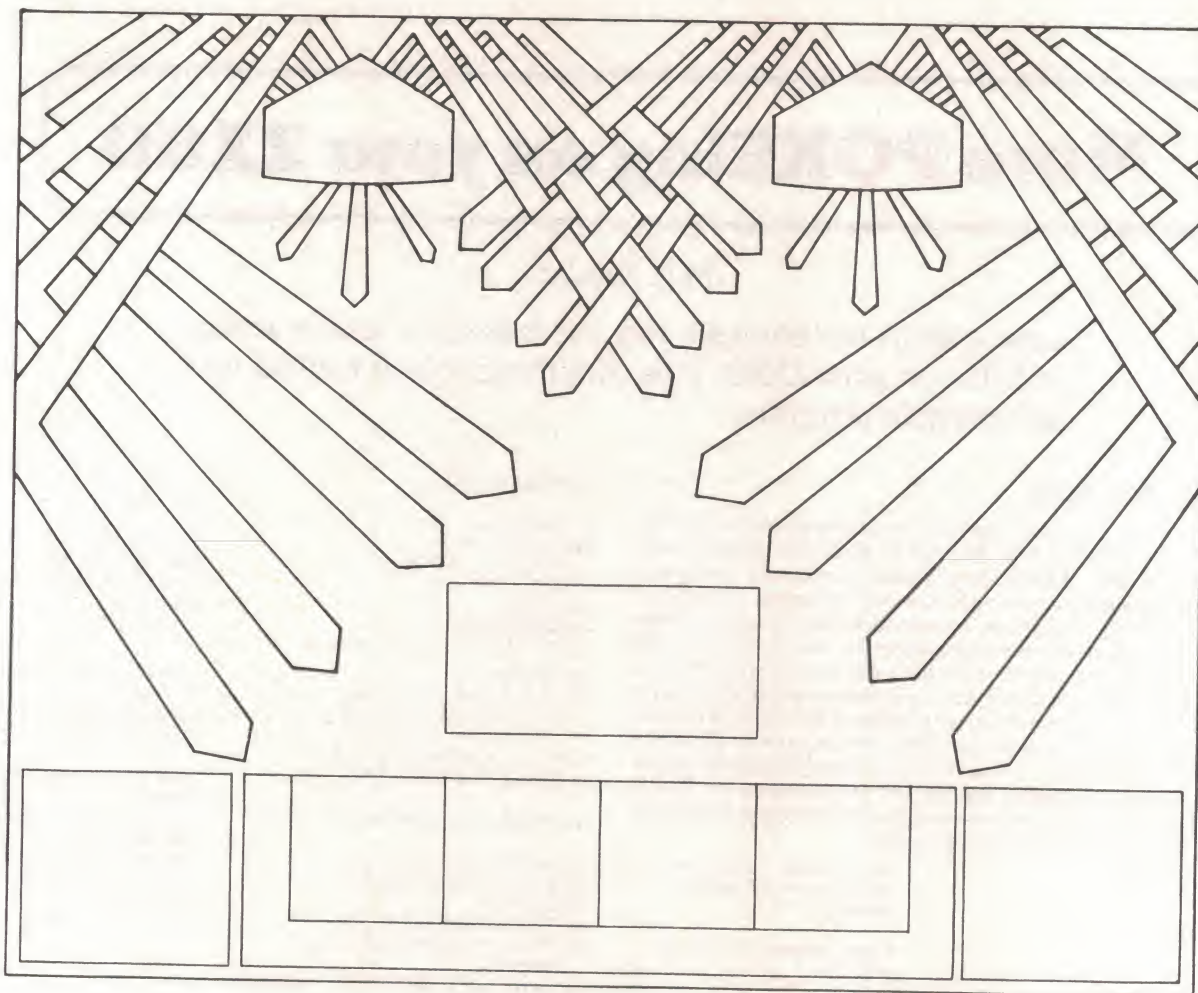

**Now the Bose® 901® Series IV system.
It overcomes the greatest obstacle to fine performance.
Your living room.**


Introducing the new Bose 901® Series IV Direct/Reflecting® speaker. With two major improvements.

There is a new equalizer with two controls that allow you to simultaneously adjust broad portions of the frequency band to compensate for acoustical differences from one living room to the next.

There is also a new driver so

advanced in materials and design that Bose has removed the power limitations for home use. Yet this speaker can still be driven with as little as ten watts per channel.

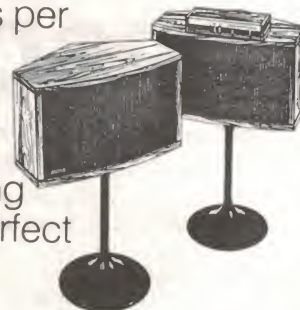The Bose 901® Series IV turns your perfect living room into the perfect listening room.



BOSE®

**BOSE AUSTRALIA INC., 11 MURIEL AVENUE, RYDALMERE, NSW 2116.
TELEPHONE (02) 684-1022, 684-1255.**

SIGHT & SOUND

Software's the key in the videodisc war

Philips might have the best system technically, Japan's VHD is moving fast and has a lot of oriental clout behind it, and RCA's Selectavision is at present the cheapest, but in the end it's the videodisc system that can provide the movies the public wants — and lots of them — that will win out in the market.

MARCH 1981 officially saw the videodisc war get under way.

Philips' laser-optical players have been test-marketed in the US for the last eighteen months or so, under the names of both Pioneer and Magnavox, but for reasons we'll explore later haven't swept the market despite this staggering time advantage. The other two systems promised as contenders in the videodisc war seemed at times as if they'd never get off the ground, but finally things are hotting up.

RCA (an American system) launched its Selectavision system on March 23 with an advertising and promotion budget of US\$15 million. It will sell for US\$499 and has a library of videodiscs priced at between US\$14 and US\$27. This library falls short by 50 of the promised 150 titles, but RCA says it will introduce another 25 in May and 25 in August.

Meanwhile the JVC-developed VHD (Video High Density) system from Japan is also a reality following the opening of a videodisc manufacturing plant in Los Angeles in March.

RCA's Selectavision

The RCA player is priced at around US\$200 cheaper than the optical players from Magnavox and Pioneer, but lacks many of the facilities that their laser system offers. The Philips/Pioneer/Magnavox players have freeze frame, random search system, stereo sound, frame-by-frame advance, numbered frames, a laser beam for a stylus and a disc that will never wear out. In contrast the Selectavision system has only mono sound, straight play, and uses a \$70 stylus that sits in a groove similar to a standard audio record; both it and the discs will wear out.

However, RCA's system is by far the cheapest, as well as being scheduled to have 200 000 players into the US market by the end of twelve months, so both Philips and VHD have been forced to buck up their ideas if they aren't to be elbowed out of the market.

Japan's VHD system

There is to all intents and purposes only one video system in Japan, the reason being that the Japanese government 'suggested' that all Japanese manufacturers get behind one system — for obvious reasons. Pioneer has even been criticised on the government TV station NHK and in the press for not joining this 'Japan Club', but by now has too many millions tied up in the optical system to change sides now. Besides, it sees the optical system as the best and plans to support it to the end.

The VHD groundswell was quite a surprise to the industry, but it was obviously provoked by Philips' slowness in getting its system going as well as it should and by Selectavision's relative shortcomings. Matsushita announced about a year ago that it planned to back this third system, developed by its subsidiary JVC, and sure enough at the 1980 Tokyo Electronics Show not only Matsushita but nearly every major Japanese manufacturer was showing prototypes of the VHD videodisc, Pioneer and Sony being the only notable exceptions.

The Japan Club is slightly less solid on the more controversial international scene, however; Toshiba and Sanyo were proposing to make optical players for Europe, RCA Selectavision players for the US, as well as VHD players for the home market. Hedging their bets?

The VHD club, consisting of Mat-



Blockbuster movies — like *The Wild Geese*, starring Richard Burton (scene above) — on software will sell videodisc systems.

sushita (National Panasonic), JVC, General Electric and Thorn/EMI, plans to press discs for the movie companies and let them market the product themselves. This will save the electronics companies millions in royalties and will also assure the movie companies of maximum profits from the movie rights — which may well make them more willing to release movies for videodisc. The discs will be distributed by the movie companies in the same way as record companies distribute their own audio discs.

The VHD Manufacturing Co., just opened in Los Angeles, will press the discs for the movie companies for between US\$5.50 and US\$6.50 each, with a minimum production run of 3000. According to Gary Dartall, who heads both VHD Programs and VHD Disc Manufacturing, approximately 200 titles will be available in substantial quantities when the VHD player hits the US later this year.

The VHD system falls about midway between Philips and RCA in the features it offers, having a random access search system with an add-on component, and not actually touching the record so there's no surface wear.

Philips' laser system

The laser videodisc system developed by Philips is in the third

corner of the video war ring. In fact they've been out there sparring for a while now, but it wasn't till the competition made serious moves that they seemed to realise the war was on in earnest.

Panicked by RCA's cheapness and the sudden groundswell towards Japan's VHD system, Pioneer and Philips have finally started a push into the US market. Pioneer started shipping in big lots last October and plans to have placed over 100 000 machines into the US market by October this year. Philips' US subsidiary Magnavox has also increased production and by October should have 60% of the US market covered, geographically speaking. So Philips may still have a chance to head off both VHD and RCA — as long as they get their software — i.e. disc — problems sorted out.

Philips has negotiated to buy Sylvania and Philco, which are leading TV manufacturers. If successful, it will give Philips 10% of the TV market in the US and a formidable back-up to its optical videodisc marketing plans.

Meanwhile, back in Europe Philips is making sure that the optical disc player is the chosen PAL standard. It has built a hardware factory in Belgium to produce players and a software factory in the UK to make the discs using an as yet

undisclosed photographic process.

The Philips videodisc will be launched in the UK this year on a test market basis, and since it is the first PAL videodisc system it is of vital interest to Australia. We will inevitably source our software from the UK because we have the PAL TV system, while Japan and America have the NTSC colour system.

So the battleground is drawn up. RCA offers a cheap and cheerful player, Pioneer and Philips a sophisticated laser system they argue is the only way to go in the future, and VHD has its system which is a cross between the two. Since the ultimate winner will be the one which offers not superb technical performance nor a cheap price, but rather the largest selection of good, up-to-date, popular movies, it has to be the software which decides the outcome of the war.

The disc situation

Lack of software — discs — lies behind Philips not having swept the videodisc market despite having over a year's lead on the Selectavision and VHD systems.

When MCA Universal and Pioneer Electronics got together a few years ago it looked like the perfect marriage. Pioneer's job was to refine the laser disc player originally developed by Philips, while MCA, which has around a 50% share of the US entertainment scene, was to develop the software and provide the library — a European system, with hardware built by a Japanese company and software manufactured and provided by an American company.

Towards the end of 1979 it became obvious that all wasn't rosy. With Philips not taking an active part in the software side of the business, MCA was not producing enough titles or solving production problems of the optical videodisc. Both RCA and Matsushita executives cite these disc problems as the reason for their going ahead with their rival systems. MCA sold 50% of its share in the Universal Pioneer company, without explanation, to IBM. This gave Pioneer 50%, MCA Universal 25%, and IBM 25%.

Pioneer and Philips, impatient with the snail-like pace MCA was proceeding at with the software, formed their own company called Optical Programme Associates (with MCA Universal and IBM) to

actively pursue the necessary software for the laser system. Pioneer has also built a disc factory in Japan.

While the new 'photographic process' by which optical system discs are made hasn't yet been revealed by Pioneer or Philips, it's obviously a very different and newer process than that for both RCA and VHD discs, which can be pressed in a factory in a similar fashion to audio discs. However, both these rival discs have to be handled very carefully. The disc in both systems comes in a 'caddie' (like a record sleeve). The caddie with the disc inside it is pushed through a slot in the front of the player, then the disc settled into the player and the caddie removed from the slot. The reverse procedure has to be gone through to remove the disc. It must therefore be practically untouched by hand, whereas the laser system disc can be thrown across the room and jumped on without damaging it.

However, even if Pioneer's new factory and Philips' new photographic process have finally ironed out problems in disc production, it'll all be academic if they can't come up with good movies and up-to-date pop concerts to go on them. MCA Universal has a vast library of movies, but for some reason hasn't been making them readily available on laser discs; there are only 200 titles available in this system after 18 months in the marketplace.

The industry calls this the 'soft software' problem, but basically they mean movies. It's movies that will sell a system; no matter how good technically or how cheap a system may be, if the public can't get the range of movies and entertainment they want to go with it, they won't be buying that system.

What about Australia?

There is one sane thought for Australians in this complex international punch-up. The various manufacturers are going to be so busy fighting each other in the lucrative US and Japanese markets that they probably won't give us a thought.

The odds are that Philips will establish a PAL optical system in Europe and that is what we will eventually get. By the time they get round to launching it here, either late this year or early 1982, the market patterns elsewhere will probably be established — and there will already be a good supply

of movies available! The only threat to Philips on the PAL front is EMI-Thorn, who are backing the VHD system.

Pioneer has started the ball rolling in Australia by selling 300 players to GMH dealers around the country, an idea based on the American General Motors deal in which Pioneer Electronics supplied some 13 000 industrial videodisc players to dealers around the US for promotion of new car models and staff training. (See box on page 133.)

There's more to this than just expanding the videodisc market into business. Managing Director of Pioneer Electronics Australia, Les Black, says that selling 300 video-

disc players has subsidised the cost of setting up a service department for videodisc players in readiness for their launch in Australia. Not bad?

But don't get too excited. He also says that he has to give Japan six months' notice for stock in the PAL format — and he won't do this until he is sure there will be software to support it.

So, unless EMI-Thorn get their PAL system off the ground in time to be serious competitors, it looks as if it's all eyes on Philips in Europe for the videodisc system that will take over the market in Australia — though we might have to wait a while yet to see it happen.

Dennis Lingane

Fast videotape copier

In the past, duplication of video tapes has had to be carried out in real time, so that a two-hour tape would take two hours to duplicate. This is one reason why there is such great interest in videodiscs, which can be produced easily in large numbers.


The helical scanning format used in video tape systems prevents high speed copying, as is done with audio tape duplication. However, Matsushita have now demonstrated a prototype high speed VHS copier which can duplicate a three-hour tape in just three minutes.

The essentials of the Matsushita system are shown in the diagram. The high coercivity master tape is wound in close contact with the blank tape and both are exposed to a magnetic field produced by the

magnetic flux generator. The method of duplication is based on the bifilar printing system for the video signal, the master tape's image being copied on to the blank tape.

However, the audio signal is transferred quite separately to the blank tape in order to achieve maximum audio quality. The whole machine has been designed for automatic operation.

Brian Dance

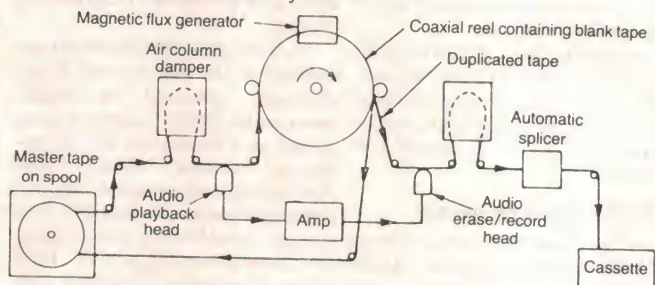

The basis of the Matsushita fast bifilar video tape duplicator.

Hitachi metal

Hitachi are currently introducing metal tapes in two new lengths as their ME46 (46 minutes' recording time) and as their ME60 (60 minutes' recording time).

The pure metallic particles in these tapes have been treated by a special process which coats each particle with a special anti-oxidant

so as to produce greatly increased particle stability.

It is claimed that the use of these tapes enables the maximum output level to be increased by 2 dB at the lower and mid-frequency ranges when compared with high quality chromium dioxide tapes. In the upper frequency range the maximum output level is 8 dB higher than that obtainable with chromium dioxide tapes, Hitachi say.

Brian Dance



Hitachi's latest VHS Recorder

Following the introduction of their VT 8000 VHS video recorder, Hitachi are now adding the VT 8500 to their range; this incorporates a sophisticated microprocessor in its circuitry.

The microprocessor enables five programmes to be recorded over a seven-day period either on the same or different channels. The principle controls are touch operated using integrated circuit logic either directly or by means of an infrared control key pad which enables no less than twelve different modes to be selected from the comfort of one's armchair.

The available modes include double speed playback, slow motion playback, freeze and advance frame, rewind/fast forward, play, record, change channel and a facility which enables the user to locate quickly any section of the tape by speeding up the playback to five times the normal speed.

Hitachi have included a test signal generator in the VT 8500 which enables the video channel of the television receiver to be accurately tuned in by using the black and white test pattern instead of having to play back a pre-recorded tape. In order to avoid damage to video

tapes from moisture accumulating during wide temperature changes, a dew detector circuit has been incorporated into the recorder, which detects the presence of moisture on the tape head and switches on a flashing warning LED indicator — apart from disabling the recorder until the condensation has evaporated.

A timer back-up circuit is incorporated into the VT 8500 so that if the power should fail for a short time, the instructions coded into the memory of the equipment will not be lost from the memory. In the record mode, users cannot accidentally switch the recorder over to a different channel whilst another channel is being watched, since an automatic channel-locking circuit is employed to prevent this.

The VT 8500 is similar in style to the VT 8000, but is one of the lightest mains-powered units on the market, with a weight of about 12 kg.

Brian Dance

Sanyo announces new Beta video cassette recorders

Sanyo Australia recently announced two new Beta format products to complement the continuing success of their VTC9300PN video cassette recorder.

First will be the Sanyo VTC 3000P second-generation Beta format portable video cassette recorder, which was launched on the Australian market in March this year.

The portable VCR will be followed in June by the release of Sanyo's

Introduction of these new products consolidates Sanyo Australia's long-term commitment to

New series TDK reel-to-reel tapes

In response to demands by professional, semi-professional, and home open-reel tape recordists for higher quality tape products, TDK (Australia) Pty Ltd have introduced two new lines of quarter-inch (6.25 mm) open reel audio tapes.

Designated TDK GX Studio frequency sensitivity of +2 dB at Mastering Series and TDK LX Pro-3 kHz, high frequency sensitivity of fessional Studio Series, both lines +6 dB at 20 kHz, bias noise level of represent significant breakthroughs -57 dB and tape distortion level of in open reel magnetic tape technology, TDK say.

The LX series is available in lengths from 1200 ft to 3600 ft and specifically for studio master use in live running times from 60 to 180 music mastering, and is, according minutes (at 19 cm/sec.) and in to the corporation, the finest newly designed super precision 10" quarter-inch open reel tape on the metal reels and 7" plastic reels. The

reels each consist of a separately moulded hub and flange to ensure perfect circularity and high strength. Of the GX series, only the 1800 ft seeking higher quality performance length, 90 minute running time, is from an open reel tape to meet de- available in Australia at this stage. manding recording applications. The GX and LX series supersede the

The GX series features TDK's old series S, L, and LB which are no newly developed ultra-fine gamma longer available. Both lines feature a ferric oxide particle tape formulation dust-proof cleaning leader tape with with extremely high output and low a timing cue. Recommended retail distortion throughout an extended prices for the GX and LX series are:

LX 35 90 \$12.30, LX 35 180M \$34.49, LX 35 90B \$13.52, LX 35 180BM \$38.16, LX 50 60B \$12.30, LX 50 120BM \$34.49, GX 35 90B at 400 Hz), low frequency sensitivity \$18.29. of +1.5 dB at 400 Hz, mid-



the Beta format in video tape equipment, and the enlarged video product range is designed to cater for all popular price points demanded by the Australian market.

On the world scene Sanyo Japan recently announced plans to manufacture VHS format VCRs in addition to the well-established Beta system. This move is designed to increase Sanyo's VCR market share in America, the UK and Europe.

With the recent decision to manu-

facture RCA, VHD and Philips videodisc systems, Sanyo aims to become the world's leading supplier of domestic video equipment. Sanyo already supplies one-third of the world's tape recorders and claims to be the leading supplier of microwave ovens.

For further information please contact Mike Hart, Australian Sales Manager, Sanyo Australia Pty Ltd, 225 Miller Street, North Sydney NSW 2060. (02)436-1122.

"Instant" purebreds just don't exist.

A good-looking component stereo system can be launched overnight. But an excellent-sounding system that will delight audiophiles is another matter. Excellent results require that each individual unit be outstanding. That takes experience and special skills beyond mere technology. It takes the hi-fi expertise of Sansui, the audio specialist with decades of dedication to 1st class reproduction.

SUPER COMPO systems weren't created overnight. From the very beginning, each unit was conceived with the other units in mind. The result is matching that goes beyond handsome styling. Or mere "power" matching. SUPER COMPO systems are distinguished by "in-depth matching." This means that certain priorities such as extremely low dynamic distortion were followed throughout.

An added feature of SUPER COMPO is the incorporation of the latest advances in electronics. The dual benefits are greater accuracy and increased operating ease. Typical refinements include computerized track sequence selection turntables, quartz-PLL digital synthesizer tuner with 12 pre-set station selection and LED station centering, full logic cassette deck with versatile auto functions, DC-servo amplifiers with auto volume adjust and LED peak power level meters. And more.

An enormous amount of care went into SUPER COMPO "in-depth" matched systems. They are the purebreds on today's market. They are for discriminating listeners who appreciate the finest.

SUPER COMPO



SUPER COMPO 9000



Sansui

SANSUI ELECTRIC CO., LTD. 14-1 Izumi 2-chome, Suginami-ku, Tokyo 168 Japan
VANFI (AUST.) PTY. LTD. 297 City Road, South Melbourne, Victoria 3205, Australia Tel: 690-6200
283 Alfred Street, North Sydney, N.S.W. 2060, Australia Tel: 929-0293

HOW TO TELL ADVENT SPEAKERS FROM EVERYBODY ELSE'S.



Graphs of frequency ranges are all well and good, but the ultimate test of Advent's superiority lies with you.

Listen to an Advent speaker pair.

And listen to the unstrained clarity of the system which is due to the excellent power response at high frequencies, and the simplicity and lack of unwanted interaction between drivers in Advent's two-way design.

Listen to Advent's low frequency capabilities which are the usable equal of any speaker's. For example, Advent will reproduce the 30 HZ organ pedal note that begins Richard Strauss's "Also Sprach Zarathustra" as room-shakingly as one could ask, providing, as the case of London CS-6609, the note is actually present on the record.

For more information phone Chadwick today on (02) 647 1103.

ADVENT

Chadwick

Chadwick Audio Furnishings Pty. Ltd.

ETI/5/81

Tune your sound

Numark EQ-2300

PROFESSIONAL HI-FI GRAPHIC EQUALIZER

The NUMARK FREQUENCY EQUALIZER MODEL EQ-2300 is a sound studio control unit incorporating the most advanced integrated circuits and precision components in its design.

SPECIFICATIONS

Frequency Response — 10 to 30,000Hz — 1dB (flat setting).


Inter Modulation Distortion — At 2 Volt output 0.05 percent less than 0.05 percent output at 2 Volt.

Hum and Noise — Shorted input — 80dB below 2 Volt output better than -80dB Shorted input below 2V output.

Output Level — Maximum 8 Volts.

Overload Indicator — Lighting up at 5 Volt output.

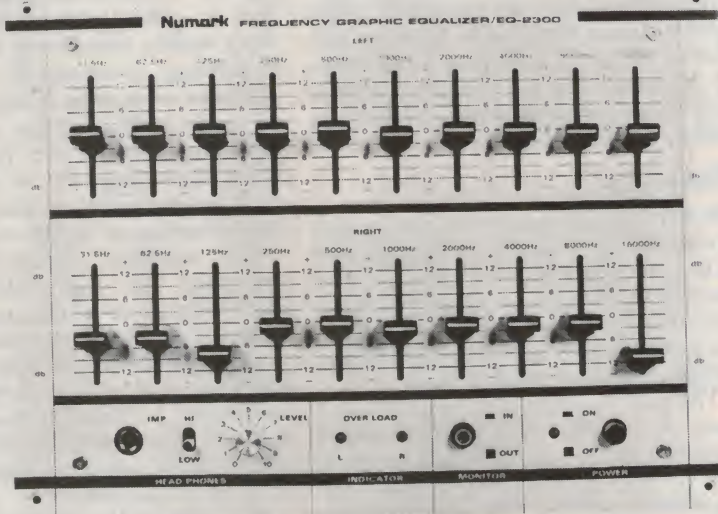Headphone Monitor — Low impedance position for 8 to 35 Ohm headphone.



R.R.P. **\$175.00**

Freedman Electronics

91a Liverpool Road, Summer Hill, NSW 2130.

Phone (02) 797-9941.

Sony TA-F80 amplifier — superb technical performance and quality sound

Louis Challis didn't care much for the look of the Sony TA-F80 amplifier, but in every other way he has nothing but praise for it.

Louis A Challis

THE SONY TA-F80 pulse-locked power supply integrated stereo amplifier is an example of a new breed of amplifier which exhibits features and performance which the average user has heard about in technical articles but not yet seen presented as a commercial article. The unit we received for reviewing is one of the first examples of this amplifier to hit the Australian market, but by the time this review comes to print you will most probably be able to purchase one in your local hi-fi shop or showroom.

In Japan this type of amplifier is readily available and has already achieved an excellent degree of acceptance; if you read Dennis Lingane's report on the 1980 Tokyo International Electronics Show in ETI, March '81, you'll understand why this is so. However, it's not just the Japanese passion for gimmickry that will be satisfied by this amplifier.

Features

The first thing you notice when you pick this amplifier up is that it weighs about half as much as any comparably rated amplifier. This is the result of an entirely different approach to the design of the power supply and also the heatsink used for the power output stage.

The power supply is novel in that it uses a 20 kHz pulse-locked circuit incorporated in a neat diecast screened can. It uses a different rectification and regulation system from conventional power supplies, achieved by rectifying the ac at the input to produce a nominal dc voltage. This dc voltage is then converted to a 20 kHz square wave, which is controlled by a feedback circuit in order to achieve correct load regulation.

The output of the unit is rectified again and filtered by two pairs of chokes and two pairs of capacitors to produce a positive and negative voltage at 51 volts.

Because of the very high frequency involved, there are no audible components produced and, more importantly, the filter capacitors are so small that isolation between the two channels is primarily designed for crosstalk requirements.

Not content with this, the Japanese designers have designed an output stage based on the use of a liquid/vapour phase heatsink radiator system. This is unusually light compared with the normal aluminium-finned heatsink, and it offers remarkable efficiency. Sony admits that this is a NASA space technology development, and say that its major advantage is the enhancement of power output stage cooling. They have incorporated very high frequency transistors (high- F_t) to reduce intermodulation distortion and provide what they describe as 'crisper sound'.



The external appearance of the amplifier is regrettably not as attractive as one would expect from the technical features incorporated within. Unlike other Sony products, which have achieved a standard of neatness and associated attractiveness acknowledged by most people in the trade and by the public, this amplifier looks much more 1970 than 1980.

The front of the amplifier features a recessed bezel right across the top with a red plastic insert. Behind this are located two arrays with 20 light-emitting diodes in each array. These indicate the peak power into eight ohms and are accompanied by engraving on

the plastic bezel of nine sets of power indications ranging between .01 and 130 watts. The bottom light in each array is continually illuminated and indicates that the power is on.

Underneath the bezel on the left is a rotary knob for turning the power on and off. There is a 4-second delay before the amplifier actually switches itself on, during which time the pulse-locked power supply comes into operation and

Measured performance of Sony TA-F80

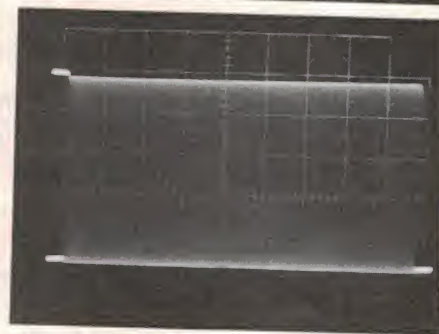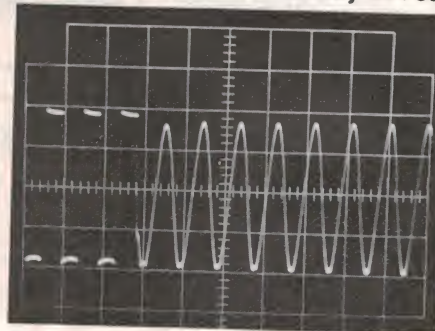


Transient overload recovery test (IHF-A-202)

1 ms/div.

50 ms/div.

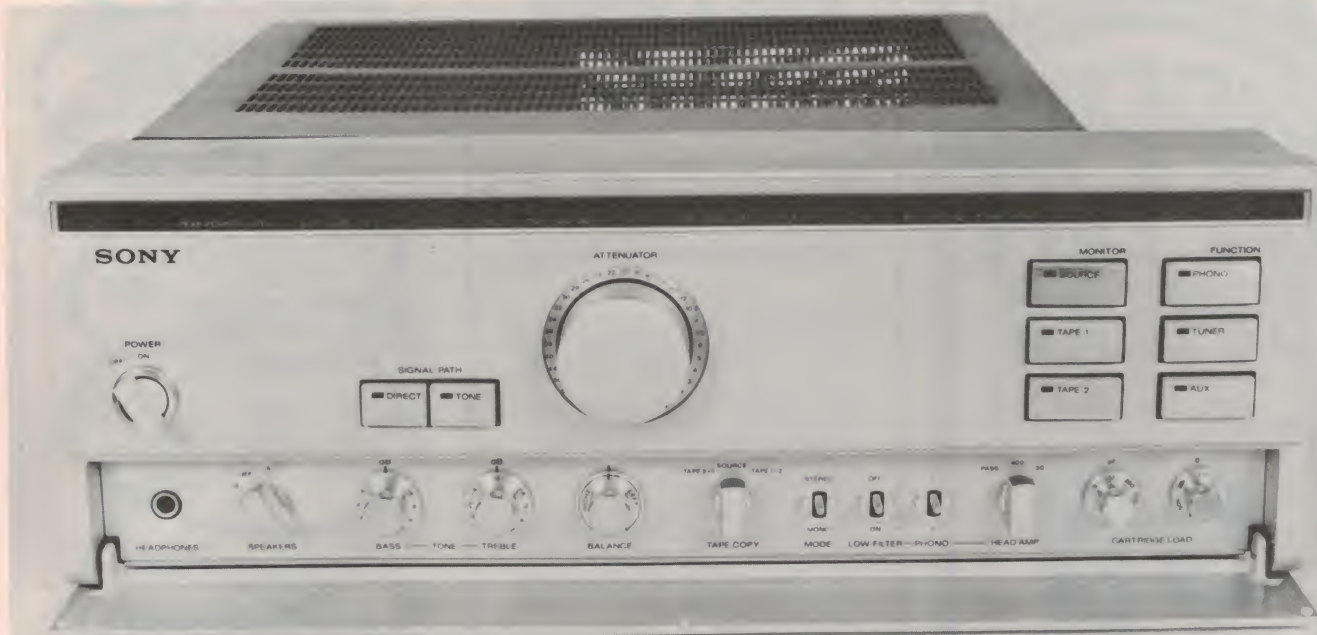10 dB overload re rated power into 8 ohms — both channels driven. Overload duration: 20 ms; repetition rate: 512 ms.



charges up the filter capacitors.

In the middle of the escutcheon is a large attenuator calibrated in dB re maximum output with typical 1 dB steps to -6 dB, 1.5 steps to -18 dB, 2 dB steps to -40 dB and 10 dB steps from -50 to -70 dB.

To the left of this volume control are two switches which allow the signal path to be switched direct or through the tone controls; each of these switches is illuminated by means of a LED inset into its face, which indicates which path has been selected.

On the extreme right hand side are six switches, also incorporating LEDs, three indicating what is being monitored (source, tape 1 or tape 2) and three for function (phono, tuner and auxiliary).

All along the bottom of the escutcheon is a hinged flap which is normally closed, behind which are the minor controls including a headphone socket and a speaker selector socket for A, B and off. I like this feature, as it helps to provide an uncluttered front panel appearance.

Behind this flap on the right are bass and treble tone controls, a balance control with a sensible central indent, a tape-copying function switch with positions of source, tape 2 to tape 1, and tape 1 to tape 2. To the right of these controls toggle switches are provided for stereo/mono, low filter on and off, phono 1 or phono 2.



The next control is a rotary switch to activate the head amp for moving coil cartridge, with positions for impedances

of three ohms, 40 ohms and a pass position if it is not required. The final two switches provide the cartridge loading facilities, with switch-selectable input capacitors of 100, 130, 200, 300 and 400 pF and input impedances of 100k, 50k, 20k and 100 ohms.

The rear of the amplifier is rather different from other units in that the rear panel only features four pairs of screw-up terminals for two sets of speakers, and one switched and two unswitched ac outlets for parallel-pin mains plugs. (This feature will obviously be deleted from the normal units designed for the Australian market).

Inside the amp

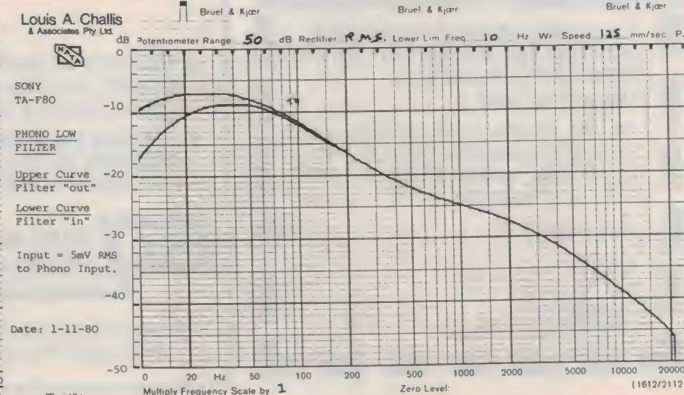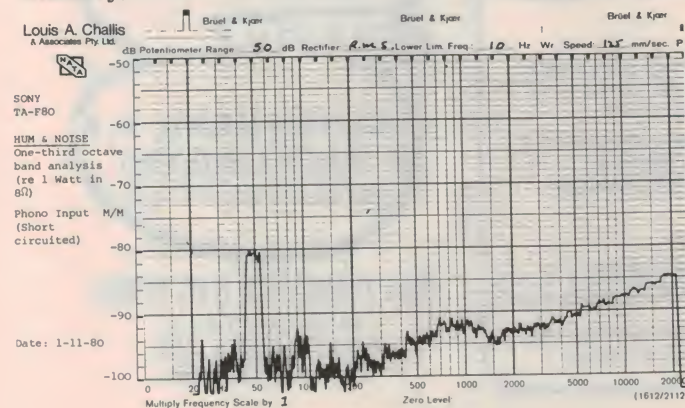The main electronic section of the amplifier is not as wide as the front



WANTED

RIPPED OFF TAPE BUYERS

Are you tired of paying too much for your cassettes and accessories? Your problems are over ... for one dollar!

\$1.

You receive:—

- A Dindy Super C46 cassette. The superior low noise tape with a 5 year guarantee that can save you up to 50% on comparable quality imported tapes.
- A Dindy catalogue packed with savings on tapes and audio accessories.
- A special introductory offer too good to refuse.



To: DINDY SOUND WAREHOUSE
15 BOUNDARY STREET (P.O. BOX 55)
RUSHCUTTERS BAY 2011
TEL: (02) 33 5293

20,000 people have bought over 1,000,000 cassettes from us. They all can't be wrong. \$1 spent could save you hundreds.

Mr/Mrs/Miss


Address



ETI P/code



NORTRONICS AUDIO & DIGITAL TAPE HEADS

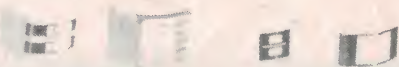

for long life extended response

- Replacement heads for cassette decks, reel to reel decks, cartridges and cassette recorders. Also professional recorders and duplicators.
- Will fit AMPEX, SCULLY, TEAC, ATC, GATES, PENTAGON and many more.
- Specification sheet of all Nortronics heads available on request.
- Complete range of Alignment tapes for cassette, reel to reel and cartridge decks.
- REGULAR MAINTENANCE ENSURES CONTINUED OPTIMUM PERFORMANCE. Nortronics manufacturers a full range of audio care products.

MAGNETIC TAPE
DEVELOPER



ALIGNMENT
TAPES




SPlicing
BLOCKS



SPlicing TABS

TAPE
HEAD
CLEANER

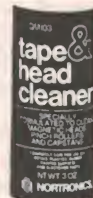

- NORTRONICS audio care products are designed to care for and maintain your valuable recording equipment.
- SEND TWO 22c STAMPS FOR OUR FREE BROCHURE ON THE COMPLETE NORTRONICS ACCESSORIES RANGE.

E.I. EMAC INDUSTRIES Pty.Ltd.

2 Bengal Crescent, Mount Waverley,
Vic. 3149. Ph: (03) 277-9989.

ONE STOP

PROFESSIONAL
SOUND EQUIPMENT
OPEN SAT. 10-1

POWER AMPS.

JANDS

4 WAY X-OVERS
MIXERS

SPEAKERS
IN STOCK!

CELESTION
ETONE

JBL

DSA CUSTOM
CABINETS

Full
range of
P.A. & Inst.
Cabinets
available!
W's 4560's
cases etc



FENDER TAMA
VOX MARSHALL

LIGHTING

QLD AGENCY
BARRETT'S

PAR CANS TRUSSES TREES SPOTS
DIMMERS CHASERS ETC

HIRE
&
SALES

HARDWARE

SESSION CATCHES. PLUGS
CANNONS. FANS. X-OVERS
JACKS. CABLE. GAFFE
BOLTS. NUTS. TOOLS. ETC. ETC.

HIRE!

A SOUND SYSTEM
400 WATTS - 10000
COMPLETE SET UPS
Hire a gtr. or bass amp!

BUY & SELL!

**SECOND HAND, P.A.
+ BACKLINE EQ!**
Guitars & Drums too!

DSA CONCERT SYSTEMS

10 Heussler Terrace,
Milton, Brisbane. 4064.
Phone (07) 36-6755.

panel and consequently an edge of the front panel extends out to the right hand side. This provides a convenient access point for making direct connections into the preamplifier stage.

The connections for all low-level signals are provided at the rear of this section by a series of coaxial sockets. The phono sockets are gold-plated and the designations for circuit connections are sensibly screen-printed on the side of the adjacent painted steel cover.


The inside of the amplifier is extremely neat, the most outstanding features being the 'pulse-locked power supply' and the liquid/vapour phase cooling heatsink. One thing very clearly noticeable is the logical layout, which minimises unnecessary wiring and 'crossed wiring' paths. One other feature is the neat circuitry and chokes in the output stage feedback path, directly connected to the unusual output power stages, and a fast relay switching system to prevent you from destroying those stages.

On test

The objective testing of the amplifier proved how outstandingly good this unit is. The frequency response with the tone controls disconnected extends from 1 Hz to beyond 100 kHz with an absolute flatness of better than ± 1 dB. With the tone controls centred and activated the frequency response is still 8 Hz to beyond 100 kHz.

The sensitivities for the moving magnet cartridge input are 250 microvolts with a 350 millivolt overload point, whilst for the moving coil cartridge input they are 12 microvolts with 17 millivolts overload point. The harmonic distortion is less than .007% at 120 W output at all frequencies and still less than .008% at the 1 W level.

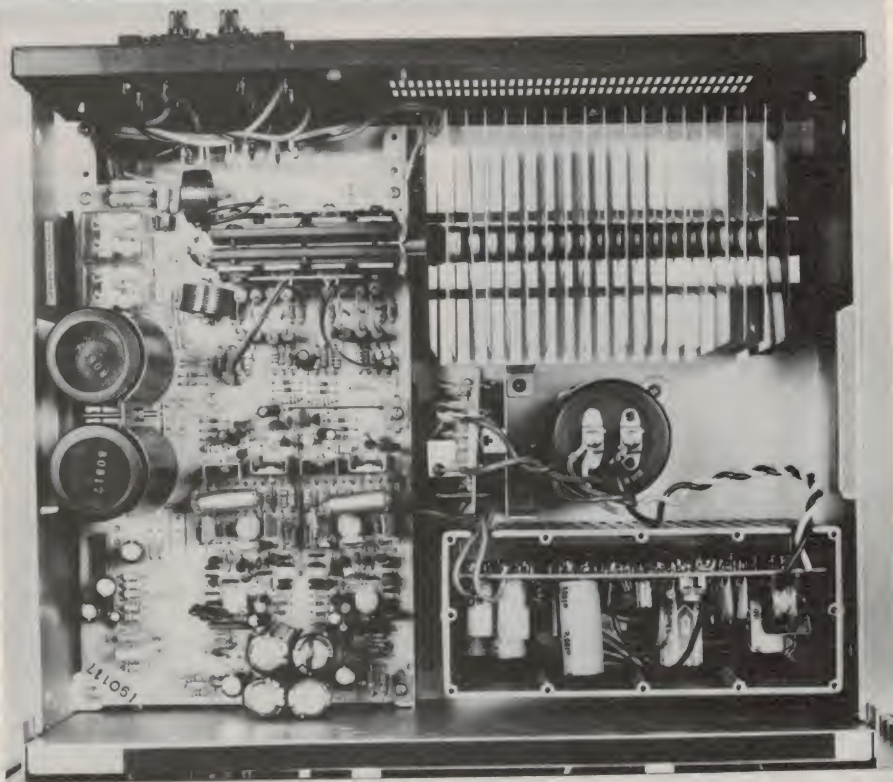The transient intermodulation distortion is very much less than 0.05%,



Internal view of the TA-F80. The power amplifier board runs along the left hand side, with the power output devices at the rear. The vapour-phase heat pipe and heatsink runs from the output devices to the right. The switchmode power supply is in the compartment at right front (lid off). The preamp is in its own shielded compartment at the front (not visible).

whilst the hum and noise levels are -81 dB(A) for the auxiliary, -80 dB(A) for the moving magnet input and -78 dB(A) relative to the moving coil cartridge input, with the volume control set for 1 W output. The transient overload recovery test shows an excellent but not perfect recovery response from overload clipping.

The tone controls offer a reasonable ± 9 dB boost and cut at 50 Hz and ± 9 dB boost and cut at 20 kHz.



The phono 'low filter' response can only be exhibited through the phono input and from this it can be seen that


7 dB of cut is provided at 10 Hz as a means of reducing wow components from being amplified in the main amplifier, should this prove to be a problem.

All in all the measured performance equals or exceeds the manufacturer's stated figures by a fair margin; the distortion figures are particularly good.

In use

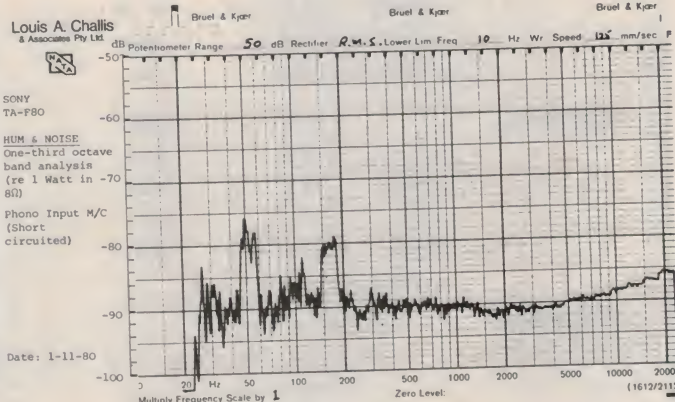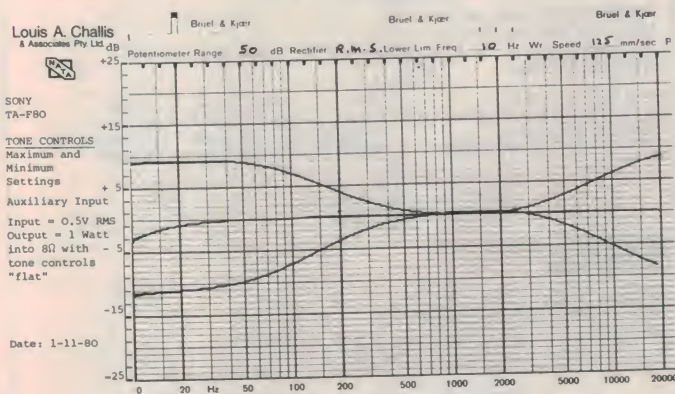In practical usage this amplifier is no slouch. I used it at home to play classical music in conjunction with a series of other record players and cassette players that we have recently reviewed, ▶



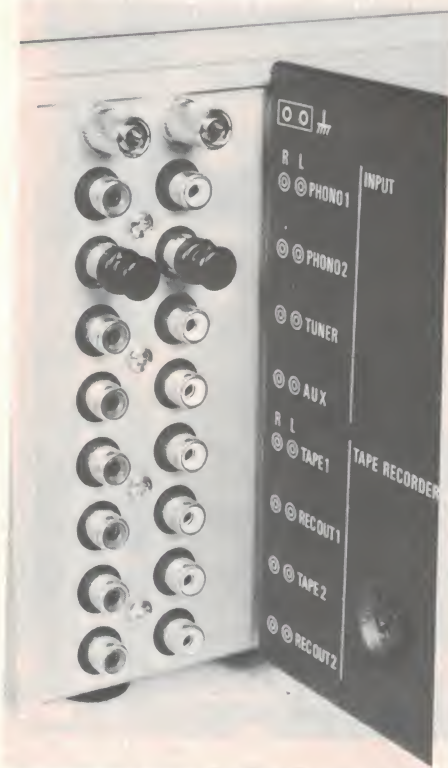

The input terminals are behind the front panel and go direct to the preamp pc board with minimum lead length.

and found its performance superlative, particularly with moving coil cartridges and no less with moving magnet cartridges.

The impedance and capacitance adjustment capabilities make it possible to trim the frequency linearity of each respective cartridge to achieve a flatter response than would be normally obtainable without protracted and messy adjustments at the input terminals. This feature alone places it in keeping with some of the more expensive and esoteric amplifiers which I have reviewed over the last year (although, I must admit, this is already an esoteric amplifier).

I played many new records both conventional and direct to disc, many of them from Sony/CBS in Japan, and they provided a degree of brilliance and natural fidelity which (with the best loudspeakers) was breathtaking. This amplifier was the main one I used in my evaluation of the B & W 801 series speakers (see ETI, Feb. 1981), and it helped to provide some of the purest and sweetest sound imaginable.

Because of the power to weight ratio of this amplifier we took it into the field to provide high-powered test signals in a number of unusual locations. With

continuous outputs of 125 W and with tone-burst testing to detect flutter echoes in auditoria, the amplifier proved that it not only has good performance, but can maintain that performance for extended periods of time even with nasty signals that would be expected to destroy its output stages and thoroughly test its protection circuitry.

I don't particularly like the appearance of the Sony TA-F80 amplifier, but I must admit I have more than just a begrudging respect for its technical panache and the quality of the amplified signals it produces.

SONY TA-F80 AMPLIFIER

Dimensions:	430 mm wide x 410 mm deep x 160 mm high
Weight:	9.9 kg
Manufactured in:	Japan by Sony Corporation
Price:	\$1499.00
Distributed by:	Sony Australia Pty Ltd 453 Kent St, Sydney.

Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.



MEASURED PERFORMANCE OF SONY TA - F80 S.N. 201992

FREQUENCY RESPONSE:

(-3dB re 1 Watt, 0.5V
Input to Aux)

Left 1 Hz to 100kHz
Right 1 Hz to 100kHz

Tone Controls Defeated

Tone Controls Centred

Left 8 Hz to > 100kHz
Right 8 Hz to > 100kHz

SENSITIVITY:

(for 1 Watt in 8 Ω)

	Left	Right
AUX	14mV	14mV
TUNER	14mV	14mV
TAPE	14mV	14mV
PHONO M/M	252 μV	250 μV
PHONO M/C	12 μV	12 μV
OVERLOAD M/M	360mV	350mV
OVERLOAD M/C	17mV	17mV

INPUT IMPEDANCE:

	Left	Right
AUX	50k Ω	54k Ω
TUNER	50k Ω	54k Ω
TAPE	50k Ω	54k Ω
PHONO	46k Ω	47k Ω

(100pf/50k Ω)

OUTPUT IMPEDANCE:

43 milliohms (@ 1kHz)

DC on output line

Left	50mV
Right	50mV

HARMONIC DISTORTION:

(A) (At Rated power of 120 Watts
into 8 Ω = 31 Volts)

	100Hz	1kHz	6.3kHz
2nd	-54.1	-86.2	-85.1dB
3rd	-59.6	-	-91.9dB
4th	-96.7	-	-91.2dB
5th	-	-	-dB
THD	0.007	0.005	0.007%

(B) (At 1 Watt into 8 Ω)

	100Hz	1kHz	6.3kHz
2nd	-83.4	-87.3	-85.9dB
3rd	-88.9	-96.1	-87.6dB
4th	-97.0	-	-dB
5th	-	-	-dB
THD	0.008	0.005	0.006%

TRANSIENT INTERMODULATION DISTORTION:

< 0.1%
(3.15kHz square wave and
15kHz sine wave mixed 4:1)

NOISE & HUM LEVELS:

re 1 Watt into 8 Ω)	AUX	-79 dB (Lin)	-81 dB(A)
(with volume control set for 1 Watt output with,	PHONO M/M	-75.5dB (Lin)	-80 dB(A)
	PHONO M/C	-72 dB (Lin)	-78 dB(A)
	0.5V input (Aux)		
	5mV input (Phono M/M)		
	0.5mV input (Phono M/C)		

MAXIMUM OUTPUT POWER AT CLIPPING POINT:

(IHF -A - 202)
(20ms burst repeated at 500ms
intervals)

89 V P-P

= 124 Watts


Dynamic Headroom = 0.1 dB (re 120 Watts)



audio-technica®

...scenario for superb sound

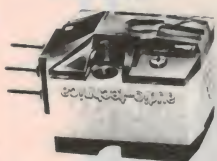LATEST RELEASE! DUAL MOVING COIL PHONO CARTRIDGE AT32



Recommended Retail \$219


If you could look through a microscope you could see the most finely polished gem quality diamond stylus, nude mount.

A precision finished square shank that gives absolutely true angle of alignment.

The AT32 Moving Coil Cartridge is of the lowest mass weight with smooth accurate trackability. The response and range is higher than most human ears can interpret.

In the AT1100 arm it becomes an incomparable combination.

AT1100 TONEARM

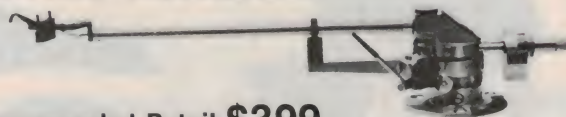

Recommended Retail \$399

AT1100 is a new low-mass tonearm with a plug-in, integrated arm. Precision fabricated, main features include extremely low mass, immunity to resonance, and damping to reduce IM distortion and enable high trackability.

Unusual features include the integrated tonearm which eliminates connector ring resonance and weight. All electrical contacts are gold plated. The machined aluminium head shell weighs only 3 grams, and the pipe 6.5 grams. To further reduce weight, the counterweight mass is concentrated in one small area along the tonearm axis. The extra rigid pipe is heat-hardened aluminium alloy. Computer type silver lead wires use teflon insulation for efficient transmission of high frequencies.

available at all quality hi fi dealers

If you have any supply problems however, please contact the nearest Maurice Chapman outlet to ascertain your closest supply source.

THE MAURICE CHAPMAN GROUP PTY. LIMITED

44 Dickson Ave. Artarmon, NSW 2064. Phone (02) 438-3111 • 150 Burwood Rd, Hawthorn, Vic. 3122. Phone (03) 818-1730
• Perth (09) 446-5679 • Brisbane (07) 261-1513 • Adelaide (08) 272-8011

PRE-STOCKTAKE SALE

next thing you know
RESISTORS
ALL 1/2 & 1/4 watt
2c
ALL 1 watt
4c
we'll be giving them away

TTL and CMOS at Supa Low Prices

7401	23c	4001	23c
7405	23c	4002	25c
7410	23c	4006	1.16
7413	43c	4007	31c
7420	23c	4012	14c
7430	23c	4014	96c
7440	23c	4018	98c
7441	98c	4022	1.08
7445	52c	4025	23c
7446	93c	4027	45c
7460	23c	4028	93c
7470	37c	4029	1.33
7472	52c	4049	37c
7475	36c	4050	53c
7480	92c	4071	23c
7482	1.37	4081	23c
7483	1.37	4416	48c
7491	68c	4449	23c
7492	53c	4513	1.93
7496	72c	4518	1.89
74121	34c	4520	1.08
74141	107	74C02	26c

supa special!
All values of SINGLE GANG
ROTARY POTS Just 40c.
ALL DOUBLE GANG 80c.

supa value
BC 548 TRANSISTORS
ONLY 8c!
top quality

SUPA LOW PRICES ON ELECTRO'S

1,000uf 35v.R.T.	60c
1,000uf 50v.R.T.	93c
2,500uf 16v.R.T.	56c
2,500uf 25v.R.T.	64c
3,300uf 16v.R.T.	90c

DAVE RYALL ELECTRONICS

657 PITTWATER ROAD, DEE WHY, NSW. PH (02) 982-7500.

Mail Order PO Box 176, Dee Why, NSW 2099.

Our new Systems Technician Apprenticeship scheme is more than just an Apprenticeship.

**Applications close
3 July, 1981**



Opportunity to work in electronics.

Tomorrow's aircraft and ground electronic systems will be highly complex, to say the least.

That's why we're looking for young, alert people interested in electronics and aircraft to be trained as Systems Technicians.

It's a highly specialised field that not only requires an analytical approach to problem solving but the potential to move into a management position very early in your career.

Areas of involvement include flight, propulsion, environmental, navigation, weaponry, electronic warfare, radar and computers.

Opportunity to receive a higher than normal standard of training.

After completing your certificate of Technology/Trade Training course, you'll spend four to five years gaining practical field experience as Tradesman. Then, if selected, you'll undertake a specially designed six months RAAF Systems Technicians programme that includes developing your management and communication skills plus further specialised systems instruction. On graduation you will be a fully qualified Senior Non Commissioned Officer

Systems Technician in either the Aircraft, Avionics or Ground Electronics fields.

Opportunity for promotion.

Imagine, you could be a Commissioned Officer in your early 30's with great future prospects in the Engineer Branch of Today's space-age Air Force.

Opportunity to get valuable work experience.

These days, successfully completing an Apprenticeship doesn't automatically guarantee you a secure, well-paid job. We do!

Opportunity to travel and make more friends.

Initially, you'll go to Laverton (Vic.) or Wagga (NSW) depending on your specialised field.

Then you could find yourself working at any one of our many bases.

Wherever you are, there'll be excellent sports and social facilities at your disposal.

Opportunity to do something for yourself now!

If you're aged between 16-21 years, have Year 11 (Year 12 preferred) education with

passes in Mathematics, Physics and English, are an Australian citizen and can meet our other entry requirements, talk to an Air Force Careers Adviser now! Alternatively, send the coupon and we'll send you the facts.

Adelaide:	212 1455	Parramatta:	635 1511
Brisbane:	226 2626	Perth:	325 6222
Canberra:	82 2333	Sydney:	212 1011
Hobart:	34 7077	Townsville:	71 3191
Melbourne:	61 3731	Wollongong:	28 6492
Newcastle:	2 5476		

To: RAAF CAREERS ADVISER, G.P.O. Box XYZ in the capital city nearest you. Yes! I am interested in a RAAF career. Please send me full details.

Name: _____

Address: _____

State: _____ Postcode: _____

Date of Birth: ____/____/____

RCOT.455.FP.31.ET

You're somebody in Today's Air Force

Authorised by Director-General Recruiting Dept. Defence RCOT.455.FP.31.ET

PIONEER

Why Videodisc?

- ★ Laser Optical Video - Uniquely clear
- ★ Laser Beam Audio - True High Fidelity sound
- ★ Two sound channels for stereo Music or dual languages
- ★ Fast access to any point - easy to operate
- ★ Durable discs actually never wear out
- ★ Inexpensive discs with large, ever-growing selection
- ★ First laser beam consumer product in history

Why Pioneer Videodisc?

- ★ Pioneer - the world leader in High Fidelity
- ★ Slow motion capability (forward & reverse)
- ★ Freeze frame capability
- ★ Frame-by-frame (step) forward & reverse
- ★ Totally compatible with all high fidelity systems
- ★ You can build an entire Pioneer component system around this extraordinary product
- ★ First laser beam consumer product in history



Pioneer have opted for the Philips laser-read videodisc system. No doubt you would too — if model Kerry Healey made the invitation!

Videodisc — waiting in the wings

The battle lines have been drawn, the software is being sorted out and World War III (for the domestic videodisc market) appears to have commenced with test market skirmishes over the horizon. Be ready for when they strike up the Colonel Bogey march!

Brian Dance

DISCS WERE WIDELY USED for audio recording long before magnetic tape recorders became widely available. The pattern has been completely reversed in video recording with video tapes and cassettes available whilst we still await the first commercially available videodiscs! However, the battle for the videodisc market is rapidly heating up with two systems expected to be available by late 1981 and a third system in 1982.

The videodisc market is believed to be extremely attractive and more and more manufacturers are deciding to take part in its development. Indeed, the US consultants Arthur D. Little

produced a report recently in which they forecast that, within three years, videodisc machine production should exceed that of video cassette recorders.


They expect that over half of American homes will have a video disc player by this time.

Laser-optics system


The Philips/MCA system is handled by Magnavox and Pioneer in the USA and the unit comes with a price tag of US\$750. The surface of the 300 mm (12") disc is covered with a reflective coating into which tiny pits only 600 nm wide by 100 nm in depth are burned by a laser. (For comparison, a human blood

cell has a diameter of about 8000 nm!) A small helium-neon laser is used to read information from the spiral tracks of the disc on playback. Each disc has 54 000 tracks and each track contains the information for a single picture frame. The tracks are 1.6 μm apart on a 2.5 μm pitch, the disc rotating at 1800 rpm to provide a playing time of up to 30 minutes. However, it is possible to extend the playing time to one hour per side of the disc by adjusting the speed of rotation in proportion to the decreasing circumference, the track being read so that the laser tracks the disc at a constant linear velocity.


The Philips playback system requires ►

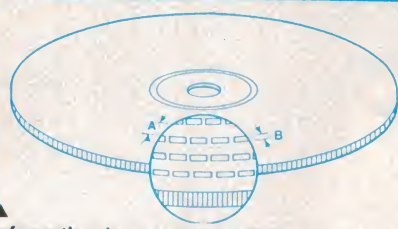

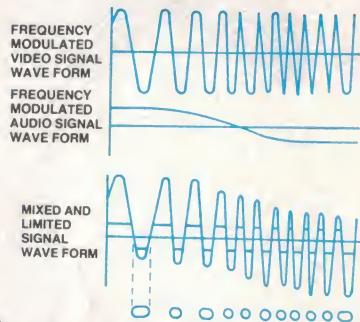
▲ Information is encoded on Philips' Discovision disc as tiny pits only $0.6\text{ }\mu\text{m}$ wide (dimension B) by $0.1\text{ }\mu\text{m}$ deep, spaced $1.6\text{ }\mu\text{m}$ apart (dimension A).



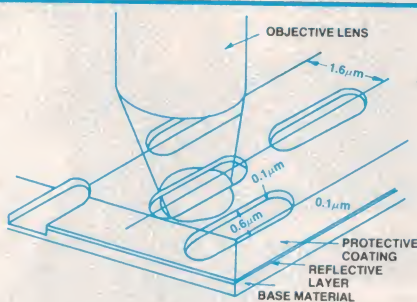▲ The optical pulses from the micropits are demodulated to produce both video and audio carrier signals, which are subsequently converted into picture and sound.



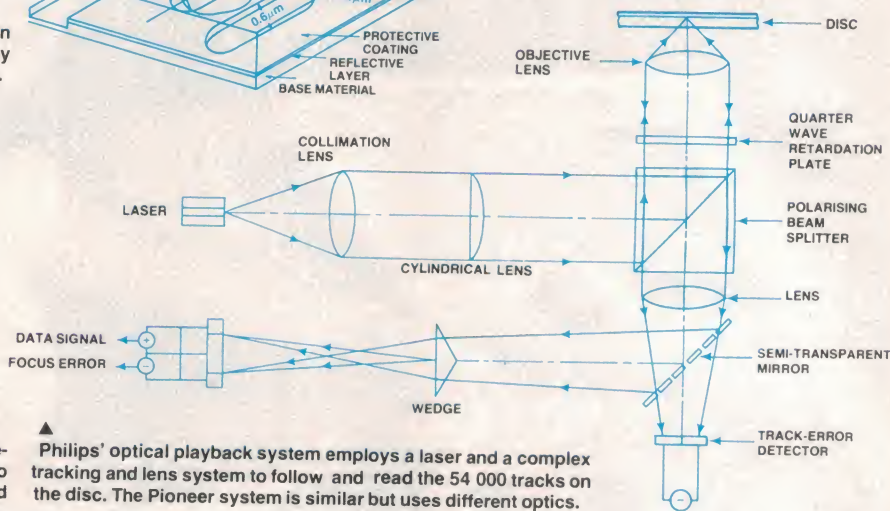◀ A laser reads the length of the microscopic pits, which contains the encoded information.



▲ Philips' optical playback system employs a laser and a complex tracking and lens system to follow and read the 54 000 tracks on the disc. The Pioneer system is similar but uses different optics.

precise tracking of the laser spot beam together with servo control and time base correction to account for any warping of the disc. It is claimed that the laser modulated discs provide optimum picture resolution together with a long life, while the pits provide very high information storage density. The video blanking bandwidth can exceed 8 MHz. It seems likely that this system may offer sharper images than capacitive tracking systems.


RCA System

The RCA Selectavision system employs a metal electrode attached to the back of a diamond stylus with a $5\text{ }\mu\text{m} \times 2\text{ }\mu\text{m}$ tip. This stylus follows the track of a groove cut in a vinyl disc which is electrically conductive and utilises the capacitance variations arising from small depressions (known as 'pits') at the bottom of the groove. These changes in capacitance are employed to modulate the amplitude of a composite frequency carrier which is subsequently decoded and fed into the aerial terminals of a television receiver.

It is claimed that this capacitive stylus system offers the principal advantages of low cost and ease of manufacture. The selling price of the RCA type players has been forecast to be less than US\$500 in the world markets. This may make it the cheapest videodisc system to become available in the fairly near future, although with a launching date in the world markets of 1982 (and probably somewhat earlier in the USA), it will probably be the latest system to appear in the videodisc race.

STOP PRESS!

Philips NV of the Netherlands, which with its American partner MCA was first to market a videodisc player in the US, will also be the first to do so in Europe. The company plans to start selling a PAL version of its optical player in the UK this spring with 100 titles in its catalogue. That number will be doubled during the first year, Philips' officials insist. Meanwhile Thorn EMI Ltd, the UK champion of the video high-density capacitive grooveless disc developed by Victor Co. of Japan, will ready a plant for producing master discs from tape this year in preparation for a 1982 launch of VHD players in that country. RCA Corp, the third main competitor, also plans to have PAL and Secam versions of its Selectavision players on the market in 1982.

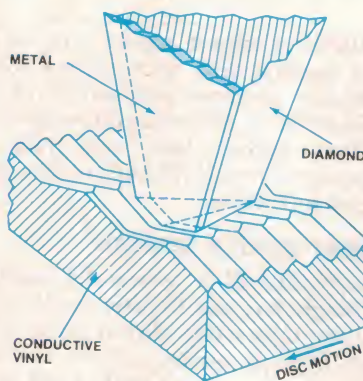

RCA's Selectavision system uses a metal-diamond composite stylus running in modulated grooves on the disc. The stylus tip is only $5\text{ }\mu\text{m}$ by $2\text{ }\mu\text{m}$ and the groove pitch is $2.6\text{ }\mu\text{m}$. Wear is said to be its biggest problem.

The RCA system employs grooves on a $2.6\text{ }\mu\text{m}$ pitch so that a 300 mm disc rotating at 450 rpm will provide up to an hour's playing time per side. No tracking control mechanism nor a servo-controlled loop is required in this system. The main disadvantages are stylus wear, which is understood to limit the life of the capacitive pick-up to some 500 hours of playing time, and the relatively limited video and audio bandwidths. The luminance bandwidth is quoted as 3 MHz and the chrominance bandwidth as 500 kHz, while the audio bandwidth extends to 15 kHz (being encoded onto the disc with 716 kHz and 905 kHz carrier signals).

JVC system

The Video High Density (VHD) system is also a capacitive pick-up type, but does not depend on grooves in the disc for guiding the movement of the stylus across the disc. Capacitive encoded tracking information is included on the disc alongside the video programming information. The stylus does not move in a groove, but sits on the smooth surface of the disc. Minute indentations or pits provide capacitive variations to the pick-up which translates them into electrical signals. Movement of the stylus is controlled by a servo-mechanism which uses the tracking information encoded on the disc.

The VHD capacitive system provides a luminance bandwidth of about 3.1 MHz and includes a full video carrier pedestal up to 6.6 MHz. The audio bandwidth extends to 20 kHz with a signal-to-noise ratio of 60 dB.

THE DEVELOPMENT OF VIDEO DISCS

Since they are only just about to be marketed, you might think that research into videodiscs has only been going for a few years. But as long ago as 1928 John Logie Baird demonstrated his "Phonovision" disc and in 1935 discs for use with the low definition Baird television system were on sale in London. They played for about six minutes per side, revolving at 78 rpm, and used a thorn needle (of a type used in some audio discs of the time) to detect a low bandwidth signal recorded in the groove modulations. They didn't catch on!

There are severe technical problems associated with the development of a high resolution videodisc system and several manufacturers have had to drastically revise their estimates of when their systems would be ready. Philips, for example, said in 1974 that they expected to be able to market their optical system later that same year.

The choice of a basic videodisc system appears to lie between mechanical, optical, capacitive and magnetic pick-up systems. Many attempts have been made to develop each of these basic techniques into a practical system.

The idea of using a mechanical pick-up was not abandoned after the failure of the earliest videodisc systems. A "Teldec" system developed by Telefunken in Germany and by Decca in England was introduced in 1970, but it was not on the market for long because of the very limited playing time of about 5 minutes per side. The disc rotated at 1500 rpm, contained one complete interlaced picture per revolution and was lifted upwards by air pressure so that it came into contact with the pick-up head. Good picture quality was obtained by the use of frequency modulation of the recorded signal.

The best known optical system is the Philips/MCA VLP (Video Long Play) contactless technique discussed elsewhere in this article. However, other manufacturers have carried out a more limited amount of work on optical systems. In particular, Hitachi has developed a technique using a 305mm diameter disc rotating at only 6 rpm. The luminance, chrominance and sound signals are recorded on the disc in the form of 1mm diameter holograms. A small laser is used to scan the disc on replay. It remains to be seen whether any optical technique will ever be evolved which will provide both recording and replay facilities to the domestic user, but little work yet seems to have been done on this problem. Optical techniques would become much more viable if it became possible to use semi-conductor lasers.

Magnetic videodisc techniques may offer the best solution to the problem of providing recording and replay facilities to the domestic user at the present time. There are some systems using magnetic discs marketed for the professional broadcaster which re-record on a magnetic disc continuously. The maximum storage time is less than a minute, which makes them very suitable for action replays in televised sports events, but not for very much else. Great efforts have been made to develop other magnetic disc systems for the consumer market, but nothing has yet materialised. One system developed in the early 1970s using a 305 mm diameter disc gave a total playing time of nearly an hour for the two sides, but was never produced commercially.

The video signal-to-noise ratio is quoted as 42 dB.

The life of the stylus is of the order of 2000 hours (four times that of the grooved RCA system), but the servo mechanism required raises the cost of both the discs and of the equipment.



Dave Daly, Vice President of RCA, has every reason to look confident. Their Selectavision system was first on the market, and at the lowest price. But it has fewer features than the competing systems.

The discs are somewhat smaller than used in the Philips and RCA systems (260 mm dia.) and revolve at 900 rpm.



This system has been developed by the Japanese Victor Company (JVC) and will be manufactured in the USA by General Electric Company and by Thorn-EMI in Europe; Matsushita of Japan is also involved. Although the first discs are being made in Japan, Thorn-EMI is trying to establish a plant in England for disc manufacture and GE are likely to manufacture discs in the USA. Players for these videodiscs can also replay suitable digital audio discs.

The VHD system provides access to any point randomly chosen on a disc more quickly than those systems in which the stylus must follow some form of groove. It can provide special effects such as a still picture, fast or slow motion replay, etc. It is rather remarkable that the discs can be manufactured using existing audio disc pressing equipment.

In the recording process for the production of the master disc, a single laser beam is split into two parts, one half

being used for recording the information and the other half being used to record the tracking signal. The master disc is made of glass coated with a photosensitive material and the recording must be carried out in a dust-free room. The laser beams are moved along a radius of the disc at constant speed, whilst the disc rotates at 900 rpm. Fine pits are thus recorded spirally on the glass disc which is then used to make a metallic master disc by the conventional process used for audio recordings.

The VHD discs sold to consumers are of conductive polyvinyl chloride (PVC) and have a life of some 10 000 playings. A sapphire stylus is employed, this stylus being mounted at the end of a cantilever arm with a magnet on the opposite end. Fixed coils are mounted near to the magnet and a single coil is wound around (but not in contact with) the magnet. In addition, a pair of vertical coils are mounted on either side of the single coil in phase opposition to one another. This arrangement enables ▶

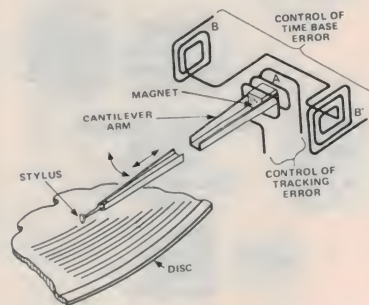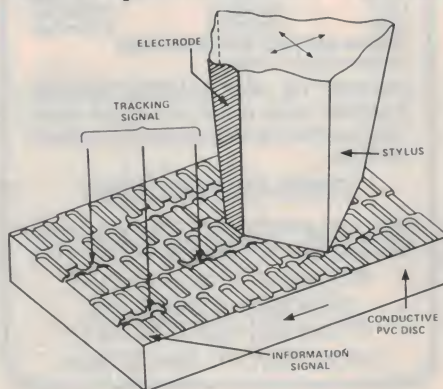


The VHD system from JVC employs a capacitive pickup system reading microscopic pits in the conductive plastic disc, tracking signals encoded on the disc providing information to a servo system that drives the stylus across the disc. Stylus life is said to be around four times that of the RCA system.



GOOD WILL INSTRUMENTS TEST EQUIPMENT

NEW
FOR
1981

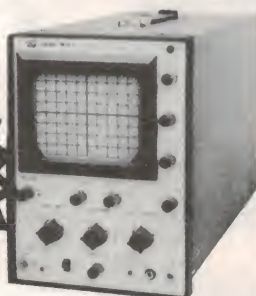

INTRODUCTORY OFFER

SPECIAL
\$275.00
(NORMALLY \$295.00)

5 INCH 6.5MHz
OSCILLOSCOPE
G.W. — GOS-955A

SPECIFICATIONS GOS-955A

Vertical Deflection: 10mV/DIV, 1/1, 1/10, 1/100, and GND, DC: DC-6.5MHz (-3dB), AC: 2Hz-6.5MHz (-3dB), 1MΩ ± 5 percent within 35PF, 600VP-P or 300V (DC plus AC peak); 250mV/DIV or better, DC-500KHz (-3dB), 1MΩ ± 10 percent within 35PF. Time Base: 10Hz to 100KHz in 4 ranges and fine control. Less than 5 percent Internal and External.

Synchronization: Internal - & +; external; line 0-140° for line frequency sweep. INT: more than 1 DIV. EXT: more than 2V p-p

Calibration: 50mV p-p 1KHz square wave
CRT Type: 130mm Round screen C.R.T.
Blanking: G1

Function Generator GFG-8015

(Sine/Square/Triple
0.2-2MHz. Triangle
pulse, ramp wave).

\$185



Digital Multimeter GDM-8035

(3½ digital AC/DC VA ohm).
\$265

GPS-3020

D.L. Regulated
Power Supplies
From \$100



Audio Signal Generator GAG-808A

(10Hz-1MHz)
(Sine/square wave)
\$189




Digital
Frequency
Counters
From \$358

RADIO PARTS GROUP

562 Spencer Street, West Melbourne
Phone (03) 329-7888
1105 Dandenong Road, East Malvern
Phone (03) 211-8122

ELECTROCRAFT

Will put you in the
picture.

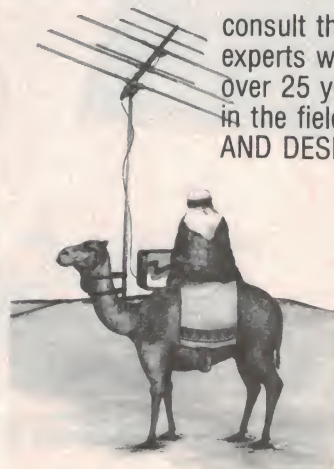

consult the
experts with
over 25 years
in the field —
AND DESERT!

NEW. MH 26. 26dB GAIN VHF-UHF 75ohm 40-850MHz MAST HEAD AMPLIFIER.

Fully protected against static and surges
on the power line. Automatically earths to
mast.

FM. AERIALS

FMG
FMG.2
FMG.4
FMG.5
FMG.6
FM.700
FM.3
FM.353
207/345

GAIN

1.9dB
7.0dB
8.5dB
8.2dB
8.7dB
7.5dB
6.0dB
6.0dB
8.0dB

UHF & VHF Ch.O.ANTENNAS

Hills

TC10/B4	Ch:28	471-605Mhz	10.6dB Gain
TC18/B4	Ch:28	471-605Mhz	13.2dB Gain
TC10/B5	Ch's 2.7.9.10	616-850Mhz	10.6dB Gain
TC18/B5	Ch's 2.7.9.10	616-850Mhz	13.2dB Gain

Channel Master

M2	B/4 & 5	500-850MHz	9.5dB Gain
M3	B/4 & 5	500-850MHz	10.5dB Gain
M4	B/4 & 5	500-850MHz	12.0dB Gain
4225-4	Bay Bow Tie	500-850MHz	12.0dB Gain

VHF Chs 0.2.7.9.10 ANTENNAS

Hills

3/5.0	8 element	High Gain
TL3/0	10 element	High Gain
TL4/0	12 element	V/High Gain
EFC3/03	Anti-Ghost	V/High Gain
PF7/10	Anti-Ghost	City Area

Channel Master

3110/A	Anti-Ghost	City Area
311/0	Anti-Ghost	
CX7	Good all rounder	
CX13	Anti-Ghost	High Gain
CX17	Anti-Ghost	V/High Gain
CX21	Anti-Ghost	V/High Gain

(CROWN ANTENNA ROTATOR \$99.00)

All plus postage or freight.

**NOTICE TO INSTALLERS/WHOLE-
SALEERS:** Save dollars on coaxial cable.
Ring now for the best prices and cable in
Australia.

FREE ADVICE GIVEN

ELECTROCRAFT

68 Whiting Street, Artarmon,
NSW 2064. PO Box 398.
Phone (02) 438-4308 ext 6.
Hours: Mon.-Fri. 8am to 5pm.

BREMI

STABILIZED POWER SUPPLIES



BRS 36 DUAL STABILIZED POWER SUPPLY

Output voltage: 0 - ± 30VDC. Current: 0 - 5A.
Dimensions: 360x145x430mm. Weight:
16kg.



BRS 41 STABILIZED POWER SUPPLY

Output voltage: 0 - 30VDC. Current: 0 - 5A.
Dimensions: 144x145x310mm. Weight:
7.1kg



BRS 38 STABILIZED POWER SUPPLY

Output voltage: 0 - 30VDC. Current: 0 - 10A.
Dimensions: 322x335x148mm. Weight:
13.2kg.



BRI 8200 DIGITAL FREQUENCY METER

Frequency range: 1 Hz - 220 MHz. Display: 7
digit 1/2" Led. Gate Time: 1 sec. VHF input:
10mV RMS from 1 to 100MHz — 15mV RMS
from 100 to 150 MHz. - 20mV RMS from 150
to 200 MHz — 30 mV RMS from 200 to 220
MHz.

ELECTROMARK PTY. LTD.

40 Barry Avenue, Mortdale,
NSW. 2223.
Phone (02) 533-4896.



A Matsushita executive demonstrates the VHD system at last year's Consumer Electronics Show. It takes a vinyl disc that must be loaded with a caddie like the RCA system, but it has stereo (an add-on) and offers random access, freeze-frame etc.

the stylus to be moved transversely and longitudinally as the current flowing in the coils varies. The coil currents are controlled by the tracking error signals and timebase error signals. However, a command to move the stylus to a particular track can also be used to control the coil current.

JVC claim that their use of a relatively conventional disc production technique is a great advantage of their system over optically based videodisc systems.

Thorn's recent acquisition of the EMI group of companies opens up an enormous source of film and record material for this Japanese-UK-US group to use in video and digital audio discs encoded in the JVC standard. The availability of suitable software (video and audio material) will play a vital part in the success or failure of videodisc systems.

Matsushita (who market Technics and Panasonic products) have decided to abandon their own videodisc system in favour of the JVC system and have now made an agreement with JVC. The original Matsushita system employed a direct contact stylus and a rigid disc.

Conclusions

It seems probable that the three incompatible videodisc systems will exist side by side at least in the early 1980s, so this could mean that people who want to be able to play any videodisc will be involved in expensive investments.

In spite of the current interest in videodiscs, one must remember that people will not want to replay their favourite videodisc as often as they play their favourite audio discs and this may well affect the chances of videodiscs attaining the widespread use essential for their success. However, if a wide range of material is available on disc at

reasonable prices, it seems certain that there is a pretty good market for high quality systems.

The picture quality provided by videodiscs is certainly superior to that from domestic video cassette recorders. The most expensive videodisc system (Philips) will be cheaper than videotape systems (apart from its better quality pictures) and will be one of the most flexible disc systems. The JVC system offers the highest storage density of any of the videodisc systems.

It is interesting to note that videodiscs are no longer limited to the domestic consumer market. Videodiscs are very suitable for the storage of computer type information and it could well be that this application will help enormously to spur on manufacturers to invest more heavily in videodiscs generally, since there is also an enormous potential market in the business and other data storage computer fields. When compared with conventional magnetic recording techniques for digital data storage, videodiscs offer greater bit densities (with storage capacities of around 10^{10} bits per disc surface), virtually error-free recording, probably lower cost per stored bit and a true archival storage capability in which the recorded data is unalterable.

One of the most interesting developments from the business world came in news released from Drexler Technology (one of the leading companies in Silicon Valley) in May 1980 about a 300 mm disc system intended for use as a computer memory device which can easily be recorded upon as well as played back. Drexler claims that by early 1982 two-sided discs produced in quantities of 100 000 or more will be able to store 2500 Mbytes at a cost of about two cents per Mbyte. Drexler state that this may

be compared with current costs of 40 cents for tape cartridges or about \$3 for magnetic discs and several hundred dollars for magnetic bubble memories. Drexler also claims that 20 000 document copies could be stored on a disc at a cost of ¼ cent per copy for use in an electronic filing system! This type of disc, known as the Drexon D-1201, is the first of its kind to become commercially available and will sell for \$3500 per disc in quantities of 20.

Also announced in May 1980 was an agreement between Xerox and Thomson CSF for the development of optical disc systems for data processing.

Other companies, including Philips and IBM, are also entering the videodisc business field. It seems certain that activity in this field will sooner or later be a helpful stimulus to the consumer field. Indeed, it may well be that the days of the conventional floppy disc are numbered and that the consumer and business videodisc markets will be able to teach the computer world a thing or two!

COMMERCIAL APPLICATIONS

Pioneer Electronics Australia is to provide GMH with its laser technology videodisc system for use as a communications medium for GMH dealers. This makes Australia the first country outside North America to adopt videodisc technology in a commercial application on any large scale.

The videodisc will replace 'live' training and promotional services and obviate the need for dealers to attend regional and national conferences and seminars; all new product information and sales and promotional instruction will be distributable on videodisc.

The GMH Video Centre, as the system is called, consists of a Discovision 7820 industrial laser videodisc player (produced by Universal Pioneer Corporation), a TV monitor and optional Pioneer sound system. Features of the 7820 videodisc are fast visual scanning in both forward and rewind modes, single frame display and chapter search.


The software for the GMH Video Centre is made to master-tape stage in Australia by AAV and then sent to Discovision Associates in the US, where the image is transferred to disc.

General Motors in the USA and Canada have already used the laser videodisc throughout their domestic dealer network, and GMH will be able to use any relevant North American material as well as their own Australia-oriented videodiscs.

The complete Video Centre sells to GMH dealers for under \$4000, and orders are currently being taken from dealers for installation in May this year.

Pioneer regard this new commercial application of the laser communications medium, which they claim to be "the most advanced method of communication ever", as a highly important step in the progress of the laser videodisc system.

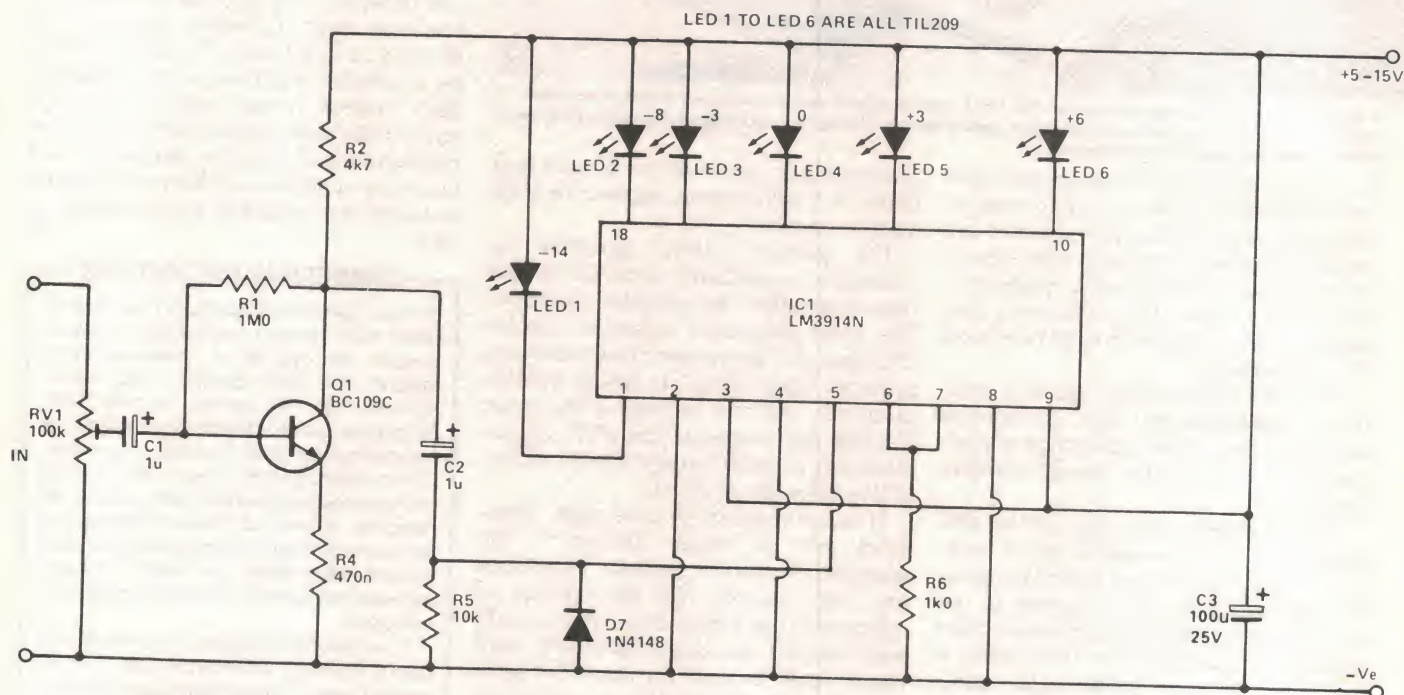Simple LED VU meter covers 20 dB range in six steps



THIS VERY SIMPLE peak reading VU meter circuit uses six LEDs to indicate six signal levels. Indicators are provided at -14, -8, -3, 0, +3, and +6 dB or any other levels having the same spacing (e.g. -17, -11, -6, -3, 0, and +3 dB, if preferred). Only about 24 mV peak-to-peak is needed in order to activate the highest LED indicator, and so the circuit is sufficiently sensitive to be used with any normal item of audio equipment.

The circuit is based on an LM3914N bargraph display driver device (IC1), which can be used to drive up to ten LEDs. This is connected so that with 0.12 V at the input only the first output is activated (goes low). With the input raised to 0.24 V the second output is activated as well, 0.36 V activates three outputs and so on up to an input of 1.2 V or more whereupon all ten outputs are activated. In this circuit only LEDs 1, 2,

3, 5, 7, and 10 are included in the display, and these are LED1 to LED6 respectively.

The input signal is taken to a variable attenuator (R1), which enables the sensitivity of the circuit to be set at the correct level. The signal is then passed to a low gain common emitter amplifier based on Q1 which gives a tenfold boost in the sensitivity of the circuit, and ensures that it is adequate in this respect for all normal requirements. C2 couples the output from Q1 to the input of IC1. R5 is the input bias resistor for IC1, and D7 protects IC1 against an excess negative input voltage. Of course, IC1 only responds to the positive half cycles at its input, and this gives generally satisfactory results in practice. R6 sets the current fed to each LED at about 12 mA, but as the circuit only responds to positive input half cycles the LEDs can switch on for a

maximum of about 50% of the time. This gives an effective LED current of about 6 mA. The quiescent current consumption of the unit is about 8 mA, rising to an absolute maximum of about 44 mA with all six LEDs activated.

To calibrate the unit a 0 dB test signal should be fed into the monitored equipment, and R1 is then adjusted for the lowest sensitivity that does not cause the 0 dB LED to extinguish. The input impedance of the unit is about 80k and it will only lightly load the monitored equipment if the source impedance is 10k or lower.

SHORT CIRCUITS is a feature that lies somewhere between Ideas for Experimenters and complete Projects. Generally, the items published in Short Circuits will involve tried circuits that have not necessarily been fully developed, but fairly complete details are included as a guide to readers. Unfortunately, owing to the nature of these items, we cannot give further details other than what is provided in the article. Contributions for Short Circuits are always welcome.

**NEW
FROM
SHURE**

**StarMaker™
SERIES**

SM77 • SM78
cardioid dynamic microphones
that give you great sound,
outstanding performance . . . and looks.



SM77EB

SM78TN

SM77TN

SM78EB

StarMaker new light heavyweights are around 28% lighter than similar stage microphones. Yet they offer everything you've come to expect from Shure—consistently high performance, tailored frequency response, ruggedness and reliability. And they're available with or without cable.

The StarMaker SM78 is "first choice" for rock, pop, R & B, country, gospel and jazz vocalists. Available in colour choice of black or tan.

The SM77 is especially effective on instrumental pick-up where brilliant and defined sound is demanded. Available in colour choice of black or tan.

CHECK THESE GREAT FEATURES

Lightweight, tough . . . aluminium alloy case, 28% lighter, rugged as ever.

Enhanced intelligibility and sound . . . tailored frequency response, upper and mid-range presence peak.

Durable, good looking finish . . . exclusive SUEDECOAT™ finish—tough, non-reflective, rust and tarnish resistant.

Custom designed carrying case . . . cushions and protects against vibration or shock. Included at no extra cost.

For technical service and advice, contact the Audio Engineers representative at the office in your State:—

CHECK THESE SPECIFICATIONS

Frequency Response: 50-15,000 Hz.

Polar Pattern: Cardioid (unidirectional), rotationally, symmetric about axis, uniform with frequency.

Impedance: Microphone rating impedance is 150 ohms (180 ohms actual) for connection to microphone inputs rated at 19 to 300 ohms.

®



SHURE

®

send this coupon to:

AUDIO ENGINEERS, 342 Kent Street,
SYDNEY, N.S.W. 2000. Tel. 29 6731.

Please send me your 'free' brochure on Shure
"StarMaker" series. (PLEASE PRINT) Name & Address

Name: _____

Address: _____

Postcode: _____

ETI581

AUDIO ENGINEERS PTY. LTD.
342 Kent Street,
SYDNEY, N.S.W. 2000.

AUDIO ENGINEERS (Vic.)
2A Hill Street,
THORNBURY, Vic. 3071.

ATHOL M. HILL P/L
Unit 5/66 Wellington Street,
PERTH. W.A. 6000.

AUDIO ENGINEERS P/L (Qld.)
51A Castlemaine Street,
MILTON, Qld. 4064.

NOMIS ELECTRONICS P/L
689 South Road,
BLACK FOREST, S.A. 5035.

HAWKINS AE162

Dick Smith's P-360 turntable

For a reasonably priced turntable, Louis Challis found Dick Smith's P-360 model to be good value for money, needing only a high-quality cartridge for top performance.


Louis A Challis

THE P-360 is a neat turntable providing many popular features, such as direct drive in preference to belt or rim drive and most particularly an auto return function. The direct drive incorporates a Matsushita Electric DCL-15U1 motor system; this large-selling motor is often chosen by manufacturers when they do not wish to develop and manufacture their own.

This motor and drive are rigidly screwed to a particle board and plywood-fabricated plinth, which is well finished in a metallic lacquer to give the appearance of a metallic or plastic moulding. The unit also incorporates a removable single-piece acrylic moulded cover with spring-loaded hinges which slip into sockets at the back of the plinth.

Features

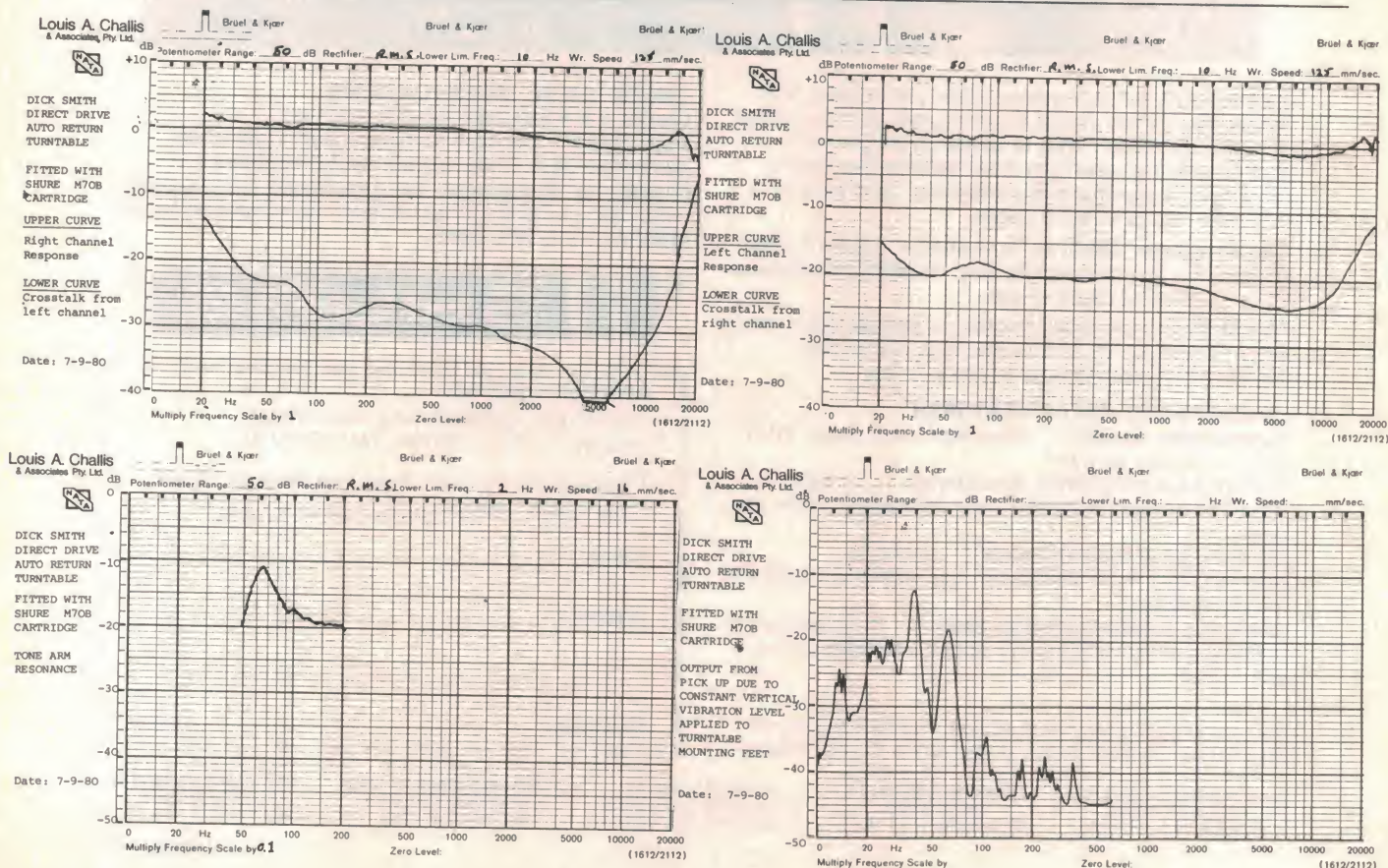The number of controls provided for the turntable are minimal, the left hand side of the deck featuring two knurled speed controls for 33 $\frac{1}{3}$ and 45 rpm, adjacent to which is a pedestal incorporating a strobe light approximately 20 mm from the edge of the platter rim. The rim incorporates four separate





strobes for 33 $\frac{1}{3}$ and 45 rpm and for 50 Hz and 60 Hz respectively. This of course blows Dick's statement that "this unit has been designed for Australia", but did anyone really believe that anyway?

On the right side of the plinth are two buttons, the one on the left providing for selection of 45 and 33 $\frac{1}{3}$ rpm whilst the one on the right is a cut control to terminate the playing of a record before the end of the selection. Behind the speed selection and cut control is a strange knob incorporating an extended aluminium arm, whose function is to initiate the play sequence. Immediately behind this is the tone arm rest and the S-shaped tone arm, integrally mounted in its own black escutcheon. The escutcheon provides an oil-damped tone arm

lift control, spring-activated anti-skate control setting and a well-designed and reasonably light tone arm assembly, complete with balance weight designed to provide up to 3 grams of static balance.

The turntable platter is a solid die casting from aluminium alloy, which weighs 1.45 kg. This is surmounted by a rubber mat to give a small degree of additional damping. The plinth is supported by four rubber and plastic mounts to supply a small degree of vibration isolation to compensate for only 2 mm static deflection. Under the platter is a lever provided with seven slots to allow for variations in the speed of the tone arm movement when cueing onto or returning from the record. This is one function which is not

normally user-selectable and does add a degree of flexibility.

The head shell on the tone arm features an EIA plug-in connector and the unit tested had a universal head shell already fitted, in this case with a Shure M70-B cartridge.

On test

The objective testing of the basic turntable and tone arm showed it to have performance characteristics which ranged between good and excellent. The wow is 0.1% peak to peak, the flutter 0.04% weighted rms and .08% unweighted, whilst the rumble is -65 dB weighted — which is bordering on excellent.

The cartridge fitted has a frequency ►

We didn't get the lion's share of the capacitor market by pussyfooting around.

EX STOCK ALL STATES

We got it by holding inventories of components running into millions of dollars and having stock available on tap in every State. — We wouldn't attempt to supply the nation with minimal stock from one central store.

QUALITY

We got it by setting the highest standards in quality and reliability. Our original RB's, RT's and 'Greencaps' are now the industry standard against which other capacitors are judged.

BUYING OFFICES

We got it by establishing buying offices in the heart of the offshore manufacturing areas to ensure low costs and continuity of supply. We have offices in Tokyo and Hong Kong and are the sole agents for Elna, Samhwa, Nissei and Taiyo, the acknowledged world leaders in capacitor production.

AUSTRALIAN OWNED

We are a stable Australian owned Company with the background and people to know and understand our customers' requirements.



FULL DATA AVAILABLE
ON REQUEST


SOANAR

Soanar Electronics Pty Ltd


A member of the A & R Soanar Electronics Group
30 Lexton Road, Box Hill, Vic., 3128. Australia

VICTORIA: 89 0661
N.S.W. 789 6733
Sth. AUST: 51 6981

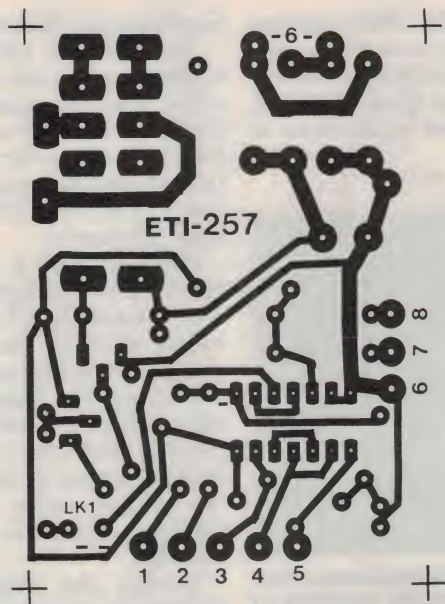QUEENSLAND: 52 1131
WEST. AUST. 381 9522
TASMANIA: 31 6533



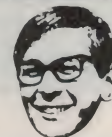Artwork for the pc board for the ETI-257
Universal Relay Driver Board (see pages 53-55).



ELECTRONIC TECHNICIANS

We require the services of several electronic technicians to work in our Service Department at North Ryde. The work involves repair of an enormous variety of electronic equipment in our air conditioned workshops. Applicants should ideally possess the E&C certificate, have had several years experience in the industry and be able to work without supervision. Salary negotiable and generous staff benefits apply. If you think that you're the person that we need, please apply in writing to:

Gary Crapp
Service Manager
DICK SMITH ELECTRONICS
P.O. Box 321, North Ryde
N.S.W. 2113.

DSE928

The **NEW**
HEWLETT-PACKARD
HP 41C V
with 2000 plus
PROGRAM LINES
\$412 (\$370)

SYSTEM 1
HP41C V and card
reader \$630 (\$565)

SYSTEM 2
HP41C V, card reader
and printer
\$1066 (\$958)



QUAD MEMORY MODULE for
HP41C (1600 steps) \$122 (\$109)
HP41C Calculator \$318 (\$285)
HP34C Calculator \$192.50 (\$173)
HP33C Calculator \$115 (\$103)
HP32E Calculator \$69.95 (\$62.50)

HP's POST FREE
Send SAE for complete
HP price list.
(Prices in brackets
exclude sales tax.)

FINAL WEEKS

To install your **COMPUTER** for the new financial year, and receive your investment allowance this year — we are geared to do it.

We specialise in
comprehensive proven
packages on
INTERTEC,
SORD and
DIABLO
SYSTEMS for



DIABLO 3000

WHOLESALE
MANUFACTURERS
RETAILERS
GENERAL BUSINESS
WORD PROCESSING
REAL ESTATE
JOB COSTING

SPARE PARTS
BUS OPERATORS
PRINTERS
MOTOR DEALERS
GLASS CUTTING
TEXTILE INDUSTRY
FURNITURE MANUFACTURERS

**NOW IS THE TIME
TO BUY YOUR Ti59**


NEW LOW PRICE!

TEXAS Ti59
Only \$285 (\$255)
PC100C PRINTER \$245 (\$219)
PACKAGE DEAL
Ti59 and PC100C
\$510 (\$454)
POST FREE — MAY/JUNE

**NON-PROGRAMMABLE
POCKET L.C.D.
WITH EVERYTHING
CASIO fx8100**

46 scientific
functions.
Plus clock, alarm, 2
count-down alarms,
auto calendar, 1/100
sec. stopwatch,
hourly time signal.
\$45 (\$39.90)
P&P \$1.00

(Prices in brackets
exclude sales tax.)

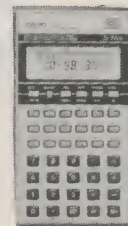

Calculator & Computer

DISTRIBUTORS


3 ROWLEY STREET,
SEVEN HILLS, NSW 2147.

PHONE 8.30 am to 3.30 pm
(02) 624-8400 or 624-8849



HITACHI OSCILLOSCOPES


2 YEAR WARRANTY

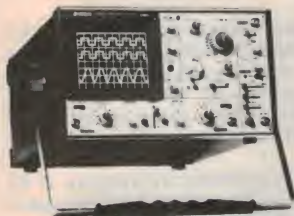

V550 50 MHz

\$1,795

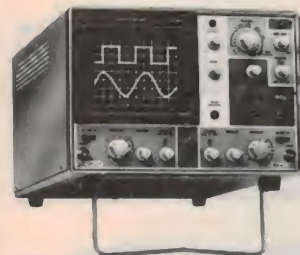
Professional quality oscilloscope with many unique usable features: 50 MHz Dual Trace, Third Trace Trigger View, 1 mV/Div. Sensitivity, Delayed Sweep, X10 Sweep Magnification. Equivalent Oscilloscopes cost 100s of dollars more. Supplied under contract to the A.B.C.



V302 30 MHz

\$955

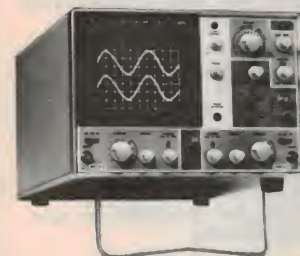Dual Trace 30 MHz 1 mV Sensitivity per division. Built in delay line plus many other features. Ideal for general purpose, transceiver and TV service, and digital use. The only 30 MHz 1 mV oscilloscope available for less than \$1,000. In use by the CSIRO.



V152 15 MHz

** New low price. **

\$572

Dual Trace 15 MHz, 1 mV Sensitivity, XY operation, TV sync separator circuit. Sweep times magnifier (10 times) Trace rotation Z Axio Input. Excellent value for money. Supplied to many Government Departments and National TV Service Companies.

HITACHI-
YOUR MIGHTY
RIGHT HAND!



Hitachi new generation oscilloscopes are unequalled for reliability, operating ease, technical features and value for money. You can confidently buy HITACHI Test Instruments for year after year of trouble-free use.

Prices + S/Tax 15%. Subject to change. FOT Sydney.

HITACHI AVAILABLE FROM:-

N.S.W. Radio Dispatch Service, David Reid Electronics, Standard Components, Emtronics. D.G.E. Systems Newcastle.
Vic. Ellistronics, G.B. Telespares, David Reid Electronics, ECQ Electronics, J. H. Magrath & Co. Pty. Ltd.
Qld. Audiotronics, ECQ Electronics, St. Lucia Electronics.
S.A. Bee Jay Electronics.
W.A. Reserve Electronics.
Tas. George Harvey Electric Launceston and Hobart

Standard Components Pty. Ltd. "STOCKISTS IN ALL STATES"

10 Hill St., Leichhardt N.S.W. 660-6066



MAIL ORDER TO AUSTRALIA

32 Lloyd Avenue, Cremorne,
Sydney 2090.
(02) 908-2235. Tlx AA20149.

BUSINESS HOURS: Our office is open between 9 and 5 weekdays and also 7 to 10pm Monday through Thursday so that our Australia wide clients can use STD when it's cheap (after 9pm save 60 percent on your call).

SERVICE: We provide full service, equal to any in the business, on all our lines. We support fully the manufacturer's warranty and provide complete after warranty service.

PAYMENTS: 1. Personal cheque — allow time to clear.
2. Bank cheque, postal/money order or cash.

A receipt will be issued immediately for all monies received.

If you desire the protection of a written contract between us we can issue you with a Proforma Invoice.

PLEDGE: If your order cannot be supplied ex-stock a despatch date will be specified on the invoice/receipt. Failure to despatch by this date will require us to immediately and automatically issue a full refund unless instructed otherwise by the customer.

APPLE DISCOUNTED AND NOW ... FREIGHT CHARGES SLASHED

We can ship door-to-door anywhere in Australia for:

\$15 each

Computers, disk drives, pascal, graphics tablets — everything except big printers and colour monitors (which cost more) and peripheral cards (costing less — \$4.00 by certified mail). And this includes full insurance.

THIS MONTH'S SPECIAL

(Order this month.
Deliver next)

DISK DRIVE WITHOUT CONTROLLER

\$470 Tax Free. \$540 Tax Paid.

Our free software and hardware catalogue has our complete range and prices, all of which are substantially discounted.

16k Apple II plus, \$1403. Disk & Controller, \$725.
16k Apple II plus & 32k, \$1541. Green Screen Monitor, \$342.

For tax free prices divide by 1.15.
(Prices subject to change and exclude delivery)

Our range includes all Apple products and those of CCS and Mountain Computing.

- good and top quality monitors
- printers, Trendcom, Microline 80, Epson MX80 Paper Tiger, Anadex and Sanders
- the best in business, gaming and educational software
- card reader

MINI-MART

Where readers can advertise — For Sale/Wanted/Swap/Join.

• We'll publish up to 24 words (maximum) totally free of charge for you, your club or your association. Copy **must** be with us by the 1st of the month preceding the month of issue. Please — **please** — print or type adverts clearly, otherwise it may not turn out as you intended! Every effort will be made to publish all adverts received however, no responsibility for so doing is accepted or implied. Private adverts only will be accepted. We reserve the right to refuse adverts considered unsuitable.

• **Conditions:** Name and address plus phone number (if required) must be included within the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Adverts must relate to electronics, audio, communications, computing etc — general adverts cannot be accepted. Send your advert to:
ETI Mini-Mart, Modern Magazines
15 Boundary St,
Rushcutters Bay NSW 2011

AUDIO

GRAPHIC EQUALISER, new, 10 knobs each channel, \$169. Amplifier, 40 W/rms each channel, new, \$179. Phone Paul (02)30-1839.

FOR SALE: Brand new ETI Series 3000 compact 20W amplifier \$90. G. Rlm, 20 Cheverton Rd, Lower Plenty Vic. (03)439-9138.

QUAD electrostatic treble panels, improved, \$100 each. B&W electrostatic panels for DM 70 speakers, as new with guarantee, half price, \$150 each. Phone Otto (02)29-6197.

FOR SALE: JVC add-on rear amp, 100 W, built-in 5-band equal. Remote volume control also. As new \$100. Phone Pat (02)259-5080 a.h.

SPEAKERS: JBL pro monitors, best JBLs in Australia. Replacement value of \$5000 — stunning performance. Must sell, \$3750 — Melbourne (03)99-1047.

WANTED: Members to enjoy sound magazines, printed magazines, round robins, tapespondence. Full details: The Tape Club of Australia, P.O. Box 118, Wellington NSW 2820.

COMMUNICATIONS

WANTED: COLLINS R391 (or R390) com. recvr. top and bottom cover plates, modules, tools, valves. D. Bruce (03)93-1638, 3 Shadwell St, Cheltenham Vic 3192.

MISCELLANEOUS

DATA PRECISION MOD. 935 DMM portable, LCD. 0.1% accuracy. New — in original packing, and all accessories. \$120 ono. Phone (07)286-2665.

KLEEN BOND 48-inch pan-brake sheet metal bender. Designed for all those sheet metal tasks, electronic chassis or box trailers, \$950. 487-2972.

FREE COMPUTER DATING — the ultimate in compatibility. All ages. Absolutely free. Send large self addressed envelope to 24a Simpson St, Bondi NSW 2026.

FREE Friden Flexowriter (110 Vac) with tape reader and punch. Old home-made audio CRO \$20. EA 110 SW receiver \$40. Phone (02)456-1958.

WANTED: Service manual for a Siemens 100, mk1, 3-row telex machine. Will pay up to \$10. Phone Frank, 318-4297 or 67-1707, any time.

SOFTWARE for TRS-80 and other Z-80 systems. Editors, assemblers, word processor, games etc. Write for list. P.O. Box 545, Toowong, Qld 4066. Phone (07) 371-4477.

WANTED: Documentation, circuit diagram for DGZ80 kit from Applied Technology. Info required on 74S200 (or replacement) and 82S123 (programmed) chips. Pay \$5 for photocopy. Jim Buchanan, 14 Nolan Way, Bateman, WA 6155. Phone (09) 332-4713.

TELETYPE MOD 15 governed 110 V motors, \$7.50 ea. Oiled paper tape, 70¢ per 8" roll. 46 Gloucester St (Nth), Sydney, NSW 2000. Phone 27-2982 a.h.

SELL: VIDEO PLUS VDU for Aim/Sym/Kim computers. Complete with 8K RAM, ASCII keyboard, 2K EPROM and full documentation — \$260 o.n.o.. Ian Hoskin, 38 Errington St, Plympton, SA 5038. Phone (08) 293-6305.

DG640 VDU board, complete, \$75 o.n.o. KT9500 kit, complete, \$55 o.n.o. John Petersson, 15 Robinson St, O'Connor, ACT 2601. Phone 72-3730 b.h.

SELL: One ASR-33 teletype, \$570 o.n.o. One Teletype 28D printer with 2650 interface, \$120. Padstow NSW, (02) 239-0311 ext 5557.

SELECTRIC PRINTER, heavy duty, tractor feed wide paper. Interface and Z80 driver software. Plus 3 spare machines for parts. \$350. Alan Peek, (02) 89-1450.

SORCERER computer, 48K, VDU, cassette, games and general ledger program to suit small business, cost \$2350, sell for \$1500, as new. Stanley Falinski, (02) 451-9443.

PROGRAMS for unexpanded Sinclair ZX-80, 3 for \$2, complete listings and notes. Elkhorne, 15 Myella Dr, Chigwell, Tas 7011.

WANTED: TINY BASIC (2-3K) for 2650 mini-computer. Would pay for cassette or listing. Phone (02) 389-1418, Paul. 1/149 Victoria Rd, Bellevue Hill, NSW 2023.

ETI-641 S100 PRINTER — EUY 10E023LE printer mechanism, 2½ rolls of paper, S100 logic board, fully assembled (with character generating ROM), sample printout, good condition, \$125. John Francis (02) 649-9155.

FRIDEN FLEXOWRITER computer I/O, upper case only, fitted with ASCII paper tape punch reader, \$300. R. Long, 46 Gloucester St, Sydney (02) 27-2982 a.h.

DREAM 6800 OWNERS, I would like to share. Please send SSAE for some useful routines. Frank Rees, 27 King St, Boort, Vic 3537.

SELL: Synertek SYM-1 with cables, \$175. Contact Simon Wardrop, 3 Gwenda Ave, Blackburn, Vic 3130. (03) 878-0469.

COMPUTERS

WANTED: Cromemco System 3, complete or in parts, and/or Persci 277 disk drive. Phone Mark (03)870-4017 (ah).

FOR SALE: ZX80 with power pack, memory expansion board, memory chips and ZX80 companion book. Very little use. \$250. Phone (02)597-1239 ah.

OSI C4P/C8P programs. Four original programs including a great low res. graphics utility \$10. Peter Bessell, P.O. Box 1220, Southport 4215.

COPYRIGHT: The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Modern Magazines (Holdings) Ltd or from the copyright holders.

LIABILITY: Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any components parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid. The Publisher accepts no responsibility for unsolicited manuscripts, illustrations or photographic material.



SPECIAL OFFER!! — direct from ETI



HERE IS A MOST UNUSUAL SPECIAL OFFER.

Our company has for sale 1500 of the most superbly made binders you've ever seen in your life!

We bought them for a data service which has since closed down. They are specifically intended to hold data sheets and similar material which must be referred to constantly. All those for sale are brand spanking new — but we can show you some old ones that have been in constant hourly use for over 20 years and they are still as new!

We know this sounds like hyperbole, but these devices can only be described by using superlatives. They're made (like a Rolls-Royce!) by the Swedish company Aggripa.

For example, the hinge assemblies are made of heavy-gauge plated steel. The spine and all outer edges of the covers are heavy-gauge enamelled steel. Apart from the steel hinges holding the covers, the spine itself is hinged down the centre, enabling the binder to lie completely flat for easy insertion and removal of material.

As may be seen from the pix, material is held in place by an eight-hole pin mechanism — actuated by a remote control trigger at the bottom of the spine.

These binders are ideal for housing valued reference material, data sheets, etc, etc.


These binders are not normally obtainable in small numbers — if they were the retail price would be at least \$25 each.

We are offering them exclusively to ETI readers for the absolute bargain price of \$10 each (plus \$2.00 post and packing). See also inset table for quantity prices.

These binders may be inspected at our Sydney and Melbourne offices during normal working hours.

UNCONDITIONAL MONEY-BACK GUARANTEE.

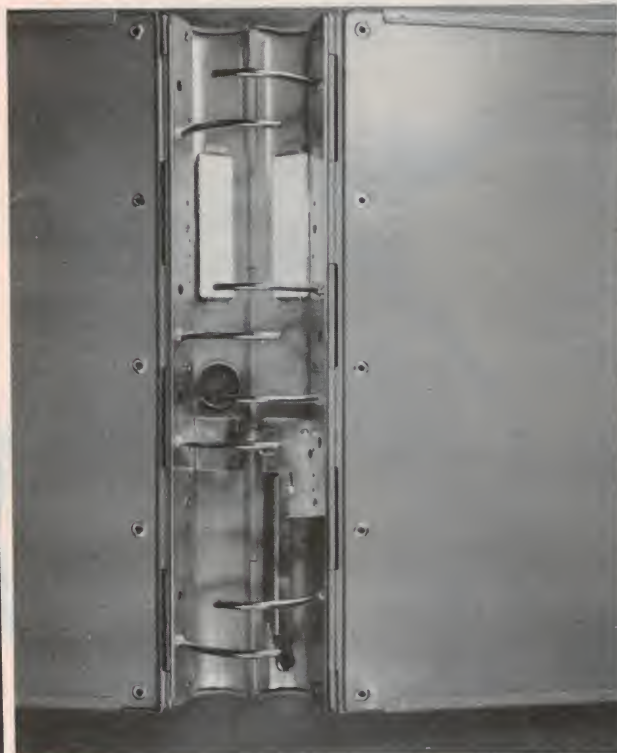ETI guarantees to return the purchase price in full and without query to any reader/s not totally satisfied with their purchase, providing the goods are undamaged and returned within seven days of receipt.



PLEASE FORWARD (QTY) OF BINDERS.

I ENCLOSE CHEQUE/POSTAL NOTE FOR

Name

Address

..... Postcode

Please make out cheques to ETI and forward together with order to BINDER OFFER, Electronics Today International, 15 Boundary St, Rushcutters Bay NSW 2011.

PRICES

1 - 5	\$10 each	plus \$2.00 each p & p.
6 - 24	\$9.00 each	free
25 plus	\$8.00 each	free

Join the people who have made the Air Force their life



"I've seen a lot of Australia. Now I'm looking forward to being posted overseas."



"I enjoy being a member of the team that keeps our F111's fully operational."



"You're trained to work on some of the most advanced equipment in the world."



"The opportunities for promotion with more pay and responsibility are there."



"You don't mind working hard if it's for a specific purpose like the country's security."



"At 23 I found myself promoted to Section Head. That kept me on my toes."



"It isn't all work I have time to relax and play my favourite sport."



"The training has set me up with a career for life — it's really professional."

The satisfaction and rewards are immense.

A new lifestyle. New friends. New interests. New qualifications. New places visited.

And you start on full adult pay too! After training we'll pay you even more! Then there's four weeks annual leave and the opportunity to continue studying for higher qualifications. So if you want to reach a higher rank, it's up to you.

It's not an easy life.

Success demands application. A disciplined approach to your work. What's more, you'll be part of a special team that's proud to wear the Air Force uniform.

Normally you'll work a five day week. But at times we expect you to do extra duties.

You must be prepared to join us for a minimum of six years and be prepared to live and work on any one of our bases.

Your future.

Is it in Flight Systems, Propulsion Systems, Air Frames, Telecommunications, Engineering, Administration, Weaponry, Supply or Motor Transport?

The choice is vast. The scope unrivalled.

So if you're aged between 17 and 34 years (17 and 43 years if no trade training is required), an Australian citizen or meet our nationality requirements, we would like to meet you. (People with civilian qualifications and experience are most welcome to apply.) Enquiries are also invited for Apprenticeships.

Today, walk into the Air Force Recruiting Office nearest you and have a chat with a Careers Adviser. The address is in the phone book. It could be your first important step to an exciting new career.

Alternatively send the coupon or phone for the facts:

Brisbane:
226 2626
Wollongong:
28 6294
Hobart:
34 7077
Melbourne:
61 3731

Townsville:
71 3191
Parramatta:
635 1511
Adelaide:
212 1455
Newcastle:
2 5476

Sydney:
212 1011
Canberra:
82 2333
Perth:
325 6222

To:
RAAF CAREERS
ADVISER, G.P.O. Box XYZ
in the capital city nearest you
Yes! I am interested in an RAAF
career. Please send me full details.

Name

Mr/Miss

Address

State

Postcode

Date of Birth: / /

RG.417.FP.11ET

You're somebody in Today's Air Force

Authorised by Director-General Recruiting Dept. Defence

RG.417.FP.11ET



Electronics Today International is published by Modern Magazines (Holdings) Ltd, 15 Boundary St, Rushcutters Bay NSW 2011. It is printed (in 1981) by Offset Alpine, cnr. Wetherill and Derby Sts, Silverwater NSW, and distributed by Gordon and Gotch.

Editor

Roger Harrison VK2ZTB

Technical Editor

David Tilbrook VK2YMI

Production Editor

Jane Clarke B.A. (Hons)

Editorial Staff

William Fisher B.Sc. (Hons)

J.B. Scott B.Sc./B.E. (Hons)

VK2YBN

Graeme Teesdale

Jan Vernon B.A.

Phil Wait VK2DKN

Art Direction and
Technical Photography

Ivy Hansen

Layout

Bill Crump

Reader Services

Jan Collins

Managing Editor

Collyn Rivers

Acoustical Consultants

Louis Challis & Associates

Mail enquiries: There is no charge for replies, but a foolscap-sized, stamped, addressed envelope must be enclosed. Queries relating to projects can only be answered if related to the item as published. We cannot advise on modifications to projects, other than errata or addenda, nor if a project has been modified or if components are other than specified. We try to answer letters as soon as possible. Difficult questions may take time to answer.

Phone enquiries: We can only answer readers' technical enquiries by telephone after 4.30 pm. In enquiring by telephone about back issues or photostats, please ask for the Subscriptions Department.

(02)33-4282

Editorial and Sales Office:

**4th Floor, 15 Boundary St, Rushcutters Bay NSW 2011. Ph. 33-4282;
Tlx: 27243**

Sales Manager: **Bob Taylor**

Sales Admin: **Jan Collins**

(address as above)

Melbourne: Virginia Salmon, 150 Lonsdale St,
Melbourne Vic 3000. Ph: 662-1222; Tlx AA34543.

Adelaide: Admedia Group, 24 Kensington Rd, Rose
Park SA 5067. Ph: 332-8144; Tlx AA82182.

Brisbane: Geoff Horne Agencies, 16 Bellbowrie
Centre, Bellbowrie Qld 4070. Ph: 202-6813.

Perth: Aubrey Barker, 133 St Georges Terrace, Perth
WA 6000. Ph: 322-3184; Tlx: AA93810

New Zealand: Geoff Collins, P.O. Box 39163, Auckland
NZ. Ph: (9)760-150.

United Kingdom: Australian Consolidated Press,
Ludgate House, 107 Fleet St, London EC4A 2AL.
Ph: 353-1040; Tlx: 267163.

Japan: Genzo Uchida, Bancho Media Services,
15 Sanyocho, Shinjuku-Ku, Tokyo 160. Ph: 359-8866;
Cable: Eibanchorito; Tlx: BMSINC J25472 Tokyo.

USA: Peter Samuel, Australian Consolidated
Press, 444 Madison Avenue, New York NY 10022.
Ph: 751-3383; Tlx: 620892.

ORDER FORM

I enclose \$ for (tick appropriate box/es). All prices include postage.

Send orders to: ETI, 4th Floor, 15 Boundary St, Rushcutters Bay NSW 2011. Phone: (02)33-4282.

☐

Subscriptions

\$23.30 per year within Australia

\$

\$28.80 overseas (surface mail)

\$

Airmail rates on application

NAME (Please print)

☐

Back issues

\$2.50 from April 1977 on (October 1978 unavailable)

ADDRESS

☐

or photocopies

\$2.50 per article per issue

Project No. Month Year \$

Project No. Month Year \$

Project No. Month Year \$

Project No. Month Year \$

Please attach a list if more than four required.

☐

Binders

No. @ \$6.10 in NSW

\$

No. @ \$7.50 in other states

\$

POSTCODE



A COUPLE OF MONTHS ago Dregs asked readers to send in examples of names matching occupations. We've had quite a response, including a whole list from C. Hignett of Kirwan, Qld, who acknowledges the UK Sunday Times as the publishers of the original list but thought they were worth reprinting anyway. Here goes: Messrs Doolittle and Dalley - Estate agents.

Messrs Welsh and Robb — Solicitors
Dr Dottie — Psychiatrist
Mr Smellie — Sanitary inspector
Mr Cheater — Tax inspector
Mr Boddy — Undertaker
Mr Graves — Cemetery caretaker
Police Constable Caution
Messrs Plummer and Leek — you guessed it!

Plus a whole family called Snoring who live in the village of Gotobed.

Craig Air of Belrose, NSW, also wrote to tell us of teachers at his school whose names match their subjects: there's Mr Weldon, the metalwork teacher, Mr Levy, the commerce teacher, Mrs Tucker, who teaches cooking, and a music teacher by the name of Mrs Organ. Craig reckons it's all one of the Ministry of Education's new schemes for helping new Year 7 students find their way around the school — he could be right.

And our typesetter here at ETI tells us of her mother's chiroprapist, a lady called Miss Trotter, who lives at Randwick — which of course is where the racetrack is!

Pun punts

February's puns occasioned a rush of creativity (??), or maybe that should be a rash... Anyhow, away we go with an entry from James Gallagher of Beecroft, in Sydney. James sent in a number of songs and question-answer puns, but his best effort was a limerick: There was a technician called John Who swallowed a 16K ROM He tried on a buss But it caused such a fuss That his bytes performed functions all wrong!

Hot on his heels came an entry from 15-year-old Paul Richardson of Redcliffs in Victoria. He had two question-answer puns, again on a computing theme. His best (?) was: Q: What does a shepherd have in



Wayne Cantell, Editor of sister journal *Modern Motor*, clowning around at the Fleurs antenna test range of Sydney University (at Kemp's Creek) during measurement trials of vehicle radar cross-sections for our March issue lead article on Police Radar Traps.

common with a computer?

A: They both have rams!

Then Bert Hansen sent in one that would have the Commissioner for Community Relations, Mr Grassby, after us if we printed it. Sorry Bert. However, this month's prize pun came from B.P. Dilworth of Curre King Island, off Tasmania. Apart from sending two dozen puns, Mr Dilworth sent us a dozen or so cartoons. We might get round to the cartoons some other time. His winning pun combined a literary and computing theme! If Shakespeare had discovered Boolean Algebra before Boole did, perhaps Hamlet's famous soliloquy would have turned out: BB or BB!

Your copy of *Computers & Computing* is on its way, Mr Dilworth.

Our Managing Editor, Collyn Rivers,

punster extraordinaire, thought up a Shakespearean pun ages ago, and your Editor has been seeking an opportunity to embarrass him with it ever since. It's not as subtle as Mr Dilworth's effort, but here it is, anyway:

"Shakespeare, reflecting upon the demise of live music in Elizabethan pubs, was heard to say: 'Now is the winter of our discotheque'!"

At this stage, we should warn readers that this madness has to stop! All good things come to an end, and the Great Dregs Pun Competition will end with the July 1981 issue. After a run of 12 months, it's about time we found some other curiosity to have fun with in Dregs. Get those entries in before 15 May. Don't miss the July issue — new Dregs competition coming up!

UNTIL WE DEVELOPED THE STEREO GROOVE, HI-FI WAS PRETTY HO-HUM!



The world of hi-fi owes a lot to the original and continuing innovation of JVC. Few companies, if any, have done as much to help turn records and record-players into the virtual musical instruments they are today... or to lead the way in developing so many *firsts* in the more recent concepts of sound amplifiers, cassette decks and computer-designed speaker

systems. Hi-fi, as we know it today, had its beginnings in 1956, with JVC's development of the 45°/45° groove for stereo records. The fact that this system still remains as the world standard is, in itself, outstanding testimony to the technology of JVC. The development revolutionised not only the record-making industry, in which we've been involved since 1930; it also paved the way for enormous advancement in the design and engineering of record-playing equipment. Now, hi-fi has expanded to



R-S77. Super-A FM/AM Stereo receiver

embrace a wealth of highly-sophisticated electronic equipment; and it's not surprising that JVC has continued to play a leading role in so much of its development.




HR-3660 EA. VHS Colour Video Cassette recorder

THAT WASN'T OUR ONLY FIRST, EITHER.

We also pioneered Japan's television industry, introducing their first TV receiver just over 40 years ago. A more recent innovation is VHS, the home video recording system now gaining world-wide acceptance as *the* system for such equipment. In the course of staying ahead, we've introduced a number of world *firsts* of radical importance: the Quartz Lock turntable is one of them.

THE QUARTZ LOCK TURNTABLE. MANY TIMES MORE ACCURATE.

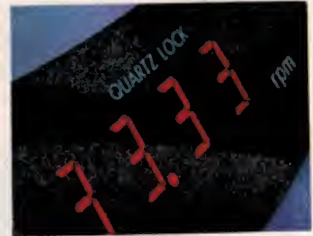It stands to reason that if your equipment is at the top end of the range, then your turntable must be capable of comparable performance. Only Quartz Lock ensures this, tying the speed of the turntable to the unvarying pulse of the atom, and providing a level of accuracy far in excess of conventional turntables.



MORE MILESTONES IN HI-FI.

To match the superb quality of Quartz Lock, we produced the S.E.A. graphic equalizer system. Then we refined it to such a degree it even compensates for the effect your furniture has on sound when it leaves the speakers! To expand the capabilities of tape, we designed ANRS and



SEA-80. Stereo Graphic Equalizer

Super ANRS — automatic noise reduction systems which not only reduce distortion and 'hiss' but actually extend the dynamic range of the tape. Similarly, with speakers: at JVC we employ computers in their design to help provide the ultimate in sound reproduction.

AND NOW, SUPER-A.

In its own way, as significant a hi-fi development as the stereo groove. Imagine an amplifier which combines the *best* features of the two recognised amplifier classes (A and B)... an amp which combines the *efficiency* of one with the *low distortion* of the other. Some engineers said it couldn't be done; but not those at JVC. Enter the Super-A amplifier... the *latest* JVC *first*!

Distributed and Serviced by...
HAGEMEYER

THE FUTURE.


It's already with us. For instance, we were so far ahead in the new metal tape technology that our cassette decks were metal-compatible before the tapes were generally available. And now there's the JVC Electro-Dynamic Servo Tonearm, damping tonearm resonance by means of a purely electronic system and two 'thinking' linear motors. Who was it who dubbed JVC, 'the innovators'?





TELETEXT

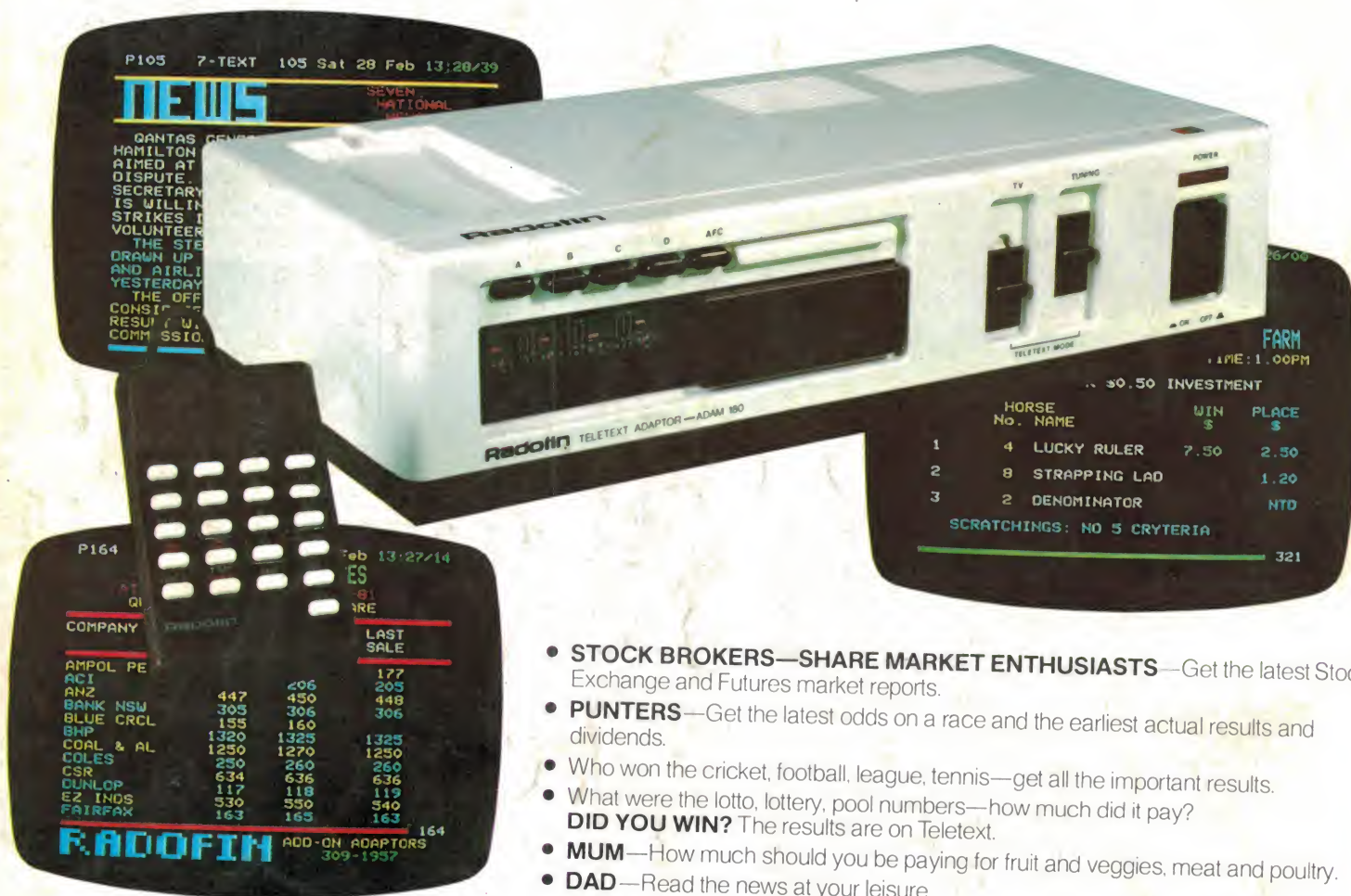The Information Computer
you access on your own Television



- **STOCK BROKERS—SHARE MARKET ENTHUSIASTS**—Get the latest Stock Exchange and Futures market reports.
 - **PUNTERS**—Get the latest odds on a race and the earliest actual results and dividends.
 - Who won the cricket, football, league, tennis—get all the important results.
 - What were the lotto, lottery, pool numbers—how much did it pay?
DID YOU WIN? The results are on Teletext.
 - **MUM**—How much should you be paying for fruit and veggies, meat and poultry.
 - **DAD**—Read the news at your leisure.
 - **KIDS**—Enjoy mastermind, jokes, graphics and puzzles.
 - What will the weather be like tomorrow in Brisbane, Sydney, Perth, New York, Athens, London—**IT'S ALL ON TELETEXT.**
- GET ALL THIS INFORMATION** and much more from the **FREE** electronic newspaper of the 80's—**YOUR OWN** television set with an **ADAM 180 TELETEXT ADAPTOR** by **RADOFIN ELECTRONICS (AUST).**

THE ADAM 180 TELETEXT ADAPTOR by

RADOFIN ELECTRONICS (AUST)

5 Curlewis Street, Bondi, NSW 2026, AUSTRALIA

Telephones: (02) 309 1957 or (02) 309 1904